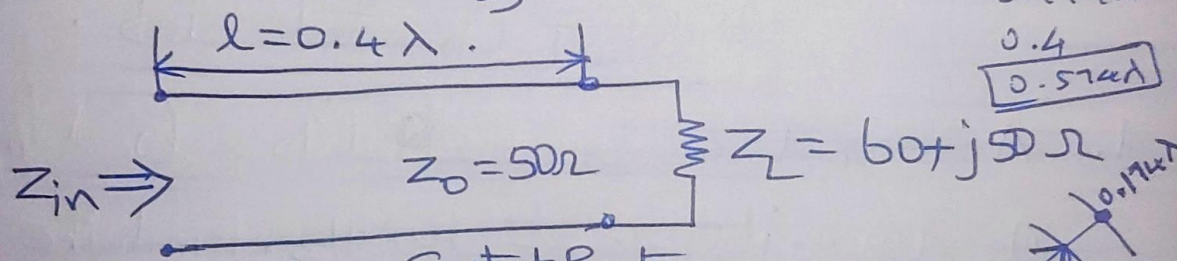


7/2

1

- Use the Smith chart to find the following Quantities for the transmission line circuit, shown in the figure (i) VSWR, (ii) Reflection Coefficient at load (Γ_L), (iii) Load Admittance Y_L , (iv) Input Impedance (v) Distance from the load to the first Voltage minimum (dV_{min}) (vi) Distance from the load to the first voltage maximum (dV_{max}).




0.174λ
0.4
0.574λ

Solution:

$Z_{in} = \bar{Z}_{in} \cdot Z_0$
 $= 25 + j21$
 $Z_{in} = 0.5 + 0.42j$
 $\bar{Y}_L = 0.5 - 0.42j$
 $Y_L = 0.01 - j8.4 \times 10^{-3}$

Normalized Load Impedance,

$\bar{Z}_L = \frac{Z_L}{Z_0} = 1.2 + j1$

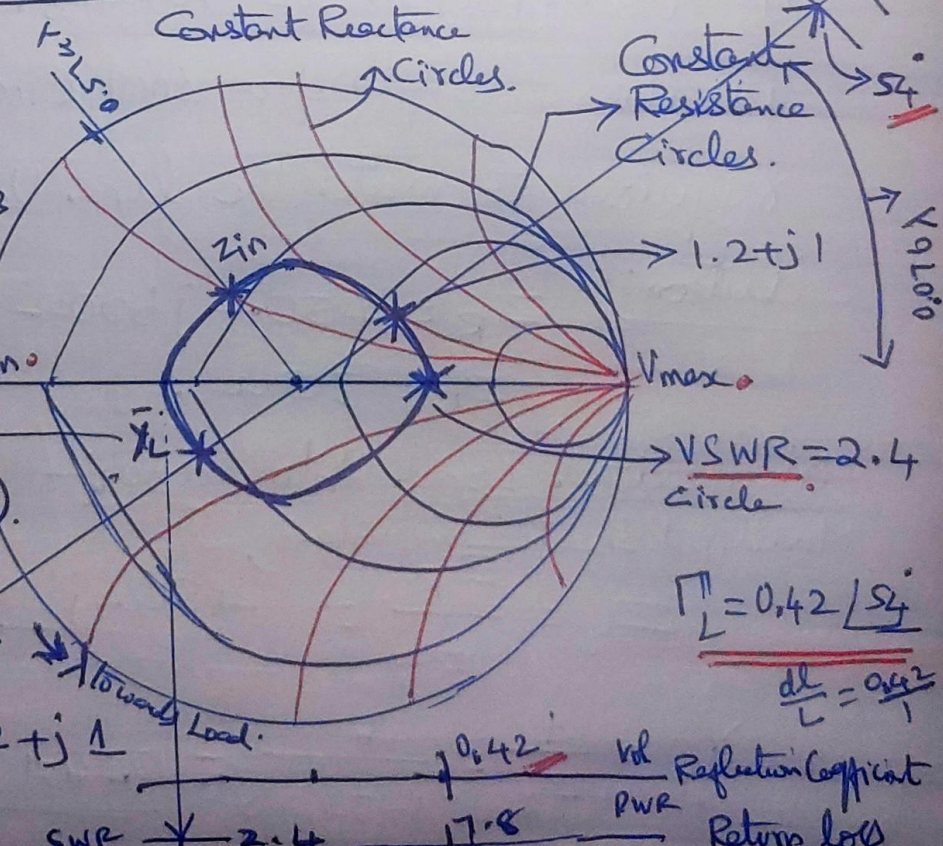


$\Gamma_L = 0.42 / 54^\circ$
 $\frac{dL}{L} = \frac{0.42}{1}$

SWR 2.4 17.8 Return loss

(2)

Single Stub Matching

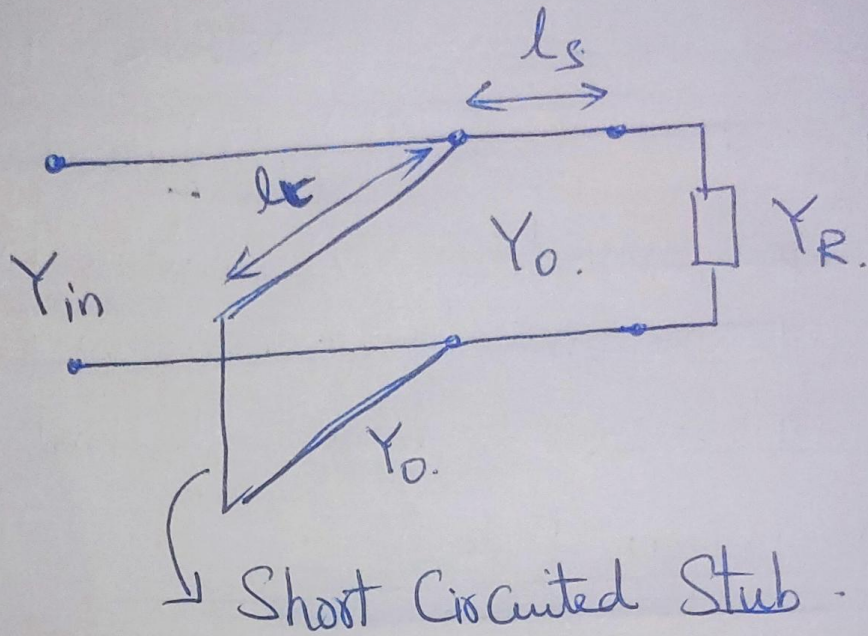

Short Circuited Stub.

1. A 300Ω T-line is connected to a load impedance of $450 - j600\Omega$ at 10MHz . Find the position & length of a short circuited stub required to match the line using Smith chart.


Solution:- $Z_R = 450 - j600\Omega$.
 $Z_0 = 300\Omega$.

Normalized Load Admittance:- Y_r .

Normalized Load Impedance,

$$Z_r = \frac{Z_R}{Z_0} = \frac{450 - j600}{300} = 1.5 - j2.0.$$
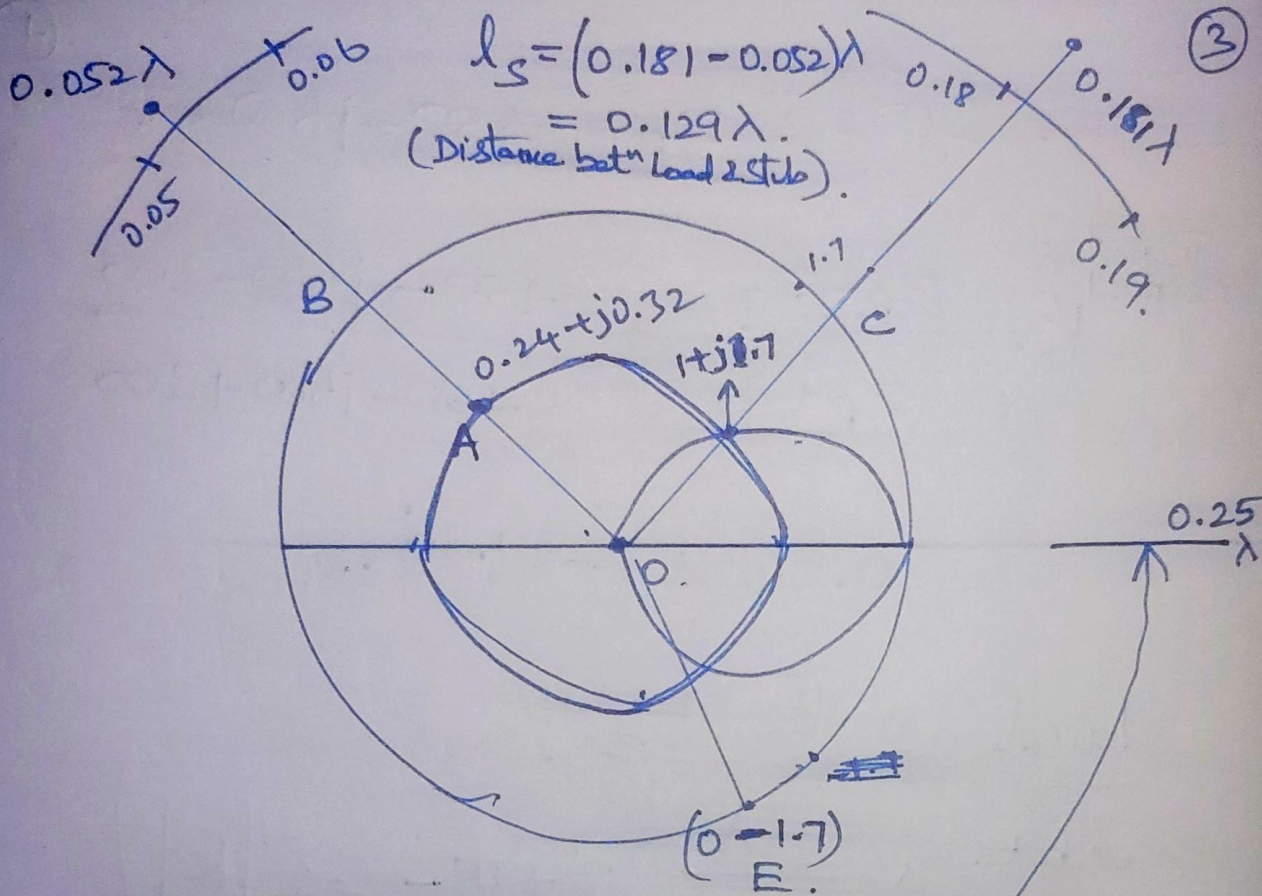
$$Y_r = \frac{1}{Z_r} = \frac{1}{1.5 - j2.0} = \underline{0.24 + j0.32}.$$



Position of the stub, l_s
 (i.e., Distance between
 load & stub)

$$\underline{l_s = 0.129\lambda}$$

Length of the short Circuited
 stub, $\underline{l_t = 0.085\lambda}$

$$\boxed{l_t = 0.085\lambda}$$

$(0.355 - 0.250)\lambda$

(4)

$$Z_0 = 300\Omega; Z_L = 450 - j600\Omega.$$

$$\text{Reflection Coefficient, } K = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{450 - j600 - 300}{450 - j600 + 300}$$

$$= 0.6439 \angle -37.30^\circ.$$

Location of the stub

$$\text{w.k.t. } l_s = \frac{\lambda}{4\pi} \left[\phi + \pi - \cos^{-1}|K| \right]$$

$$l_s = \frac{\lambda}{720^\circ} \left[-37.30^\circ + 180^\circ - 49.92^\circ \right]$$

$$l_s = \frac{\lambda}{720^\circ} [92.783] \Rightarrow \boxed{l_s = 0.1289\lambda}$$

$$l_s' = \frac{\lambda}{4\pi} \left[\phi + \pi + \cos^{-1}|K| \right] \Rightarrow \boxed{l_s' = 0.2675\lambda}$$

$$\text{Length of the stub: } l_t = \frac{\lambda}{2\pi} \tan^{-1} \left(\frac{\sqrt{1 - |K|^2}}{2|K|} \right)$$

$$\boxed{l_t = 0.085\lambda}$$

Location of the stub should be nearer to the Load

$$l_t' = \frac{\lambda}{2\pi} \tan^{-1} \left(\frac{\sqrt{1 - |K|^2}}{-2|K|} \right) = 0.414\lambda.$$

(5)

Stub Matching :-

1. Reflection Coefficient :-

$$K = \frac{Z_R - Z_0}{Z_R + Z_0} ; K = |K| \angle \phi.$$

2. Position of the stub :-

$$d = l_s = \frac{\lambda}{2\pi} \cdot \tan^{-1} \sqrt{\frac{Z_R}{Z_0}}.$$

$$l_s = \frac{\lambda}{4\pi} \left[\phi + \pi - \cos^{-1} |K| \right]$$

(or) \rightarrow Angle of Reflection Coefficient.

\rightarrow Magnitude of Reflection Coefficient.

3. Length of the stub :-

$$l_t = \frac{\lambda}{2\pi} \tan^{-1} \left[\frac{\sqrt{Z_0 Z_R}}{Z_R - Z_0} \right]$$

$$l_t = \frac{\lambda}{2\pi} \tan^{-1} \left[\frac{\sqrt{1 + |K|^2}}{2|K|} \right]$$

1. A dipole antenna whose Input Impedance is 100Ω to be matched at a frequency of 100MHz to a transmission line having characteristic Impedance of 600Ω by means of short Circuited stub. Determine the location and length of the stub.

Solution:-

Given, $Z_R = 100\Omega$; $Z_0 = 600\Omega$; $f = 100\text{MHz}$.

$$\lambda = \frac{c}{f} = \frac{3 \times 10^8}{100 \times 10^6} = \underline{\underline{3\text{m}}}.$$

Location of the Stub :-

$$\begin{aligned} l_s &= \frac{\lambda}{2\pi} \tan^{-1} \sqrt{\frac{Z_R}{Z_0}} \\ &= \frac{3}{2\pi} \tan^{-1} \sqrt{\frac{100}{600}} \end{aligned}$$

$$= \frac{3}{2\pi} \times 22.2^\circ \times \left(\frac{\pi}{180^\circ} \right) \quad \left\{ \begin{array}{l} \text{Converting from} \\ \text{degree to radians} \end{array} \right. \quad (7)$$

$$\boxed{l_s = 0.185 \text{ m}}$$

Length of the stub:-

$$l_t = \frac{\lambda}{2\pi} \tan^{-1} \left[\frac{\sqrt{Z_0 Z_R}}{Z_R - Z_0} \right]$$

$$= \frac{3}{2\pi} \tan^{-1} \left[\frac{\sqrt{(100)(600)}}{100 - 600} \right] \Rightarrow \frac{3}{2\pi} \tan^{-1} \left(\frac{244.95}{-5} \right)$$

$$= \frac{3}{2\pi} (-26.1^\circ) \Rightarrow \frac{3}{2\pi} (180^\circ - 26.1^\circ)$$

$$= \frac{3}{2\pi} \times 153.9^\circ \quad \left\{ \begin{array}{l} \text{Converting from} \\ \text{degree to radians} \end{array} \right.$$

$$\Rightarrow \frac{3}{2\pi} \times 153.9^\circ \times \frac{\pi}{180^\circ}$$

$$\boxed{l_t = 1.28 \text{ m}}$$

2. A load $(50 + j100)\Omega$ is connected across a 50Ω line. Design a short circuited stub to provide matching between the Z_S & Z_L at a signal frequency of 30 MHz . (8)

Solution:-

Given:- $Z_0 = 50\Omega$; $Z_R = (50 + j100)\Omega$
 $f = 30\text{ MHz}$

$$\lambda = \frac{c}{f} = \frac{3 \times 10^8}{30 \times 10^6} = 10\text{ m.} \quad \boxed{\lambda = 10\text{ m}}$$

Reflection Coefficient :-

$$K = \frac{Z_R - Z_0}{Z_R + Z_0} \Rightarrow \frac{(50 + j100) - 50}{(50 + j100) + 50} \Rightarrow \frac{j100}{100 + j100}$$

$$K = \frac{100 \angle 90^\circ}{141.4 \angle 45^\circ} \Rightarrow \boxed{K = 0.707 \angle 45^\circ}$$

$$\boxed{|K| = 0.707 \quad ; \quad \phi = 45^\circ = \frac{\pi}{4}}$$

Location of the stub:-

9

$$l_s = \frac{\lambda}{4\pi} [\phi + \pi - \cos^{-1} |K|]$$
$$= \frac{10}{4\pi} \left[\frac{\pi}{4} + \pi - \cos^{-1}(0.707) \right] \Rightarrow \underline{\underline{2.5 \text{ m}}}$$

\downarrow
 $45^\circ = \frac{\pi}{4}$

3. A UHF lossless transmission line working at 1 GHz is connected to an unmatched line producing a reflection coefficient of $0.5(0.866 + j0.5)$. Calculate the length & position of the stub used to match the line.

Solution:-

Given:- Reflection Coefficient, $K = 0.5(0.866 + j0.5)$
 $f = 1 \text{ GHz}$

$$K = 0.433 + j0.25 = 0.5 \angle 30^\circ \quad \lambda = \frac{c}{f}$$

$$\boxed{\lambda = 0.3 \text{ m}}$$

$$|K| = 0.5 \quad \& \quad \phi = 30^\circ = \frac{\pi}{6}$$

position of the stub:-

(10)

$$\begin{aligned}l_s &= \frac{\lambda}{4\pi} \left[\phi + \pi - \cos^{-1}|K| \right] \\&= \frac{0.3}{4\pi} \left[\frac{\pi}{6} + \pi - \cos^{-1}|0.5| \right] \cdot \left[\begin{array}{l} \cos^{-1}(0.5) = 60^\circ \\ = \pi/3 \end{array} \right] \\&= \frac{0.3}{4\pi} \left[\frac{5\pi}{6} \right] \cdot \boxed{l_s = 0.625 \text{ m}}\end{aligned}$$

Length of the stub:-

$$\begin{aligned}l_t &= \frac{\lambda}{2\pi} \tan^{-1} \left\{ \frac{\sqrt{1 + |K|^2}}{2|K|} \right\} \\&= \frac{0.3}{2\pi} \tan^{-1} \left\{ \frac{\sqrt{1 + 0.5^2}}{2(0.5)} \right\} \\&= \frac{0.3}{2\pi} \tan^{-1}(0.866) = \frac{0.3}{2\pi} \cdot (40.8925^\circ) \\&= \frac{0.3}{2\pi} \left[40.8925 \times \frac{\pi}{180^\circ} \right] \Rightarrow 0.0341 \text{ m} \\&\quad \boxed{l_t = 3.41 \text{ cm}}\end{aligned}$$