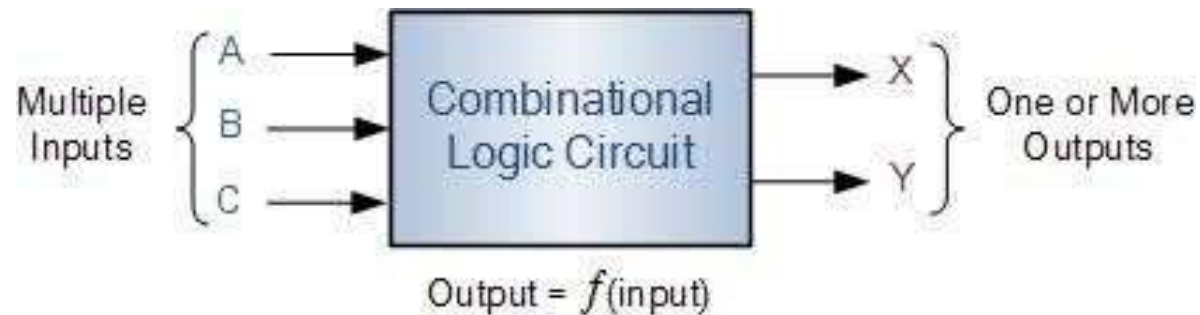


Unit - III

Sequential Circuits

Combinational Logic


- The outputs depend only on the state of the inputs all of the time. Any change in the state of one of the inputs will ripple through the circuit immediately.
 - Examples of combinational logic are NAND and NOR gates, Inverters, and Buffers. These four logic gates form the basis of almost all combinational logic circuits as well as **flip flops**.



Sequential Logic

- Has **memory**; the circuit stores the result of the previous set of inputs. The current output depends on inputs **in the past as well as present inputs**.
 - The basic element in sequential logic is the **bistable latch** or **flip-flop**, which acts as a memory element for one bit of data.
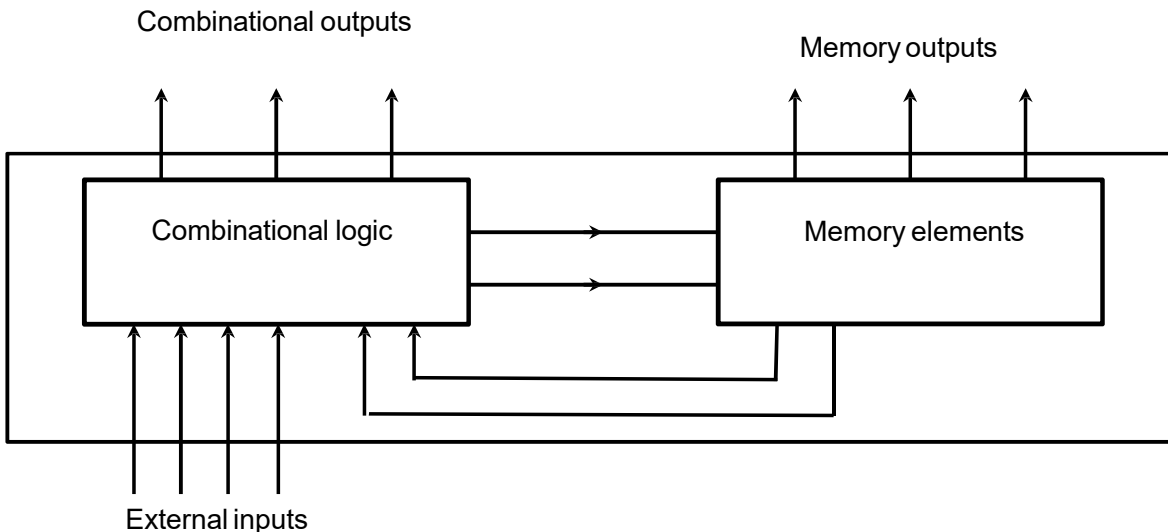
$$Z = f(A_t, A_{t-1}, \dots, B_t, B_{t-1}, \dots, C_t, C_{t-1}, \dots, D_t, D_{t-1}, \dots)$$




Two types:

- Finite memory system (only couple of previous inputs)
- Infinite memory system (all the past inputs)

Sequential circuit = Combinational logic + Memory Elements


Digital Circuits

Combinational Logic Circuit

 

- output depends on present inputs
- consisted of logic gates and combinational logic subsystems (multiplexer, etc)
- Applications: ALU, PLDs





Sequential Logic Circuit

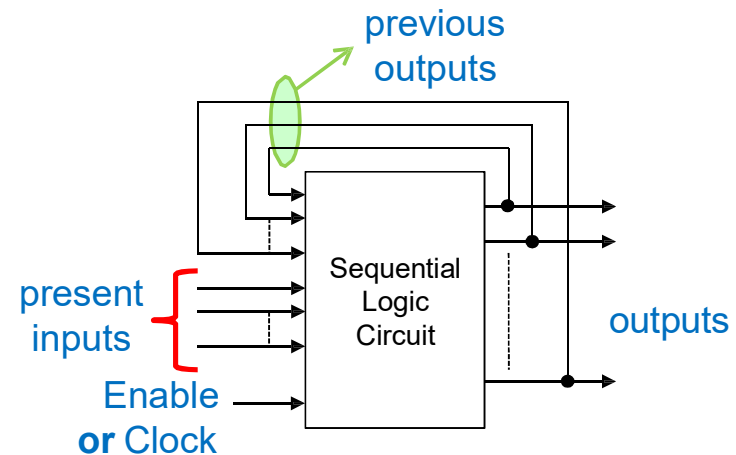

- output depends on present inputs and previous outputs
- enable or clock signal is used to synchronize the output change with time
- Applications: Counters, Shift registers


Design of basic storage element

- Digital circuit with feedback

    

SR Latch (NOR Gates)

 The **SR latch** is a circuit with two cross-coupled **NOR gates** or two cross-coupled **NAND gates**. It has two inputs labeled S for set and R for reset.



(a) Logic diagram

S	R	Q	Q'
1	0	1	0
0	0	1	0
0	1	0	1
0	0	0	1
1	1	0	0

(b) Function table

 


FIGURE 5.3

SR latch with NOR gates

R	S	Q	Q ⁺
0	0	Q	Q
0	1	X	1
1	0	X	0
1	1	X	Invalid


State table

Next state equation:

$$Q^+ = S + R'Q$$

SR Latch (NAND gates)

 The **SR latch** is a circuit with two cross-coupled **NOR gates** or two cross-coupled **NAND gates**. It has two inputs labeled **S** for set and **R** for reset.



S	R	Q	Q'
1	0	0	1
1	1	0	1 (after $S = 1, R = 0$)
0	1	1	0
1	1	1	0 (after $S = 0, R = 1$)
0	0	1	1 (forbidden)

(b) Function table


 
 


FIGURE 5.4
SR latch with NAND gates

SR Latch timing diagram

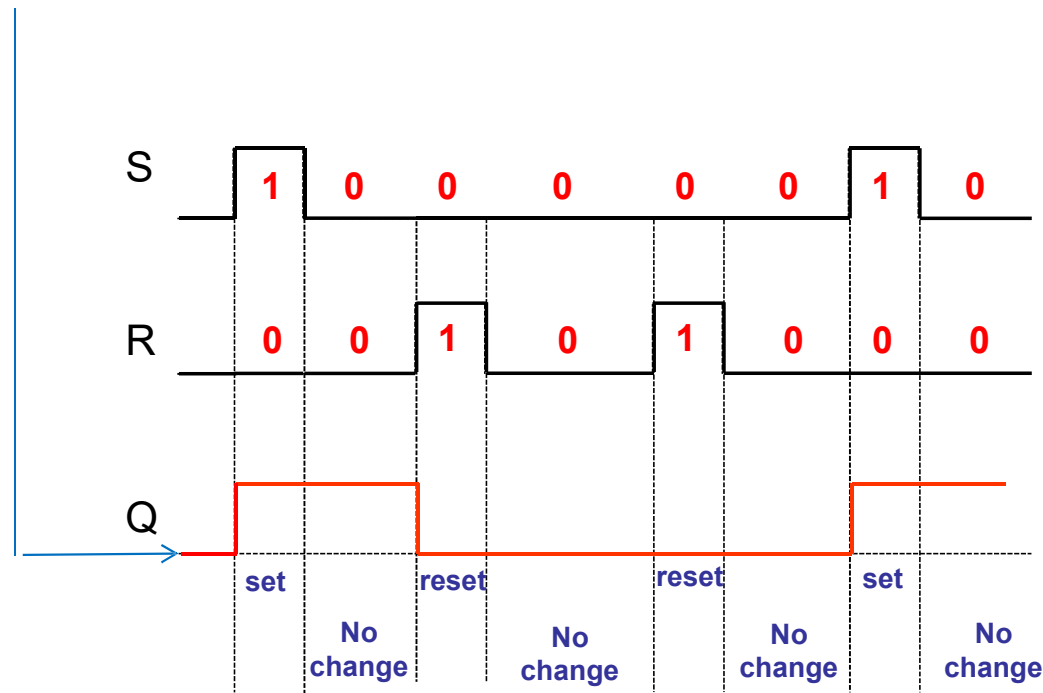- Draw the output waveform for the S, R inputs shown below for an active high input SR latch
- Assume $Q=0$ initially




S	R	Q	Q'
1	0	1	0
0	0	1	0 (after $S = 1, R = 0$)
0	1	0	1
0	0	0	1 (after $S = 0, R = 1$)
1	1	0	0 (forbidden)

 
(b) Function table

Gated SR Latch

- The operation of the basic SR latch can be modified by providing an additional control input that determines when the state of the latch can be changed. In Fig. 5-5, it consists of the **basic SR latch** and **two additional NAND gates**.



(a) Logic diagram

 


En	S	R	Next state of Q
0	X	X	No change
1	0	0	No change
1	0	1	$Q = 0$; reset state
1	1	0	$Q = 1$; set state
1	1	1	Indeterminate

(b) Function table


FIGURE 5.5
SR latch with control input

Gated SR Latch Timing diagram

1. Gated SR Latch

 


EN	S	R	Q
0	x	x	No change
1	0	0	No change
1	0	1	0 (Reset)
1	1	0	1 (Set)
1	1	1	Invalid

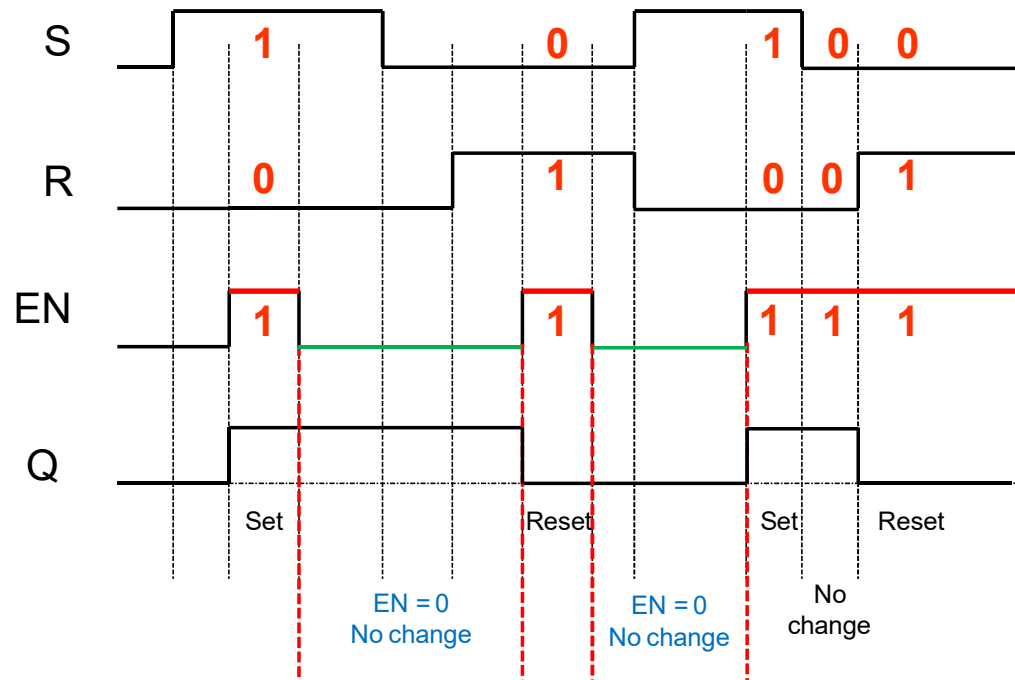

Assume Q=0 initially

Gated Latch

 


Level enabled

EN = 1, normal latch operation


EN = 0, no change in output even when inputs change

Flip-flop

 



Edge-triggered

CLOCK (CLK) signal

 

Flip Flops Vs Latches

- A flip flop is an electronic circuit with two stable states that can be used to store binary data.
- The stored data can be changed by applying varying inputs.
- **Latches and flip-flops** are circuit elements whose output depends not only on the current inputs, but also on previous inputs and outputs.
- The **difference between a latch and a flip-flop** is that a **latch** does not have a clock signal, whereas a **flip-flop** always does.

  

Flipflops

❑ A Flip Flop is a memory element that is capable of storing one bit of information.

❖ A flip flop can maintain a binary state for an unlimited period of time as long as-

(i) Power is supplied to the circuit.

(ii) or until it is directed by an input signal to switch states

Types of Flipflops

- SR Flip Flop
- JK Flip Flop
- D Flip Flop
- T Flip Flop


Latch VS Flipflop

Latches	Flip Flops
Latches are building blocks of sequential circuits and these can be built from logic gates	Flip flops are also building blocks of sequential circuits. But, these can be built from the latches.
Latch continuously checks its inputs and changes its output correspondingly.	Flip flop continuously checks its inputs and changes its output correspondingly only at times determined by clocking signal
The latch is sensitive to the duration of the pulse and can send or receive the data when the switch is on	Flipflop is sensitive to a signal change. They can transfer data only at the single instant and data cannot be changed until next signal change. Flip flops are used as a register.
It is based on the enable function input	It works on the basis of clock pulses
It is a level triggered, it means that the output of the present state and input of the next state depends on the level that is binary input 1 or 0.	It is an edge triggered, it means that the output and the next state input changes when there is a change in clock pulse whether it may a +ve or -ve clock pulse.

Steps to design Flipflops

- Circuit diagram using universal gates
- Truth Table
- Characteristics Equation
- Excitation Table
- State Diagram
- Timing (or) Switching (or) Waveform Diagram

S-R Flip flop

 

(i) Circuit diagram

(ii) Characteristics Table

C	S	R	Q_n	Q_{n+1}	State of Operation
1	0	0	0	0	hold
1	0	0	1	1	
1	0	1	0	0	clear (reset)
1	0	1	1	0	
1	1	0	0	1	set
1	1	0	1	1	
1	1	1	0	?	indeterminate
1	1	1	1	?	— avoid

(iii) Characteristic Equation

$$Q_{n+1} = S + Q_n R'$$


SR

	$\bar{S}\bar{R}$	$\bar{S}R$	SR	$S\bar{R}$
\bar{Q}_n			X	1
Q_n	1		X	1

(iv) Excitation Table


Q_n	Q_{n+1}	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

(v) State Diagram

 

(V) Timing (or) Switching (or) Waveform Diagram





When $Q_n=1$

 


<i>C</i>	<i>S</i>	<i>R</i>	Q_n	Q_{n+1}
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	?
1	1	1	1	?

(ii) Characteristics Table

Timing diagrams

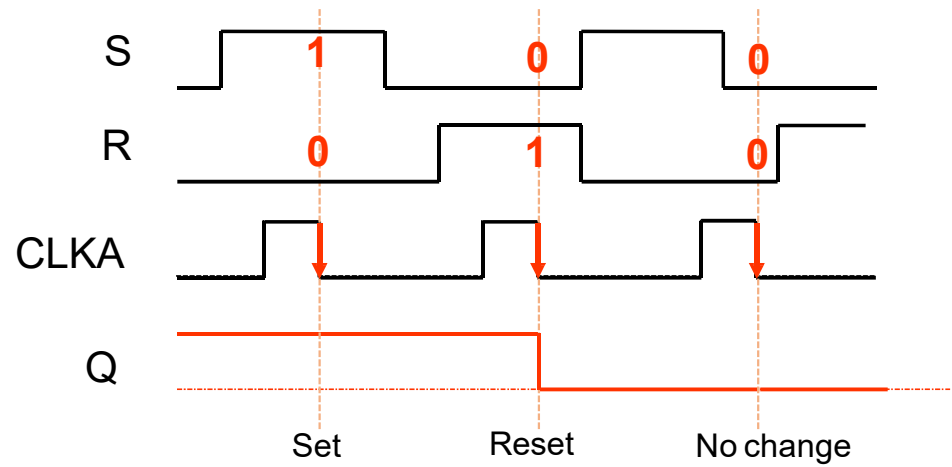 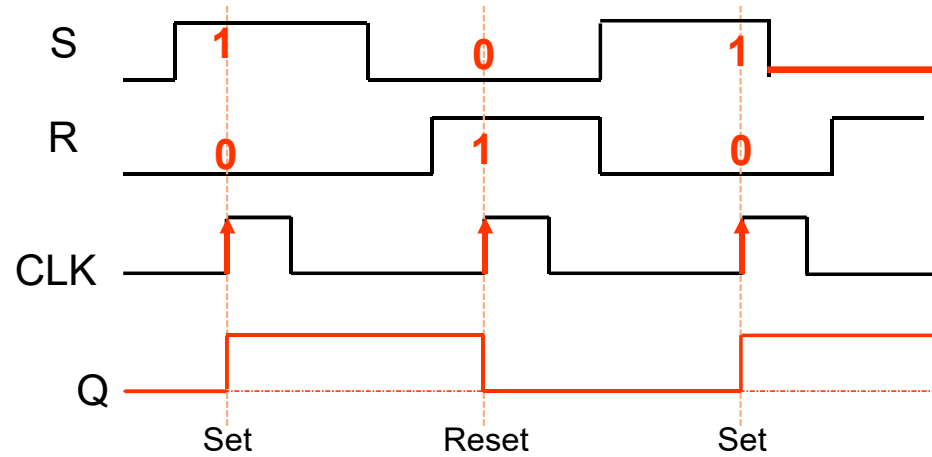 

D - Flip flop

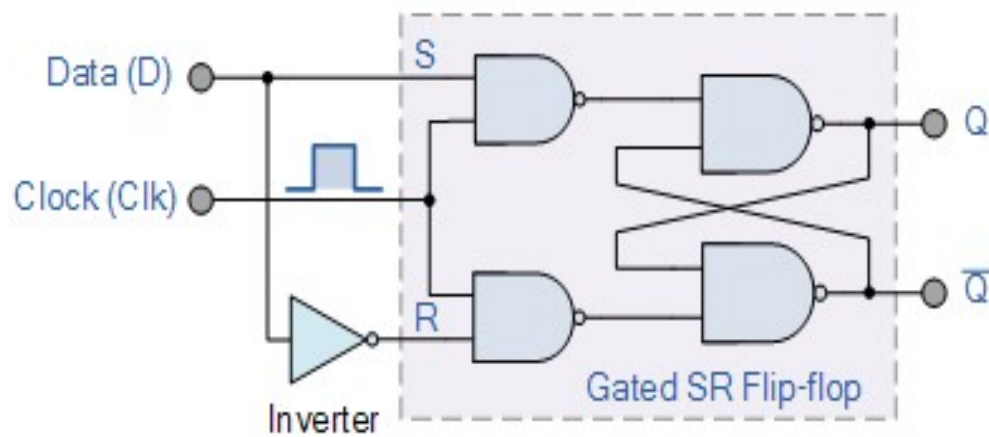

(i) Circuit diagram

C	<i>D</i>	Q_n	Q_{n+1}	State of Operation
1	0	0	0	Clear (reset)
1	0	1	0	
1	1	0	1	Set
1	1	1	1	

(ii) Characteristics Table

(iii) Characteristic Equation


$$Q_{n+1} = D$$

	Q_n'	Q_n
D'	0	0
D	1	1


(iv) Excitation Table

Q_n	Q_{n+1}	D
0	0	0
0	1	1
1	0	0
1	1	1

(v) State Diagram

 

 
(V) Timing (or) Switching (or) Waveform Diagram





(ii) Characteristics Table

C	D	Q_n	Q_{n+1}	State of Operation
1	0	0	0	Clear (reset)
1	0	1	0	
1	1	0	1	Set
1	1	1	1	


timing diagrams

 

Assume Q=0 initially

  


Assume Q₁=0 initially

 

J-K Flip flop

- A J-K flip-flop behaves in the same fashion as an R-S flip-flop except for one of the entries in the function table.
- In the case of an R-S flip-flop, the input combination $S = R = 1$ are prohibited.
- In the case of a J-K flip-flop, the output of the flip-flop toggles, that is, it goes to the other state, for $J = K = 1$.
- Thus, a J-K flip-flop overcomes the problem of a forbidden input combination of the R-S flip-flop.

(i) Circuit diagram

 

(ii) Characteristics Table

C	J	K	Q_n	Q_{n+1}	State of Operation
1	0	0	0	0	hold
1	0	0	1	1	
1	0	1	0	0	clear (reset)
1	0	1	1	0	
1	1	0	0	1	set
1	1	0	1	1	
1	1	1	0	1	Toggle
1	1	1	1	0	

(iii) Characteristic Equation


$$Q_{n+1} = Q'_n J + Q_n K'$$

Q_n	JK			
	$\bar{J}\bar{K}$	$\bar{J}K$	JK	$J\bar{K}$
\bar{Q}_n			1	1
Q_n	1			1

(iv) Excitation Table


Q_n	Q_{n+1}	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0


(v) State Diagram

 



(V) Timing (or) Switching (or) Waveform Diagram

When $Q_n=1$

 


 

Assume Q=0 initially

 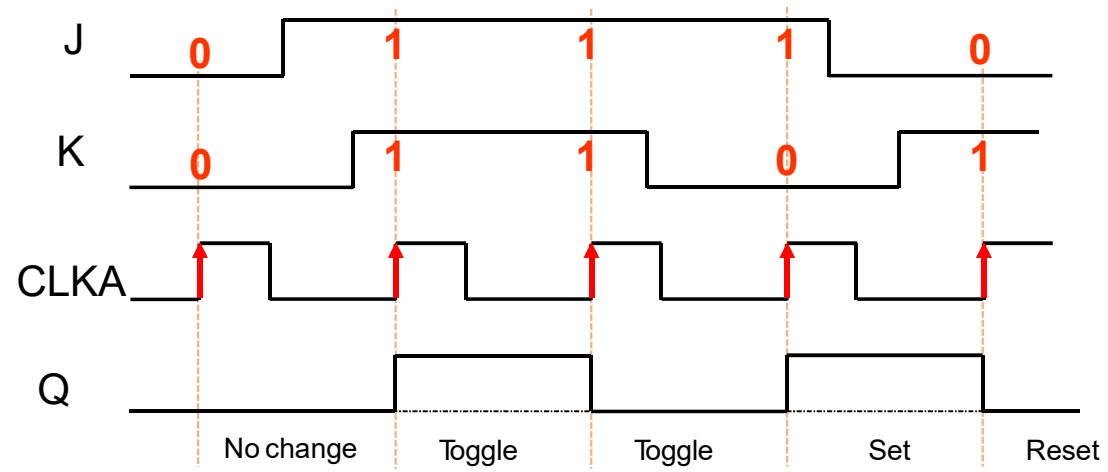


Assume Q=0 initially

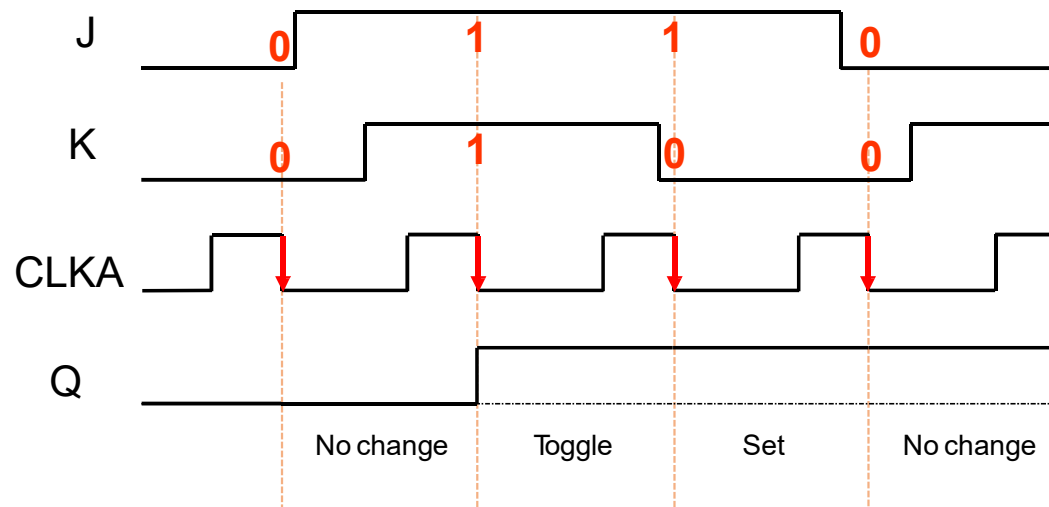

T Flipflop

(i) Circuit Diagram

 

(ii) Characteristics Table

	Previous		Next	
T	Q_{Prev}	Q'_{Prev}	Q_{Next}	Q'_{Next}
0	0	1	0	1
0	1	0	1	0
1	0	1	1	0
1	1	0	0	1

(iii) Characteristic Equation

Q_p	T	0	1
	0	0	1
1	1	1	0


The Equation we get is

$$\begin{aligned} Q &= T Q_p' + T' Q_p \\ &= T \text{ XOR } Q_p \end{aligned}$$


(iv) Excitation Table

Q	Q^+	T
0	0	0
0	1	1
1	0	1
1	1	0


(v) State Diagram

 


(vi) Timing Diagram

 


Race around condition in JK FF

 

Master slave JK flipflop

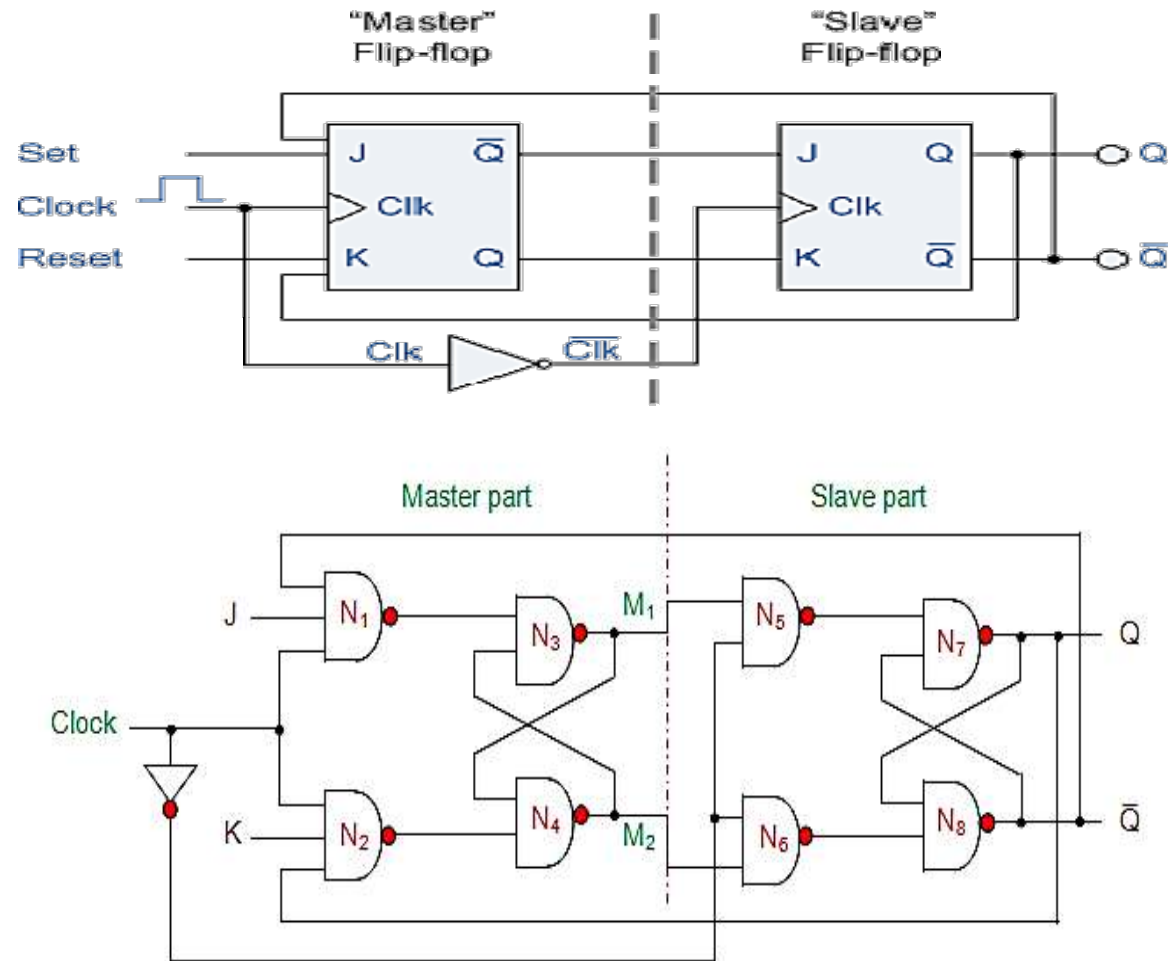

Master slave JK flipflop

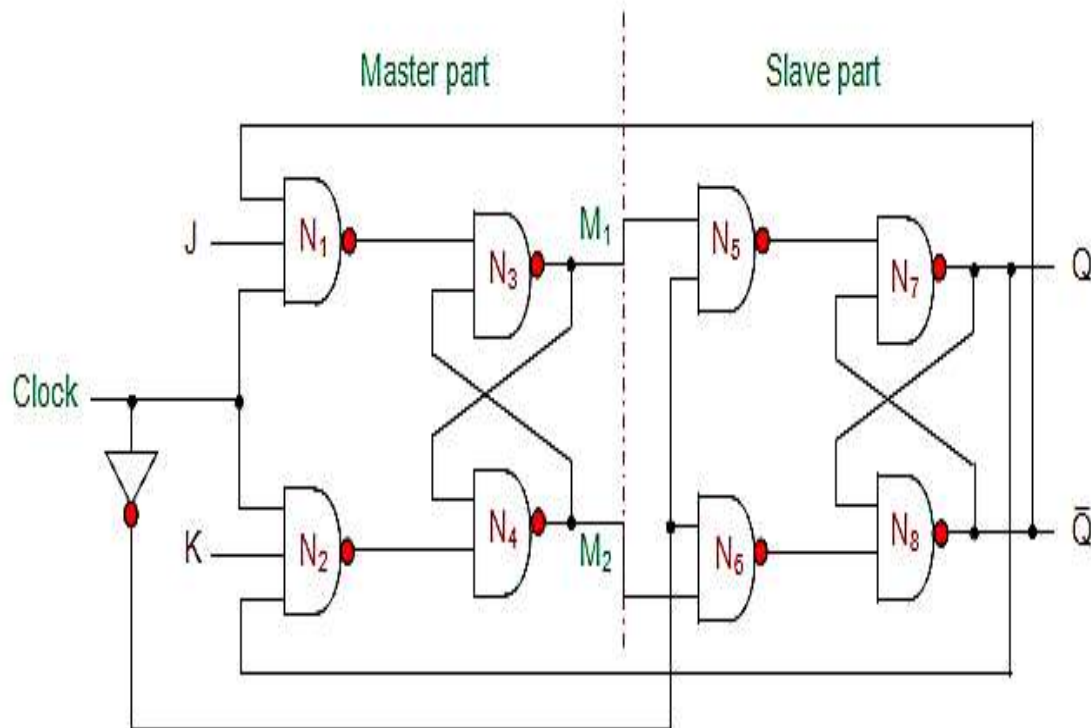

Trigger	Inputs		Output						Inference
			Present State		Intermediate		Next State		
CLK	J	K	Q	\bar{Q}	M ₁	M ₂	Q	\bar{Q}	
↑	0	0	0	1	0	1	Latched		No Change
↓			0	1	Latched		0	1	
↑			1	0	Latched		1	0	
↓			1	0	Latched		1	0	
↑	0	1	0	1	0	1	Latched		Reset
↓			0	1	Latched		0	1	
↑			1	0	Latched		0	1	
↓			1	0	Latched		0	1	
↑	1	0	0	1	1	0	Latched		Set
↓			0	1	Latched		1	0	
↑			1	0	Latched		1	0	
↓			1	0	Latched		1	0	
↑	1	1	0	1	1	0	Latched		Toggles
↓			0	1	Latched		1	0	
↑			1	0	Latched		0	1	
↓			1	0	Latched		0	1	

Table I Truth table for master-slave JK flip-flop

Master slave JK flipflop

Trigger	Inputs		Output						Inference
			Present State		Intermediate		Next State		
CLK	J	K	Q	\bar{Q}	M_1	M_2	Q	\bar{Q}	
↑	0	0	0	1	0	1	Latched		No Change
↓			0	1	Latched		0	1	
↑			1	0	Latched		1	0	
↓			1	0	Latched		1	0	
↑	0	1	0	1	0	1	Latched		Reset
↓			0	1	Latched		0	1	
↑			1	0	Latched		0	1	
↓			1	0	Latched		0	1	
↑	1	0	0	1	1	0	Latched		Set
↓			0	1	Latched		1	0	
↑			1	0	Latched		1	0	
↓			1	0	Latched		1	0	
↑	1	1	0	1	1	0	Latched		Toggles
↓			0	1	Latched		1	0	
↑			1	0	Latched		0	1	
↓			1	0	Latched		0	1	

Table 1 Truth table for master-slave JK flip-flop

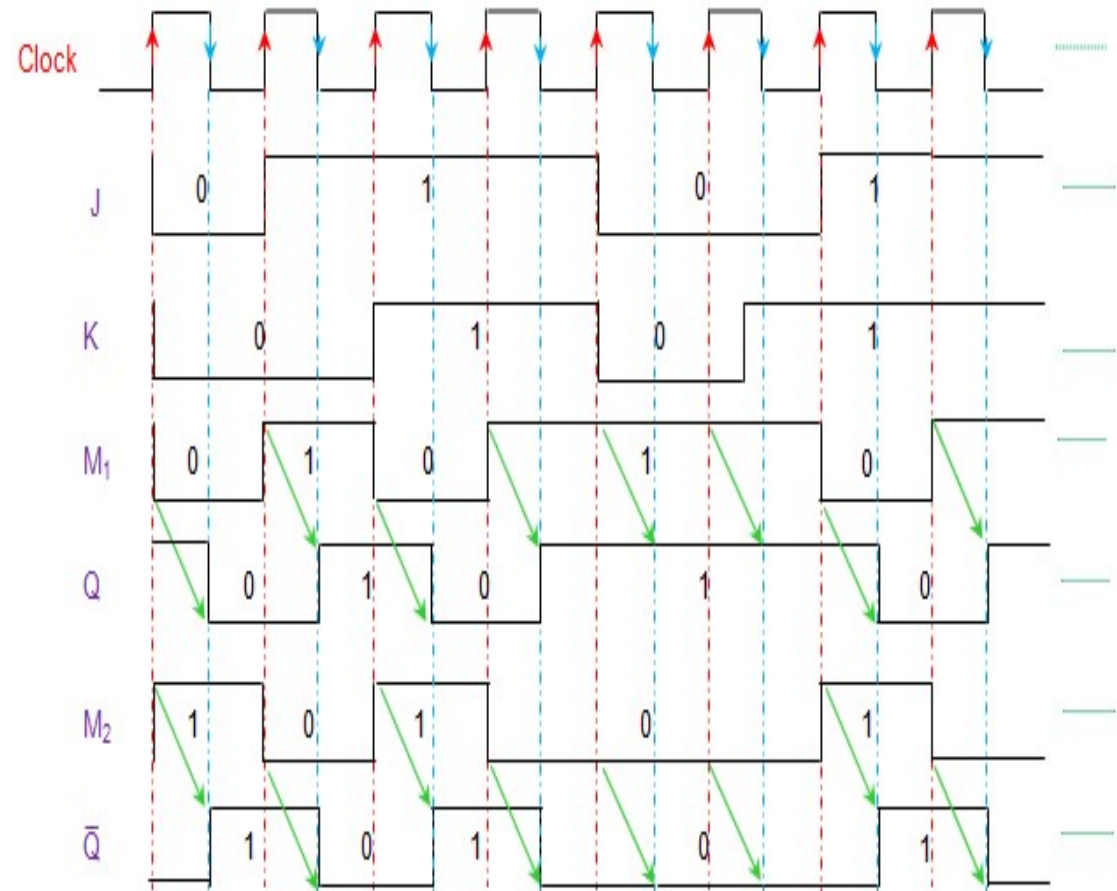


Figure 3 Timing diagram for master-slave JK flip-flop





Excitation Tables

RS FLIP FLOP							
Characteristics Table				Excitation Table			
S	R	Q_{n+1}		Q_n	Q_{n+1}	S	R
0	0	Q_n		0	0	0	X
0	1	0		0	1	1	0
1	0	1		1	0	0	1
1	1	X		1	1	X	0

JK FLIP FLOP							
Characteristics Table				Excitation Table			
J	K	Q_{n+1}		Q_n	Q_{n+1}	J	K
0	0	Q_n		0	0	0	X
0	1	0		0	1	1	X
1	0	1		1	0	X	1
1	1	Q_n'		1	1	X	0

D FLIP FLOP					
Characteristics Table				Excitation Table	
D	Q_n	Q_{n+1}		Q_n	D
0	0	0		0	0
0	1	0		0	1
1	0	1		1	0
1	1	1		1	1



T FLIP FLOP					
Characteristics Table				Excitation Table	
T	Q_n	Q_{n+1}		Q_n	T
0	0	0		0	0
0	1	1		0	1
1	0	1		1	0
1	1	0		1	1

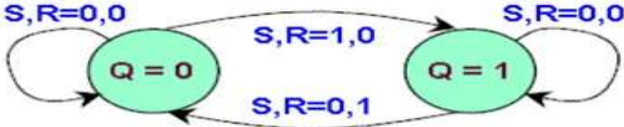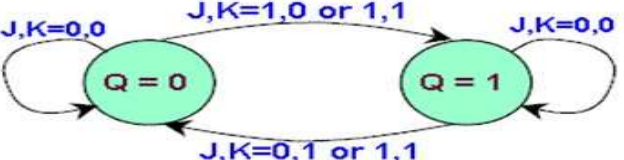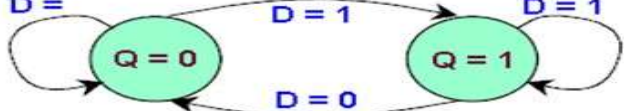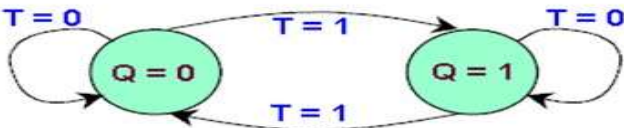NAME	STATE DIAGRAM
SR	 <p>State diagram for SR flip-flop showing two states: $Q = 0$ and $Q = 1$. Transitions are labeled with S, R values:</p> <ul style="list-style-type: none"> From $Q = 0$ to $Q = 0$: $S, R = 0, 0$ From $Q = 0$ to $Q = 1$: $S, R = 1, 0$ From $Q = 1$ to $Q = 1$: $S, R = 0, 0$ From $Q = 1$ to $Q = 0$: $S, R = 0, 1$
JK	 <p>State diagram for JK flip-flop showing two states: $Q = 0$ and $Q = 1$. Transitions are labeled with J, K values:</p> <ul style="list-style-type: none"> From $Q = 0$ to $Q = 0$: $J, K = 0, 0$ From $Q = 0$ to $Q = 1$: $J, K = 1, 0$ or $1, 1$ From $Q = 1$ to $Q = 1$: $J, K = 0, 0$ From $Q = 1$ to $Q = 0$: $J, K = 0, 1$ or $1, 1$
D	 <p>State diagram for D flip-flop showing two states: $Q = 0$ and $Q = 1$. Transitions are labeled with D values:</p> <ul style="list-style-type: none"> From $Q = 0$ to $Q = 0$: $D = 0$ From $Q = 0$ to $Q = 1$: $D = 1$ From $Q = 1$ to $Q = 1$: $D = 1$ From $Q = 1$ to $Q = 0$: $D = 0$
T	 <p>State diagram for T flip-flop showing two states: $Q = 0$ and $Q = 1$. Transitions are labeled with T values:</p> <ul style="list-style-type: none"> From $Q = 0$ to $Q = 0$: $T = 0$ From $Q = 0$ to $Q = 1$: $T = 1$ From $Q = 1$ to $Q = 1$: $T = 0$ From $Q = 1$ to $Q = 0$: $T = 1$

REGISTERS

Shift registers are types of sequential logic circuits closely related to digital counters used primarily for the **storage of data**


DATA STORAGE

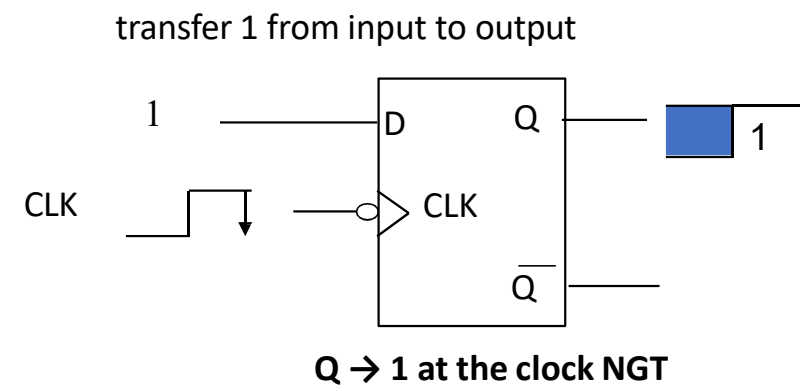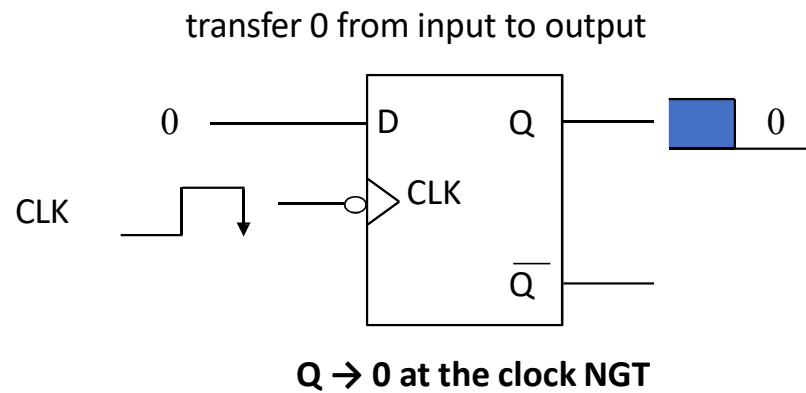

DATA STORAGE AND SHIFT

- Storage capacity (number of bits) of a register is determined by the number of flip-flops
 - One flip flop represents one bit of data storage
 - “n” number of flip-flops can store an **n-bit** data
- The FFs interconnection should facilitate
 - transfer of binary data into and out of the register, and
 - shifting data within the register one or more bit positions left or right, effected upon the application of clock pulses
- If no clock pulses are applied, there will be no data shift in the register

Ring counter

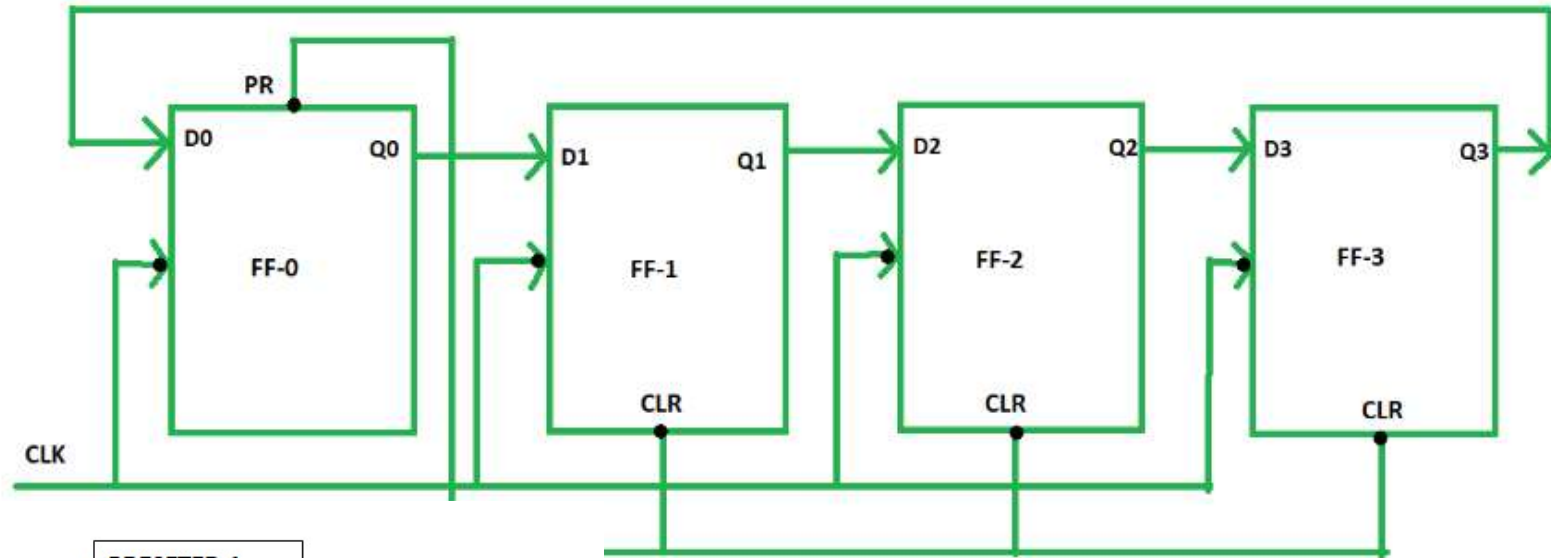


PRESETED 1

ORI	CLK	Q0	Q1	Q2	Q3
low	X	1	0	0	0
high	low	0	1	0	0
high	low	0	0	1	0
high	low	0	0	0	1
high	low	1	0	0	0

Ring Counter

- It is a Synchronous Counter.
- Also, here we use Overriding input (ORI) for each flip-flop. Preset (PR) and Clear (CLR) are used as ORI.
- When PR is 0, then the output is 1 and when CLR is 0, then the output is 0.
- Both PR and CLR are active low signal that always works in value 0.

Johnson counter

 

CP	Q1	Q2	Q3	Q4
0	0	0	0	0
1	1	0	0	0
2	1	1	0	0
3	1	1	1	0
4	1	1	1	1
5	0	1	1	1
6	0	0	1	1
7	0	0	0	1
8	0	0	0	0





- Johnson counter also known as creeping counter
- In Johnson counter, the complemented output of last flip flop is connected to input of first flip flop and to implement n-bit Johnson counter we require n flip-flop.
- It is one of the most important type of shift register counter.
- Johnson counter is a ring with an inversion.

In Johnson counter

 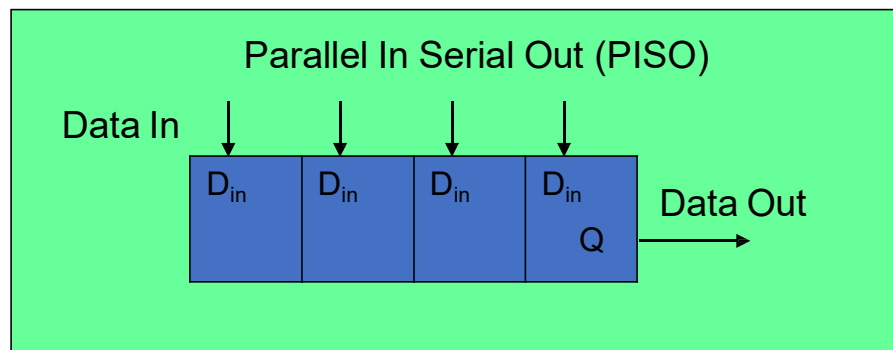  - 1.No. of states in Johnson counter = No. of flip-flop used
- 2.Number of used states= $2n$
- 3.Number of unused states= $2n - 2*n$

DATA MANIPULATION

- Data can written in and read out from a register either serially (one bit at a time) or in parallel (all bits simultaneously)



4 TYPES OF DATAMOVEMENT

Type 1 - Serial In Parallel Out (SIPO)

Data bits are entered serially into the shift register.
Each bit appears on its respective output line, and all bits are available simultaneously.

Type 2 - Serial In Serial Out (SISO)

The serial in serial out shift register accepts data serially, i.e. one bit at a time on a single line.
It produces stored information on its output also in serial form.

4 TYPES OF DATAMOVEMENT

Type 3 - Parallel In Serial Out (PISO)

Data bits are entered simultaneously into their respective stages in parallel fashion.

The output is serial i.e. shifting one bit at a time on a single line.



Type 4 - Parallel In Parallel Out (PIPO)

Data bits are entered simultaneously into their respective stages in parallel. All bits are also available at the respective output stage in parallel.

SIPO Register Basic Operation

- Accepts data serially on bit by bit basis
- Once data is stored, each data bit appears simultaneously on its respective output line
- Application of SIPO:
 - A computer or microprocessor based system commonly processes data in parallel format.
 - Hence, serial incoming data is converted into parallel format through a SIPO register

Example 1: 4-bit Shift SIPO Register

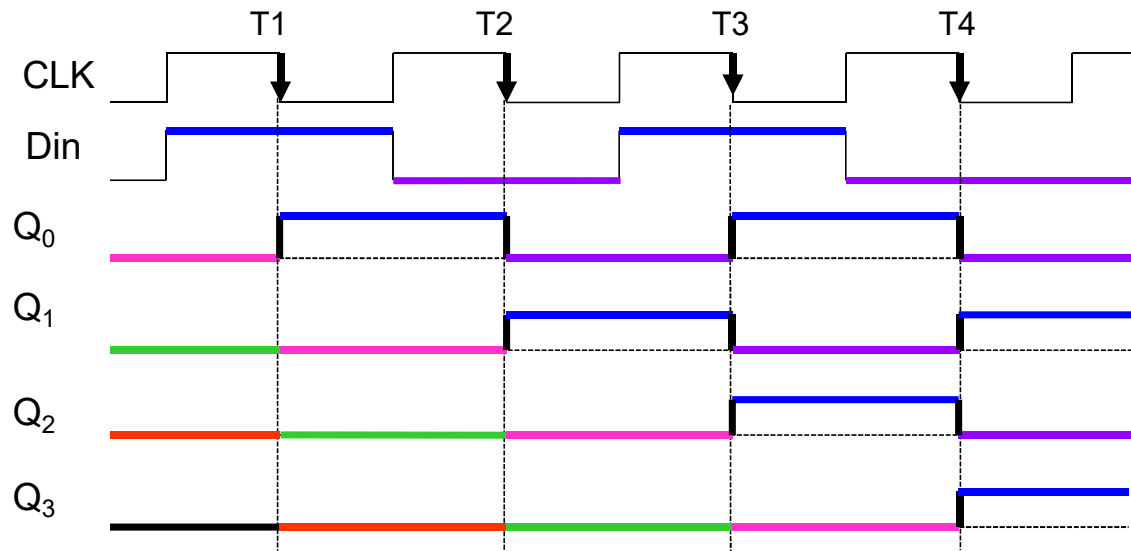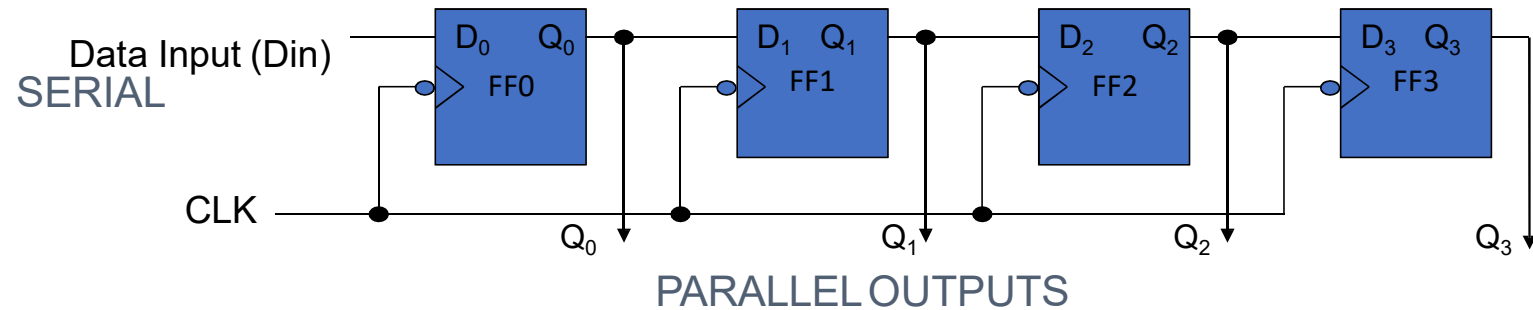



CLK	Din	Q ₀	Q ₁	Q ₂	Q ₃
Initial	x	0	0	0	0
T1	1	1	0	0	0
T2	0	0	1	0	0
T3	1	1	0	1	0
T4	0	0	1	0	1

Show the contents of the register for the data input and clock given. Initial register value is 0.

SISO Register Basic Operation


- Data is shifted into the register on bit by bit basis.
- After the data is stored completely, it can be shifted out serially upon further application of the clock pulses
- Application of the SISO Register
 - The SISO shift register can be used to provide a time delay from input to output.
 - This delay is a function of the number of FFs in the register and clock period.

4-bit SISO shift register using D-FFs

  

Data Advance (clock) connected to PGT → Data is shifted when clock signal changes from 0 to 1


Example 2: 3-bit shift SISO register

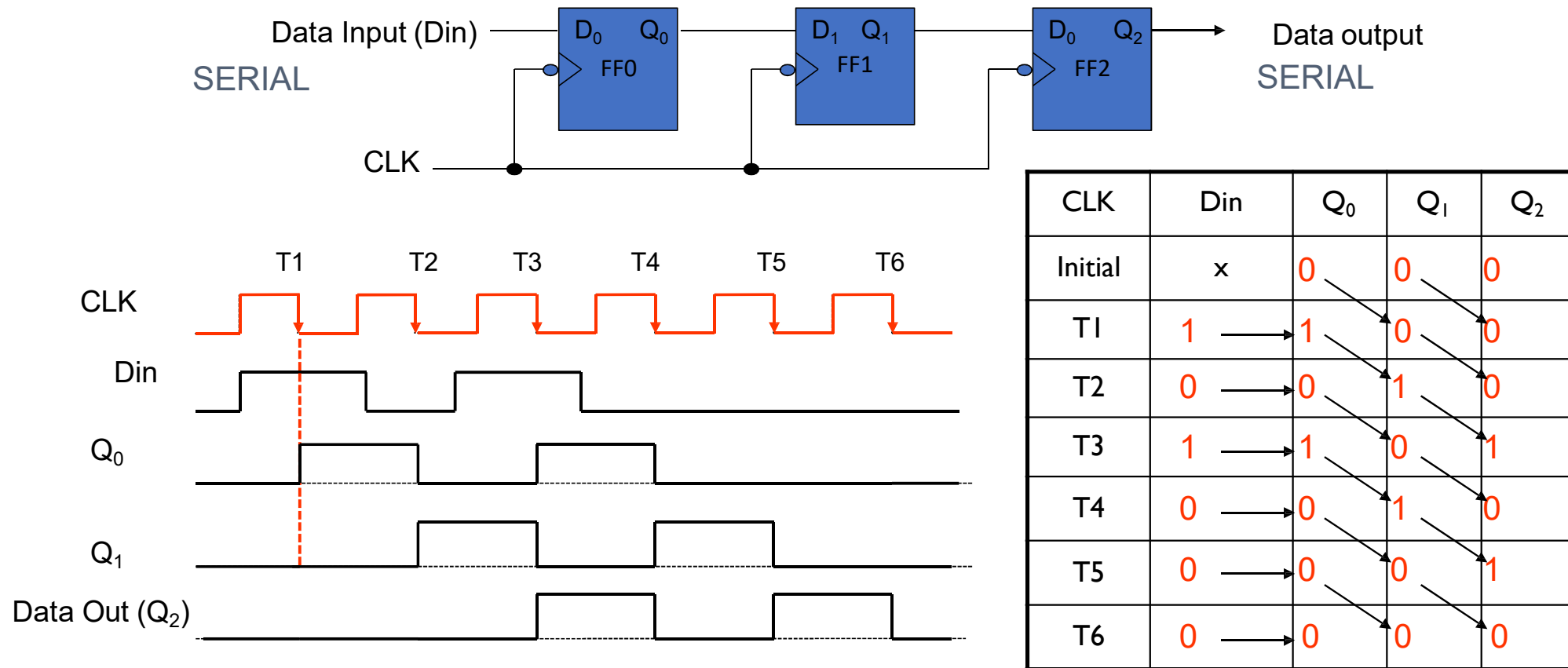

- Show the state of the output Q of the 3-bit SISO register for the data input and clock given.
Initial register value is 0.

Parallel In Parallel Out Shift Register

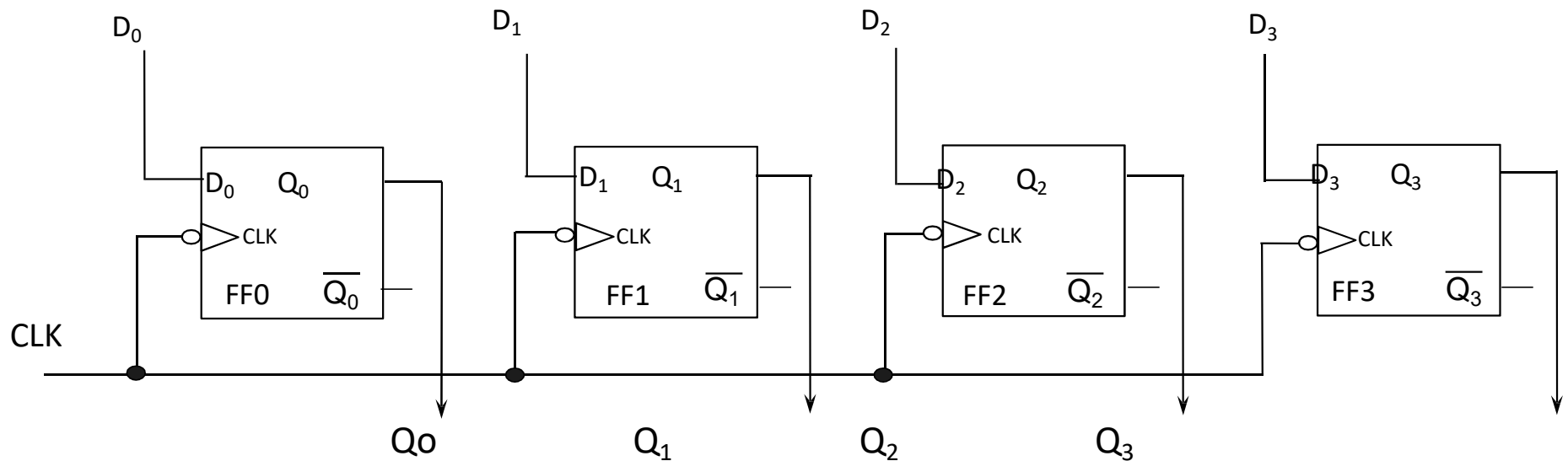
- All the data bits are entered and available on the output lines simultaneously.
- Application: For synchronization of signals and data transfer



4-bit PIPO shift register using D flip-flops

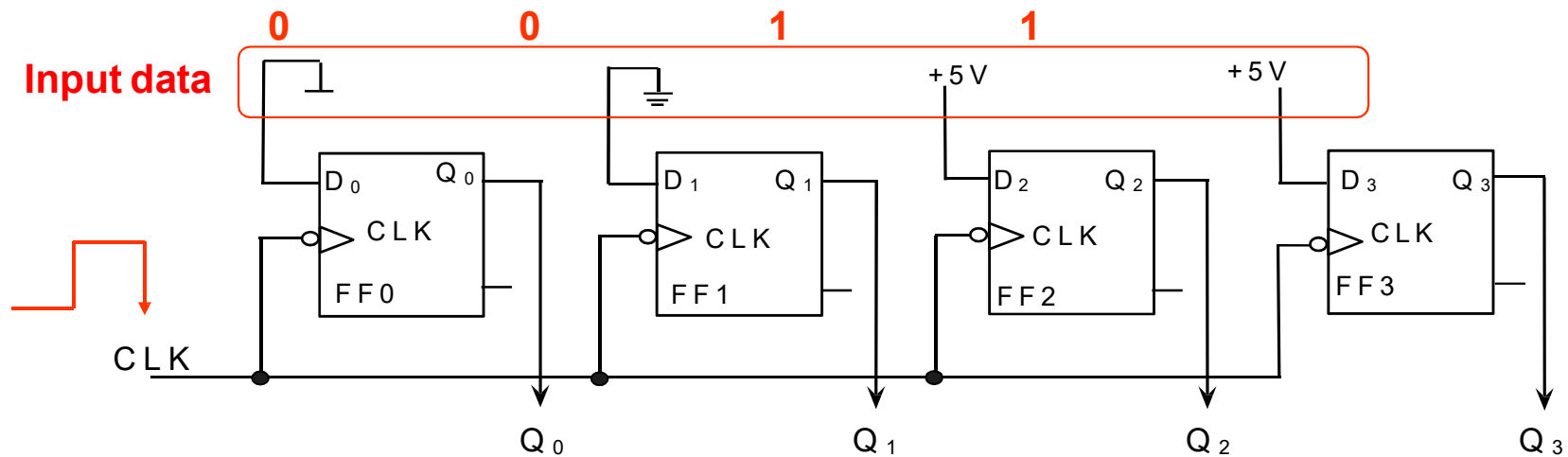Example 4

For the 4-bit PIPO register below, the initial states are given $Q_0Q_1Q_2Q_3 = 1000$. what are the outputs of registers immediately after 3rd clock pulse?



Outputs of registers will always be 0011 after first and subsequent clock pulses. Why?


Input data at D is fixed

Parallel In Serial Out Shift Register

- Loading: Data bits are loaded simultaneously in parallel to their respective flip-flops. This happens when $SH/\overline{LD} = 0$ and inputs are taken from parallel data Q_A - Q_H .
- Shifting: Once data is completely stored in the register, it is shifted out serially bit by bit. This happens when $SH/\overline{LD} = 1$ and input bit for 1st FF is taken from SER input.

Parallel In - Serial Out Shift Registers

- The circuit uses D flip-flops and NAND gates for entering data (ie writing) to the register.
- D0, D1, D2 and D3 are the parallel inputs, where D0 is the most significant bit and D3 is the least significant bit.
- To **write** data in, the **mode control line is taken to LOW** and the data is clocked in.
- The data can be **shifted** when the **mode control line is HIGH** as SHIFT is active high.

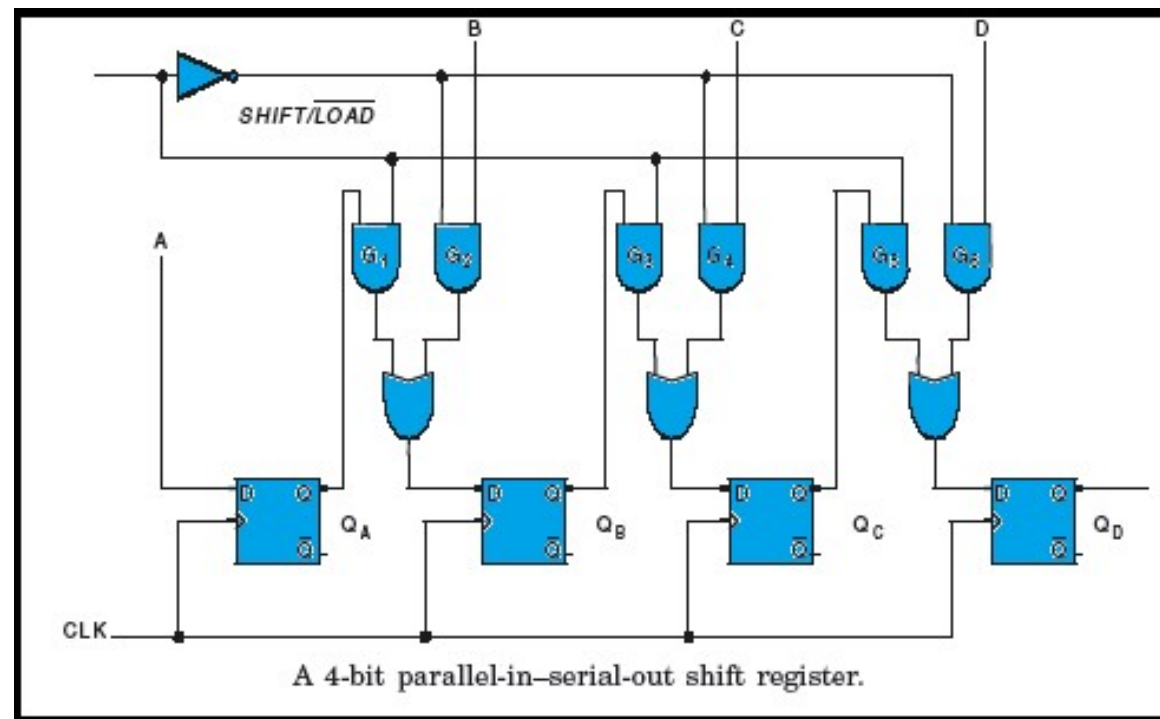


	Q ₀	Q ₁	Q ₂	Q ₃	
Clear	0	0	0	0	
Write	1	0	0	1	
Shift	1	0	0	1	
	1	1	0	0	1
	1	1	1	0	01
	1	1	1	1	001
	1	1	1	1	1001

Universal Shift Register

- The universal shift register can be defined as “The register which can be used to shift the data in both the directions like left, right and can load parallel data as well”.
- This register can perform three types of operations, stated below.
 - Parallel loading
 - Shifting left
 - Shifting right.

S0	S1	Operating Mode
0	0	Parallel Loading
1	0	Shift-Right
0	1	Shift-Left
1	1	Locked

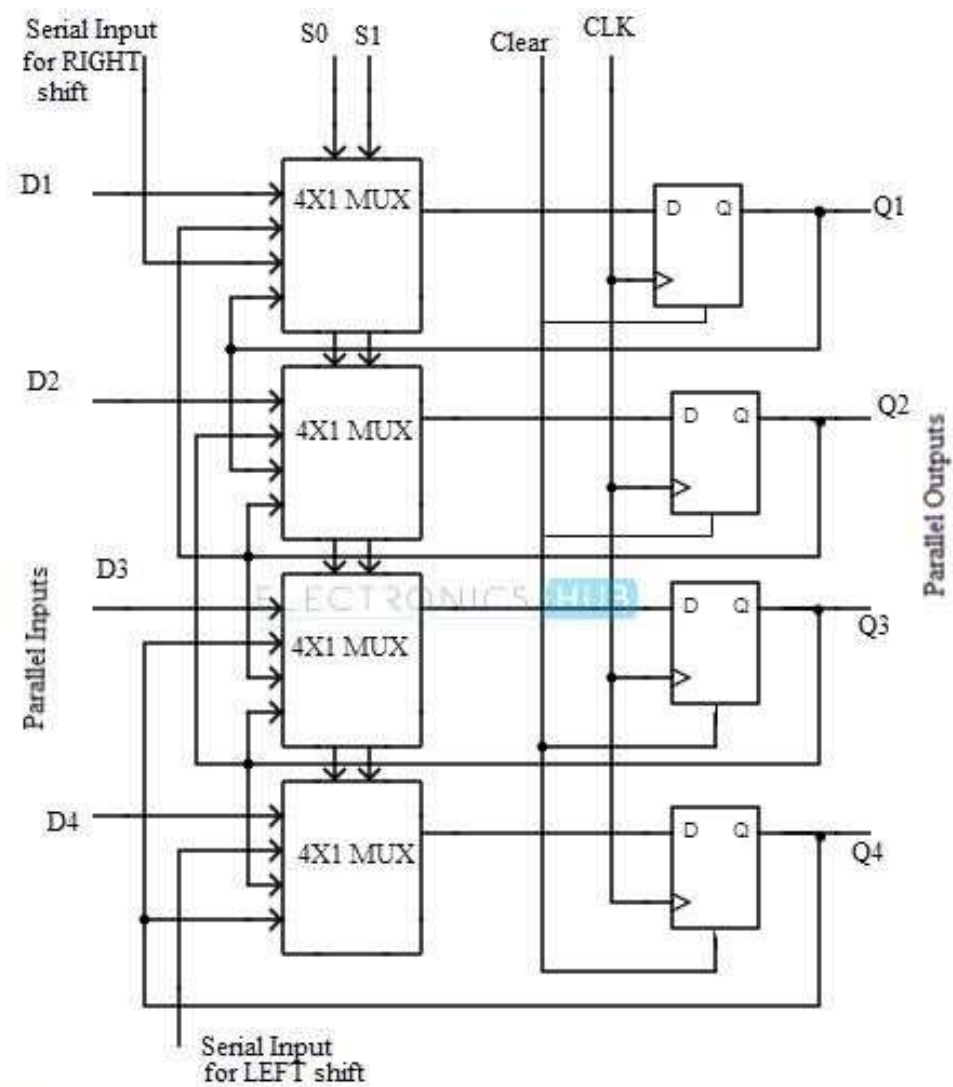

Applications of Shift Register

- Delay line
- Serial to parallel converter
- Parallel to serial converter
- Shift register counter
- Sequence generator