

SRM INSTITUTE OF SCIENCE AND TECHNOLOGY
Department of Electronics and Communication Engineering

18ECC206J-VLSI DESIGN LAB

Laboratory Manual



College of Engineering & Technology
SRM Institute of Science and Technology
Tiruchrappalli – 621 105,
Near Samamyapuram Toll Plaza,
Tamilnadu

SRM Institute of Science and Technology

Department of Electronics and Communication Engineering

Vision of the Department

1. To create and disseminate knowledge in the area of Electronics and Communication Engineering through national and international accredited educational process.
2. To facilitate a unique learning and research experience to the students and faculty.
3. To prepare the students as highly ethical and competent professionals.

Mission of the Department

1. Build an educational process that is well suited to local needs as well as satisfies the national and international accreditation requirements.
2. Attract the qualified professionals and retain them by building an environment that fosters work freedom and empowerment.
3. With the right talent pool, create knowledge and disseminate, get involved in collaborative research with reputed universities and produce competent grandaunts.

Program Educational Objectives (PEO)

Program Educational Objectives for the Electronics and Communication Engineering program describes accomplishments that graduates are expected to attain within a few years of graduation. Graduates will be able to:

PEO1: Establish themselves as successful and creative practicing professional engineers both nationally and globally in the related fields of Electronics and Communication Engineering.

PEO2: Apply the acquired knowledge and skills in solving real-world engineering problems; develop novel technology and design products, which are economically feasible and socially relevant.

PEO3: Develop an attitude of lifelong learning for sustained career advancement and adapt to the changing multidisciplinary profession.

PEO4: Demonstrate leadership qualities, effective communication skills, and to work in a team of enterprising people in a multidisciplinary and multicultural environment with strong adherence to professional ethics.

18ECC206J VLSI Design

| Sl. No. | Description of experiments | Session |
|---|---|---------|
| Software's: Synthesis tool: Xilinx ISE; Simulation tool: Modelsim Simulator /HSPICE | | |
| 1 | Lab 0: Verilog Operators | 1 |
| 2 | Lab 1: Realization of Combinational and Sequential Circuits | 2 |
| 3 | Lab 2: (a) Realization of digital circuits using behavioral modeling (b) Realization of MOS Circuit using Switch level Modeling | 3 |
| 4 | Lab 3: Design using FSM and ASM charts | 4 |
| 5 | Lab 4: Realization of VLSI Adders-I | 5 |
| 6 | Lab 5: Realization of VLSI Adders-II | 6 |
| 7 | Lab 6: Realization of VLSI Multiplier-I | 7 |
| 8 | Lab 7: Realization of VLSI Multiplier-II | 8 |
| 9 | Lab 8: Realization of RAM and ROM | 9 |
| 10 | Lab 9: Design and Analysis of CMOS inverter using HSPICE | 10 |
| 11 | Lab 10: (a) Design and Analysis of Complex CMOS gate using HSPICE (b) Design and Analysis of Pseudo NMOS gate using HSPICE | 11 |
| 12 | Lab 11: (a) Design and Analysis of AND/NAND gate in DCVSL using SPICE (b) Design and Analysis of Pass transistor gate and CPL gates using HSPICE | 12 |
| 13 | Lab 12: Design and analysis of 4- input Dynamic NAND gate using HSPICE | 13 |
| 14 | Lab 13: Model Practical Examination | 14 |
| 15 | Lab 14: End Semester Practical Examination | 15 |

1.Evaluation Scheme

| Component | Assessment Tool | Weightage |
|-------------------------------------|---|------------|
| Practical | Course Learning Assessment P1 | 5% |
| | Course Learning Assessment P2 | 7.5% |
| | Course Learning Assessment P3 | 7.5% |
| | Course Learning Assessment P4 (Model Practical Exam and Mini Project) | 5% |
| End-Semester Lab Examination | | 25% |

2.Assessment Method – Lab Report

| Component | Assessment Tool | Weightage |
|------------------------|--------------------------------------|-----------|
| Lab Report – Practical | Prelab and Post lab | 10 |
| | Design, HDL Code, In-Lab Performance | 15 |
| | Simulation and Results | 10 |
| | Lab Report | 05 |
| | Total | 40 |

- Soft copy of manual (student's Copy) will be posted in the Google classroom.
- Lab report format should follow the following details
 - Aim
 - Software required
 - Pre-Lab answers
 - Circuit Diagram, Truth table, Boolean Expression for each problem statement
 - Program code
 - Test bench code
 - Simulated output
 - Post-Lab answers
 - Results
- Lab report has to be uploaded in the Google classroom with in immediate next week.
- Design of Microprocessor components has been suggested for Mini Project Assessment.

Laboratory Report Cover Sheet

| |
|---|
| SRM INSTITUTE OF SCIENCE AND TECHNOLOGY College of Engineering and Technology Department of Electronics and Communication Engineering |
| 18ECC206J VLSI Design VI Semester, 2023-2024 (Even Semester) |

Name:

Register No.:

Title of Experiment:

Date of Conduction:

Date of Submission:

| Particulars | Max. Marks | Marks Obtained |
|--------------------------------------|------------|----------------|
| Pre-Lab and Post Lab | 10 | |
| Design, HDL Code, In-Lab Performance | 15 | |
| Output verification & viva | 10 | |
| Lab Report | 05 | |
| Total | 40 | |

REPORT VERIFICATION

Staff Name :

Signature:

Lab Experiment #1

Realization of Combinational and Sequential Circuits Using Gate-Level and Dataflow Modeling

1.1 Objective: To learn the design of combinational and sequential circuits using Gate-Level and Dataflow modeling in Verilog then simulating and synthesizing using EDA tools

1.2 Software tools Requirement

Equipment's:

Computer with Xilinx and Modelsim Software Specifications:

HP Computer P4 Processor – 2.8 GHz, 2GB RAM, 160 GB Hard Disk

Software's: Synthesis tool: Xilinx ISE

Simulation tool: Modelsim Simulator

1.3 Prelab Questions

(write pre lab Q & A in an A4 sheet)

1. List the types of design methodologies for digital design with an example?
2. Give the difference between module and module instance.
3. What are built in gate primitives?
4. Give the use of net, reg. and wire data types.
5. Declare the following variables in Verilog:


1.4.1 Problem 1: Write a Verilog code to implement Ripple Carry Adder.

The following points should be taken care of:


1. Use assign statement to design sub module half adder
2. Use gate primitives to design full adder using half adder
3. Construct the top module 4-bit ripple carry adder using 1-bit full adder

Logic Diagram – Problem 1


Half adder:

 

Full adder:

 

Ripple Carry Adder

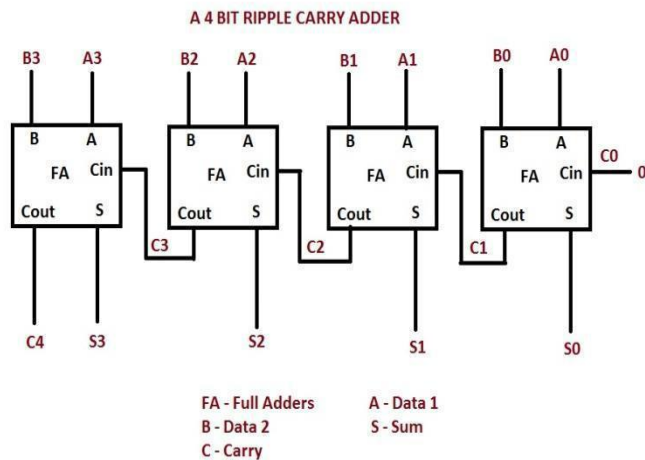

Verilog Code - Problem 1

1.(a) HALF ADDER USING DATA FLOW MODEL

```

module Half_adder(s, cout, x, y);
output s;
output cout;
input x;
input y;
assign s=x^y;
assign cout=x&y;
endmodule

// TEST BENCH
module half_adder_tb_v;
//    Inputs

reg x;
// reg y;

//Outputs

wire s; wire cout;
// Instantiate the Unit Under Test (UUT)
Half_adder uut (.s(s), .cout(cout), .x(x), .y(y) );
initial begin
// Initialize Inputs
x = 0;          y = 0;
Wait 100 ns for global reset to finish #100; x=0; y=1;

#100; x=1; y=0; #100; x=1; y=1;
Add stimulus here

end
endmodule
  
```

1.(b) FULL ADDER USING STRUCTURAL MODEL

```
module Full_adder(sum, carry, x, y, cin);
output sum;
output carry;
input x;
input y;
input cin;
wire w1,w2,w3;
Half_adder h1(w1,w2,x,y);
Half_adder h2(sum,w3,w1,cin);
or g1(carry,w2,w3);
endmodule
```

// TEST BENCH

```
module full_adder_tb_v;
// Inputs
reg x; reg y; reg cin;
// Outputs
wire sum; wire carry;
// Instantiate the Unit Under Test (UUT)
Full_adder uut (.sum(sum), .carry(carry), .x(x), .y(y), .cin(cin)); initial begin
//Initialize Inputs x = 0; y = 0; cin = 0; Wait 100 ns for global reset to finish #100; x=0;
y=0; cin=1;
// #100; x=0; y=1; cin=0; #100; x=0; y=1; cin=1; #100; x=1; y=0; cin=0; #100; x=1; y=0;
cin=1; #100; x=1; y=1; cin=0; #100; x=1; y=1; cin=1;
//Add stimulus here
end
endmodule
```

1.(c) RIPPLE CARRY ADDER USING 1-BIT FULL ADDER

```
module ripple_carry_adder(S, cout, A, B, cin);
output [3:0]S;
output cout;
input [3:0]A;
input [3:0]B;
input cin;
```

```
wire c1,c2,c3;
full_adder f1(S[0],c1,A[0],B[0],cin);
full_adder f2(S[1],c2,A[1],B[1],c1);
full_adder f3(S[2],c3,A[2],B[2],c2);
full_adder f4(S[3],cout,A[3],B[3],c3);
endmodule
```

// TEST BENCH

```
module ripple_carry_adder_tb_v;
// Inputs
reg [3:0] A; reg [3:0] B; reg cin;
```




```

// Outputs
wire [3:0] S; wire cout;
// Instantiate the Unit Under Test (UUT)
ripple_carry_adder uut (.S(S), .cout(cout), .A(A), .B(B), .cin(cin)); initial begin


//Initialize Inputs A = 0; B = 0; cin = 0;
//Wait 100 ns for global reset to finish #100; A=0; B=0; cin=1;
#100; A=0; B=1; cin=0; #100; A=0; B=1; cin=1; #100; A=1; B=0; cin=0; #100; A=1;
B=0; cin=1; #100; A=1; B=1; cin=0; #100; A=1; B=1; cin=1;
//Add stimulus here
End
endmodule

```


Waveforms – Problem 1

 

Half Adder using Data Flow Model

 

Full Adder using Structural Model

 

Ripple Carry Adder using 1-Bit Full Addder


1.4.2 Problem 2: Write a Verilog code to implement Multiplexer.

The following points should be taken care of:

1. Use data flow model to design 2x1 Multiplexer
2. Use conditional statement to design 4x1 Multiplexer
3. Use Gate Level Model to design 8x1 Mux using two 4x1 Mux and one 2x1 Mux


Logic Diagram – Problem 2

2 x 1 Multiplexer

 


| Select | Inputs | | Output |
|--------|--------|---|--------|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 |

4 x 1 Multiplexer

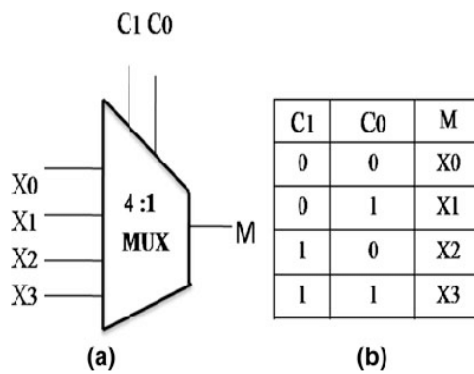

8 x 1 Multiplexer

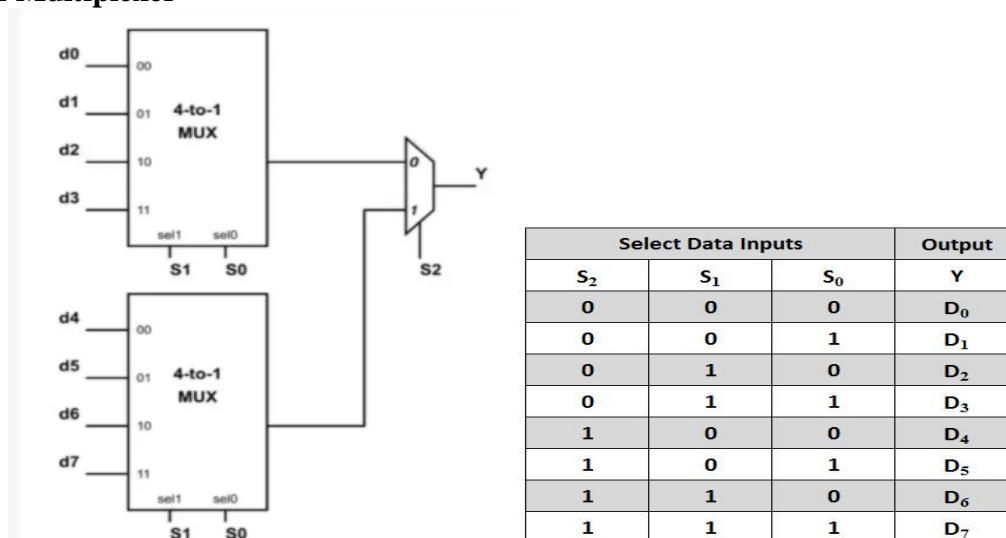

Verilog Code - Problem 2

2.(a) MUX 2 X 1 DATA FLOW MODEL

```
module mux2_1(out, A, B, s);
output out;
input A;
input B;
input s;
assign out=(s)?A:B;
endmodule
```

// TEST BENCH

```
module mux2_1_tb_v;
// Inputs
reg A; reg B; reg s;
//Outputs wire out;
//Instantiate the Unit Under Test (UUT)
mux2_1 uut (.out(out), .A(A), .B(B), .s(s));
initial begin
//Initialize Inputs A = 0; B = 0; s = 0;
//Wait 100 ns for global reset to finish #100; A=1; B=1; s=0;
#100; A=1; B=1; s=1;
//Add stimulus here
end
endmodule
```

2.(b) MUX 4 X 1 conditional statement

```
module mux4_1(out, i, s);
output out;
input [3:0]i;
input [1:0]s;
assign out = s[0]?(s[1]?i[3]:i[2]):(s[1]?i[1]:i[0]);
endmodule
```

// TEST BENCH

```
module mux4_1_tb_v;
// Inputs
reg [3:0] i; reg [1:0] s;
//Output wire out;
//Instantiate the Unit Under Test (UUT) mux4_1 uut (.out(out), .I(I), .s(s)); initial begin
//Initialize Inputs
//Wait 100 ns for global reset to finish #100; I=4'b1101; s=2'b01;
#100; I=4'b0100; s=2'b10; #100; I=4'b0111; s=2'b11;
//Add stimulus here
end
endmodule
```

MUX 8 X 1 USING 4 X 1 MUX AND 2 X 1 MUX

```
module mux8_1(out, i, s);
```

```

output out;
input [2:0]s, [7:0]i;
wire [1:0]w;
mux4__1 m1(w[0], i[3:0], s[1:0]);
mux4__1 m2(w[1], i[7:4], s[1:0]);
mux2_1 m3(out,w[0],w[1], s[2]);
endmodule

```

// TEST BENCH

```

module mux8_1_tb_v;
// Inputs
reg [2:0] s; reg [7:0] i;
//Outputs
wire out;


//Instantiate the Unit Under Test (UUT) mux8_1 uut (.out(out), .s(s), .i(i)); initial begin
//Initialize Inputs s = 0; i = 0;
//Wait 100 ns for global reset to finish #100; s=3'b000; i=8'b00000001; #100; s=3'b001;
i=8'b00000010; #100; s=3'b010; i=8'b00000100; #100; s=3'b011; i=8'b00001000; #100;
s=3'b100; i=8'b00010000;
#100; s=3'b101; i=8'b00100000;
#100; s=3'b110; i=8'b01000000;
#100; s=3'b111; i=8'b10000000;
end
endmodule

```


Waveforms – Problem 2



2 X 1 MUX Using Data Flow Model

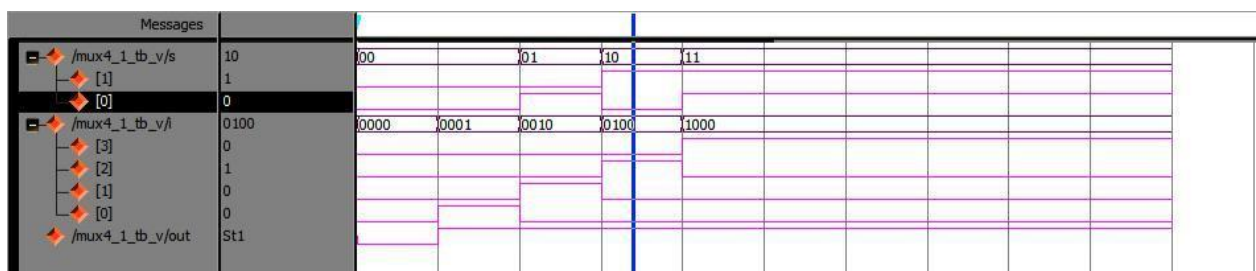

4 X 1 MUX using conditional Operator

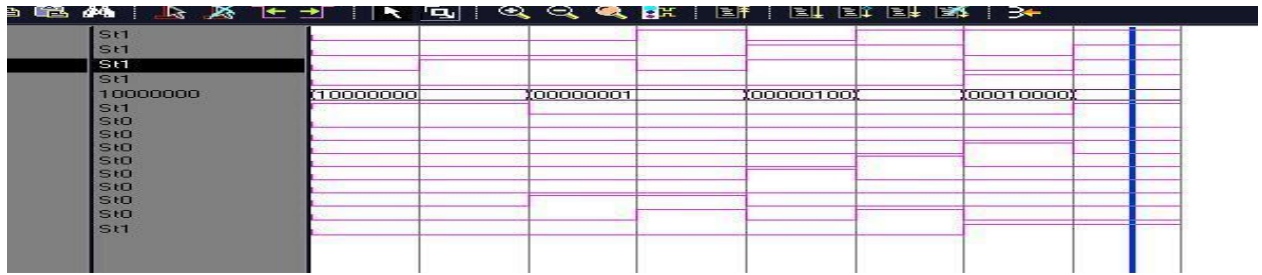


8 X 1 MUX Using 4 X 1 MUX and 2 X 1

1.4.3 Problem 3: Design of Sequential Circuits: Write a Verilog code to implement Flip flops.

The following points should be taken care of:


1. Use gate level model to design positive edge triggered SR flip
2. Use data flow model to design negative edge triggered JK flip flop

Logic Diagram – Problem 3

 



| Q | S | R | Q(t+1) |
|---|---|---|---------------|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | indeterminate |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | indeterminate |

(b) Truth table

 

Clocked SR flip-flop

| Q | J | K | Q(t+1) |
|---|---|---|--------|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 0 |

  

$$Q^+ = J \bar{Q} + \bar{K} Q$$

Verilog Code - Problem 3

3.(a) POSITIVE EDGE TRIGGERED SR FLIPFLOP USING GATE LEVEL MODEL

```
module srff(q, qbar, s, r, clk);
output q, qbar;
input s;
input r;
input clk;
    wire nand1_out;
    wire nand2_out;
    nand n1(nand1_out, clk, s);
    nand n2(nand2_out, clk, r);
    nand n3(q, nand1_out, qbar);
    nand n4(qbar, nand2_out, q);
endmodule
```

// TEST BENCH

```
module srff_tb_v;
// Inputs
reg s;
reg r;
reg clk;
// Outputs
wire q;
wire qbar;
// Instantiate the Unit Under Test (UUT)
srff uut (
.q(q),
.qbar(qbar),
.s(s),
.r(r),
.clk(clk)
);
initial begin
// Initialize Inputs
s = 0;r = 1;clk = 1;
// Wait 100 ns for global reset to finish
#100 s = 1;r = 0; clk = 1;
#100 s = 0;r = 0; clk = 1;
#100 s = 1;r = 1; clk = 1;
// Add stimulus here
end
endmodule
```

3.(b) NEGATIVE EDGE TRIGGERED JK FLIPFLOP USING DATA FLOW MODEL

```
module jkff(q,qb, clk, clr, j, k);
output q, qb;
input clk;
```

```

input clr;
input j, k;
reg q;
initial
q=0;
always@(negedge clk)
begin
q= (j & (~q)) | ((~k) & q);
end
assign qb=~q;
endmodule

```

TEST BENCH

```

module jk_tb_v;
// Inputs
reg clk;
reg clr;
reg j;
reg k;


// Outputs
wire q;
wire qb;

// Instantiate the Unit Under Test (UUT)
jkff uut (
.q(q),
.qb(qb),
.clk(clk),
.clr(clr),
.j(j),
.k(k)
);


initial begin
// Initialize Inputs
clk = 1;clr = 1;j = 0;k = 0;
// Wait 100 ns for global reset to finish
#100 clr = 0;j = 0;k = 0;
#100 clr = 0;j = 0;k = 1;
#100 clr = 0;j = 1;k = 0;
#100 clr = 0;j = 1;k = 1;
#100 clr = 0;j = 0;k = 0;
// Add stimulus here
end
always #50 clk=~clk;
endmodule

```

Waveforms – Problem 3

 

SR Flip-flop using Gate level model

 

JK Flip-flop using Data flow model

1.5 Post lab

1. Draw the block diagram of 4x16 decoder. Use 3x8 decoder to design 4x16 decoder using Gate level model.

1.6 Result:

Thus, the design of combinational and Sequential logic circuits was simulated in Verilog and synthesized using EDA tools.

Lab Experiment #2

Realization of Digital Circuits Using Behavioral and Switch Level Modeling

2.1 Objective: To realize the design of digital circuits in Verilog using behavioral and switch level modelling then simulating and synthesizing using EDA tools.

2.2 Software tools Requirement

Equipments:

Computer with Xilinx and Modelsim Software Specifications:

HP Computer P4 Processor – 2.8 GHz, 2GB RAM, 160 GB Hard Disk

Softwares: Synthesis tool: Xilinx ISE.

Simulation tool: ModelSim Simulator

2.3 Prelab Questions

(write pre lab Q & A in an A4 sheet)

1. Write the difference between initial and always block.
2. List the Reduction and Logical Operators.
3. Give the use of Blocking and Nonblocking statements.
4. Differentiate case, casex and casez statements.



2.4.1 Problem 1: Write a Verilog code to implement Flip flops.

The following points should be taken care of:

1. Use If statement to design positive edge triggered D flip
2. Use case statement to design negative edge triggered T flip flop


Logic Diagram

D flip flop

  

| T | Q | Q' |
|---|---|----|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

Verilog

 

Code - Problem 1

1.(a) POSITIVE EDGE TRIGGERED D FLIPFLOP USING IF STATEMENT

```
module dff(q, qbar, d, clk, clear);
```

```

output q;
output qbar;
input d;
input clk;
input clear;
reg q, qbar;
always@(posedge clk or posedge clear)
begin
if(clear== 1)
begin
q <= 0;
qbar <= 1;
end
else
begin
q <= d;
qbar = !d;
end
end
endmodule

```

// TEST BENCH

```

module dff_tb_v;
// Inputs
reg d;
reg clk;
reg clear;
// Outputs
wire q;
wire qbar;

// Instantiate the Unit Under Test (UUT)
dff uut (
.q(q),
.qbar(qbar),
.d(d),
.clk(clk),
.clear(clear)
);
initial begin
// Initialize Inputs
d = 0;clk = 0;clear = 1;
// Wait 100 ns for global reset to finish
#100 d = 0;clear = 0;
#100 d = 1;clear = 0;
#100 d = 1;clear = 1;
// Add stimulus here
end
always #50 clk=~clk;
endmodule

```

1.2) NEGATIVE EDGE TRIGGERED T FLIPFLOP USING CASE STATEMENT

```

module tffc(q, clk, clr, t);
output q;
input clk;
input clr;

```

```

input t;
reg q;
initial
q=0;
always@(negedge clk)
begin
case({clr,t})
2'b10: q=0;
2'b00: q=q;
2'b01: q=~q;
endcase
end
endmodule

```


// TEST BENCH

```


module tffcase_tb_v;
// Inputs
reg clk; reg clr; reg t;
//Outputs wire q;
//Instantiate the Unit Under Test (UUT) tffcase uut (.q(q),.clk(clk),.clr(clr),.t(t)); initial begin
//Initialize Inputs clk = 0; clr = 1; t = 0;
//Wait 100 ns for global reset to finish #100; clr=0;
#100; clr=0; t=1;
//Add stimulus here
end
always
#50 clk=~clk;
endmodule

```

Waveforms – Problem 1

 

D Flipflop using IF statement

 

T Flipflop using CASE statement

2.4.2 Problem 2: Write a Verilog code to implement Counters.

The following points should be taken care of:

1. Use behavioral model to design Up-Down Counter. When mode = '1' do up counting and for mode = '0' do down counting.
2. Use behavioral model to design Mod-N counter.
3. Design SISO registers using behavioral model.

Logic Diagram – Problem 2


Up-Down Counter:

| Current State | | | | Next State Count UP | | | | Next State Count Down | | | |
|---------------|----|----|----|---------------------|-----|-----|-----|-----------------------|-----|-----|-----|
| C3 | C2 | C1 | C0 | C3+ | C2+ | C1+ | C0+ | C3+ | C2+ | C1+ | C0+ |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 1 |
| 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 0 | 0 | 1 | 1 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 1 | 0 | 1 | 0 | 0 | 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 | 0 | 1 | 0 | 1 | 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 | 0 | 1 | 1 | 0 | 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 0 | 0 | 1 | 1 | 1 | 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 | 1 | 0 | 1 | 0 | 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 1 | 0 | 1 | 1 | 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 1 | 1 | 0 | 0 | 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 | 1 | 1 | 0 | 1 | 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 | 1 | 1 | 1 | 0 | 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 0 |

Mod-N Counter:

| Count | Qd | Qc | Qb | Qa |
|----------------|----|----|----|----|
| (Start) 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 2 | 0 | 0 | 1 | 0 |
| 3 | 0 | 0 | 1 | 1 |
| 4 | 0 | 1 | 0 | 0 |
| 5 | 0 | 1 | 0 | 1 |
| 6 | 0 | 1 | 1 | 0 |
| 7 | 0 | 1 | 1 | 1 |
| 8 | 1 | 0 | 0 | 0 |
| 9 | 1 | 0 | 0 | 1 |
| (New Cycle) 10 | 0 | 0 | 0 | 0 |

SISO Register:

 

Verilog Code - Problem 2

2.(1) UP DOWN COUNTER USING BEHAVIOURAL MODEL

```
module updowncntr(q, clr, clk, mode);
output reg [3:0] q;
input clr;
input clk;
input mod;
always@(posedge clk)
begin
case({clr,mod})
2'b11 : q=0;
2'b10 : q=0;
2'b01 : q=q+1;
2'b00 : q=q-1;
endcase
end
endmodule
```

// TEST BENCH

```
module updowncntr_tb_v;
// Inputs
reg clr; reg clk; reg mod;
//Outputs wire [3:0]q;

//Instantiate the Unit Under Test (UUT) updowncntr uut (.q(q),.clr(clr),.clk(clk),.mod(mod));
initial begin
// Initialize Inputs
clr = 1; clk = 0; mod = 1;
//Wait 100 ns for global reset to finish #100; clr=0;
#1000; mod=0;
//Add stimulus here
end
always
#50 clk=~clk;
endmodule
```

2.(2) Mod N-COUNTER USING BEHAVIOURAL MODEL

```
module modN_ctr
# (parameter N = 10,
parameter WIDTH = 4)
( input  clk,
input  rstn,
output reg[WIDTH-1:0] out);
always @ (posedge clk) begin
if (rstn) begin
out <= 0;
end else begin
if (out == N-1)
out <= 0;
else
out <= out + 1;
end
end
endmodule
```

// TEST BENCH

```
module modncounter_tb_v;

// Inputs
reg clk;
reg rstn;

// Outputs
wire [3:0] out;

// Instantiate the Unit Under Test (UUT)
modN_ctr uut (
.clk(clk),
.rstn(rstn),
.out(out)
);
initial begin
// Initialize Inputs
clk = 1;rstn = 1;
// Wait 100 ns for global reset to finish
#100 rstn=0;
// Add stimulus here
end
lways #50 clk=~clk;
endmodule
```

2.(3) SISO REGISTER USING BEHAVIOURAL MODEL

```
module siso_register(shift_out, shift_in, clk);
input  shift_in;
input  clk;
output shift_out;
reg shift_out;
reg [2:0] data;
always @(negedge clk)
begin
```

```
// TEST BENCH
```

```
module siso_tb_v;
```

```
// Inputs
reg shift_in;
reg clk;
// Outputs
wire shift_out;
// Instantiate the Unit Under Test (UUT)
siso_register uut (
    .shift_out(shift_out),
    .shift_in(shift_in),
    .clk(clk)
);
```


```
initial begin
// Initialize Inputs
shift_in = 1;
clk = 1;
```

```
// Wait 100 ns for global reset to finish
```


```
#100 shift_in = 0;
#100 shift_in = 1;
#100 shift_in = 0;
// Add stimulus here
```

```
end
always #50 clk=~clk;
endmodule
```


Waveforms – Problem 2

 

 Up Down counter using behavioral modelling



Mod-N counter using behavioral modelling

 


SISO register using behavioral modelling

Problem 2.4.3:

- 1.Design inverter logic using Verilog switch level modeling and verify the simulation result using test bench.
- 2.Design two inputs CMOS NAND logic using Verilog switch level modeling and verify the simulation result using test bench.
- 3.Design 2:1 Mux using CMOS switches and write Verilog coding using switch level modeling and verify the simulation result.

Logic Diagram-Problem 1

 

2.4.3 Verilog Code - Problem 1





CMOS Inverter

```
module inverter(out,data);
output out;
input data;
supply1 vdd;
supply0 gnd;
pmos p1(out,vdd,data);
nmos n1(out,gnd,data);
endmodule
```

CMOS Inverter_TB

```
module inverter_tb_v;
reg data;
inverter uut (.out(out), .data(data));
initial begin
data = 0;
#100 data = 1;
end
endmodule
```


6.4 Waveforms – Problem 1

| | | | |
|---|---------------|-----|--|
|  | /inverter/out | St1 | |
|  | /inverter/in | St0 | |
|  | /inverter/pwr | Su1 | |
|  | /inverter/gnd | Su0 | |

CMOS inverter

Logic Diagram-Problem 2

Two input NAND

 

2.4.3 Verilog Code - Problem 2

CMOS NAND Logic

```

module nandcmos(out,a,b);
  wire t;
  output out;
  input a,b;
  supply1 vdd;
  supply0 gnd;
  pmos m1(out,vdd,a);
  pmos m2(out,vdd,b);
  nmos m3(out,t,a);
  nmos m4(t,gnd,b);
endmodule

```

CMOS NAND Logic_TB

```

module nandcmos_tb_v;
  reg a; reg b;
  wire out;
  nandcmos uut (
    .out(out), .a(a), .b(b)
  );
  initial begin
    a = 0; b = 0;
    #100 a = 0; b = 1;
    #100 a = 1; b = 0;
    #100 a = 1; b = 1;
  end
endmodule

```

2.4.3 Waveforms – Problem 2


 


Fig 2.4.3 Two input NAND

Logic Diagram-Problem 3

2:1 Mux using CMOS

 

2.4.3 Verilog Code - Problem 3


CMOS Mux 2X1

```
module cmos_mux(out,s,i1,i0);
output out;
input s,i0,i1;
wire sbar;
not n1(sbar,s);
cmos(oout,i0,sbar,s);
cmos(out,i1,s,bar);
endmodule
```

CMOS Mux 2X1_TB

```
module cmos_mux_tb_v;
reg s;reg i1;reg i0;
wire out;
cmos_mux uut (.out(out), .s(s),
.i1(i1),.i0(i0));
initial begin
s = 0;i1 = 1;i0 = 0; #100;
s = 0;i1 = 0;i0 = 1; #100;
s = 1;i1 = 0;i0 = 1; #100;
s = 1;i1 = 1;i0 = 1;
end
endmodule
```

2.4.3 Waveforms – Problem 3

 

2X1 Multiplexer using CMOS

2.5 Post Lab :

Write a Verilog HDL Code to implement a SIPO and PIPO shift registers.

2.6 Result:

Thus, the design of Digital circuits using behavioral and Switch level modelling is simulated in Verilog and synthesized using EDA tools.

Lab Experiment #3

Design of Finite State Machine (FSM) and Algorithmic State

3.1 Objective:

To learn the design of Finite State Machine (FSM) and Algorithmic State Machine (ASM) for any application in Verilog, the simulating and synthesizing using EDA tools.

3.2 Tools Required:

1. Synthesis tool: Xilinx ISE
2. Simulation tool: Modelsim simulator


3.3 Pre Lab Questions:

1. Draw the simple model of FSM.
2. What is the basic Algorithm of Sequence Detector?
3. List the difference between Mealy and Moore Model.
4. What is ASM Chart and what are its main components?

3.4.1 Problem:

1. Implement Sequence recognizer for detecting three successive 1's using Mealy Model (Behavioural Modelling).

Mealy model for 111 Detector (FSM):

 

Verilog code for Mealy Model FSM: (Behavioral Modelling)

```
module fsm_111_mealey(o,reset,a,clk);
```

```
output reg o;
```

```
input reset,a,clk;
```

```
reg[1:0]pre_s, nxt_s;
```

```
initial begin
```

```

pre_s=2'b00;
end
always@(posedge clk)
begin
if(reset==1)
begin pre_s=2'b00; o=0;end
else
begin
case(pre_s)
2'b00:begin if (a==1)begin o=0; nxt_s=2'b01;pre_s=nxt_s; end
           else begin o=0; nxt_s=2'b00;pre_s=nxt_s; end end
2'b01:begin if (a==1)begin o=0; nxt_s=2'b10;pre_s=nxt_s; end
           else begin o=0; nxt_s=2'b00;pre_s=nxt_s; end end
2'b10:begin if (a==1)begin o=1; nxt_s=2'b00;pre_s=nxt_s; end
           else begin o=0; nxt_s=2'b00;pre_s=nxt_s; end end
           default:pre_s=2'b00;
           endcase
        end
end
endmodule

```

Test Bench:

```

module fsm_mealy_111_tb_v;
// Inputs
reg reset;
reg a;
reg clk;
// Outputs
wire o;
// Instantiate the Unit Under Test (UUT)
fsm_mealy_111 uut (
.o(o),
.reset(reset),
.a(a),
.clk(clk)
);
initial begin
// Initialize Inputs


```

```


reset = 1;
a = 1;
clk = 1;
// Wait 100 ns for global reset to finish
#100;
    reset = 0;
a = 1;
#100;
reset = 0;
a = 1;
#100;
reset = 0;
a = 1;
#100;
    reset = 0;
a = 0;
#100;
    reset = 0;
a = 1;
#100;
// Add stimulus here
end
    always #50 clk=~clk;
endmodule

```

Simulation Result:

 


 3.4.2 Consider the following state graph of a sequential network which has both Mealy and Moore outputs. The outputs Y1 and Y2 are the Mealy outputs and so should be conditional outputs. The Ya, Yb, and Yc are the Moore outputs so they should be part of state box. Input X can either be “0” or “1” and hence it should be part of the decision box.



Draw the ASM Chart for the above state graph and implement using Verilog.

ASM Chart:

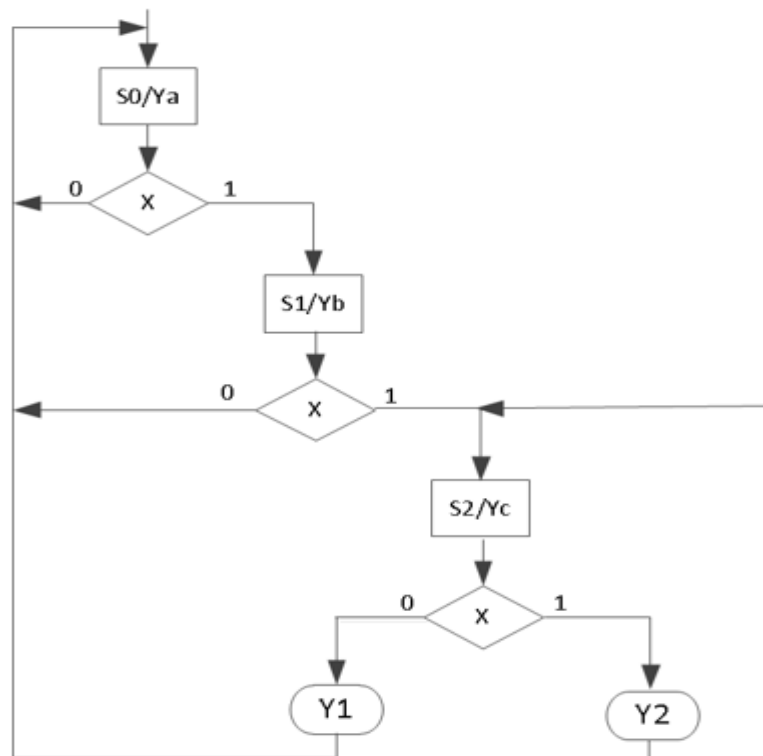

Verilog Program:

```
module asm (input clk, input x, output reg ya, output reg yb, output reg yc, output reg
y1,
output reg y2);
    reg [1:0] state, nextstate;
    parameter [1:0] S0=0, S1=1, S2=2;
    always @(posedge clk) // always block to update state
        state <= nextstate;
    always @(state or x) // always block to compute both Mealy output & next state
    begin
        y1 = 1'b0; y2 = 1'b0;
        case (state)
        S0: if(x)
            nextstate = S1;
        else
            nextstate = S0;
        S1: if(x)
            nextstate = S2;
        else
            nextstate = S0;
        S2: if(x)
            nextstate = S1;
        else
            nextstate = S2;
        endcase
    end
```

```

S1: if(x)
    nextstate = S2;
else
    nextstate = S0;
S2: if(x)
begin
    y2 = 1'b1;
    nextstate = S1;
end
else
begin
    y1 = 1'b1;
    nextstate = S0;
end
default:nextstate = S0;
endcase
end
always @(state) // always block to compute Moore output
begin
ya = 1'b0; yb = 1'b0; yc = 1'b0;
case(state)
//begin
S0: ya = 1'b1;
S1: yb = 1'b1;
S2: yc = 1'b1;
//end
default: begin
ya = 1'b0;
yb = 1'b0;
yc = 1'b0;
end
endcase

```



```
        end
    endmodule
```

Test Bench:

```
module asm_tb_v;

// Inputs
reg clk;
reg x;

// Outputs
wire ya;
wire yb;
wire yc;
wire y1;
wire y2;

// Instantiate the Unit Under Test (UUT)
asm uut (
    .clk(clk),
    .x(x),
    .ya(ya),
    .yb(yb),
    .yc(yc),
    .y1(y1),
    .y2(y2) );
initial begin
// Initialize Inputs
x = 1;
clk = 1;

// Wait 100 ns for global reset to finish
#100;
    x = 1;
#100;
x = 1;
#100;
```


```

x = 1;
#100;
x = 0;
#100;
// Add stimulus here
end

always #50 clk=~clk;
    // Add stimulus here
endmodule

```

Output:

 

3.5 Post lab Questions:

1. Write Verilog code to implement an FSM using Moore Machine.

3.6 Result:

All the FSM Logic and ASM logic were executed and verified.

Lab Experiment # 4

Realization of Carry Look-Ahead Adder

4.1 Objective: To design and simulate the carry look-ahead adder (4-bit) in verilog and synthesize using EDA tools.

4.2 Software tools Requirement

Equipment's:

Computer with Xilinx and Modelsim Software Specifications:

HP Computer P4 Processor – 2.8 GHz, 2GB RAM, 160 GB Hard Disk

Software's: Synthesis tool: Xilinx ISE

Simulation tool: Modelsim Simulator

4.3 Prelab Questions

(Write pre lab Q & A in an A4 sheet)

1. Write the expression for Propagate and generate term in a CLA.
2. List the efficient method for implementing 64- adder using CLA technique?

4.4 Problem: Write a Verilog code to implement the 4-bit Carry Look-ahead adder using structural model.

Logic Diagram:

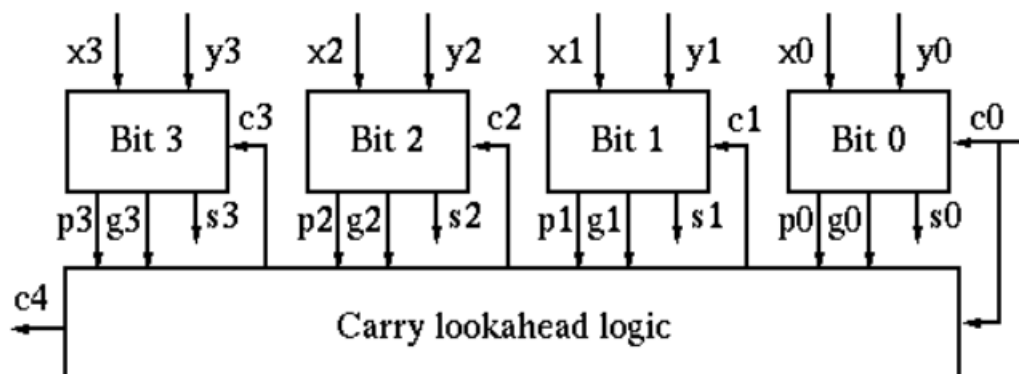


Fig. 4.1: 4-bit Carry Look-ahead Adder

Source code:

```
Module CLA_4bit(sum,c_4,a,b,c_0);
input [3:0]a,b;
input c_0;
output [3:0]sum;
output c_4;
wire p0,p1,p2,p3,g0,g1,g2,g3;
wire c1,c2,c3,c4;
assign
p0=a[0]^b[0],
p1=a[1]^b[1],
p2=a[2]^b[2],
```


```
p3=a[3]^b[3],
g0=a[0]&b[0],
g1=a[1]&b[1],
g2=a[2]&b[2],
g3=a[3]&b[3];
assign
c1=g0|(p0&c_0),
c2=g1|(p1&g0)|(p1&p0&c_0),
c3=g2|(p2&g1)|(p2&p1&g0)|(p2&p1&p0&
c_0),
c4=g3|(p3&g2)|(p3&p2&p1&g1)|(p3&p2&
p1&g0)|(p3&p2&p1&p0&c_0);
assign
sum[0]=p0^c_0,
sum[1]=p1^c1,
sum[2]=p2^c2,
sum[3]=p3^c3,
c_4=c4;
endmodule
```

Test bench:

```
module carry_lookahead_adder_tb ();
parameter WIDTH = 3;
reg [WIDTH-1:0] r_ADD_1 = 0;
reg [WIDTH-1:0] r_ADD_2 = 0;
wire [WIDTH:0] w_RESULT;
CLA_4bit #(.WIDTH(WIDTH)) carry_lookahead_inst
( .i_add1(r_ADD_1), .i_add2(r_ADD_2),
.o_result(w_RESULT) );
```

```
initial
begin
#10;
r_ADD_1 = 3'b000;
r_ADD_2 = 3'b001;
#10;
r_ADD_1 = 3'b010;
r_ADD_2 = 3'b010;
#10;
r_ADD_1 = 3'b101;
r_ADD_2 = 3'b110;
#10;
r_ADD_1 = 3'b111;
r_ADD_2 = 3'b111;
#10;
end
endmodule // carry_lookahead_adder_t
```

Simulation Waveform:

 

Simulation waveforms of carry look ahead adder

4.5 Post Lab:

1. Compare the area, delay and power report of ripple carry & carry look-ahead adder in Xilinx ISE. Create a comparison chart and justify the results.
2. List the application of CLA in VLSI Design.
3. Prepare the synthesis Chart for a 4-bit CLA.
4. Can retiming mechanism improve the speed further in CLA architecture?

4.6 Result

Thus, the design of 4-bit carry look-ahead adder circuit was simulated in Verilog and synthesized using EDA tools.

Lab Experiment # 5

Realization of Carry Skip Adder

5.1 Objective: To design and simulate the carry skip adder (4-bit) in Verilog and synthesize using EDA tools.

5.2 Software tools Requirement

Equipment's:

Computer with Xilinx and Modelsim Software Specifications:

HP Computer P4 Processor – 2.8 GHz, 2GB RAM, 160 GB Hard Disk

Software's: Synthesis tool: Xilinx ISE

Simulation tool: Modelsim Simulator


5.3 Pre Lab Questions

(Write pre lab Q & A in an A4 sheet)

1. Why Carry-Skip adder has the same critical path as regular Carry-Ripple adder.
2. List the efficient method for implementing 16 Bit - adder using Carry-Skip technique?

5.4 Problem: Write a Verilog code to implement the 4-bit Carry Look-ahead adder using structural model.

Logic Diagram:

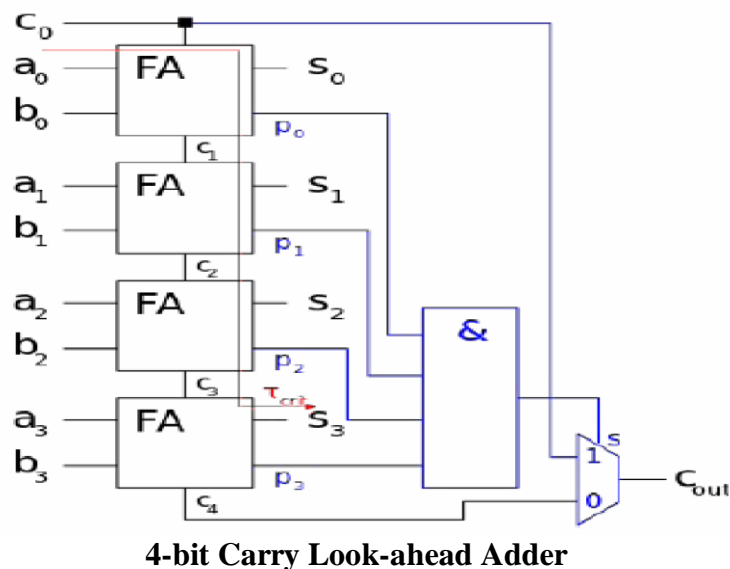

Source code:

```
module carry_skip_4bit(a, b, cin, sum, cout);
input [3:0] a,b;
input cin;
output [3:0] sum;
output cout;
wire [3:0] p;
wire c0;
wire bp;
ripple_carry_4_bit rca1 (a[3:0],b[3:0],cin, sum[3:0],c0);
propagate_p p1(a, b, p, bp);
mux2X1 m0(c0,cin,bp,cout);
endmodule
```

```
module propagate_p(a,b,p,bp);
input [3:0] a,b;
output [3:0] p;
output bp;
assign p= a^b;//get all propagate bits
assign bp= &p;// and p0p1p2p3 bits
endmodule
```

```
module ripple_carry_4_bit(a, b, cin,sum, cout);
input [3:0] a,b;
input cin;
wire c1,c2,c3;
output [3:0] sum;
output cout;
full_adder fa0(a[0], b[0],cin,
sum[0],c1);
full_adder fa1(a[1], b[1],c1,
sum[1],c2);
full_adder fa2(a[2], b[2],c2,
sum[2],c3);
full_adder fa3(a[3], b[3],c3,
sum[3],cout);
endmodule
```

TEST BENCH:


```
module carry_skip_4bit_addertb;
wire [7:0]Y;
wire carryout;
reg [7:0]A,B;
reg carryin;
carry_skip_4bit csa1 (Y,carryout,A,B,carryin);
initial
begin
```

```

$display("RSLT\tA\tB\tCYIN\tCYOUT\tSUM");
//A = 4'b0101; B = 4'b1101; carryin = 0; #50; // Set inputs and add delay
A = 0; B = 0; carryin = 0; #50; // Set inputs and add delay
A = 3; B = 2; carryin = 1; #50; // Set inputs and add delay
A = 7; B = 10; carryin = 0; #50; // Set inputs and add delay
A = 15; B = 15; carryin = 1; #50; // Set inputs and add delay
A = 255; B = 55; carryin = 0; #50; // Set inputs and add delay
A = 255; B = 255; carryin = 1; #50; // Set inputs and add delay
/*
//if ( (carryout == 1 ) && (Y === 4'b0010) )
if ( (carryout == 1 ) && (Y === 2) )
$display("PASS\t%p\t%p\t%d\t=\t%d\tp%p",A,B,carryin,carryout,Y);
else
$display("FAIL\t%p\t%p\t%d\t=\t%d\tp",A,B,carryin,carryout,Y);
*/
end
//enabling the wave dump
initial begin
$dumpfile("dump.vcd"); $dumpvars;
end
endmodule

```

Simulation Waveform:

 

Simulation waveform of carry skip adder

5.5 Post Lab:

1. Write a Verilog code to design 4 Bit Carry Save Adder.

5.6 Result

Thus, the design of 4-bit carry look-ahead adder circuit was simulated in Verilog and synthesized using EDA tools.

Lab Experiment #6

Realization of Multiplier-1

6.1 Objective: To design and simulate the Braun array multiplier in Verilog and synthesize using EDA tools.

6.2 Software tools Requirement:

Equipment's:

Computer with Xilinx and Modelsim Software Specifications:

HP Computer P4 Processor – 2.8 GHz, 2GB RAM, 160 GB Hard Disk

Software's: Synthesis tool: Xilinx ISE

Simulation tool: Modelsim Simulator


6.3 Prelab Questions:

(write pre lab Q & A in an A4 sheet)

1. What is called Booth recoding?
2. Give the booth's recoding transformation of the following number 01111001(0).
3. Give the difference between Booth's recoding and modified booth's recoding?

6.4 Problem: Write a Verilog code to implement the 4-bit Braun Array multipliers using structural model.

Logic Diagram

 

4-bit Braun Array multiplier

Verilog Code

```
module braun(a, b, p); input [3:0] a;
    input [3:0] b;
    output [7:0] p;
wire w0,w1,w2,w3,w4,w5,w6,w7,w8,w9,w10,w11,w12,w13,w14,w15,w16,w17,
w18, w19,w20,w21,w22,w23,w24,w25,w26,w27,w28,w29;

    and g0 (w0, a[3], b[0]);
    and g1 (w1, a[2], b[0]);
    and g2 (w2, a[1], b[0]);
    and g3 (p[0],a[0], b[0]);
    and g4 (w6, a[3], b[1]);
    and g5 (w3, a[2], b[1]);
    and g6 (w4, a[1], b[1]);
    and g7 (w5, a[0], b[1]);
    and g8 (w12, a[3], b[2]);
    and g9 (w13, a[2], b[2]);
    and g10(w14, a[1], b[2]);
    and g11(w15, a[0], b[2]);
    and g12(w21, a[3], b[3]);
    and g13(w22, a[2], b[3]);
    and g14(w23, a[1], b[3]);
    and g15(w24, a[0], b[3]);

    fa_df f0 (w8 , w7 , w0 , w3 , 1'b0);
    fa_df f1 (w10 , w9 , w1 , w4 , 1'b0);
    fa_df f2 (p[1], w11 , w2 , w5 , 1'b0);
    fa_df f3 (w17 , w16 , w6 , w13, w7);
    fa_df f4 (w19 , w18 , w8 , w14, w9);
    fa_df f5 (p[2], w20 , w10, w15, w11);
    fa_df f6 (w26 , w25 , w12, w22, w16);
    fa_df f7 (w28 , w27 , w17, w23, w18);
    fa_df f8 (p[3], w29 , w19, w24, w20);
    fa_df f9 (p[6], p[7], w21, w25, w31);
    fa_df f10(p[5], w31 , w26, w27, w30);
    fa_df f11(p[4], w30 , w28, w29, 1'b0);
endmodule

// TEST BENCH
module braun_test_v;
// Inputs
reg [3:0] a;
reg [3:0] b;
// Outputs
wire [7:0]p;
// Instantiate the Unit Under Test (UUT) braun uut (
```

```

.a(a),
.b(b),
.p(p));

```


```
// Initialize Inputs
```

$$\mathbf{b} = \mathbf{0};$$

```
#100;a=1101; b=1001;
```

end

endmodule

 

Thus, the design of 4-bit Braun array multiplier circuit was simulated in Verilog and synthesized using EDA tools.

Lab Experiment #7

Realization of Multiplier-II

7.1 Objective: To design and simulate the Wallace tree multiplier in Verilog and synthesize using EDA tools

7.2 Software tools Requirement

Equipment's:

Computer with Xilinx and Modelsim Software Specifications:

HP Computer P4 Processor – 2.8 GHz, 2GB RAM, 160 GB Hard Disk

Software's: Synthesis tool: Xilinx ISE

Simulation tool: Modelsim Simulator

7.3 Pre Lab Questions


(Write pre lab Q & A in an A4 sheet)

1. How carry save multiplier differs from array multiplier?
2. Why the partial sum adders are arranged in tree like fashion?

7.4 Problem:

Write a Verilog code to implement the 4-bit Wallace tree multipliers using structural model.

Logic Diagram:

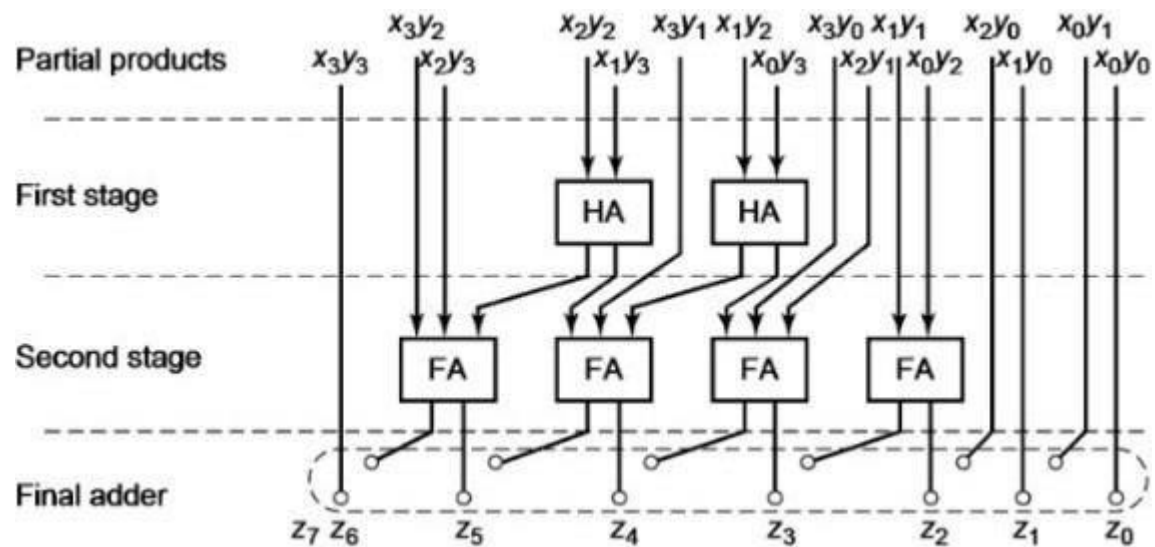

7.1 4-bit Wallace tree multiplier

Source code:

```
module wallace_tree_mul(a, b, z); input [3:0] a;
input [3:0] b;
output [7:0] z;
wire [32:0] w;
and g1 (z[0], a[0], b[0]);
```


```

and g2 (w[27], a[0], b[1]);
and g3 (w[0] , a[1], b[0]);
and g4 (w[1] , a[2], b[0]);
and g5 (w[2] , a[0], b[2]);
and g6 (w[3] , a[1], b[1]);
and g7 (w[4] , a[1], b[1]);
and g8 (w[5] , a[3], b[0]);
and g9 (w[6] , a[0], b[3]);
and g10(w[7] , a[1], b[2]);
and g11(w[8] , a[3], b[1]);
and g12(w[9] , a[1], b[3]);
and g13(w[10], a[2], b[2]);
and g14(w[11], a[2], b[3]);
and g15(w[12], a[3], b[2]);
and g16(w[13], a[3], b[3]);
ha_gate h0(w[16], w[17], w[10], w[9]);
ha_gate h1(w[14], w[15], w[7], w[6]);
ha_gate h2(z[1] , w[28], w[27], w[0]);
fa_df f0(w[19] , w[20] , w[2] , w[3] , 1'b0);
fa_df f1(w[21] , w[22] , w[4] , w[5] , w[14]);
fa_df f2(w[23] , w[24] , w[15] , w[8] , w[15]);
fa_df f3(w[25] , w[26] , w[17] , w[11] , w[12]);
fa_df f4(z[2] , w[29] , w[0] , w[1] , w[28]);
fa_df f5(z[3] , w[30] , w[20] , w[21] , w[29]);
fa_df f6(z[4] , w[31] , w[22] , w[23] , w[30]);
fa_df f7(z[5] , w[32] , w[24] , w[25] , w[31]);
fa_df f8(z[6] , z[7] , w[26] , w[13] , w[32]);
endmodule

Test bench:
module wallace_test_v;
// Inputs reg [3:0] a;
reg [3:0] b;
// Outputs wire [7:0] z;
// Instantiate the Unit Under Test (UUT) wallace_tree_mul uut (
.a(a),
.b(b),
.z(z));
initial begin
// Initialize Inputs a = 0;
b = 0;
//wait 100 ns for global reset to finish
#100a=1101; b=1001;
end
endmodule

```

Simulation Waveform:

 

Simulation waveform of Wallace tree multiplier

7.5 Post Lab:

1. Write the Verilog code for 4-bit Baugh Woolley multiplier in structural modelling and implement using EDA tools.

7.6 Result

Thus, the design of 4-bit Wallace tree multiplier circuit was simulated in Verilog and synthesized using EDA tools

Lab Experiment #8

Realization of Memory

8.1 Objective:

Design memory using Verilog and Simulate using Xilinx Tool.

8.2 Software tools Requirement:

Equipment's:

Computer with Xilinx and Modelsim Software Specifications.
HP Computer P4 Processor – 2.8 GHz, 2GB RAM, 160 GB Hard Disk.

Software's:

Synthesis tool: Xilinx ISE.
Simulation tool: Modelsim Simulator.


8.3 Prelab:

- 1.What are the different types of memory? Compare its performance.
- 2.Write the difference between static and dynamic memory.
- 3.Define port for 32*64k RAM memory.

8.4.1 Problem Statement 1:

- 1.Design a 16X4 RAM Memory.

Logic Diagram:

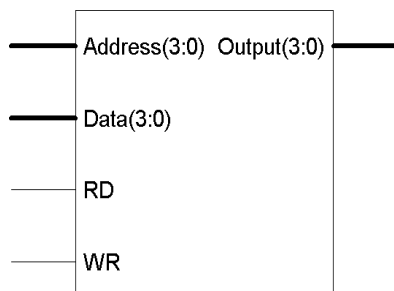

Program:

```
module Memory_Design( Data, RD, WR, Address, Output);input[3:0] Data;input RD, WR; input[3:0] Address; output reg[3:0] Output;reg[3:0] Temp;always@(Address)beginif(WR)beginRAM[Address]=Data; Temp=RAM[Address];endif(RD)
```

```

begin
Output=RAM[Address];
end
end
endmodule

```

TEST BENCH:

```

module RAM_Test_v;
// Inputs
reg [3:0] Data;reg RD;
reg WR;
reg [3:0] Address;
// Outputs
wire [3:0] Output;
// Instantiate the Unit Under Test (UUT)
emory_Design uut
(.Data(Data),.RD(RD),.WR(WR),.Address(Address),.Output(Output));
initial begin
    Data = 4'b0000;      RD = 0;      WR = 1;      Address = 4'b0000; #30;
    Data = 4'b0001;      RD = 0;      WR = 1;      Address = 4'b0001; #30;
    Data = 4'b0010;      RD = 0;      WR = 1;      Address = 4'b0010; #30;
    Data = 4'b0011;      RD = 0;      WR = 1;      Address = 4'b0011; #30;
    Data = 4'b0100;      RD = 0;      WR = 1;      Address = 4'b0100; #30;
    Data = 4'b0101;      RD = 0;      WR = 1;      Address = 4'b0101; #30;
    Data = 4'b0110;      RD = 0;      WR = 1;      Address = 4'b0110; #30;
    Data = 4'b0111;      RD = 0;      WR = 1;      Address = 4'b0111; #30;
    Data = 4'b1000;      RD = 0;      WR = 1;      Address = 4'b1000; #30;
    Data = 4'b1001;      RD = 0;      WR = 1;      Address = 4'b1001; #30;
    Data = 4'b1010;      RD = 0;      WR = 1;      Address = 4'b1010; #30;
    Data = 4'b1011;      RD = 0;      WR = 1;      Address = 4'b1011; #30;
    Data = 4'b1100;      RD = 0;      WR = 1;      Address = 4'b1100; #30;
    Data = 4'b1101;      RD = 0;      WR = 1;      Address = 4'b1101; #30;
    Data = 4'b1110;      RD = 0;      WR = 1;      Address = 4'b1110; #30;
    Data = 4'b1111;      RD = 0;      WR = 1;Address = 4'b1111; #30;

    RD = 1;      WR = 0;      Address = 4'b0000; #30;
    RD = 1;      WR = 0;      Address = 4'b0001; #30;

```



```


RD = 1;      WR = 0;      Address = 4'b0010; #30;
RD = 1;      WR = 0;      Address = 4'b0011; #30;
RD = 1;      WR = 0;      Address = 4'b0100; #30;
RD = 1;      WR = 0;      Address = 4'b0101; #30;
RD = 1;      WR = 0;      Address = 4'b0110; #30;
RD = 1;      WR = 0;      Address = 4'b0111; #30;
RD = 1;      WR = 0;      Address = 4'b1000; #30;
RD = 1;      WR = 0;      Address = 4'b1001; #30;
RD = 1;      WR = 0;      Address = 4'b1010; #30;
RD = 1;      WR = 0;      Address = 4'b1011; #30;
RD = 1;      WR = 0;      Address = 4'b1100; #30;
RD = 1;      WR = 0;      Address = 4'b1101; #30;
RD = 1;      WR = 0;      Address = 4'b1110; #30;
RD = 1;      WR = 0;      Address = 4'b1111; #30;
#100;

```

End

endmodule

Simulation Output:

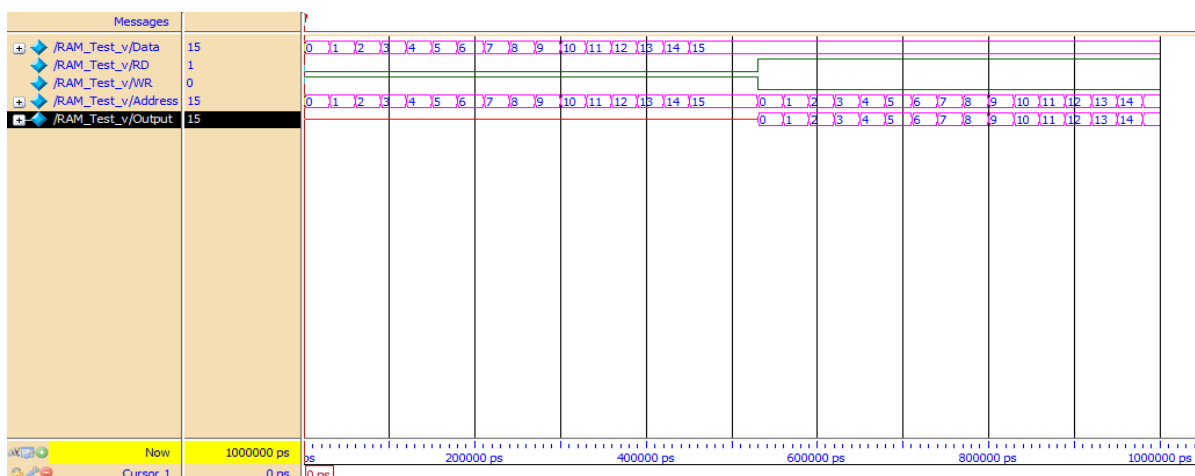


Statement 2:

8.4.2 Problem Design 16X4 ROM Memory.

To Design a 16x4 ROM in Verilog and Simulate using Xilinx Tool.

Block Diagram:

 

Program:

```
Module ROM_16x4(Address, RD, Output);input[3:0] Address;
input RD;
output reg[3:0] Output;reg[3:0] ROM[15:0];
initial
begin
ROM[4'b0000]=4'b1111;ROM[4'b0001]=4'b1110;
ROM[4'b0010]=4'b1101;          ROM[4'b0011]=4'b1100;          ROM[4'b0100]=4'b1011;
ROM[4'b0101]=4'b1010;          ROM[4'b0110]=4'b1001;          ROM[4'b0111]=4'b1000;
ROM[4'b1000]=4'b0111;          ROM[4'b1001]=4'b0110;          ROM[4'b1010]=4'b0101;
ROM[4'b1011]=4'b0100;          ROM[4'b1100]=4'b0011;          ROM[4'b1101]=4'b0010;
ROM[4'b1110]=4'b0001; ROM[4'b1111]=4'b0000;
end
always@(RD , Address)begin
if(RD)
begin
Output=ROM[Address];
end
end
endmodule
```

Test Bench:

```
module ROM_Test_v;
// Inputs
reg [3:0] Address;reg RD;
// Outputs
wire [3:0] Output;
// Instantiate the Unit Under Test (UUT)
ROM_16x4 uut (.Address(Address),.RD(RD),.Output(Output));initial begin
// Initialize Inputs
```

```

Address = 4'b0000;          RD = 1;      #50;

Address = 4'b0001;          RD = 1;      #50;

Address = 4'b0010;          RD = 1;      #50;

Address = 4'b0011;          RD = 1;      #50;

Address = 4'b0100;          RD = 1;      #50;

Address = 4'b0101;          RD = 1;      #50;

Address = 4'b0110;          RD = 1;      #50;

Address = 4'b0111;          RD = 1;      #50;

Address = 4'b1000;          RD = 1;      #50;

Address = 4'b1001;          #50;

Address = 4'b1010;          #50;

Address = 4'b1011;          #50;

Address = 4'b1100;          #50;

Address = 4'b1101;          #50;

Address = 4'b1110;          #50;


Address = 4'b1111;          #50;

end

endmodule

```

Simulation:

 

8.5 Post Lab:

Draw the block diagram and explain about FIFO memory.

8.6 Result:

Design of a 16x4 ROM in Verilog is Performed and Verified using Xilinx Tool.

Lab Experiment #9

Design and Analysis of CMOS inverter using LTSPICE

9.1 Objective: To learn the design of CMOS inverter in circuit level and get the spice netlist using LTSPICE tool.

9.2 Software tools Requirement

Equipment's:

LTSPICE software


9.3 Prelab Questions

(Write pre lab Q & A in an A4 sheet)


1. What are the advantages of SPICE software?
2. What are the differences between enhancement and depletion mode transistors?
3. What is the difference between strong 1 and weak 1?
4. What is meant by transistor sizing?

9.4 Problem 1: Design and analyse the CMOS inverter in circuit level, verify the transfer characteristics and infer the SPICE netlist using LTSPICE.


9.4.1 Logic Diagram

 

 9.4.2 Circuit design of CMOS Inverter in LTSPICE:



9.4.3 Output of CMOS INVERTER:

 

9.4.4 SPICE NETLIST:

```
* C:\Users\PRITHIVI\Documents\LTspiceXVII\INVERTER.asc
V1 IN 0 PULSE(0 5 0 0 0 5m 10m 100)
V2 VDD 0 5
M1 OUT IN 0 0 NMOS
M2 VDD IN OUT VDD PMOS
.model NMOS NMOS
.model PMOS PMOS
.lib C:\Users\PRITHIVI\Documents\LTspiceXVII\lib\cmp\standard.mos
.tran 50m
.backanno
.end
```

9.5 Post lab

1. Perform DC Analysis for CMOS Inverter in LTSPICE.

9.6 Result:

Thus, the design and analysis of CMOS Inverter has been performed, transfer characteristics have been verified using LTSPICE tool.

Lab Experiment #10

Design and Analysis of Complex CMOS gates and Pseudo NMOS gates using LTSPICE

10.1 Objective: To learn the design of Complex CMOS gates and Pseudo NMOS gates in circuit level and get the spice netlist using LTSPICE tool.

10.2 Software tools Requirement

Equipment's:

LTSPICE software

10.3 Prelab Questions

(Write pre lab Q & A in an A4 sheet)

1. What is meant by Pseudo NMOS logic?
2. What are the advantages and drawbacks of Pseudo NMOS?
3. In Pseudo NMOS logic, PMOS transistor operates in _____.
4. What is meant by body effect?
5. What are the different types of operating region in MOSFET?


10.4 Problem 1:

Design and analyse the Complex CMOS gate in circuit level, verify the transfer characteristics and infer the SPICE netlist using LTSPICE.


10.4.1 Problems:

1. Design complex CMOS logic for $OUT = \sim(A+BC)$.
2. Design and analysis of Pseudo NMOS gate Inverter using LTSPICE.

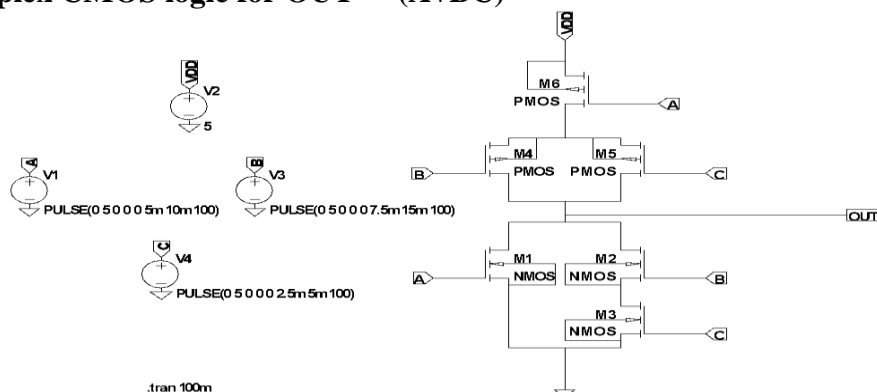10.4.2 Complex CMOS logic for $OUT = \sim(A+BC)$



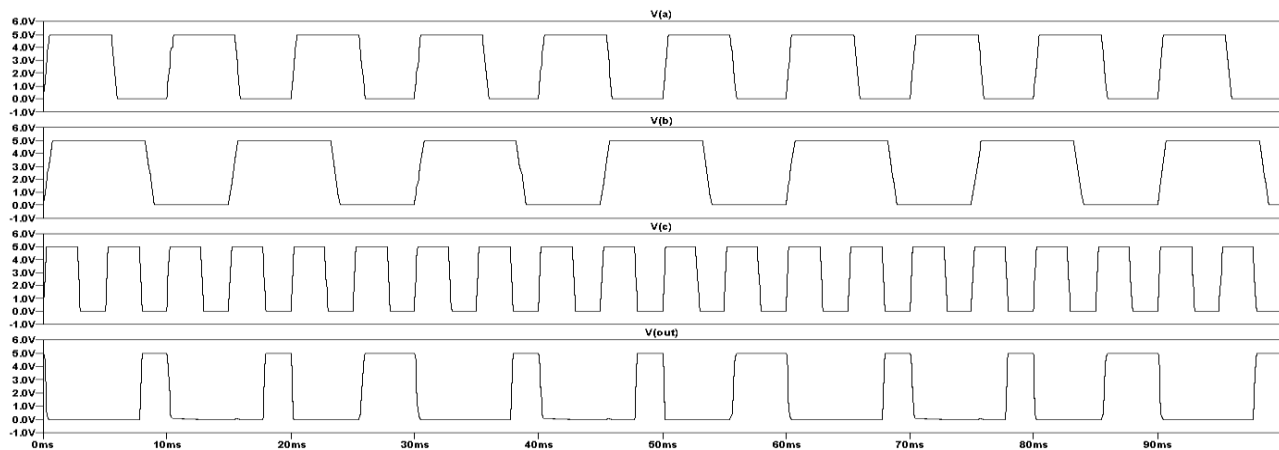10.4.3 Output of complex CMOS logic for $OUT = \sim(A+BC)$




10.4.4 SPICE NETLIST:

```
* C:\Users\PRITHIVI\Documents\LTspiceXVII\A+BC_COMPLEXGATE.asc
M1 OUT A 0 0 NMOS
M2 OUT B N002 N002 NMOS
M3 N002 C 0 0 NMOS
M4 N001 B OUT N001 PMOS
M5 N001 C OUT N001 PMOS
M6 VDD A N001 VDD PMOS
V1 A 0 PULSE(0 5 0 0 0 5m 10m 100)
V2 VDD 0 5
V3 B 0 PULSE(0 5 0 0 0 7.5m 15m 100)
V4 C 0 PULSE(0 5 0 0 0 2.5m 5m 100)
.model NMOS NMOS
.model PMOS PMOS
.lib C:\Users\PRITHIVI\Documents\LTspiceXVII\lib\cmp\standard.mos
.tran 100m
.backanno
.end
```


10.4.5 Pseudo NMOS gate Inverter:

W/L ratio of PMOS: 4/2, NMOS:24/2.

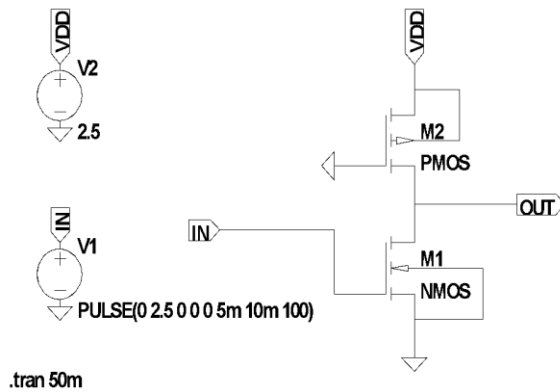

10.4.6 Pseudo NMOS Inverter output:

10.4.7 SPICE NETLIST :

 

```
* C:\Users\PRITHIVI\Documents\LTspiceXVII\PSEUDO NMOS INVERTER.asc
V1 IN 0 PULSE(0 2.5 0 0 0 5m 10m 100)
V2 VDD 0 2.5
M1 OUT IN 0 0 NMOS l=2 w=24
M2 VDD 0 OUT VDD PMOS l=2 w=4
.model NMOS NMOS
.model PMOS PMOS
.lib C:\Users\PRITHIVI\Documents\LTspiceXVII\lib\cmp\standard.mos
.tran 50m
.backanno
.end
```

10.5 Post lab:

1. Design Complex CMOS logic $Out = \sim(AB+CD)$ in LTSPICE.
2. Design Pseudo NMOS NAND gate in LTSPICE.

10.6 Result:

Thus, the design and analyse of Complex CMOS gate and Pseudo NMOS gate have been performed and its transfer characteristics is verified using LTSPICE tool.

Lab Experiment # 11

Design and Analysis of DCVSL, CPL and Pass Transistor Logic using LTSPICE

11.1 Objective: To learn the design of **DCVSL, CPL and Pass Transistor Logic** in circuit level and get the spice net list using LTSPICE tool.

11.2 Software tools Requirement

Equipment's:
LTSPICE software

11.3 Pre lab Questions

(Write pre lab Q & A in an A4 sheet)

1. Differentiate Dynamic and Domino CMOS logic
2. Explain Domino CMOS logic with an example.

11.4 Problem 1:

- 1a) Design and analyze Differential Cascode Voltage Switch Logic(DCVSL) using LTspice
- 1b) Design and analyze the complementary Pass transistor Logic for a 2 input AND/NAND in circuit level, verify the characteristics and infer the SPICE netlist using LTSPICE.

Problem 2:

- 2a) Design and analyze the complementary Pass transistor Logic for a 2 input OR/NOR in circuit level, verify the characteristics and infer the SPICE netlist using LTSPICE.

Problem 3:



- 3a) Design and analyze the Pass transistor Logic for a 2 input AND in circuit level, verify the characteristics and infer the SPICE netlist using LTSPICE.

Problem 4:


- 4a) Design and analyze the Pass transistor Logic for a 2 input XOR in circuit level, verify the characteristics and infer the SPICE netlist using LTSPICE.

11.4.1 Circuit Diagram

a.)DCVSL –NAND gate

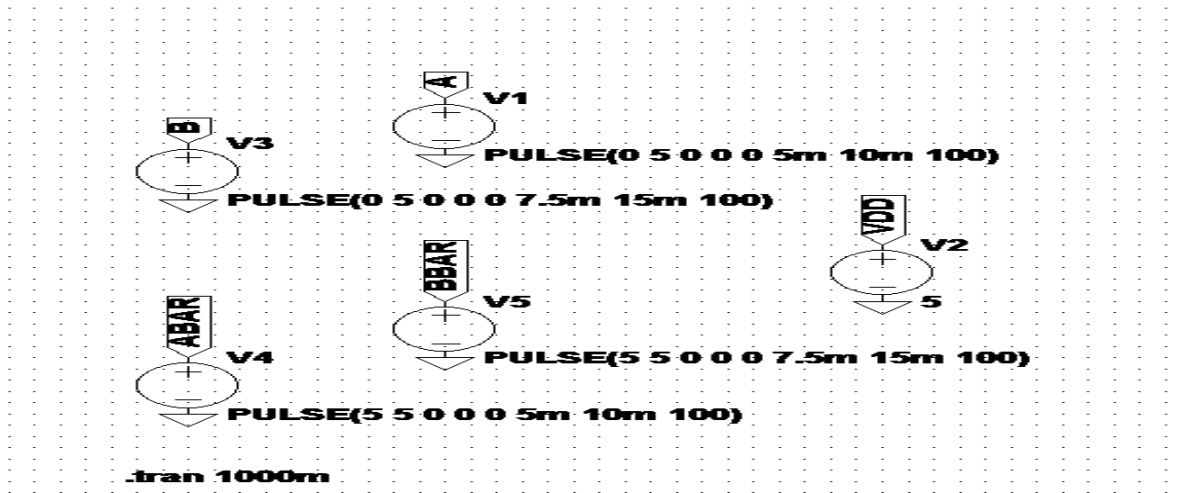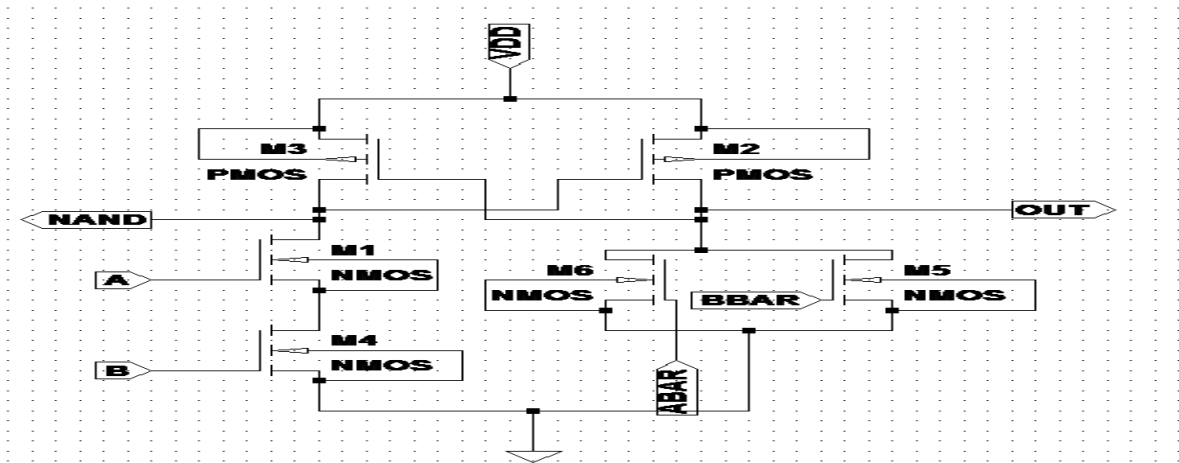

11.4.1a) OUTPUT

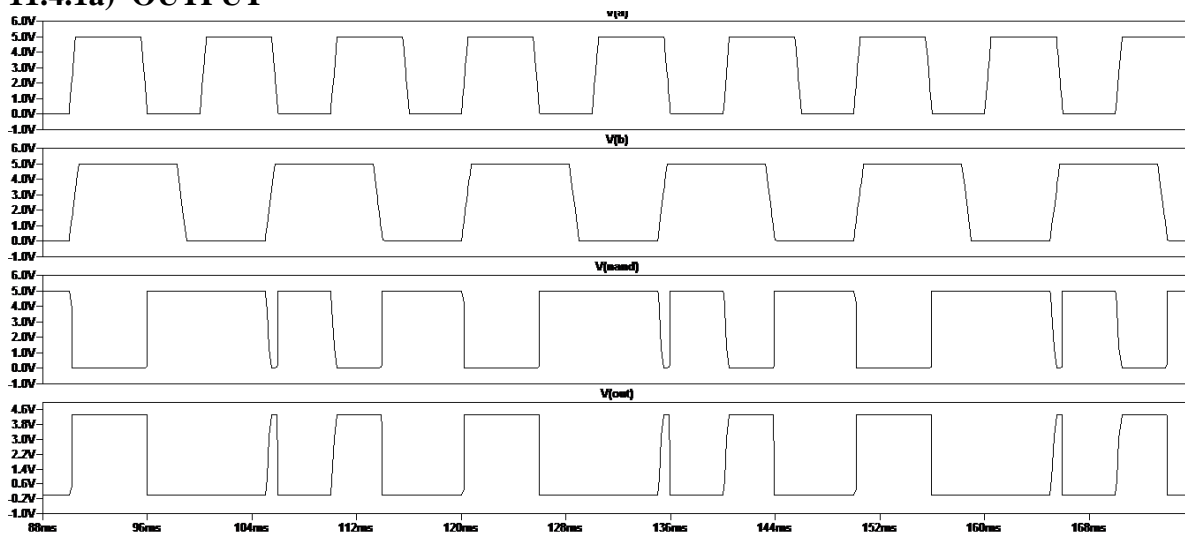

11.4.1a)Spice Netlist:


* C:\Users\PRITHIVI\Documents\LTspiceXVII\DCVSL.asc
M2 VDD NAND OUT VDD PMOS l=2 w=80

```


M3 VDD OUT NAND VDD PMOS l=2 w=4
M1 NAND A N001 N001 NMOS l=2 w=20
M4 N001 B 0 0 NMOS l=2 w=20
M5 OUT BBAR 0 0 NMOS l=2 w=10
M6 OUT ABAR 0 0 NMOS l=2 w=10
V1 A 0 PULSE(0 5 0 0 0 5m 10m 100)
V2 VDD 0 5
V3 B 0 PULSE(0 5 0 0 0 7.5m 15m 100)
V4 ABAR 0 PULSE(5 5 0 0 0 5m 10m 100)
V5 BBAR 0 PULSE(5 5 0 0 0 7.5m 15m 100)
.model NMOS NMOS
.model PMOS PMOS
.lib C:\Users\PRITHIVI\Documents\LTspiceXVII\lib\cmp\standard.mos
.tran 1000m
.backanno
.end

```

1b) AND/NAND gate using CPL:

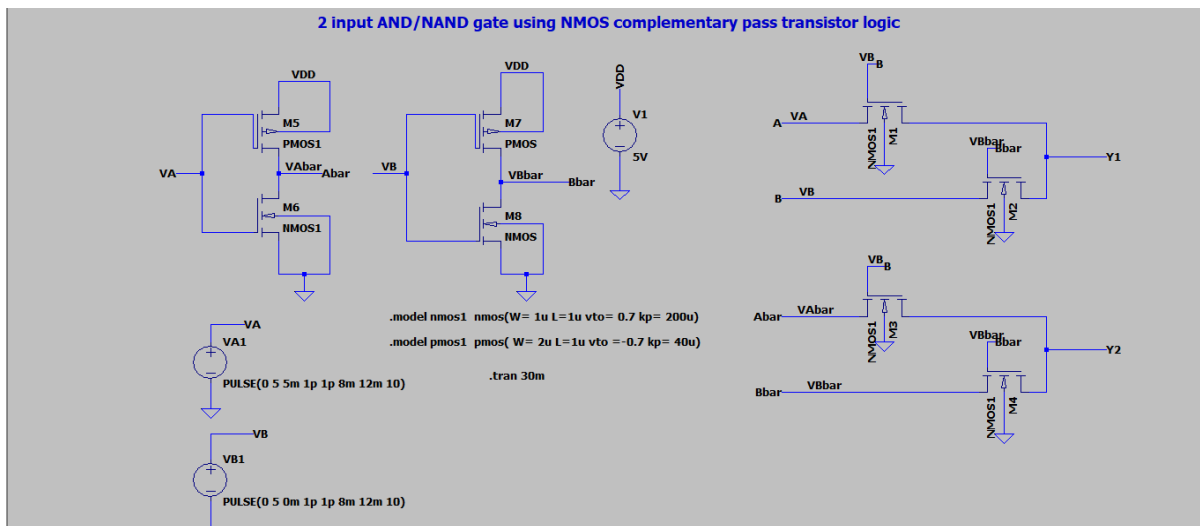

11.4.1b)Output

 


SPICE NETLIST:


- * F:\AND.asc

- M1 Y1 VB VA 0 NMOS1 l=1u w=1u
- M2 Y1 VBbar VB 0 NMOS1 l=1u w=1u
- M3 Y2 VB VAbar 0 NMOS1 l=1u w=1u
- M4 Y2 VBbar VBbar 0 NMOS1 l=1u w=1u
- M5 VDD VA VAbar VDD PMOS1
- M6 VAbar VA 0 0 NMOS1 l=1u w=1u
- V1 VDD 0 5V
- VA1 VA 0 PULSE(0 5 5m 1p 1p 8m 12m 10)
- VB1 VB 0 PULSE(0 5 0m 1p 1p 8m 12m 10)
- M7 VDD VB VBbar VDD PMOS
- M8 VBbar VB 0 0 NMOS
- .model NMOS NMOS
- .model PMOS PMOS
- .lib C:\Users\AJAY GOVINDAN\Documents\LTspiceXVII\lib\cmp\standard.mos
- .model nmos1 nmos(W= 1u L=1u vto= 0.7 kp= 200u)
- .model pmos1 pmos(W= 2u L=1u vto =-0.7 kp= 40u)
- .tran 30m
- * 2 input AND/NAND gate using NMOS complementary pass transistor logic
- .backanno
- .end

11.4.2) OR/NOR CPL LOGIC:

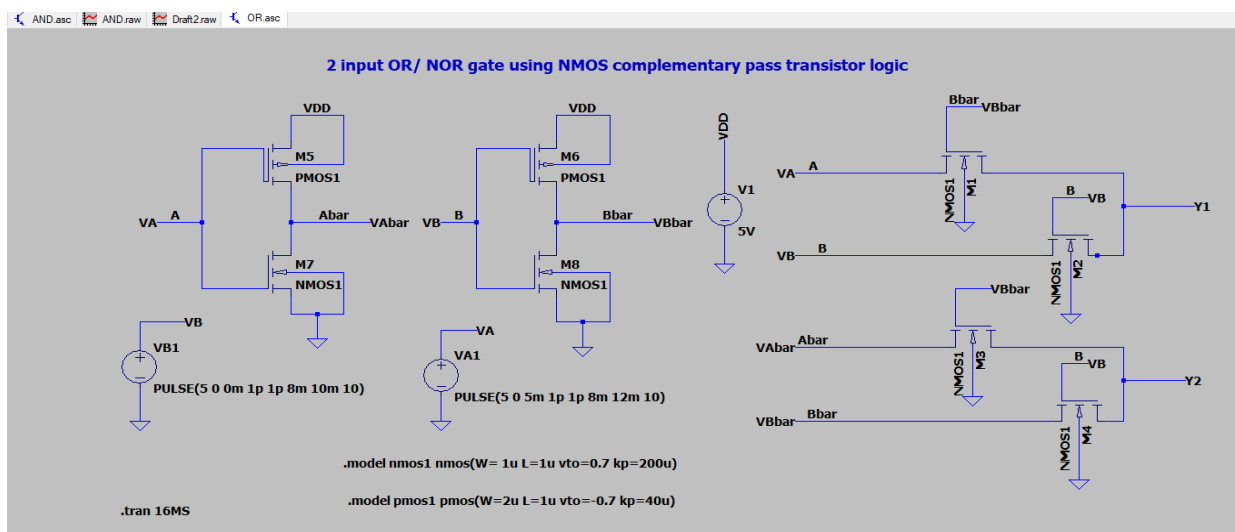


11.4.2 OUTPUT:

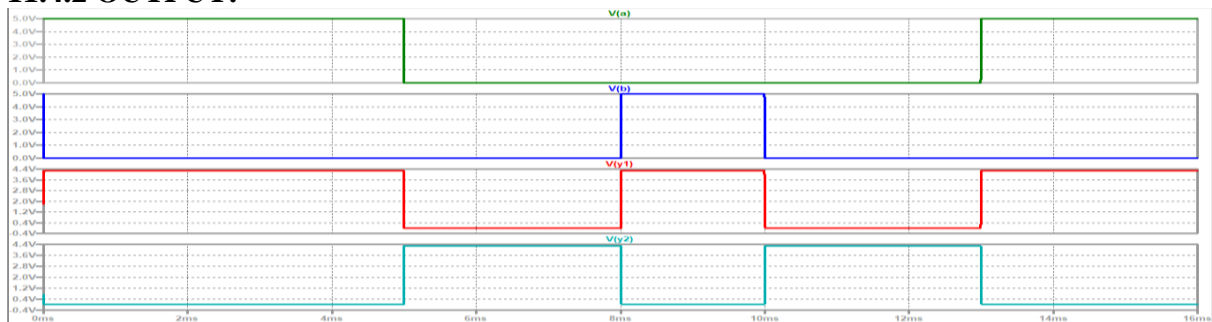


11.4.2 Spice Netlist:

- * F:\OR.asc
- M1 Y1 Bbar A 0 NMOS1
- M2 Y1 B B 0 NMOS1
- M3 Y2 Bbar Abar 0 NMOS1
- M4 Y2 B Bbar 0 NMOS1
- M5 VDD A Abar VDD PMOS1
- M6 VDD B Bbar VDD PMOS1
- M7 Abar A 0 0 NMOS1
- M8 Bbar B 0 0 NMOS1
- V1 VDD 0 5V
- VA1 A 0 PULSE(5 0 5m 1p 1p 8m 12m 10)
- VB1 B 0 PULSE(5 0 0m 1p 1p 8m 10m 10)
- .model NMOS NMOS
- .model PMOS PMOS
- .lib C:\Users\AJAY GOVINDAN\Documents\LTspiceXVII\lib\cmp\standard.mos
- * 2 input OR/ NOR gate using NMOS complementary pass transistor logic
- model nmos1 nmos(W= 1u L=1u vto=0.7 kp=200u)
- model pmos1 pmos(W=2u L=1u vto=-0.7 kp=40u)
- tran 16MS
- backanno
- end

11.4.3 AND GATE USING PTL:

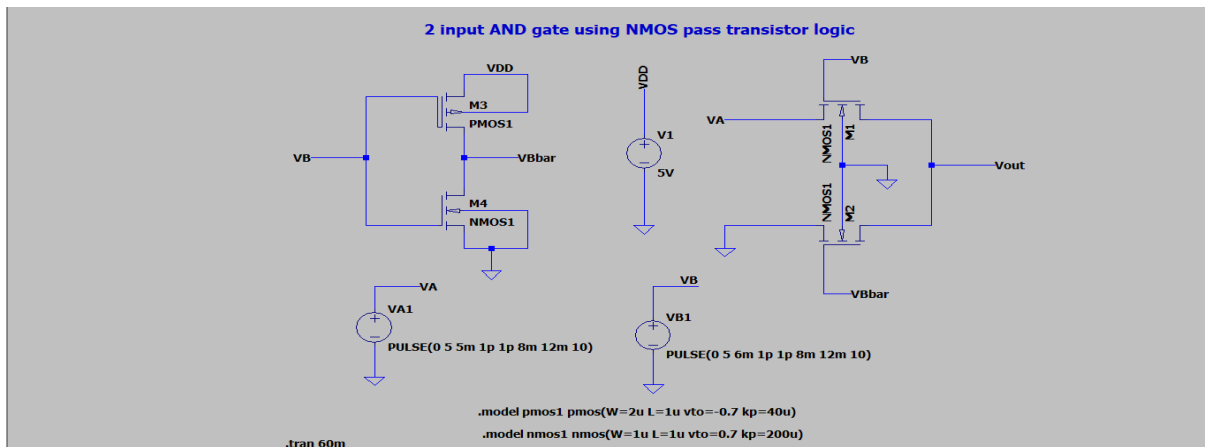


11.4.3 Output

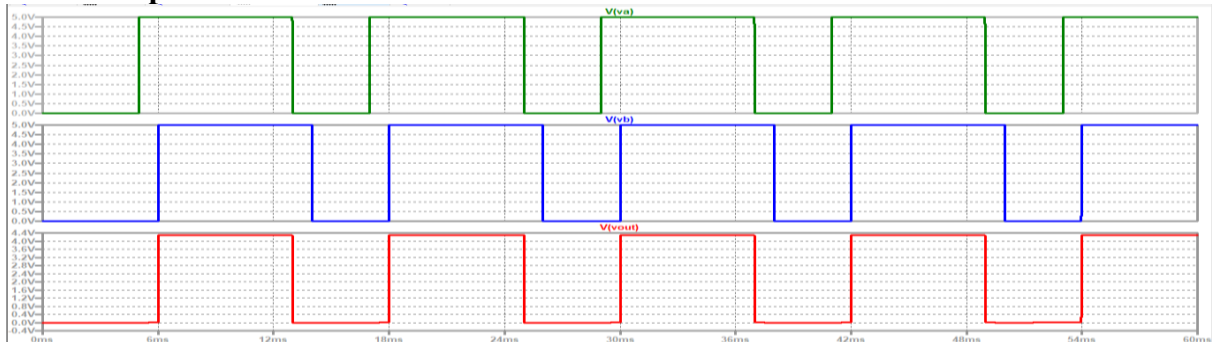


11.4.3 SPICE NETLIST:

- * F:\ANDPTL.asc
- M1 Vout VB VA 0 NMOS1
- M2 Vout VBbar 0 0 NMOS1
- M3 VDD VB VBbar VDD PMOS1
- M4 VBbar VB 0 0 NMOS1
- V1 VDD 0 5V
- VB1 VB 0 PULSE(0 5 6m 1p 1p 8m 12m 10)
- VA1 VA 0 PULSE(0 5 5m 1p 1p 8m 12m 10)
- .model NMOS NMOS
- .model PMOS PMOS
- .lib C:\Users\AJAY GOVINDAN\Documents\LTspiceXVII\lib\cmp\standard.mos
- * 2 input AND gate using NMOS pass transistor logic
- .model pmos1 pmos(W=2u L=1u vto=-0.7 kp=40u)
- .model nmos1 nmos(W=1u L=1u vto=0.7 kp=200u)
- .tran 60m
- .backanno
- .end

11.4.4 XOR GATE USING PTL

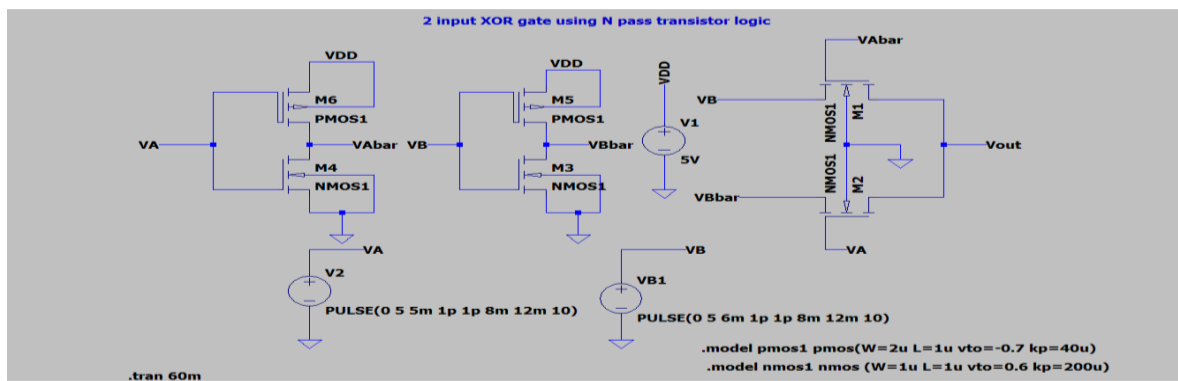

11.4.4 OUTPUT :

 

11.4.4 Spice Netlist:

- * F:\XORPTL.asc
- M1 Vout VAbar VB 0 NMOS1
- M2 Vout VA VBbar 0 NMOS1
- M3 VBbar VB 0 0 NMOS1
- M4 VAbar VA 0 0 NMOS1

- M5 VDD VB VBbar VDD PMOS1
- M6 VDD VA VAbar VDD PMOS1
- V1 VDD 0 5V
- VB1 VB 0 PULSE(0 5 6m 1p 1p 8m 12m 10)
- V2 VA 0 PULSE(0 5 5m 1p 1p 8m 12m 10)
- .model NMOS NMOS
- .model PMOS PMOS
- .lib C:\Users\AJAY GOVINDAN\Documents\LTspiceXVII\lib\cmp\standard.mos
- * 2 input XOR gate using N pass transistor logic
- .model pmos1 pmos(W=2u L=1u vto=-0.7 kp=40u)
- .model nmos1 nmos(W=1u L=1u vto=0.6 kp=200u)
- .tran 60m
- .backanno
- .end

11.5 Post lab:

1. Realize tri-state buffer circuit.

11.6 Result:

Thus, the design and analysis of DCVSL, CPL and Pass transistor design have been performed and its characteristics are verified using LTSpice tool.

LAB EXPERIMENT # 12

Dynamic NAND gate

12.1 Objective: To study and design the two inputs n-type dynamic NAND gate using HSPICE and verify the simulation result.

12.2 Software required: Hspice

12.3 Pre-lab Questions

1. Differentiate static and dynamic CMOS logic.
2. Explain NORA CMOS logic.

12.4 Design two input dynamic NAND Gate

Circuit Diagram:

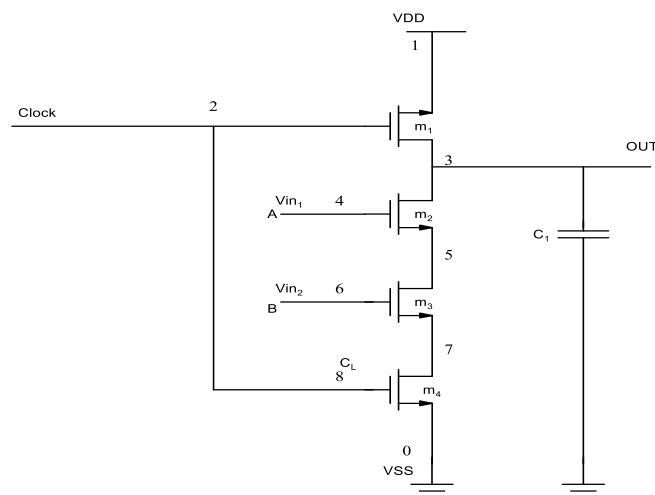


Figure 1. Two input dynamic NAND gate

12.4 Spice Netlist:


```
.option post
.include c:\synopsys\tsmc018.lib
vdd 1 0 dc 1.8v
vin1 4 0 pulse(-5 5 2ns 2ns 2ns 80us 160us) //(input A)
vin2 6 0 pulse(-5 5 2ns 2ns 2ns 50us 100us) //(input B)
vin3 2 0 pulse(-5 5 2ns 2ns 2ns 50us 100us) //(CLOCK)
vin4 8 0 pulse(-5 5 2ns 2ns 2ns 50us 100us) //(CLOCK)
m1 3 2 1 1 cmosp w=4u l=180nm
m2 3 4 5 5 cmosn w=2u l=180nm
m3 5 6 7 7 cmosn w=2u l=180nm
m4 7 8 0 0 cmosn w=2u l=180nm
```

```

c1 3 0 100p // (CAPACITOR→ Vary the capacitor value to see the dynamic performance)
.tran 100u 800u
.plot v(3) v(4) V(6)
.end

```

OUTPUT : N TYPE DYNAMIC- NAND GATE

 

12.7 Netlist :

```

.option post
.include c:\synopsys\tsmc018.lib
* t58f spice bsim3 version 3.1 parameters
*
* spice 3f5 level 8, star-hspice level 49, utmost level 8
*
* temperature_parameters=default
*
vdd 1 0 dc 1.8v
vin1 4 0 pulse(-5 5 2ns 2ns 2ns 80us 160us)
vin2 6 0 pulse(-5 5 2ns 2ns 2ns 50us 100us)
vin3 2 0 pulse(-5 5 2ns 2ns 2ns 50us 100us)
vin4 8 0 pulse(-5 5 2ns 2ns 2ns 50us 100us)
m1 3 2 1 1 cmosp w=4u l=180nm
m2 3 4 5 5 cmosn w=2u l=180nm
m3 5 6 7 7 cmosn w=2u l=180nm
m4 7 8 0 0 cmosn w=2u l=180nm
c1 3 0 100p
.tran 100u 800u
.plot v(3) v(4) v(6)
.end

*****
dynamic nand
***** mos model parameters          tnom= 25.000 temp= 25.000
*****
*****

```

```
***      model parameters  model name:  0:cmosn  model type:nmos  ***
*****
```

```
*** general parameters ***
deriv= 0.
```

```
*** level 49  model parameters  ***
```

```

hspver= 2006.03      level= 49
version= 3.1      paramchk= 0
apwarn= 1      lite= 0
vgslim= 0      binUnit= 1
capMod= 2      xpart= 0.5
mobMod= 1      nqsMod= 0
stiMod= 0      elm= 5
sfvtflag= 0      tox= 4.1e-009 meter
      xj= 1e-007 meter      binflag= 0
lmin= 0 meter      lmax= 0 meter
wmin= 0 meter      wmax= 0 meter
lref= 0 meter      wref= 0 meter
lint=1.69004e-008 meter      wint= 0 meter
lmult= 1      wmult= 1
ll= 0      lln= 1
lw= 0      lwn= 1
lwl= 0      wl= 0
wln= 1      ww= 0
wwn= 1      ww1= 0
dwg=-4.72872e-009 m/V      dwb=-2.45241e-009 m/V^1/2
a0= 2      ags= 0.444996 V^-1
b0=1.90108e-007 meter      b1=4.99995e-006 meter
keta= -0.0164863 V^-1      voff= -0.0948017 V
ngate= 0 cm^-3      vbx= 0 V
vbm= -3 V      xt= 1.55e-007 meter
vth0= 0.366247 V      nch=2.3549e+017 cm^-3
nsub= 6e+016 cm^-3      nlx=1.63068e-007 meter
gamma1= 0 V^-1/2      gamma2= 0 V^-1/2
k1= 0.5865 V^1/2      k2= 0.00112727
k3= 0.001      k3b= 0.0294061 V^-1
w0= 1e-007 meter      dvt0= 1.20646
dvt1= 0.421549      dvt2= 0.0197749 V^-1
dvt0w= 0 meter^-1      dvt1w= 0 meter^-1
dvt2w= 0 V^-1      dsub= 0.0145467
eta0= 0.00223093      etab=6.02898e-005 V^-1
u0= 273.809 cm^2/V/sec      ua=-1.40499e-009 m/V
ub=2.40832e-018 (m/V)^2      uc=6.50483e-011 V^-1
vsat= 135501 m/sec      a1=0.000386877 v^-1
a2= 0.464027      delta= 0.01 V
rdsw= 123.338 ohm-um      prwg= 0.5 V^-1
prwb= -0.197728 V^-1/2      wr= 1
pclm= 1.38221      pdiblc1= 0.176279
```

```

pdiblc2= 0.00166653      pdiblc3= -0.1 V^-1
pscbe1=8.91287e+009 V/m   pscbe2=7.34961e-009 V/m
drout= 0.769469          pvag= 0.00168592
nfactor= 2.18601         cdsc= 0.00024 f/m^2
cdscb= 0 f/V/m^2         cdsd= 0 f/V/m^2
cit= 0 f/m^2             alpha0= 0 m/V
beta0= 30 V              dlc=1.69004e-008 meter
dwc= 0 meter             clc= 1e-007 meter
cle= 0.6                 cgso= 8.23e-010 f/m
cgdo= 8.23e-010 f/m      cgbo= 1e-012 f/m
cgsl= 0 f/m              cgdl= 0 f/m
ckappa= 0.6              cf= 0 f/m
tnom= 300.15 K           kt1= -0.11 V
kt1l= 0                  kt2= 0.022
ute= -1.5                ua1= 4.31e-009 m/V
ub1= -7.61e-018 (m/V)^2  uc1= -5.6e-011 m/V^2
at= 33000 m/s            prt= 0
using Berkeley noise model noiMod= 2
noia=1.31826e+019         noib= 144544
noic=-1.24516e-012        em= 4.1e+007
ef= 0.92                 af= 1
kf= 0                    gdsnoi=-1.23457e-029
using Hspice diodes       using ACM
acm= 0                   hdif= 0 meter
ldif= 0 meter            js= 0 amp/m^2
jsw= 0 amp/m             xti= 0
n= 1                     cj=0.000946643 f/m^2
mj= 0.382027             pb= 0.8 V
cjsw=2.60815e-010 f/m     mjsw= 0.102322
php= 0.8 V               pbsw (not used)
cjgate=2.60815e-010 f/m   cjswg (not used)
mjswg (not used)          pbswg (not used)
lketa= 0.00716508         wketa=-0.00288098
pketa=-0.00675928         pvth0=-0.00219937
pk2= 0.00159325          peta0=0.000100316
pu0= 6.77752             pua=5.50542e-012
pub=8.84133e-025          pvsat= 2006.29
prdsw= -0.936896

```

```

*****
***      model parameters  model name: 0:cmosp  model type:pmos  ***
*****

```

```

*** general parameters ***

```

```

deriv= 0.

```

```

*** level 49 model parameters ***

```

```

hspver= 2006.03          level= 49
version= 3.1              paramchk= 0
apwarn= 1                 lite= 0

```

vgslim= 0 binUnit= 1
 capMod= 2 xpart= 0.5
 mobMod= 1 nqsMod= 0
 stilMod= 0 elm= 5
 sfvtflag= 0 tox= 4.1e-009 meter
 xj= 1e-007 meter binflag= 0
 lmin= 0 meter lmax= 0 meter
 wmin= 0 meter wmax= 0 meter
 lref= 0 meter wref= 0 meter
 lint=2.94454e-008 meter wint= 0 meter
 lmult= 1 wmult= 1
 ll= 0 llm= 1
 lw= 0 lwn= 1
 lwl= 0 wl= 0
 wln= 1 ww= 0
 wwn= 1 wwl= 0
 dwg=-2.79872e-008 m/V dwb=-4.83797e-010 m/V^{1/2}
 a0= 1.99766 ags= 0.418694 V⁻¹
 b0=1.94918e-007 meter b1=6.42291e-007 meter
 keta= 0.0166345 V⁻¹ voff= -0.095236 V
 ngate= 0 cm⁻³ vbv= 0 V
 vbm= -3 V xt= 1.55e-007 meter
 vth0= -0.390601 V nch=4.1589e+017 cm⁻³
 nsub= 6e+016 cm⁻³ nlx=1.19407e-007 meter
 gamma1= 0 V^{-1/2} gamma2= 0 V^{-1/2}
 k1= 0.534131 V^{1/2} k2= 0.0395326
 k3= 0 k3b= 7.49162 V⁻¹
 w0= 1e-006 meter dvt0= 0.506055
 dvt1= 0.242384 dvt2= 0.1 V⁻¹
 dvt0w= 0 meter⁻¹ dvt1w= 0 meter⁻¹
 dvt2w= 0 V⁻¹ dsub= 0.00181655
 eta0= 0.0010355 etab=-0.00043584 V⁻¹
 u0= 115.689 cm²/V/sec ua=1.57375e-009 m/V
 ub=1.87431e-021 (m/V)² uc= -1e-010 V⁻¹
 vsat= 113098 m/sec a1= 0.474915 v⁻¹
 a2= 0.300003 delta= 0.01 V
 rdsw= 198.321 ohm-um prwg= 0.5 V⁻¹
 prwb= -0.498665 V^{-1/2} wr= 1
 pclm= 1.32999 pdiblc1= 0.00176656
 pdiblc2=7.72839e-007 pdiblc3= -0.001 V⁻¹
 pscbe1=4.87218e+010 V/m pscbe2= 5e-010 V/m
 drout= 0.00101189 pvag= 0.0209921
 nfactor= 2 cdsc= 0.00024 f/m²
 cdsch= 0 f/V/m² cdsd= 0 f/V/m²
 cit= 0 f/m² alpha0= 0 m/V
 beta0= 30 V dlc=2.94454e-008 meter
 dwc= 0 meter clc= 1e-007 meter
 cle= 0.6 cgso= 6.35e-010 f/m
 cgdo= 6.35e-010 f/m cgbo= 1e-012 f/m
 cgsl= 0 f/m cgdl= 0 f/m

```

ckappa=    0.6          cf=    0 f/m
tnom=    300.15 K      kt1=   -0.11 V
kt1l=     0           kt2=    0.022
ute=     -1.5         ua1=  4.31e-009 m/V
ub1= -7.61e-018 (m/V)^2  uc1= -5.6e-011 m/V^2
at=    33000 m/s      prt=     0
using Berkeley noise model    noiMod=    2
noia=3.57457e+018          noib=    2500
noic=2.6126e-011          em=   4.1e+007
ef=    1.1388          af=     1
kf=     0           gdsnoi=-1.23457e-029
using Hspice diodes          using ACM
acm=     0           hdif=    0 meter
ldif=    0 meter      js=     0 amp/m^2
jsw=     0 amp/m      xti=     0
n=       1           cj=0.00114452 f/m^2
mj=  0.409952          pb=  0.846869 V
cjsw=2.49075e-010 f/m      mjsw=  0.347856
php=  0.846869 V          pbsw (not used)
cjgate=2.49075e-010 f/m      cjswg (not used)
mjswg (not used)          pbswg (not used)
lketa=-0.00149587          wketa=  0.0222457
pketa=-0.00253656          pvth0= 0.00230202
pk2= 0.00182191          peta0=2.82779e-005
pu0= -1.55806           pua=-6.36889e-011
pub=  1e-021           pvsat=  49.842
prdsw=  9.05753

```

Model: 0:cmosn

W = 1.99e-006, L = 1.8e-007

dynamic nand

***** operating point information tnom= 25.000 temp= 25.000

***** operating point status is voltage simulation time is 0.

node =voltage node =voltage node =voltage

+0:1 = 1.8000 0:2 = -5.0000 0:3 = 1.8000

+0:4 = -5.0000 0:5 = 1.2000 0:6 = -5.0000

+0:7 = 600.0000m 0:8 = -5.0000

dynamic nand

***** transient analysis tnom= 25.000 temp= 25.000

a

legend:

a: v(3)

b: v(4)

c: v(6)

```

time      v(3)
(abc ) -10.0000 -5.0000 0. 5.0000 10.0000
      +      +      +      +      +
0. 1.800 +-----+-----2-----+-----+-----a-----+-----+-----+-----+
100.0000u 1.800 + + 2 + + a + + + +
200.0000u 1.800 + + c + + a + b + +
300.0000u 1.800 + + 2 + + a + + + +
400.0000u 1.800 + + c + + a + b + +
500.0000u 1.800 + + c + + a + b + +
600.0000u 1.800 + + 2 + + a + + + +
700.0000u 1.800 + + c + + a + b + +
800.0000u 1.800 + + 2 + + a + + + +
      +      +      +      +      +

```

B

dynamic nand

```

***** job statistics summary      tnom= 25.000 temp= 25.000
*****

```

total memory used 161 kbytes

```

# nodes = 9 # elements= 10
# diodes= 0 # bjts = 0 # jfets = 0 # mosfets = 4
# va device = 0

```

```

analysis      time  # points  tot. iter  conv.iter

op point      0.03    1      32
transient     0.05    9     2016    560 rev= 114
readin        0.01
errchk        0.00
setup         0.00
output        0.00
total cpu time 0.14 seconds
job started at 12:36:05 02/26/2020
job ended at 12:36:05 02/26/2020

```

12.5 Post Lab Questions:

- 1.Design the n-type dynamic NOR gate using the HSPICE.
- 2.Realize n –type dynamic AND gate using the HSPICE.

12.6 Result:

Thus the design of two input dynamic NAND gate, MOS transistor level using HSPICE was studied and simulated.