



# SRM INSTITUTE OF SCIENCE AND TECHNOLOGY

## TIRUCHIRAPPALLI CAMPUS

Ans. 1, A, B,  $B_{in}$ , D and  $B_{out}$  are respectively the minuend, the subtrahend, the BORROW - IN, the DIFFERENCE output and the Borrow - out in the case of full subtractor. Determine the bit status of D and  $B_{out}$  for the following values of A, B and  $B_{in}$ .


BLOCK DIAGRAM.

a).  $A = 0, B = 1, B_{in} = 1$ .

b).  $A = 1, B = 1, B_{in} = 0$

c).  $A = 1, B = 1, B_{in} = 1$ .

d).  $A = 0, B = 0, B_{in} = 1$ .

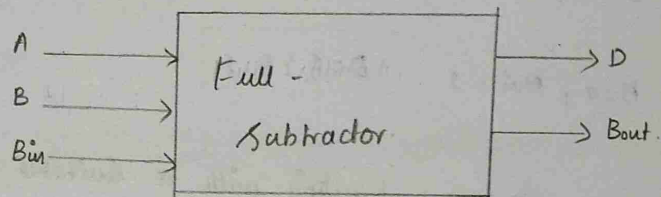

TRUTH TABLE FOR FULL SUBTRACTOR,

A	A	B	$B_{in}$	D	$B_{out}$
0	0	0	0	0	0
1	0	0	1	1	1
2	0	1	0	1	1
3	0	1	1	0	1
4	1	0	0	1	0
5	1	0	1	0	0
6	1	1	0	0	0
7	1	1	1	1	1

(i). Difference,

A	$B_{in}$	$B'B_{in}'$	$B'B_{in}$	$BB_{in}$	$BB_{in}'$
		00	01	11	10
A' 0		0	1		1
A 1		1		1	

$$D = AB'B_{in}' + A'B'B_{in} + AB B_{in} + A'B B_{in}'$$

(ii). Borrow,

A	$B_{in}$	$B'B_{in}'$	$B'B_{in}$	$BB_{in}$	$BB_{in}'$
		00	01	11	10
A' 0			1	1	1
A 1				1	

$$D = A'B_{in} + BB_{in} + A'B$$

$$D = B_{in}(A' + B) + A'B$$



# SRM INSTITUTE OF SCIENCE AND TECHNOLOGY

## TIRUCHIRAPPALLI CAMPUS

- a).  $A=0, B=1, B_{in}=1$   $D=0; B=1$
- b).  $A=1, B=1, B_{in}=0$   $D=0; B=0$
- c).  $A=1, B=1, B_{in}=1$   $D=1; B=1$
- d).  $A=0, B=0, B_{in}=1$   $D=1; B=1$

4). Implement the Boolean function with a Suitable multiplexer,

$$f(A, B, C) = \pi(1, 2, 5).$$

$\pi$  represents Maxterm,

where output are represented by 0.


D	A	B	C	y
0	0	0	0	1
1	0	0	1	0
2	0	1	0	0
3	0	1	1	1
4	1	0	0	1
5	1	0	1	0
6	1	1	0	1
7	1	1	1	1

$\rightarrow y=c'$

$\rightarrow y=c$

$\rightarrow y=c'$

$\rightarrow y=1$

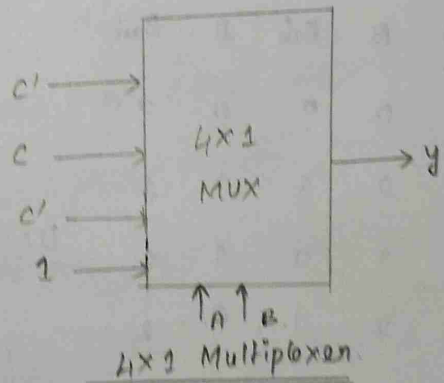



# SRM INSTITUTE OF SCIENCE AND TECHNOLOGY


## TIRUCHIRAPPALLI CAMPUS

Q. Design a 10 line decoder to BCD priority Encoder.

8 4 2 1

$D_{\text{input}}$	$D_0$	$D_1$	$D_2$	$D_3$	$D_4$	$D_5$	$D_6$	$D_7$	$D_8$	$D_9$	A	B	C	D
0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
1	X	X	0	0	0	0	0	0	0	0	0	0	0	1
2	X	X	1	0	0	0	0	0	0	0	0	0	1	0
3	X	X	X	1	0	0	0	0	0	0	0	0	1	1
4	X	X	X	X	1	0	0	0	0	0	0	1	0	0
5	X	X	X	X	X	1	0	0	0	0	0	1	0	1
6	X	X	X	X	X	X	1	0	0	0	0	1	1	0
7	X	X	X	X	X	X	X	1	0	0	0	1	1	1
8	X	X	X	X	X	X	X	X	1	0	1	0	0	0
9	X	X	X	X	X	X	X	X	X	1	1	0	0	1

Block diagram

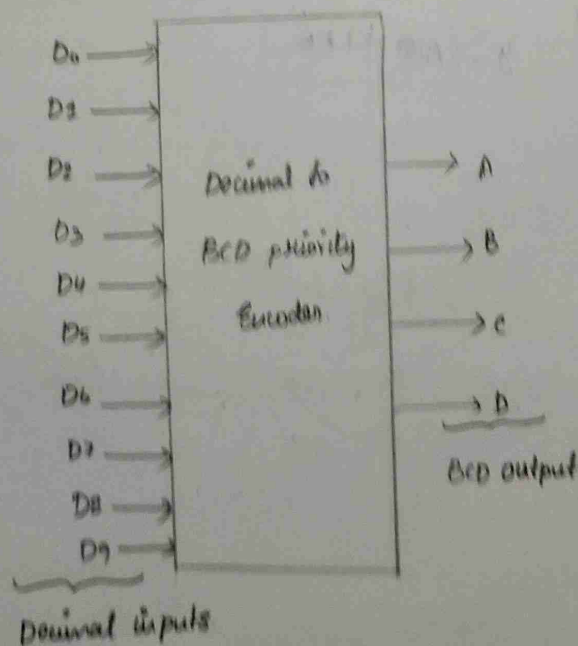





SRM INSTITUTE OF SCIENCE AND TECHNOLOGY  
TIRUCHIRAPPALLI CAMPUS

- 6). A Combinational circuit is defined by  $F = \sum (0, 2, 5, 6, 7)$ . Hardware implement the Boolean function  $F$  with a suitable decoder and an external OR/NOR gate having the minimum number of inputs.

D	A	B	C	y.
0	0	0	0	1
1	0	0	1	0
2	0	1	0	1
3	0	1	1	0
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	1

$$y = A'B'C' + A'Bc' + AB'C + ABc' + ABC.$$

$$= A'C'(B'+B) + AB(C+C') + AB'C$$

$$= A'C' + AB + AB'C.$$

$$y = A'C' + A(B+B'C).$$

$$y = A'B'C' + A'Bc' + AB'C + ABc' + ABC.$$


$$= A'C'(B'+B) + AB(C'+C) + AB'C.$$

$$= A'C' + A(B+B'C) = A'C' + A(B+C).$$

$$x(y+z) = xy + yz$$

$$= A'C' + AB + AC.$$

$$y = (A \oplus C)' + AB.$$

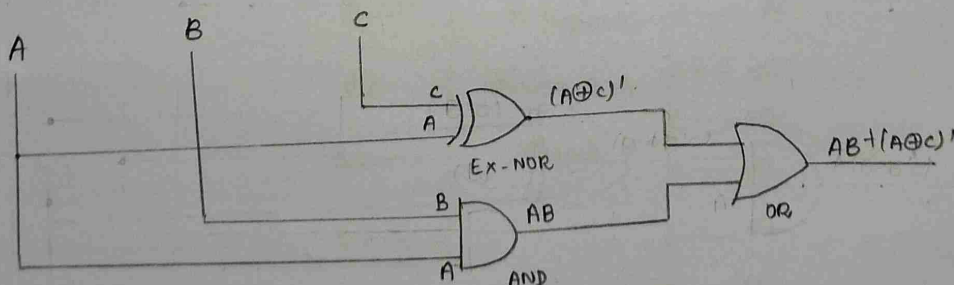



3

**SRM INSTITUTE OF SCIENCE AND TECHNOLOGY**  
TIRUCHIRAPPALLI CAMPUS

2). Determine the number of half and full adder circuit blocks required to construct a 64-bit binary parallel adder. Also, determine the number and type of additional logic gates needed to transform this 64-bit adder into a 64-bit adder-subtractor.

(i). A 64-bit binary parallel adder requires 1 half adder and 63 full adders.

(ii). To transform a 64-bit adder into a 64-bit adder-subtractor, we need to add 64 XOR gates and 64 AND gates.

- XOR Gates : 64
- AND Gates : 64
- The total number of additional logic gates is 128.


$$[64 \text{ bit adder}] + [64 \text{ XOR gates}] + [64 \text{ AND gates}] = 64\text{-bit adder subtractor.}$$





# SRM INSTITUTE OF SCIENCE AND TECHNOLOGY TIRUCHIRAPPALLI CAMPUS


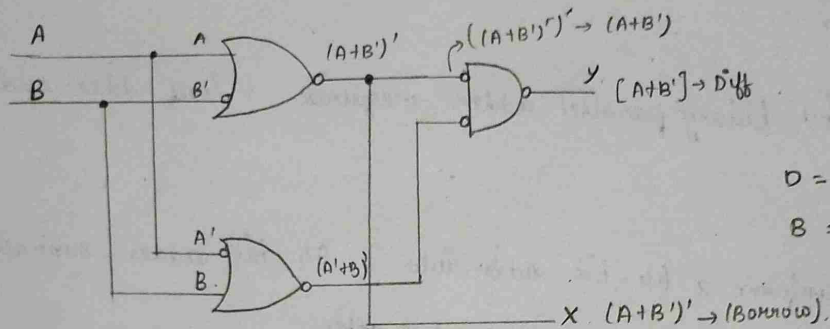
31. Prove that the logic diagram of fig performs the function of half subtractor provided that  $y$  represents the difference output and  $x$  represents the Borrow output.



Design of half - subtractor,

A	B	diff	Borr.
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

K-map. For difference.

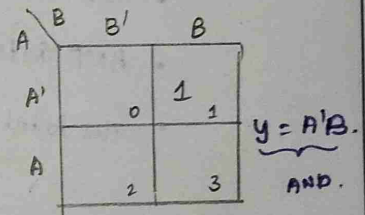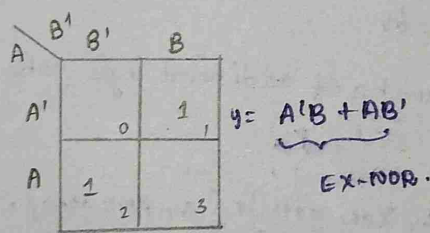

For Borrow =  $A'B$

For Difference =  $A'B + AB'$

From the above logic diagram, it is seen that  $y$  (Difference) is  $A \oplus B$  that is EX-OR, and  $x$  (Borrow) is  $A'B$  (AND gate).

Hence, it is proved.