

Exp. No: 01

Date: 21-07-23

## P-N JUNCTION DIODE CHARACTERISTICS

Aim:

To Study the Volt-Ampere characteristics of Silicon P-N Junction Diode and to find cut-in voltage, Static and dynamic resistances.


APPARATUS REQUIRED:

S.No	APPARATUS	TYPE	RANGE	QUANTITY
01	PN Junction Diode	IN4001		1
02	Resistance		1K ohm, 10% tolerance, 1/2 watt reading	1
03	Regulated Power Supply		[0-30V], 2A Rating	1
04	Ammeter	MC	[0-30]mA, [0-500]μA	Each 1
05	Voltmeter	MC	[0-1]V, [0-30]V	Each 1
06	Bread Board			1
	Connecting Wires			Few




## CIRCUIT DIAGRAM:


### FORWARD BIAS:

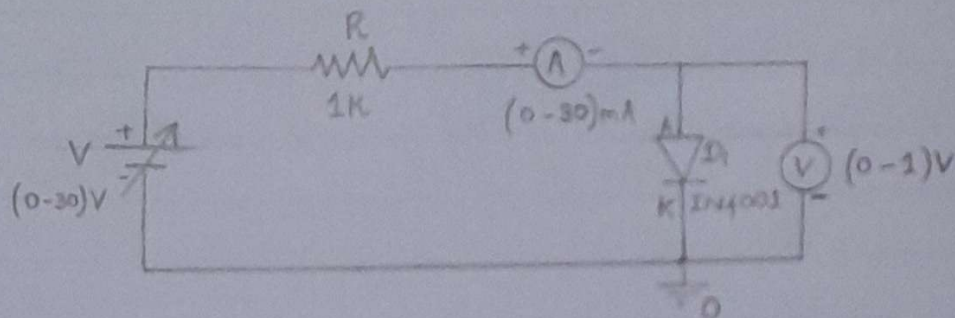

### REVERSE BIAS:

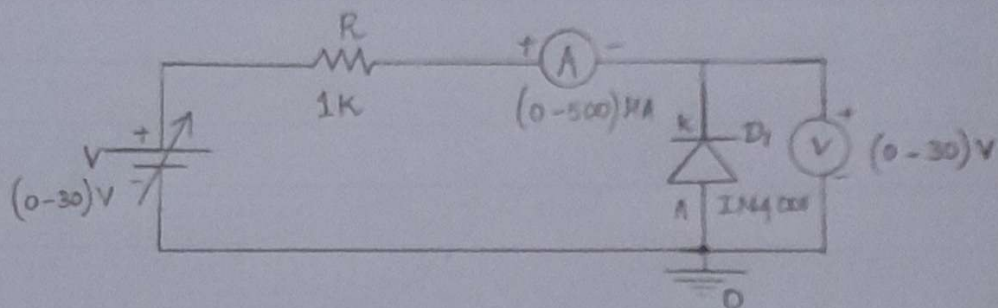

## MODEL GRAPH:

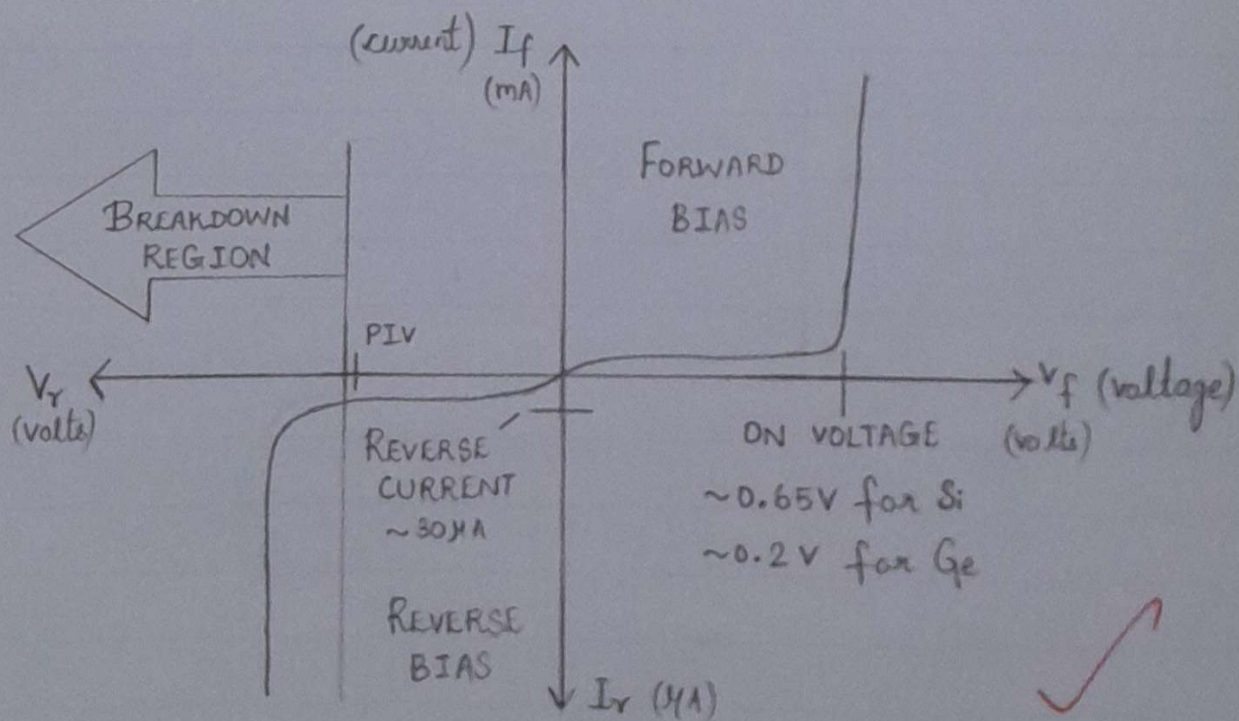



Exp. No: 02

Date: 28-07-23

## ZENER DIODE CHARACTERISTICS

### AIM:

To Study the volt-Ampere characteristics of Zener diode and to measure the Zener breakdown voltage.


### APPARATUS REQUIRED:

S.No	APPARATUS	TYPE	RANGE	QUANTITY
01	Zener Diode	$I_z 6.2$		1
02	Resistance		1Kohm, 10% tolerance, 1/2 watt rating	1
03	Regulated Power Supply		(0-30V), 2A rating	1
04	Ammeter	mc	[0-30] mA	1
05	Voltmeter	mc	(0-1)V, (0-10)V	1
06	Bread Board			1
	Connecting wires			Few




## CIRCUIT DIAGRAM:


### FORWARD BIAS:

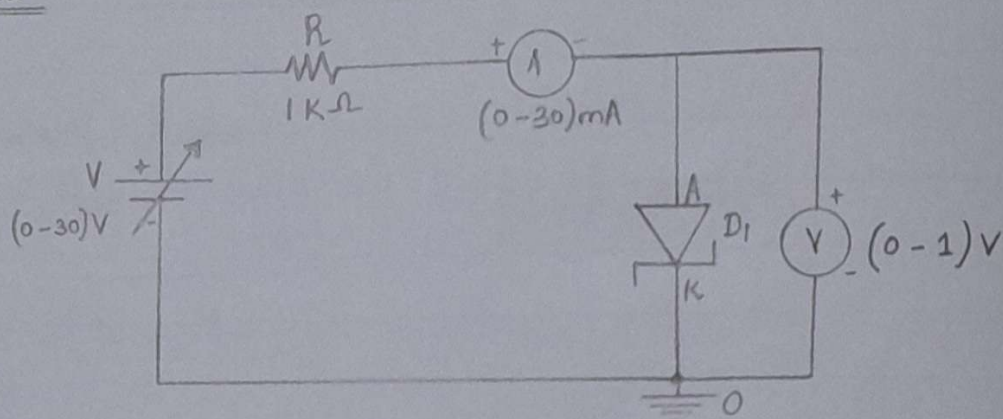


### REVERSE BIAS:

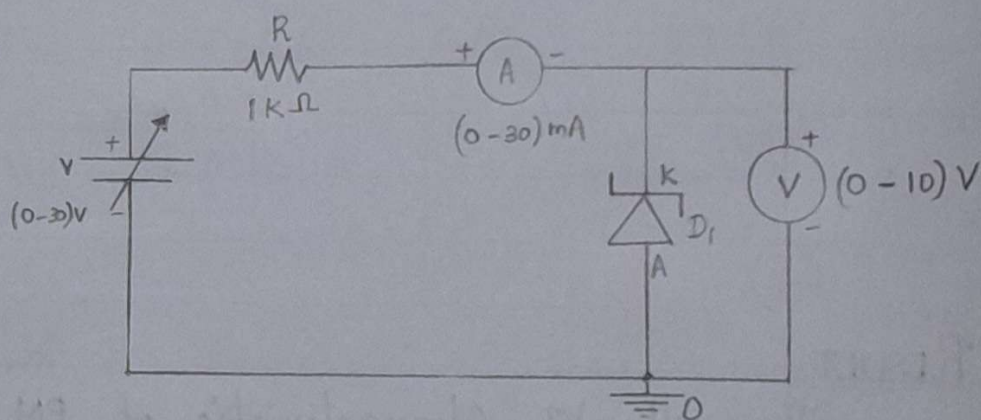

### ZENER DIODE SYMBOL:

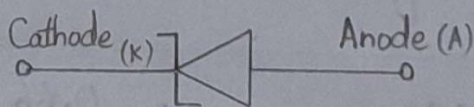

### MODEL GRAPH:

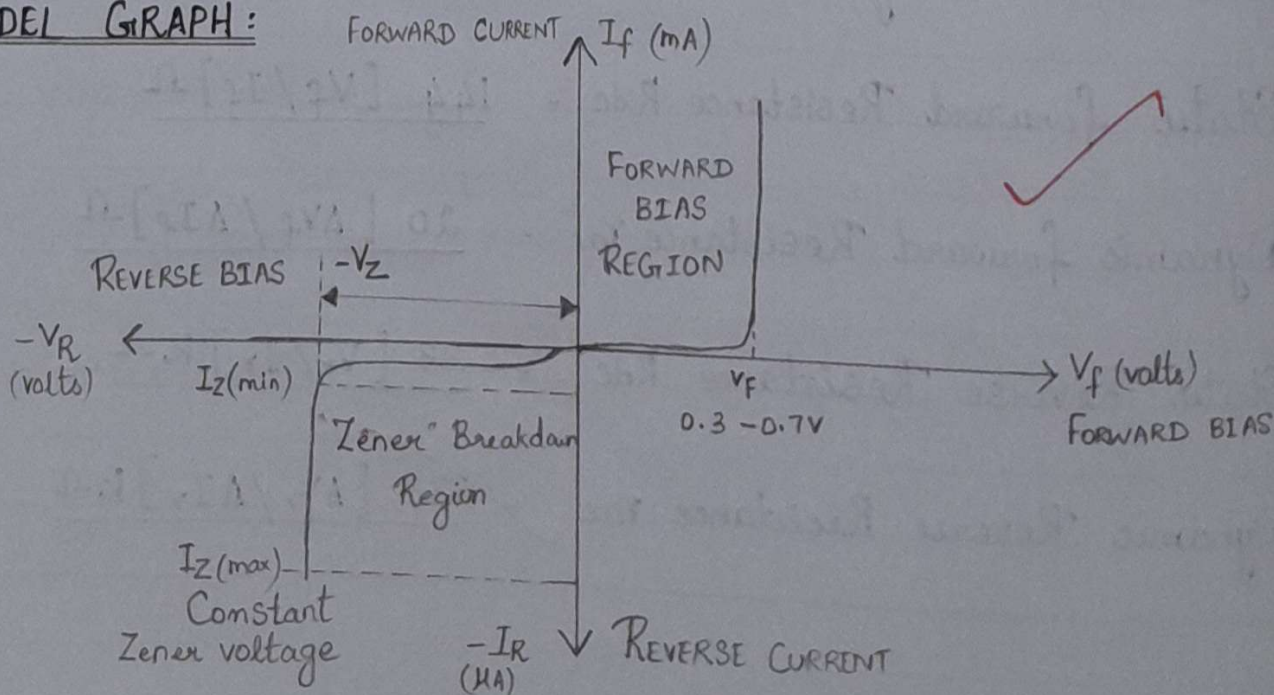



Ex. No: 03

Date: 04-8-23

DIODE RECTIFIER CIRCUITS - HALF WAVE RECTIFIERAIM:

To design and construct the diode rectifier circuit and analyze the following Parameters.


- To plot output waveform of the HWR.
- To find ripple factor using formulae
- To find the efficiency

APPARATUS REQUIRED:


S. No	APPARATUS	TYPE	RANGE	QUANTITY
01	Step down transformer		[6-0-6]V, 500mA, 1A rating	1
02	Resistance		470 ohm, 10% tolerance, 1/2 watt rating	1
03	Capacitor		470 $\mu$ F	1
04	Bread board Connecting wires			1 Few
05	Diode	IN4001		




## CIRCUIT DIAGRAM:

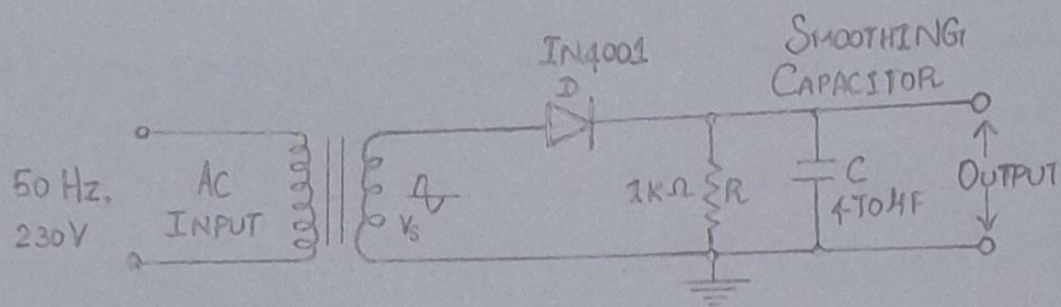



## MODEL GRAPH:

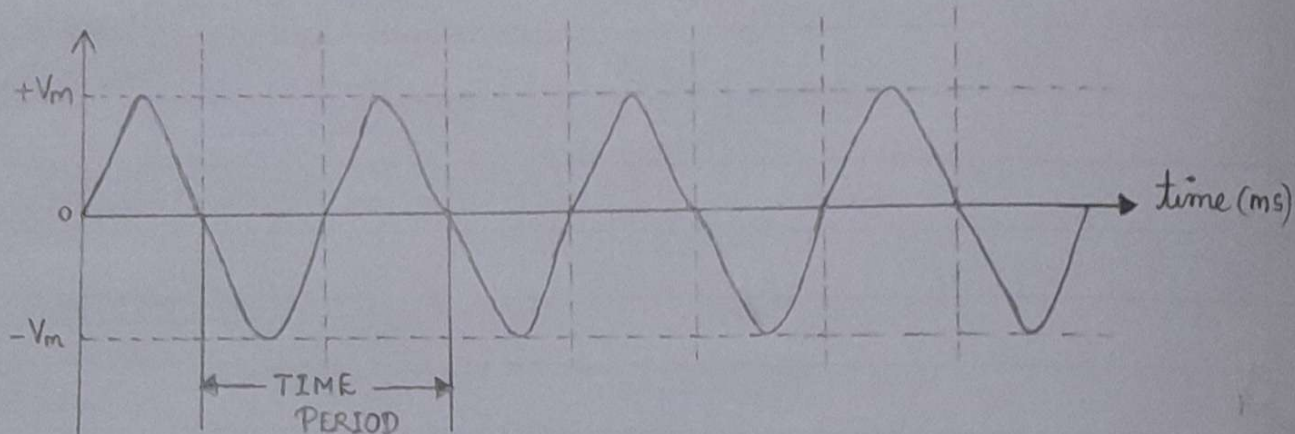

INPUT SIGNAL

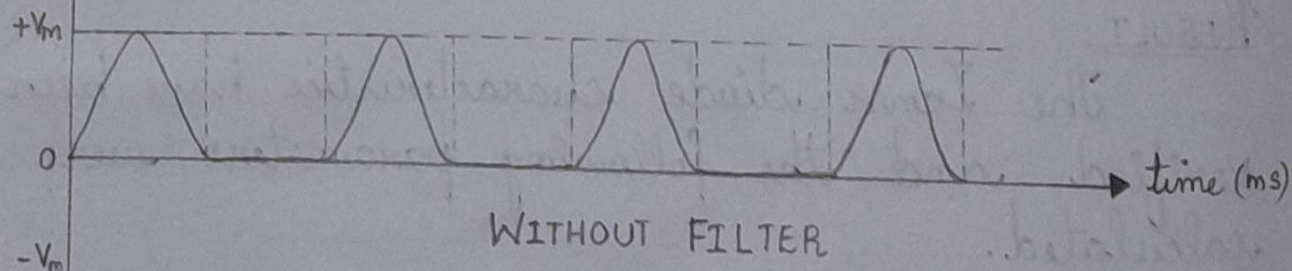

WITHOUT FILTER

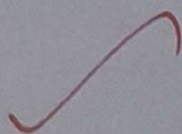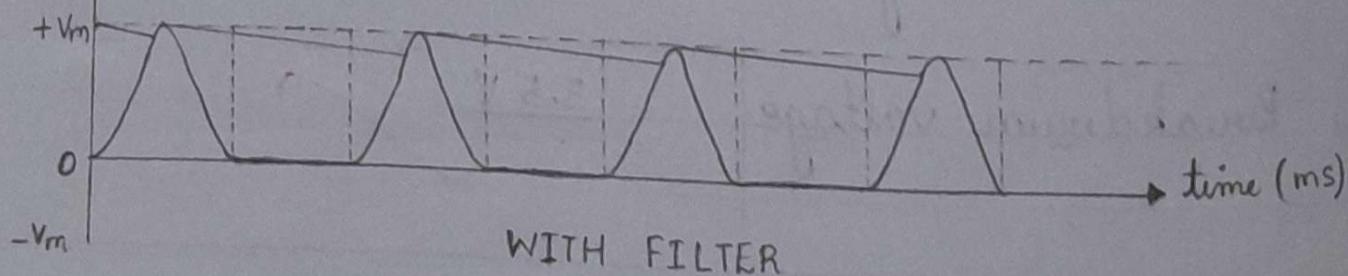



Exp. No: 04

Date: 18-08-23

## DIODE RECTIFIER CIRCUITS - FULL WAVE RECTIFIER

Aim:

To design and construct diode rectifier circuit and analyze the following parameters.


- To plot output waveform of the FWR
- To find ripple factor using formulae
- To find the efficiency.

APPARATUS REQUIRED:




S.No	APPARATUS	TYPE	RANGE	QUANTITY
1.	Step down transformer		(6-0-6), 500 mA, 1A rating.	1
2.	Resistance		470 ohm, 10% tolerance, 1/2 watt rating	1
3.	Capacitor		470 $\mu$ F	1
4.	Diode	IN4001		2
5.	Bread Board			1
	Connecting wires			Few



## CIRCUIT DIAGRAM:

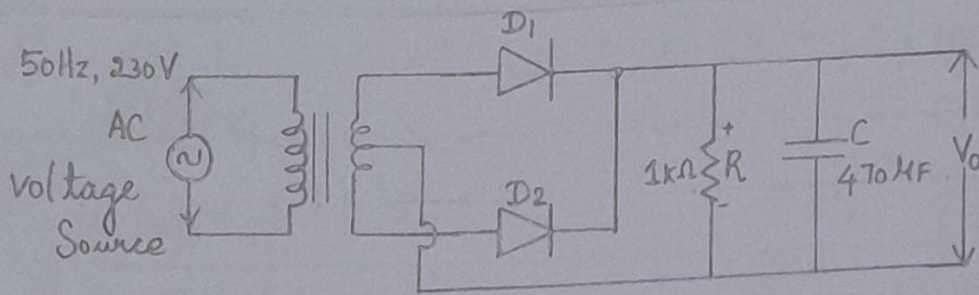

## MODEL GRAPH:

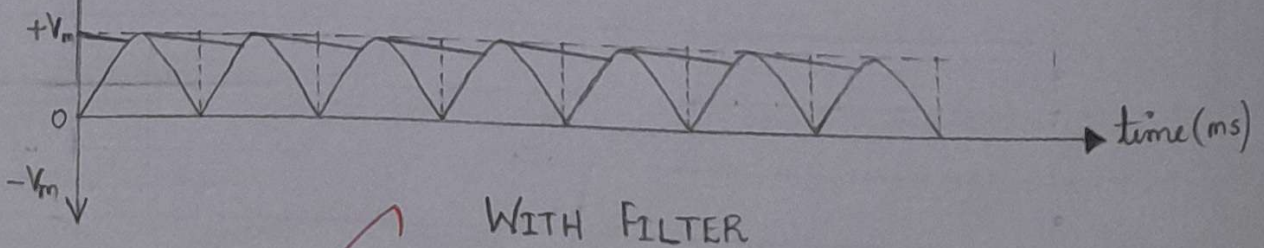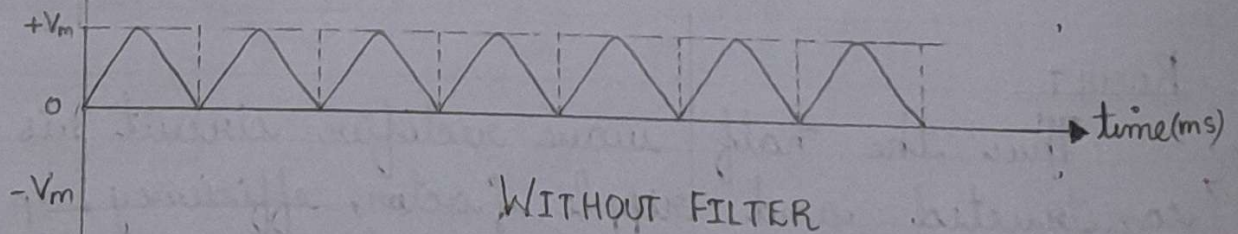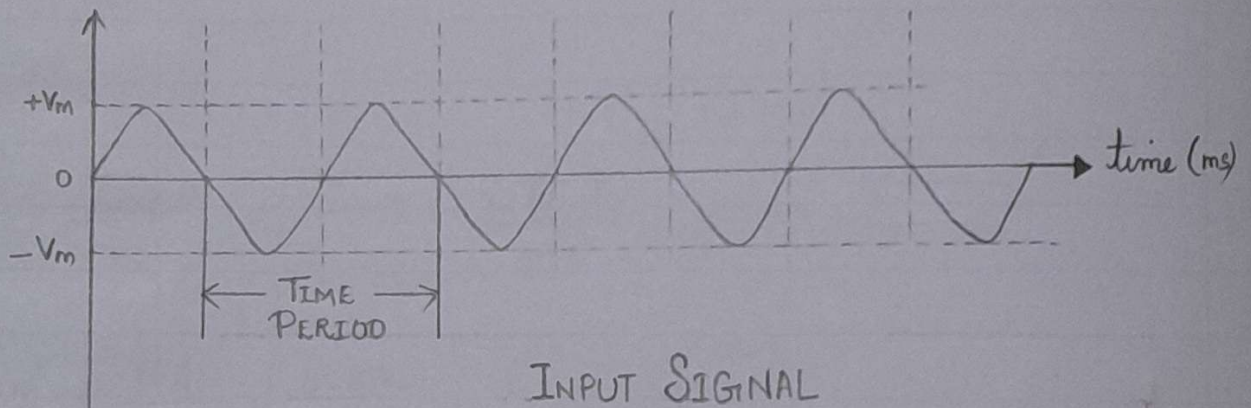



Exp. No: 05

Date: 28-08-23

## DIODE CLIPPER & CLAMPER

### AIM:


To Construct and test the clipper and clamper circuits.

### APPARATUS REQUIRED:


S.No	COMPONENTS	SPECIFICATION	QUANTITY
1.	CRO	(0-20M) Hz	1
2.	Function generator		1
3.	Resistor	10K- $\Omega$	1
4.	Capacitor	0.1 $\mu$ F	1
5.	Diode	IN4007	1
6.	Bread board	-	1
7.	Connecting wires	-	-





## POSITIVE CLIPPER:

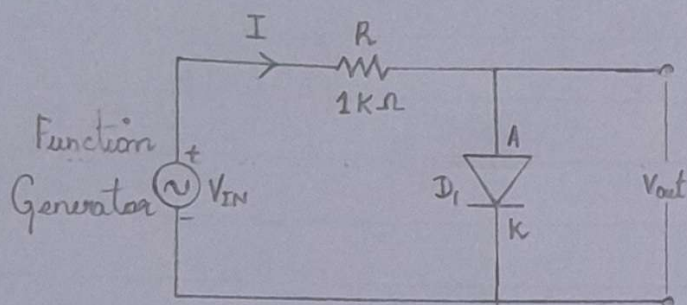

## NEGATIVE CLIPPER:

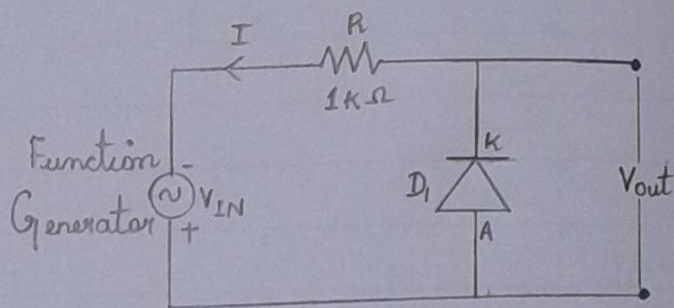

## MODEL GRAPH:

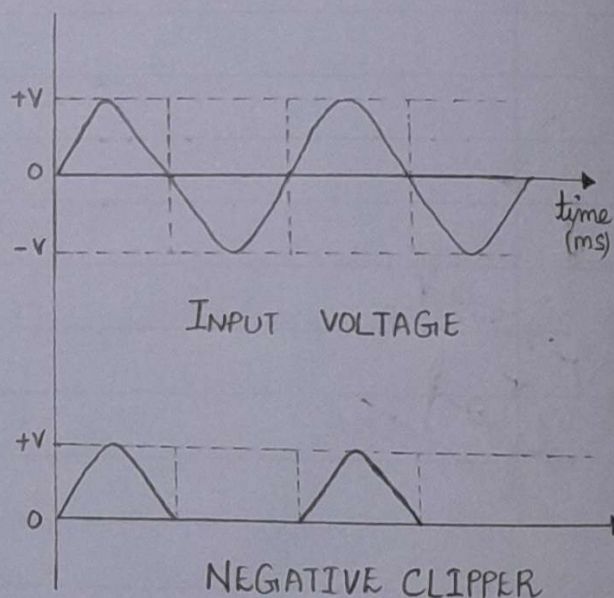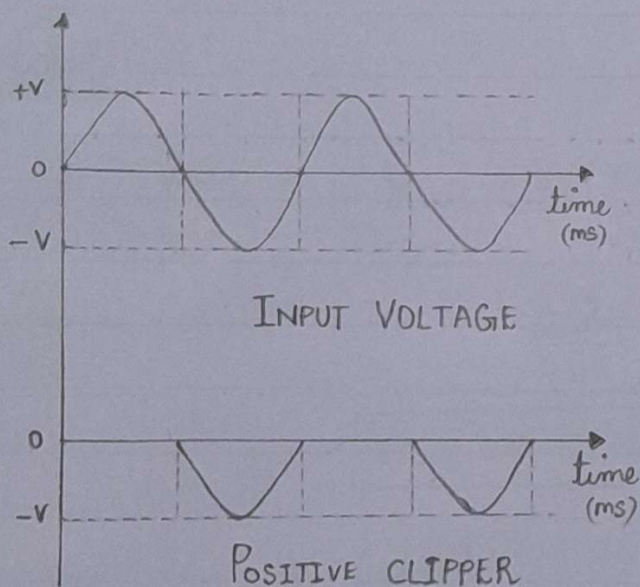


## OBSERVATION:


	INPUT VOLTAGE	OUTPUT VOLTAGE	INPUT FREQUENCY	OUTPUT FREQUENCY
POSITIVE CLIPPER	2.0 V	2.0 V	7.5 KHz	7.5 KHz
NEGATIVE CLIPPER	2.0 V	-2.0 V	7.5 KHz	7.5 KHz




## POSITIVE CLAMPER:

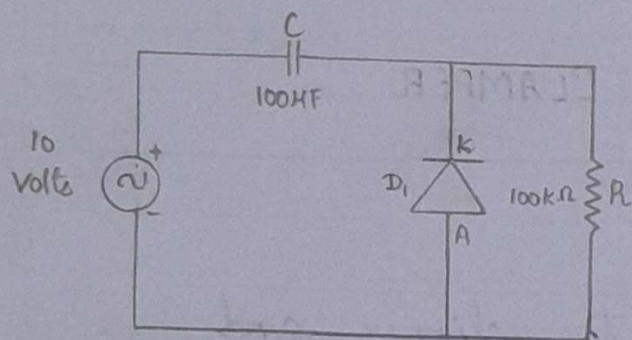

### MODEL GRAPH:


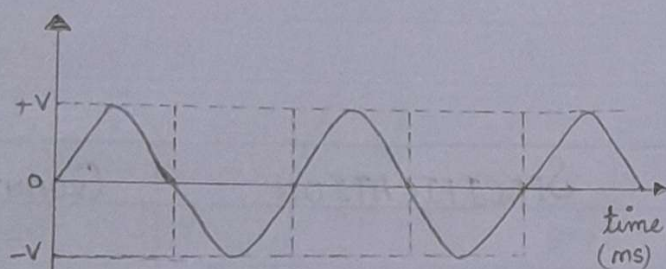


INPUT SIGNAL

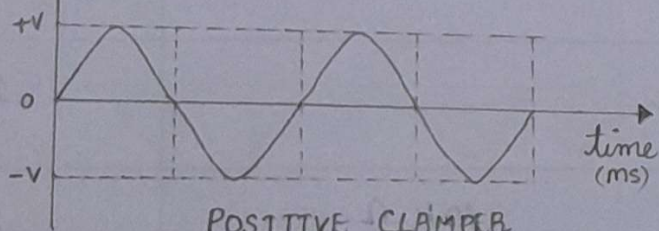


POSITIVE CLAMPER

## NEGATIVE CLAMPER:

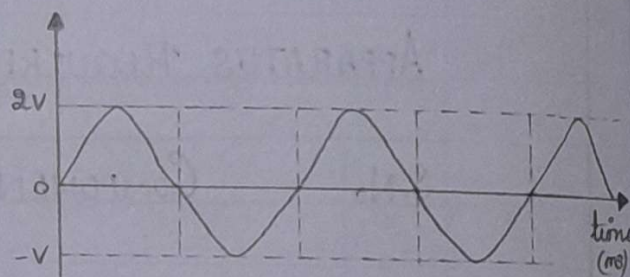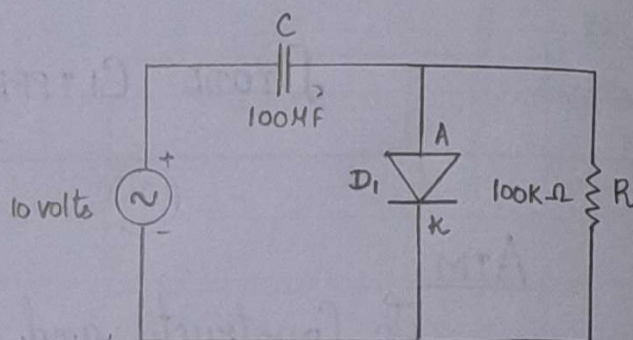

INPUT SIGNAL

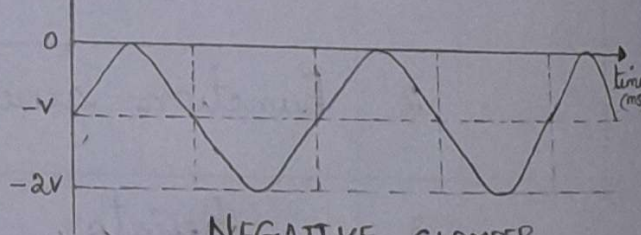

NEGATIVE CLAMPER

### OBSERVATION:

	INPUT VOLTAGE	OUTPUT VOLTAGE	INPUT FREQUENCY	OUTPUT FREQUENCY
POSITIVE CLAMPER	2.0V	2.0V	7.65 KHz	7.65 KHz
NEGATIVE CLAMPER	2.0V	-2.0V	7.65 KHz	7.65 KHz



Exp. No: 04  
Date: 04.07.23

## CHARACTERISTICS OF BJT

Aim:


To draw the input and output characteristics of transistor connected in common emitter (CE) configuration.

APPARATUS REQUIRED:

S.No	COMPONENT	SPECIFICATION	QUANTITY
1.	Transistor	BC 107	1
2.	Regulated Power Supply	(0-30)V	2
3.	Resistor	1K $\Omega$	1
4.	Ammeter	(0-500)mA, (0-30)mA	1
5.	Voltmeter	(0-20)V	2
6.	Bread board	-	1
7.	Connecting wires	-	-




## CIRCUIT DIAGRAM:

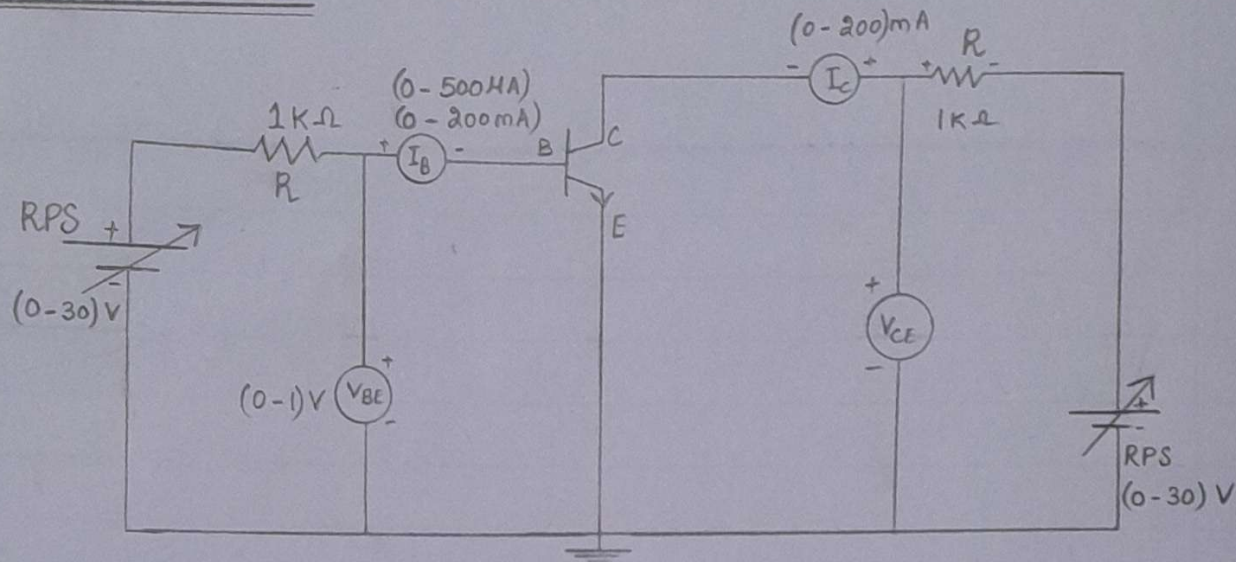


## MODEL GRAPH:
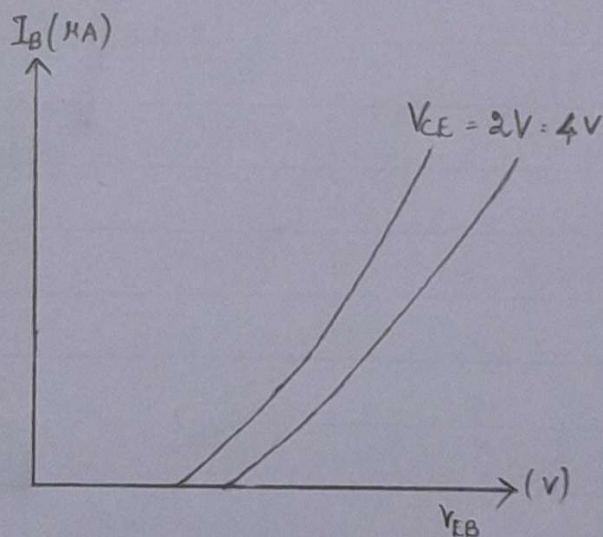
### INPUT CHARACTERISTICS OF COMMON EMITTER TRANSISTOR:


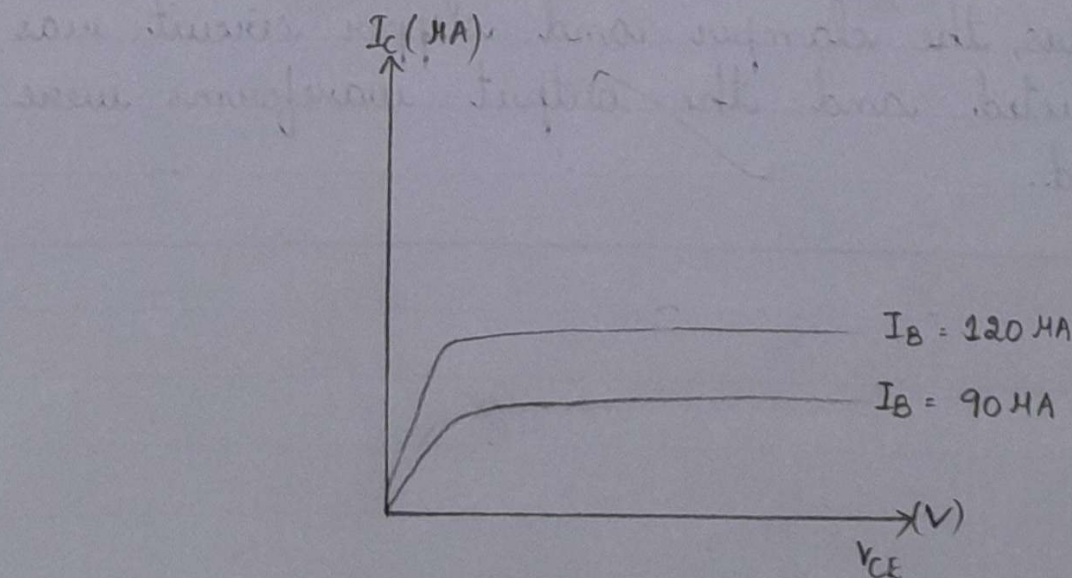
### OUTPUT CHARACTERISTICS OF COMMON EMITTER TRANSISTOR:





Exp. No: 07

Date: 22.09.23


## CHARACTERISTICS OF METAL OXIDE SEMICONDUCTOR FIELD EFFECT TRANSISTORS (MOSFETS)

Aim:

To obtain the drain characteristics and transfer characteristics of MOSFET.


APPARATUS REQUIRED:

S.No	APPARATUS	TYPE	RANGE	QUANTITY
1.	MOSFET	IRF150	-	1
2.	Resistor	-	500 $\Omega$ , 1K $\Omega$	1 each
3.	DC Power Source	-	5V	1 each
4.	Connecting wires	-	-	-

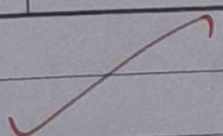




## CIRCUIT DIAGRAM :

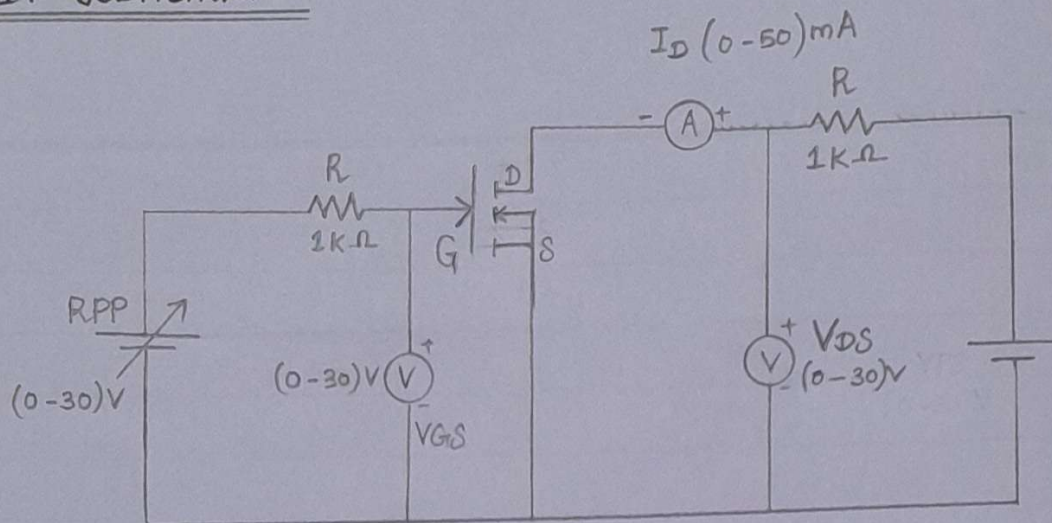

## MODEL GRAPH :

## TRANSFER CHARACTERISTICS :

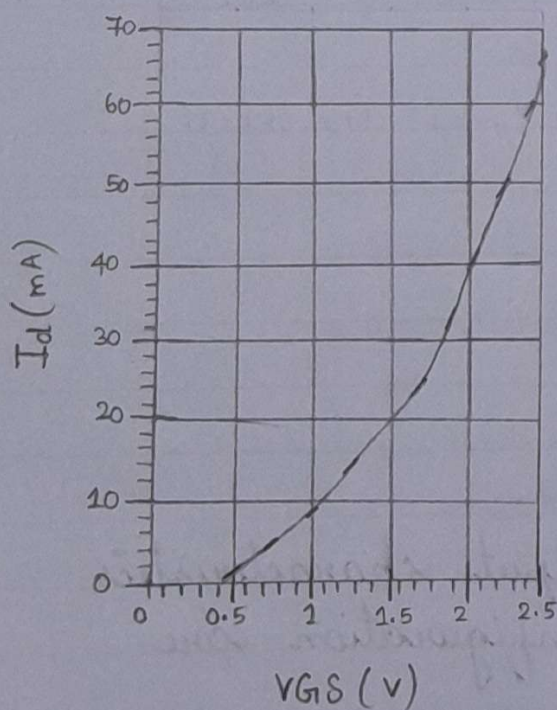

## DRAIN CHARACTERISTICS :

