

①

COURSE CODE & TITLE : 21ECC 2025ANALOG & LINEAR ELECTRONICS.PART-A.

- 1) a) Limits the low frequency response
- 2) b) $I_E = 1.025$ $\beta = 40$
- 3) b) Decreases
- 4) b) Reducing channel length
- 5) a) bka

PART-B6. CHARACTERISTICS OF CE, CB, CC amplifiers.


	Input impedance	Output impedance	Gain
CE	Low	High	$A_i, A_v = \text{high}$
CB	Very low	Very high	$A_i < 1$ A_v less than CE
CC	Very high	Low	A_i is High $A_v < 1$

(4 marks)

7. The half-power or 3-dB bandwidth is the width of the range of positive frequencies where a peak value at


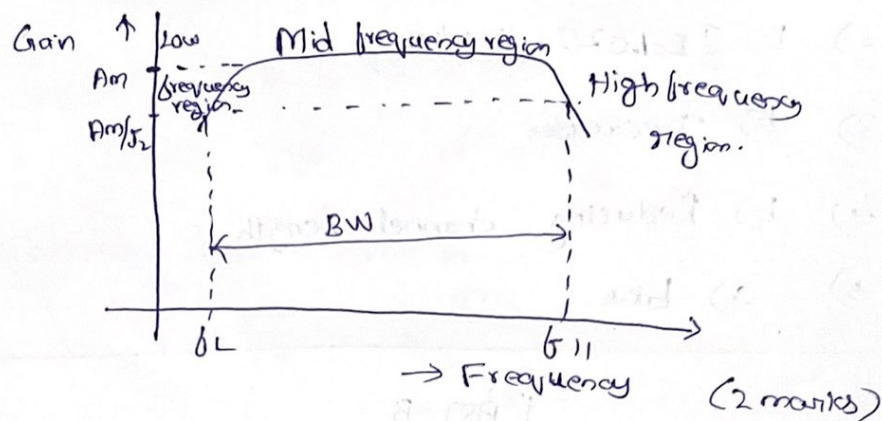
(2)

Zero or infinite frequency (low-pass and high pass signals) or at a center frequency (bandpass signals) is attenuated to 0.707 the value at a peak (2 marks)



8. SMALL SIGNAL EQUIVALENT OF



Common SOURCE WITH NMOS

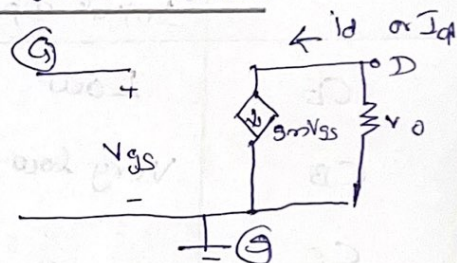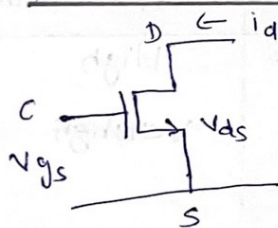

$$r_o = [\lambda I_D \phi]^{-1}$$

(2 marks)

Common SOURCE WITH PMOS TRANSISTOR

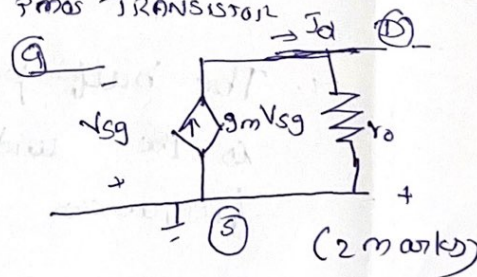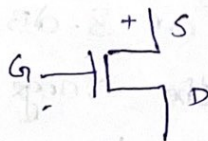

(2 marks)

(3)

PART-C


Q9. Derive expressions for the input resistance R_{in} , output resistance R_{out} , Voltage gain A_v and current gain A_i .

Given $R_E = 10k\Omega$, $R_C = 50k\Omega$,


$R_L = 10k\Omega$, $r_s = 200\Omega$, $V_{CC} = 12V$

$V_{BE} = 0.7V$, $\beta = 100$

Common Base Amplifier.

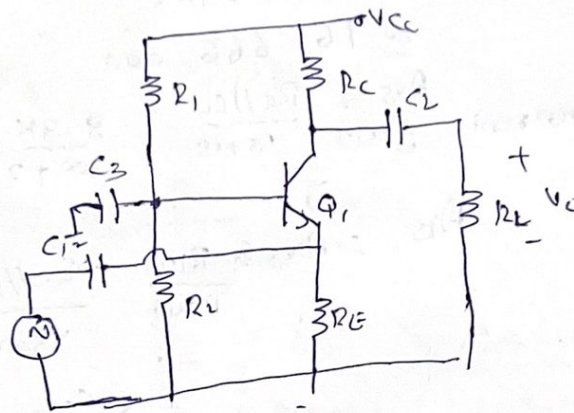

AC equivalent Ckt.

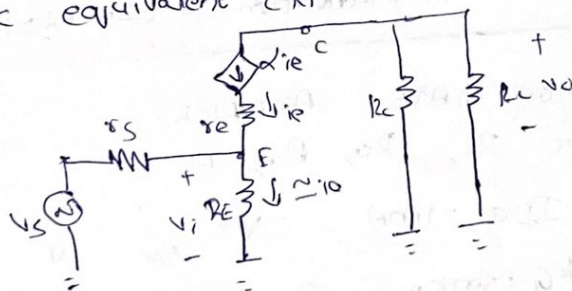

(2 marks)

Explanation (2 marks)

Input Resistance

$$R_{in} = R_E \parallel r_e$$

$$r_e \approx \frac{1}{g_m} = \frac{V_T}{I_C}$$

$$I_C = 1mA$$

$$R_{in} = 25\Omega \approx r_e$$

(2 marks)

(4)

Output resistance $R_o = R_c \parallel r_c$

$$R_o = 8.3k\Omega \quad (2 \text{ marks})$$

Voltage Gain $A_{vo} = \frac{v_o}{v_i} \bigg|_{R_L=\infty} = \frac{\alpha i_e r_c}{i_e (r_e \parallel r_c)} \approx \frac{r_c}{r_e \parallel r_c}$

$$\approx \frac{r_c}{r_e} = g_m r_c$$

$$= (0.04) (50,000)$$

$$A_{vo} = 2000$$

$$A_v = A_{vo} \times \frac{R_c}{R_c + R_L} = 2000 (8.3k\Omega)$$

$$\approx 16,666,000$$

(2 marks)

Current gain $A_{vs} = \frac{R_c \parallel R_L}{r_{s+re}} = \frac{8.3k}{200 + 25} = 37$

$$A_{is} = A_{vs} \times \frac{R_{in}}{R_{out}} = \frac{R_c \parallel R_L}{r_{s+re}} \times \frac{r_e}{R_c \parallel r_c} \approx 1$$

(2 marks)

Explanation - (2 marks)

95) Common GATE AMPLIFIER.

Derive R_i , R_o , A_v , A_i Give $I_{DQ} = 1mA$

$$V^+ = 5V$$

$$V^- = -5V$$

$$R_G = 500k\Omega$$

$$R_D = 4k\Omega$$

$$R_L = 10k\Omega$$

$$V_{TN} = 1V$$

$$K_n = 1mA/V^2$$



$$\lambda = 0$$

$$R_S = 4k\Omega$$

$$R_{S1} = 50k$$

(5)

COMMON GATE AMPLIFIER

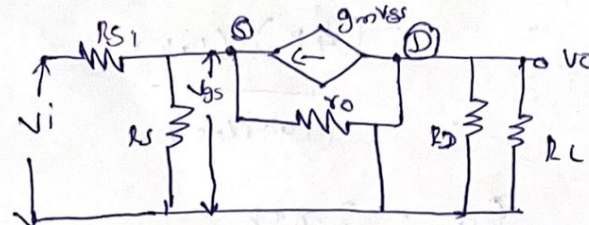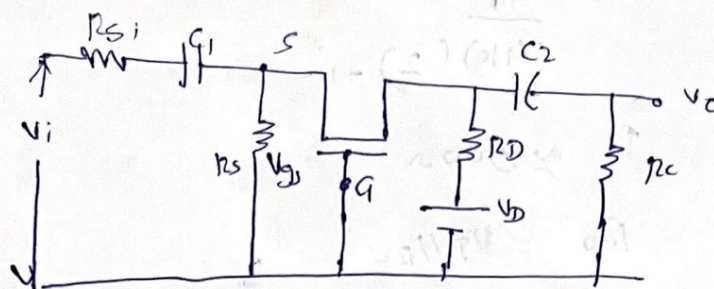

(2 marks)

$$R_i : R_s \parallel \frac{1}{g_m}$$

$$R_o : R_D \parallel R_L$$

$$A_v = \frac{g_m}{1 + g_m R_{s1}} (R_D \parallel R_L)$$

$$A_i = \frac{I_o}{I_i} = \left(\frac{R_D}{R_D + R_L} \right) \left(\frac{g_m R_{s1}}{1 + g_m R_{s1}} \right) \quad (6 \text{ marks})$$

$$I_Q = I_{DQ} = K_n (V_{GSQ} - V_{TN})^2$$

$$1 = 1 (V_{GSQ} - 1)^2$$

$$V_{GSQ} = 2V$$

$$g_m = 2K_n (V_{GSQ} - V_{TN})$$

$$= 2(1)(2-1) = 2 \text{ mA/V}$$

$$R_i : R_s \parallel \frac{1}{g_m} = \frac{R_s/g_m}{R_s + 1/g_m} = \frac{R_s}{g_m R_s + 1}$$

(6)

$$R_i = \frac{4k}{(4k)(2) + 1}$$

$$R_i \approx 500 \Omega$$

$$R_o = R_D // R_L$$

$$= \frac{(4k)(10k)}{(10k + 4k)}$$

$$R_o = 2.85k$$

$$A_v = \left(\frac{g_m}{1 + g_m R_s} \right) R_D // R_L$$

$$= \left(\frac{2}{1 + 2(50k)} \right) [2.85k]$$

$$= \left(\frac{2}{1 + 2(50)} \right) [2.85k]$$

$$A_v = \cancel{632.33} 56.43 \quad (4 \text{ marks})$$