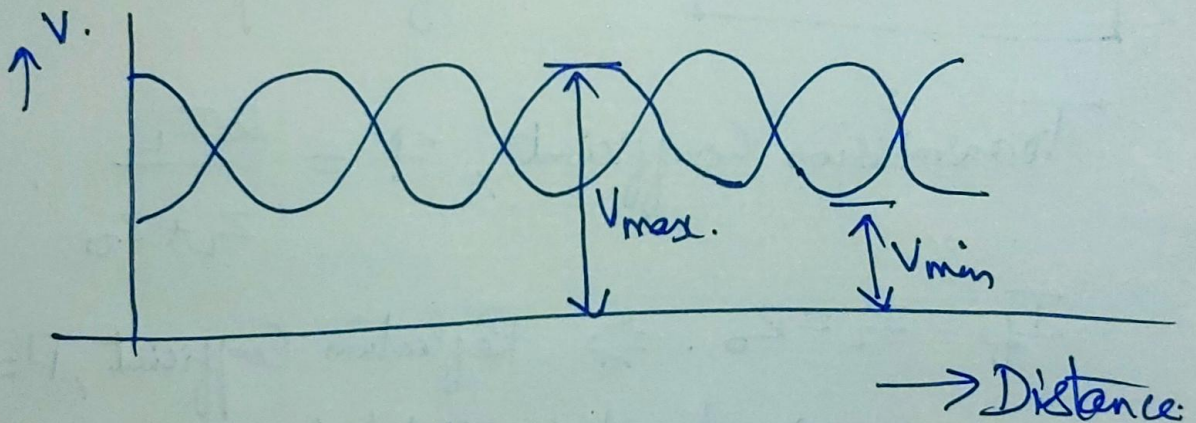



Lossless line Terminated in a short Circuit.

Standing Wave Ratio (SWR):-



$$\underline{VSWR} \Rightarrow \frac{V_{max}}{V_{min}} = \frac{1+|\Gamma|}{1-|\Gamma|} \quad (3)$$

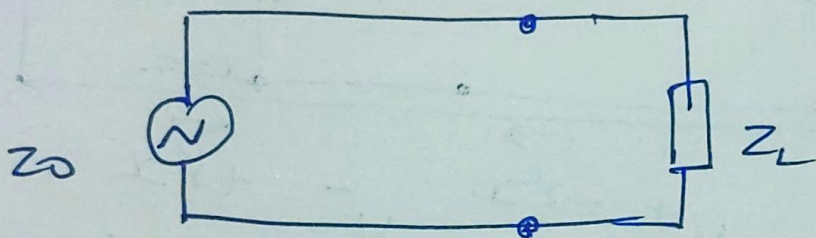$\Gamma \rightarrow$ Reflection Coefficient.



V_{max} :-


$$Z_{min} = \frac{-j}{2\beta} (\phi + (2m+1)\pi)$$

$m=0, 1, 2, 3, \dots$

V_{min} :-


$$Z_{max} = \frac{j}{2\beta} (\phi + 2m\pi)$$

$m=0, 1, 2, 3, \dots$

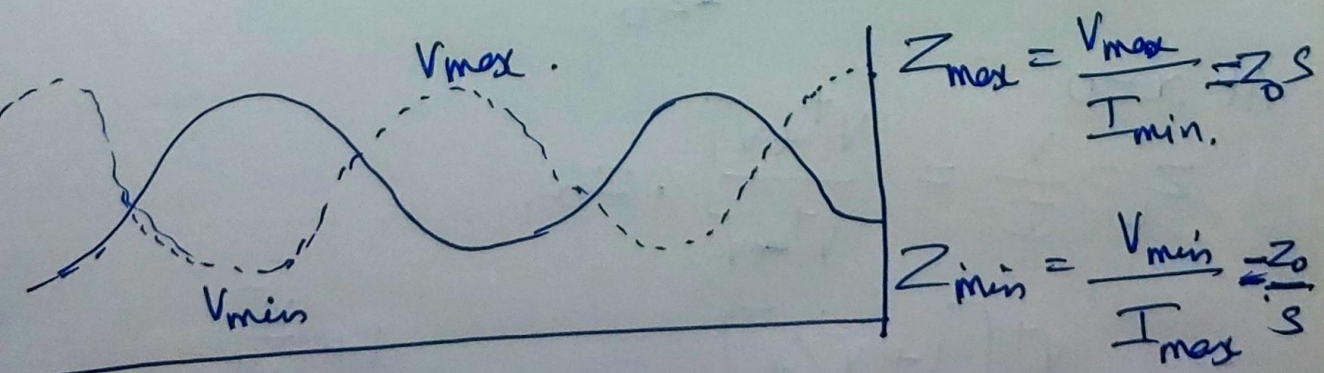

Reflection Co-efficient

①

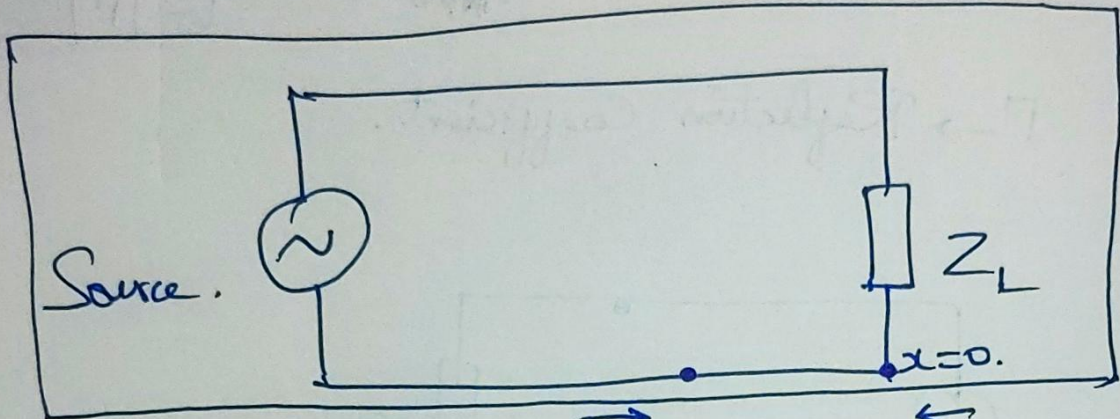

$$V(x,t) = V^+ e^{-\gamma x} + V^- e^{+\gamma x}$$

$$I(x,t) = I^+ e^{-\gamma x} + I^- e^{+\gamma x}$$


$$Z_0 = \frac{V^+}{I^+} \quad -Z_0 = \frac{V^-}{I^-}$$

$$I(x,t) = \frac{V^+}{Z_0} e^{-\gamma x} + \frac{V^-}{-Z_0} e^{+\gamma x}$$

At $x=0$

$$Z_L = \frac{V}{I} = \frac{V^+ + V^-}{V^+ - V^-} \cdot Z_0$$
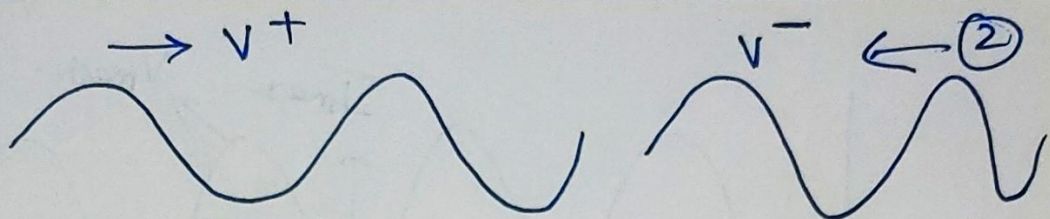
$$Z_L = \frac{V^+ \left[1 + \frac{V^-}{V^+} \right]}{V^+ \left[1 - \frac{V^-}{V^+} \right]} \cdot Z_0 \Rightarrow \frac{1 + \frac{V^-}{V^+}}{1 - \frac{V^-}{V^+}} \cdot Z_0$$



\Rightarrow Reflection Coefficient, $\Gamma \Rightarrow \frac{V^-}{V^+}$.

$$Z_L = \frac{1 + \Gamma}{1 - \Gamma} \cdot Z_0.$$

$$\boxed{\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}} \Rightarrow \text{Reflection Coefficient in terms of Impedance.}$$

Transmission Coefficient, $\tau = \frac{2Z_L}{Z_L + Z_0}$.

If $Z_L = Z_0 \Rightarrow$ Reflection Coefficient, $\Gamma = 0$.


\Rightarrow Load is Matched.

\Rightarrow Max^m power is Transferred to the load.

STUB MATCHING.

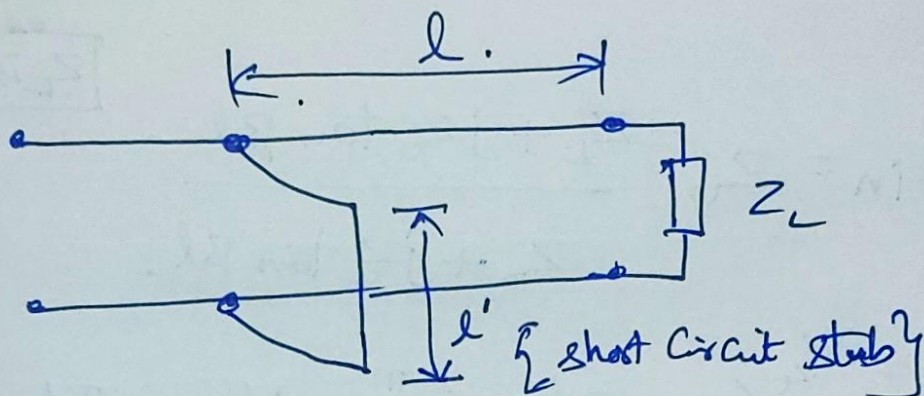(4)

To reduce Reflection, Impedance matching should be done.



The characteristic Impedance, Z_0 should be matched with the load to ensure maximum power transfer & also to withstand less to standing waves.


The reflected waves (reflected power) can damage the source.

High VSWR occurs due to Impedance mismatch between source & load.

(5)

Quarter wave Transformer.

$$l = \lambda/4.$$

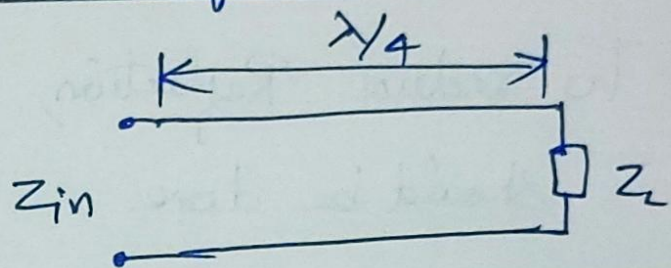

Z_L is Resistive

$$Z_{in} = Z_0 \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l}.$$


$$l = \lambda/4;$$

$$\beta l = \frac{2\pi}{\lambda} \cdot \lambda/4 = \pi/2.$$

$$\tan \beta l = \tan \frac{\pi}{2} = \infty$$

$$\Rightarrow Z_{in} = \frac{Z_0 \cdot \tan \beta l \left[\frac{Z_L}{\tan \beta l} + jZ_0 \right]}{\tan \beta l \left[\frac{Z_0}{\tan \beta l} + jZ_L \right]}$$
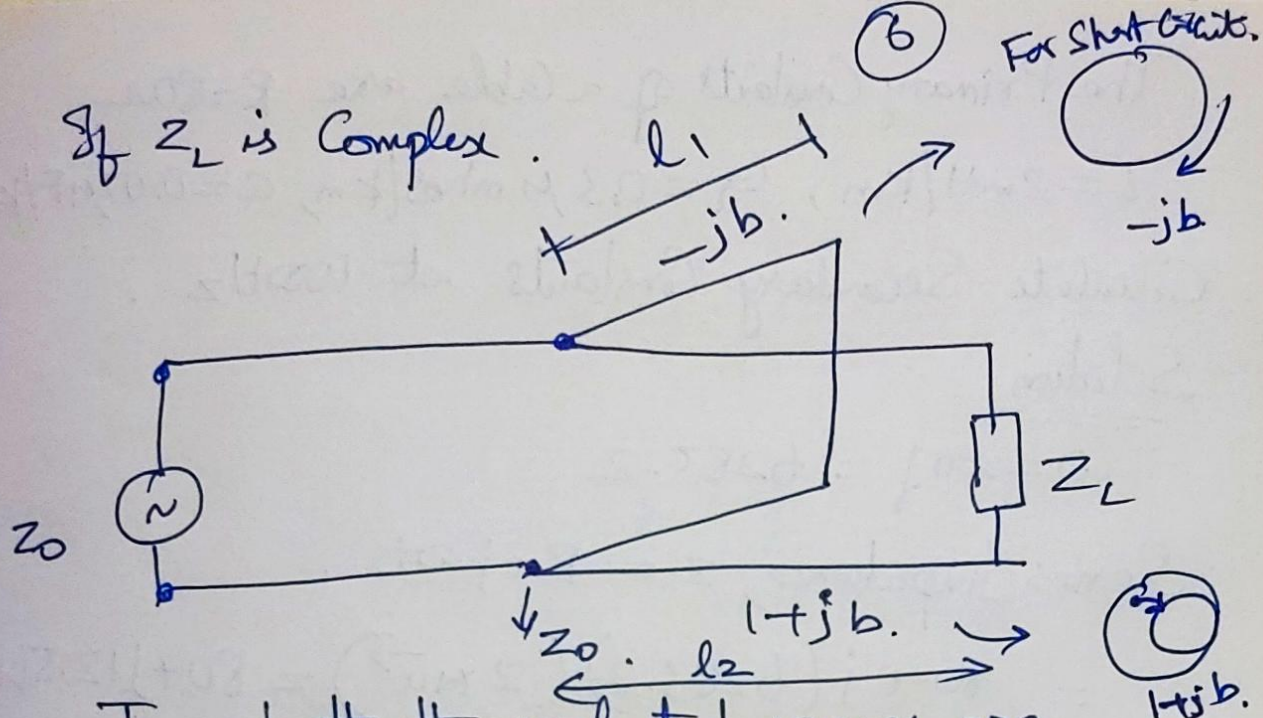
$$Z_{in} = Z_0 \left[\frac{jZ_0}{jZ_L} \right] \Rightarrow \boxed{Z_{in} = \frac{Z_0^2}{Z_L}}$$



If both the reflected waves are out of phase and of equal in amplitude,
 \Rightarrow both the reflected waves get Cancelled.

\Rightarrow Reflection is Zero

\Rightarrow Impedance is Matched.

$$Y = \frac{1}{Z_L} \Rightarrow g + jb.$$

$l \rightarrow$ length (distance) between stub & Load.

$$Y = 1 + jb \text{ at the stub. (Resistance part becomes 1)}$$

$$\Rightarrow Y_{eq} = 1 + jb - jb = 1.$$

T. Line Problem:-

The Primary Constants of a Cable are $R=80\Omega$

$$L=2\text{mH/Km}, G=0.3\text{ }\mu\text{mhos/Km}, C=0.07\text{ }\mu\text{F/Km},$$

Calculate Secondary Constants at 1000Hz .

Solution

$$\omega = 2\pi f = 6283.2$$

Series Impedance, $Z = R + j\omega L$.

$$\begin{aligned} &= 80 + j(6283.2)(2 \times 10^{-3}) = 80 + j12.566 \\ &= 80.98 \angle 8.927^\circ \end{aligned}$$

Shunt Admittance, $Y = G + j\omega C$.

$$= (0.3 \times 10^{-6}) + j(6283.2)(0.07 \times 10^{-6})$$

$$= 0.3 \times 10^{-6} + j4.398 \times 10^{-4} \Rightarrow 4.398 \times 10^{-4} \angle 89.96^\circ$$

$$\text{Characteristic Impedance, } Z_0 = \sqrt{\frac{Z}{Y}} = 429 \angle -40.52^\circ$$

Propagation Constant, $\gamma = \sqrt{Z \cdot Y}$

$$\gamma = 0.1227 + j0.1434$$

$\alpha = 0.1227 \text{ nepers/Km}$
$\beta = 0.1434 \text{ radians/Km}$