

# Gate-Level Modeling or Structural Modeling

## Gate Level


- Four levels of abstraction are used to describe the hardware.
- Gate level is low level of abstraction
- The circuit is **described in terms of gates** (e.g., and, nand, ...)
- **Verilog** description in **gate level corresponds** to logic **circuit** diagram
- Verilog supports **basic logic gates as predefined primitives**
- These primitives are instantiated like modules except that they are predefined in Verilog and do not need a module definition
- There are **two classes** of basic gates: **and/or gates** and **buf/not gates**

# Gate-Level Modeling or Structural Modeling


## Gate Types – and/or gates



and

 

nand

 

or



nor



xor



xnor

# Gate-Level Modeling or Structural Modeling

## Gate Instantiation of And/Or gates

- And/or gates have **one scalar output** and **multiple scalar inputs**.
- The **first terminal** in the list of gate terminals is an **output** and the **other terminals are inputs**.
- The **output** of a gate is **evaluated** as soon as **one of the inputs changes**.
- instance name does not need to be specified for primitives

wire OUT, IN1, IN2;

// basic gate instantiations

and a1(OUT, IN1, IN2);

nand na1(OUT, IN1, IN2);

or or1(OUT, IN1, IN2);

nor nor1(OUT, IN1, IN2);

xor x1(OUT, IN1, IN2);

xnor nx1(OUT, IN1, IN2);

// More than two inputs; 3 input nand gate



nand na1\_3inp(OUT, IN1, IN2, IN3);

// gate instantiation without instance name

and (OUT, IN1, IN2); // legal gate instantiation

# Gate-Level Modeling or Structural Modeling

Gate Types – Buf/Not gates

  

# Gate-Level Modeling or Structural Modeling

## Gate Instantiation of Buf/Not gates

- And/or gates have **one scalar input** and **one or more scalar outputs**.
- The **last terminal** in the port list is connected to the **input**. **Other terminals** are connected to the **outputs**.
- The **output** of a gate is **evaluated** as soon as **one of the inputs changes**.
- instance name does not need to be specified for primitives

// basic gate instantiations.

buf b1(OUT1, IN);

not n1(OUT1, IN);

// More than two outputs

buf b1\_2out(OUT1, OUT2, IN);

// gate instantiation without instance name

not (OUT1, IN); // legal gate instantiation

buf	in	out	not	in	out
	0	0		0	1
	1	1		1	0
	x	x		x	x
	z	x		z	x

# Gate-Level Modeling or Structural Modeling

## Gate Instantiation of Bufif/notif gates

- Gates with an **additional control signal** on buf and not gates
- These gates propagate only if their control signal is stated
- They propagate z if their control signal is not stated

//Instantiation of bufif gates

bufif1 b1 (out, in, ctrl);

bufif0 b0 (out, in, ctrl);



//Instantiation of notif gates

notif1 n1 (out, in, ctrl);

notif0 n0 (out, in, ctrl);



		ctrl			
bufif1		0	1	x	z
in	0	z	0	L	L
	1	z	1	H	H
	x	z	x	x	x
	z	z	x	x	x

		ctrl			
bufif0		0	1	x	z
in	0	0	z	L	L
	1	1	z	H	H
	x	x	z	x	x
	z	x	z	x	x

  

		ctrl			
notif1		0	1	x	z
in	0	z	1	H	H
	1	z	0	L	L
	x	z	x	x	x
	z	z	x	x	x

		ctrl			
notif0		0	1	x	z
in	0	1	z	H	H
	1	0	z	L	L
	x	x	z	x	x
	z	x	z	x	x

  

# Gate-Level Modeling or Structural Modeling

## Array of primitive Gate Instantiation

```
wire [7:0] OUT, IN1, IN2;
```

```
// basic gate instantiations
```

```
nand n_gate[7:0](OUT, IN1, IN2);
```

```
// This is equivalent to the following 8 instantiations
```

```
nand n_gate0(OUT[0], IN1[0], IN2[0]);
```

```
nand n_gate1(OUT[1], IN1[1], IN2[1]);
```

```
nand n_gate2(OUT[2], IN1[2], IN2[2]);
```

```
nand n_gate3(OUT[3], IN1[3], IN2[3]);
```

```
nand n_gate4(OUT[4], IN1[4], IN2[4]);
```


```
nand n_gate5(OUT[5], IN1[5], IN2[5]);
```

```
nand n_gate6(OUT[6], IN1[6], IN2[6]);
```

```
nand n_gate7(OUT[7], IN1[7], IN2[7]);
```

# Gate-Level Modeling or Structural Modeling

## 4-to-1 Multiplexer

 


$s1$	$s0$	$out$
0	0	$I0$
0	1	$I1$
1	0	$I2$
1	1	$I3$



# Gate-Level Modeling or Structural Modeling

## 4-to-1 Multiplexer

 


# Gate-Level Modeling or Structural Modeling
 
## Verilog Description of Multiplexer

```

module mux4_to_1 (out, i0, i1, i2, i3, s1, s0);
// Port declarations from the I/O diagram
output out;
input i0, i1, i2, i3;
input s1, s0;
// Internal wire declarations
wire s1n, s0n;
wire y0, y1, y2, y3;
// Gate instantiations
// Create s1n and s0n signals.
not (s1n, s1);
not (s0n, s0);
// 3-input and gates instantiated
and (y0, i0, s1n, s0n);
and (y1, i1, s1n, s0);
and (y2, i2, s1, s0n);
and (y3, i3, s1, s0);
// 4-input or gate instantiated
or (out, y0, y1, y2, y3);
endmodule
  
```



# Gate-Level Modeling or Structural Modeling

## Verilog Description of Multiplexer Testbench

```
module stimulus;
reg IN0, IN1, IN2, IN3;
reg S1, S0;
wire OUTPUT;
mux4_to_1 mymux(OUTPUT, IN0, IN1, IN2, IN3, S1, S0);
initial
begin
IN0 = 1; IN1 = 0; IN2 = 1; IN3 = 0;
#1 $display("IN0= %b, IN1= %b, IN2= %b, IN3= %b\n",IN0,IN1,IN2,IN3);
S1 = 0; S0 = 0;
#1 $display("S1 = %b, S0 = %b, OUTPUT = %b \n", S1, S0, OUTPUT);
S1 = 0; S0 = 1;
#1 $display("S1 = %b, S0 = %b, OUTPUT = %b \n", S1, S0, OUTPUT);
S1 = 1; S0 = 0;
#1 $display("S1 = %b, S0 = %b, OUTPUT = %b \n", S1, S0, OUTPUT);
S1 = 1; S0 = 1;
#1 $display("S1 = %b, S0 = %b, OUTPUT = %b \n", S1, S0, OUTPUT);
end
endmodule
```

### Output

IN0= 1, IN1= 0, IN2= 1, IN3= 0

S1 = 0, S0 = 0, OUTPUT = 1


S1 = 0, S0 = 1, OUTPUT = 0

S1 = 1, S0 = 0, OUTPUT = 1


S1 = 1, S0 = 1, OUTPUT = 0
 
# Gate-Level Modeling - Gate delays

- In real circuits, logic gates have delays associated with them
- **Gate delays** allow the Verilog user to **specify delays through the logic circuits**
- If no delays are specified, the **default value is zero**.
- Three types of delays from the inputs to the output of a primitive gate
  - **Rise delay**



- **Fall delay**

 

- **Turn-off delay**
  - The turn-off delay is associated with a gate output transition to the high impedance value (z) from another value

# Gate-Level Modeling or Structural Modeling

## Types of Delay Specification Syntax

// Delay of delay\_time for all transitions

and #(delay\_time) a1(out, i1, i2);

// Rise and Fall Delay Specification.

and #(rise\_val, fall\_val) a2(out, i1, i2);

// Rise, Fall, and Turn-off Delay Specification

bufif0 #(rise\_val, fall\_val, turnoff\_val) b1 (out, in, control);

## Examples of delay specification

and #(5) a1(out, i1, i2); //Delay of 5 for all transitions

and #(4,6) a2(out, i1, i2); // Rise = 4, Fall = 6

bufif0 #(3,4,5) b1 (out, in, control); // Rise = 3, Fall = 4, Turn-off = 5

# Gate-Level Modeling or Structural Modeling

## Verilog Description of 4-bit Ripple Carry full adder Testbench


```
module stimulus; // Define the stimulus (top level module)
reg [3:0] A, B; // Set up variables
reg C_IN;
wire [3:0] SUM;
wire C_OUT;
fulladd4 FA1_4(SUM, C_OUT, A, B, C_IN); // Instantiate the 4-bit full adder. call it FA1_4
Initial // Set up the monitoring for the signal values
begin
$monitor($time," A= %b, B=%b, C_IN= %b, --- C_OUT= %b, SUM=%b\n",A, B, C_IN, C_OUT, SUM);
end
Initial // Stimulate inputs
begin
A = 4'd0; B = 4'd0; C_IN = 1'b0;
#5 A = 4'd3; B = 4'd4;
#5 A = 4'd2; B = 4'd5;
#5 A = 4'd9; B = 4'd9;
#5 A = 4'd10; B = 4'd15;
#5 A = 4'd10; B = 4'd5; C_IN = 1'b1;
end
endmodule
```

### Output:


```
0 A= 0000, B=0000, C_IN= 0, --- C_OUT= 0, SUM= 0000
5 A= 0011, B=0100, C_IN= 0, --- C_OUT= 0, SUM= 0111
10 A= 0010, B=0101, C_IN= 0, --- C_OUT= 0, SUM= 0111
15 A= 1001, B=1001, C_IN= 0, --- C_OUT= 1, SUM= 0010
20 A= 1010, B=1111, C_IN= 0, --- C_OUT= 1, SUM= 1001
25 A= 1010, B=0101, C_IN= 1,, C_OUT= 1, SUM= 0000
```

# Gate-Level Modeling or Structural Modeling
 
## Verilog Description of 4-bit Ripple Carry full adder design


 
```
// Define a 1-bit full adder
module fulladd(sum, c_out, a, b, c_in);
// I/O port declarations
output sum, c_out;
input a, b, c_in;
// Internal nets
wire s1, c1, c2;
// Instantiate logic gate primitives
xor (s1, a, b);
and (c1, a, b);
xor (sum, s1, c_in);
and (c2, s1, c_in);
xor (c_out, c2, c1);
endmodule
```



```
// Define a 4-bit full adder
module fulladd4(sum, c_out, a, b, c_in);
// I/O port declarations
output [3:0] sum;
output c_out;
input [3:0] a, b;
input c_in;
// Internal nets
wire c1, c2, c3;
// Instantiate four 1-bit full adders.
fulladd fa0(sum[0], c1, a[0], b[0], c_in);
fulladd fa1(sum[1], c2, a[1], b[1], c1);
fulladd fa2(sum[2], c3, a[2], b[2], c2);
fulladd fa3(sum[3], c_out, a[3], b[3], c3);
endmodule
```

# Gate-Level Modeling or Structural Modeling

## Types of Delay Specification Syntax

```
// Delay of delay_time for all transitions
and #(delay_time) a1(out, i1, i2);

// Rise and Fall Delay Specification.
and #(rise_val, fall_val) a2(out, i1, i2);

// Rise, Fall, and Turn-off Delay Specification
bufif0 #(rise_val, fall_val, turnoff_val) b1 (out, in, control);
```

## Examples of delay specification

```
// Define a simple combination module called D
module D (out, a, b, c);
// I/O port declarations
output out;
input a,b,c;
// Internal nets
wire e;
// Instantiate primitive gates to build the circuit
and #(5) a1(e, a, b); //Delay of 5 on gate a1
or #(4) o1(out, e,c); //Delay of 4 on gate o1
endmodule
```

// Stimulus (top-level module)

```
module stimulus;
reg A, B, C;
wire OUT;
// Instantiate the module D
D d1( OUT, A, B, C);
// Stimulate the inputs. Finish the simulation at 40 time units.
initial
begin
A= 1'b0; B= 1'b0; C= 1'b0;
#10 A= 1'b1; B= 1'b1; C= 1'b1;
#10 A= 1'b1; B= 1'b0; C= 1'b0;
#20 $finish;
end
endmodule
```

