

Lecture 5 – Op-Amp Frequency Response

Review:

- Simple RC Low-Pass Filter Response

Op-Amp Frequency Response:

- Open-Loop Frequency Response
- Gain Bandwidth Product (GBWP)
- Closed-Loop Frequency Response

Bode Plots:


- Single-Pole RC LPF Frequency Response
- LM741 Open vs. Closed Loop Comparison

Bandwidth vs. Risetime Relationship

- $t_R BW \cong 0.35$

1. Simple RC Low-Pass Filter

Circuit:

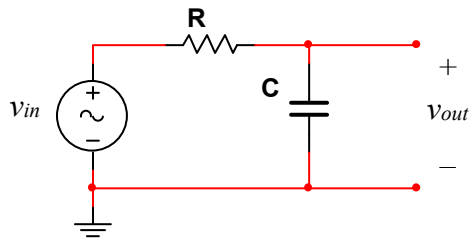

Transfer Function:

$$H(j\omega) = \frac{1}{1 + j\frac{\omega}{\omega_0}}$$

$$H(jf) = \frac{1}{1 + j\frac{f}{f_0}}$$

$$\omega = 2\pi f, \omega_0 = 2\pi f_0$$

$$f_0 = \frac{1}{2\pi RC}$$


Magnitude:

$$|H(jf)| = \frac{1}{\sqrt{1 + \left(\frac{f}{f_0}\right)^2}}$$

Phase:


$$\angle H(jf) = -\arctan\left(\frac{f}{f_0}\right)$$

Plot:

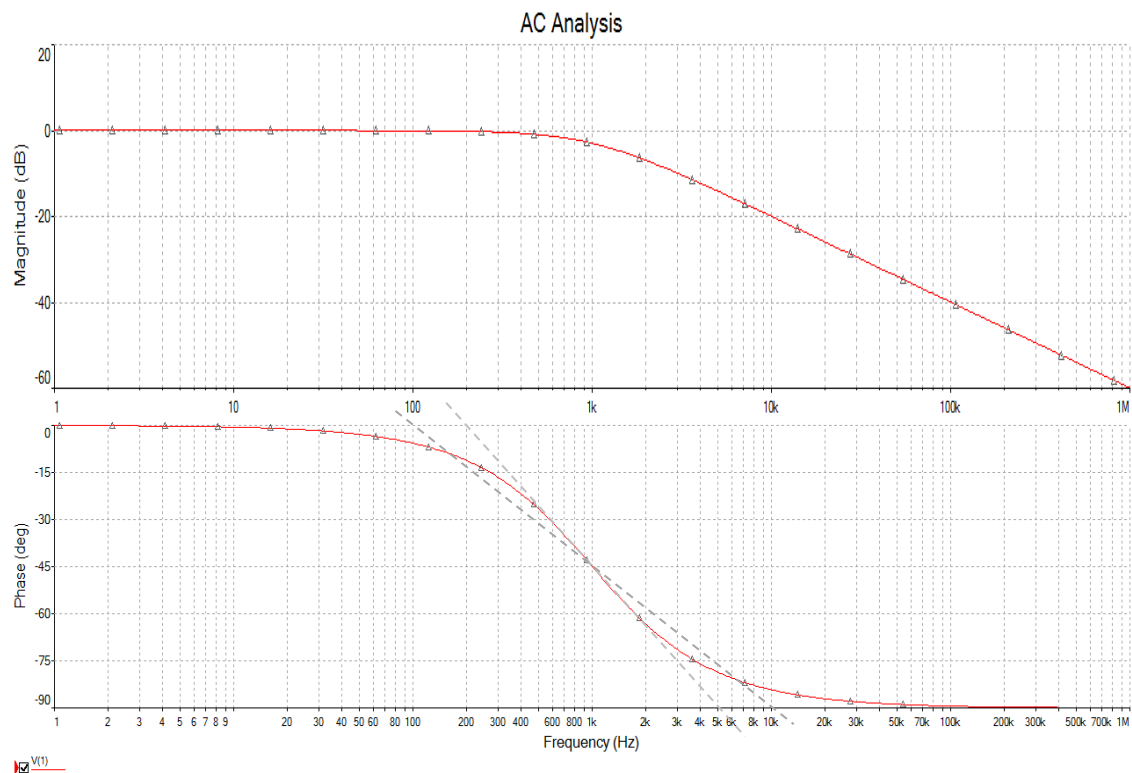

2. Op-Amp Open Loop Frequency Response

Circuit:

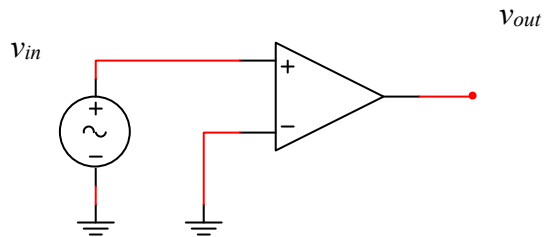

$$A(jf) = \frac{A_0}{1 + j \frac{f}{f_b}}$$

Where:


A_0 = Open-Loop DC Gain

f_b = Breakpoint Frequency

f_T = Unity Gain Frequency


Gain Bandwidth Product (GBWP)

$$GBWP = A_0 f_b = f_T \cdot 1$$

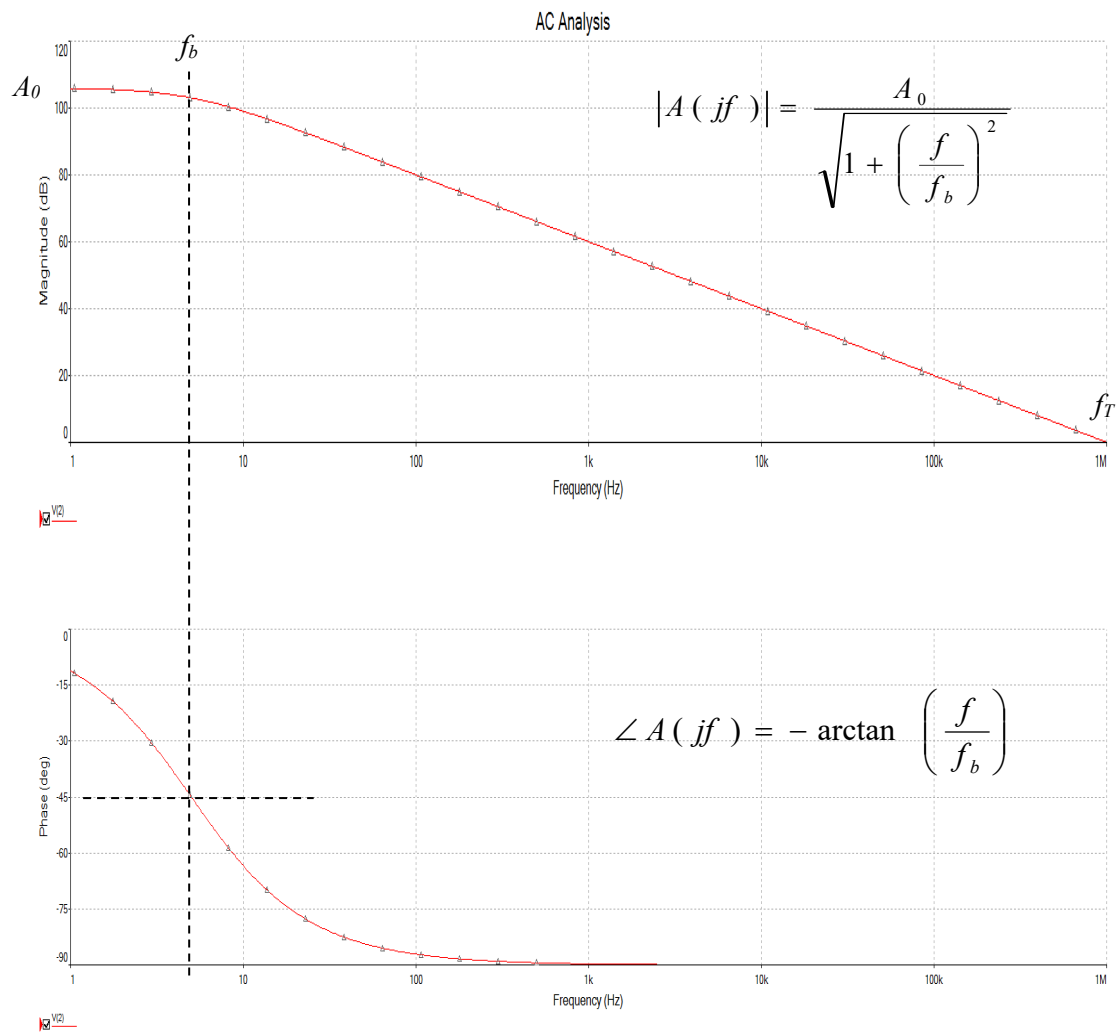

3. Op-Amp Closed-Loop Frequency Response

Background (from Control Theory):

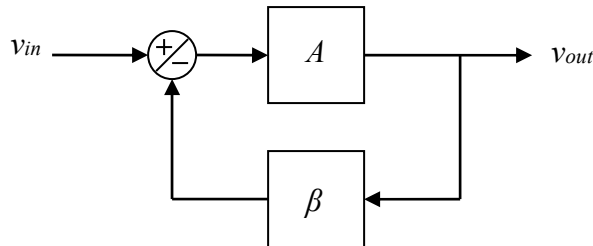


$$\frac{v_{out}}{v_{in}} \equiv A_{Closed-Loop} = \frac{A}{1 + A\beta}$$

Given that the open-loop gain A is a function of frequency and exhibits a *Low-Pass Filter Response*, it can be modeled as:

$$A = A(jf) = \frac{A_0}{1 + j \frac{f}{f_b}}$$

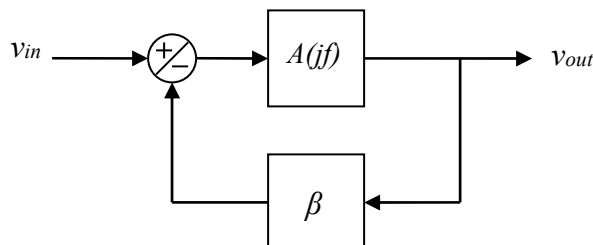where A_0 is the DC gain and f_b is the cutoff or breakpoint frequency of the open-loop response. Making this change in the control system yields:



$$A(jf)_{Closed-Loop} = \frac{A(jf)}{1 + A(jf)\beta}$$

Substituting the open-loop response into the closed-loop equation gives:

$$A(jf)_{Closed-Loop} = \frac{A(jf)}{1 + A(jf)\beta} = \frac{\left(\frac{A_0}{1 + j \frac{f}{f_b}} \right)}{1 + \left(\frac{A_0}{1 + j \frac{f}{f_b}} \right) \beta}$$

This equation can be rearranged into:

$$A(jf)_{Closed-Loop} = \frac{\left. \frac{1}{\beta} \right\} \text{Closed-Loop DC Gain}}{1 + \underbrace{\frac{1}{A_0\beta}}_{\text{Typically small enough to ignore.}} + j \frac{f}{A_0 f_b \beta} \left. \right\} \text{New cut-off frequency}}$$


$$f_c = A_0 f_b \beta = f_T \beta$$

Final Closed-Loop Frequency Response:

$$A(jf)_{Closed-Loop} \cong \frac{\frac{1}{\beta}}{1 + j \frac{f}{f_c}}$$

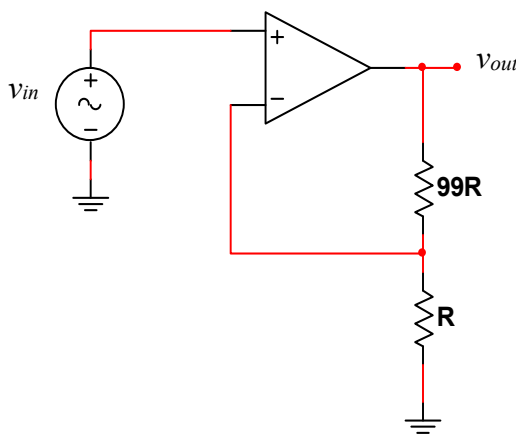Example:

Given the following op-amp circuit with $f_T = 1\text{MHz}$, plot the closed-loop frequency response, both magnitude and phase.




$$\beta = \frac{R}{R + 99R} = \frac{1}{100}$$

$$\therefore \frac{1}{\beta} = 100$$


$$f_c = f_T \beta = 1_{\text{MHz}} \left(\frac{1}{100} \right) = 10_{\text{kHz}}$$

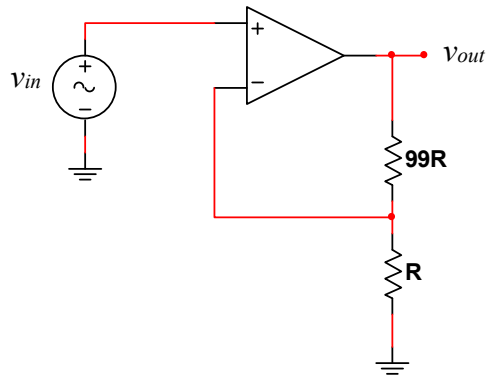4. Op-Amp Closed-Loop Frequency Response EXAMPLE:




$$A(jf)_{Closed-Loop} \cong \frac{\frac{1}{\beta}}{1 + j \frac{f}{f_c}}$$
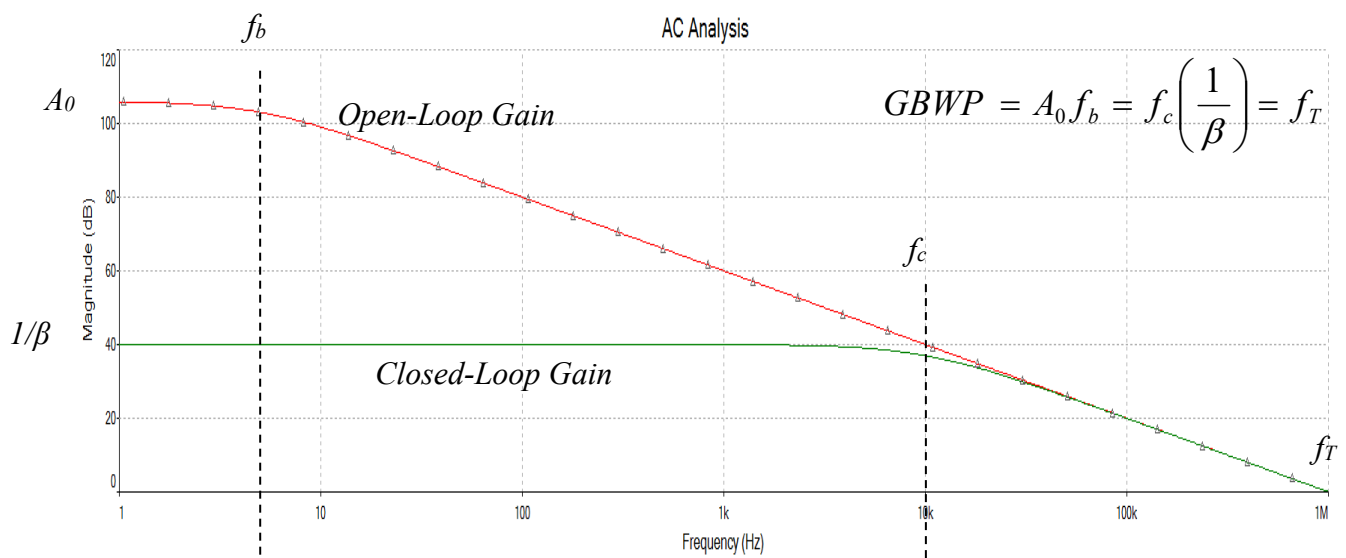
$$= \frac{100}{1 + j \frac{f}{10 \text{ kHz}}}$$



☒ V(2) ☒ V(R)

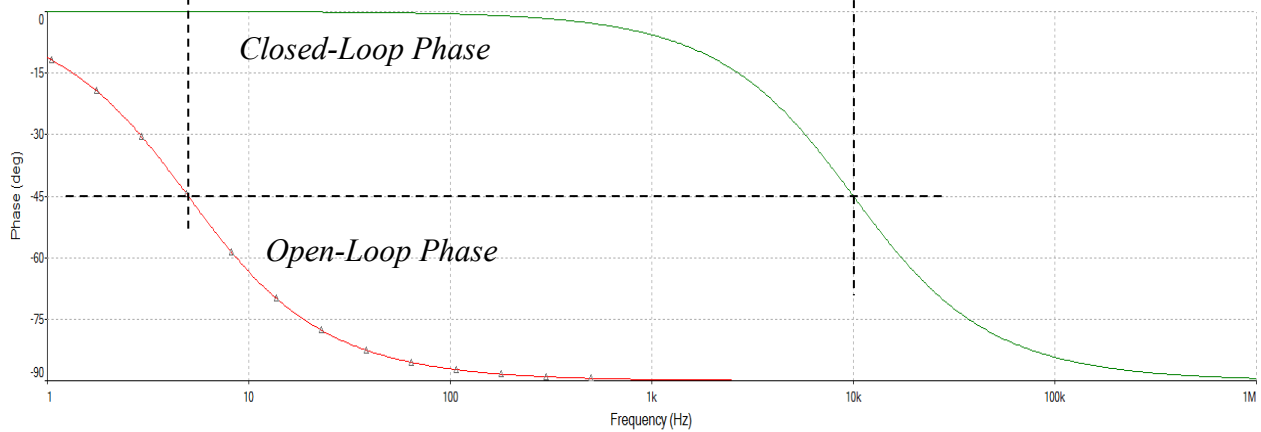

☒ V(2) ☒ V(R)