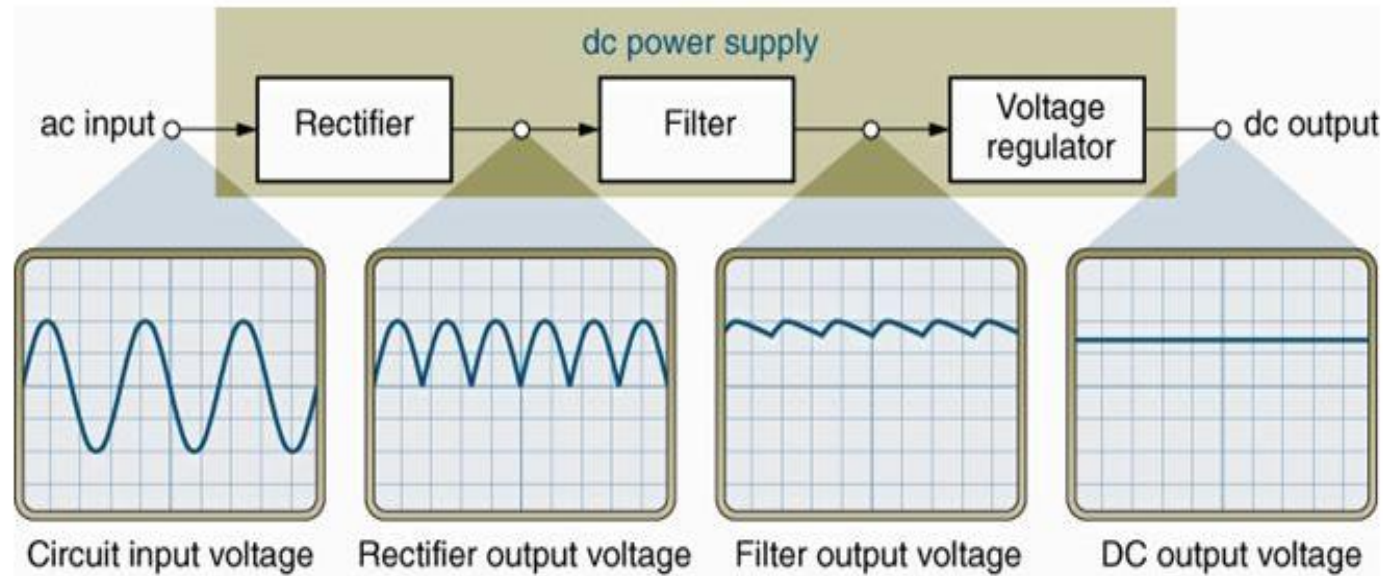



AC to DC Current

A group of circuits used to convert ac to dc.


- **Rectifier** – Converts ac to pulsating dc.
- **Filter** – Reduces variations in the rectifier output.
- **Voltage regulator** – Maintains a constant dc output voltage.



Types of Rectifier

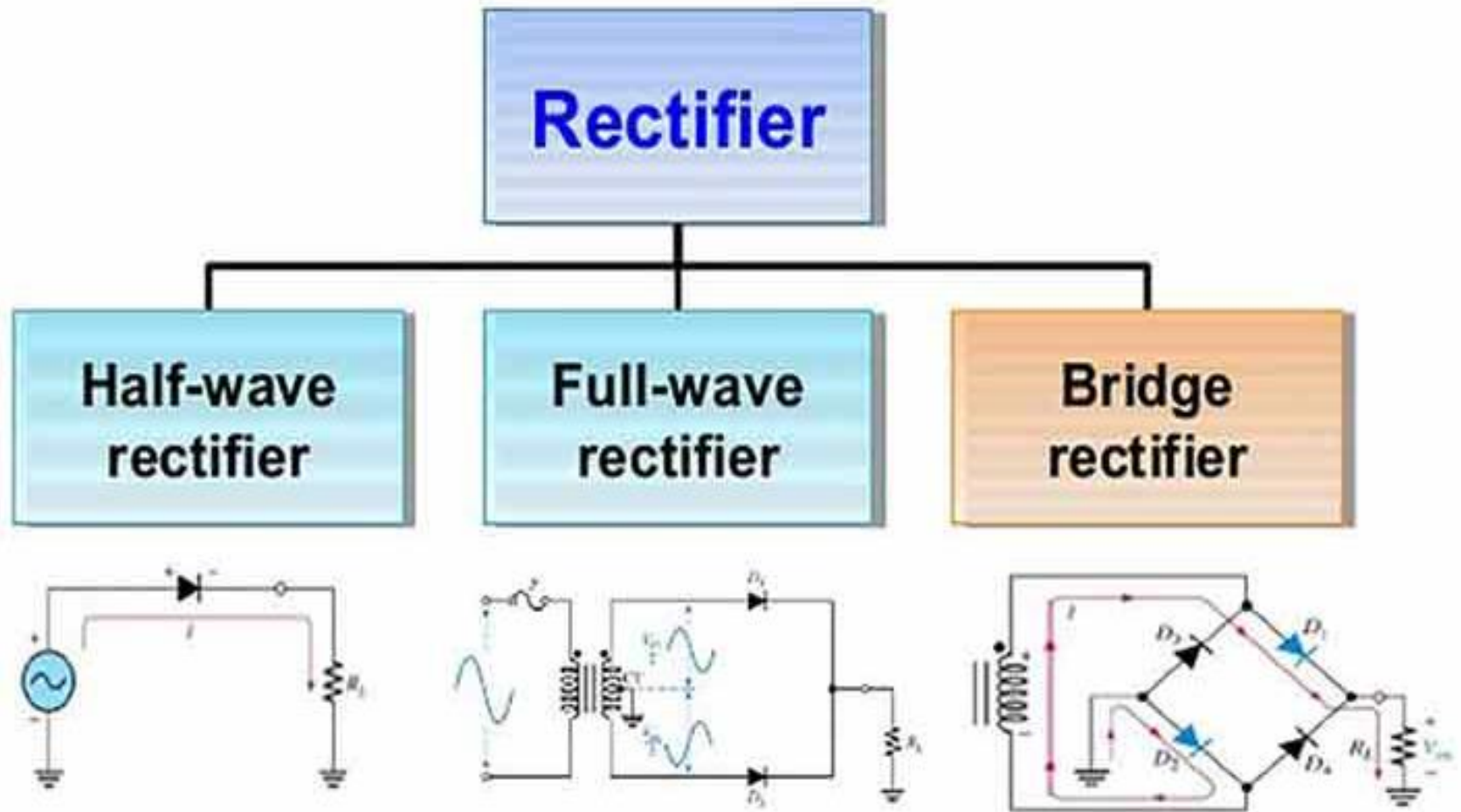


Half Wave Rectifier

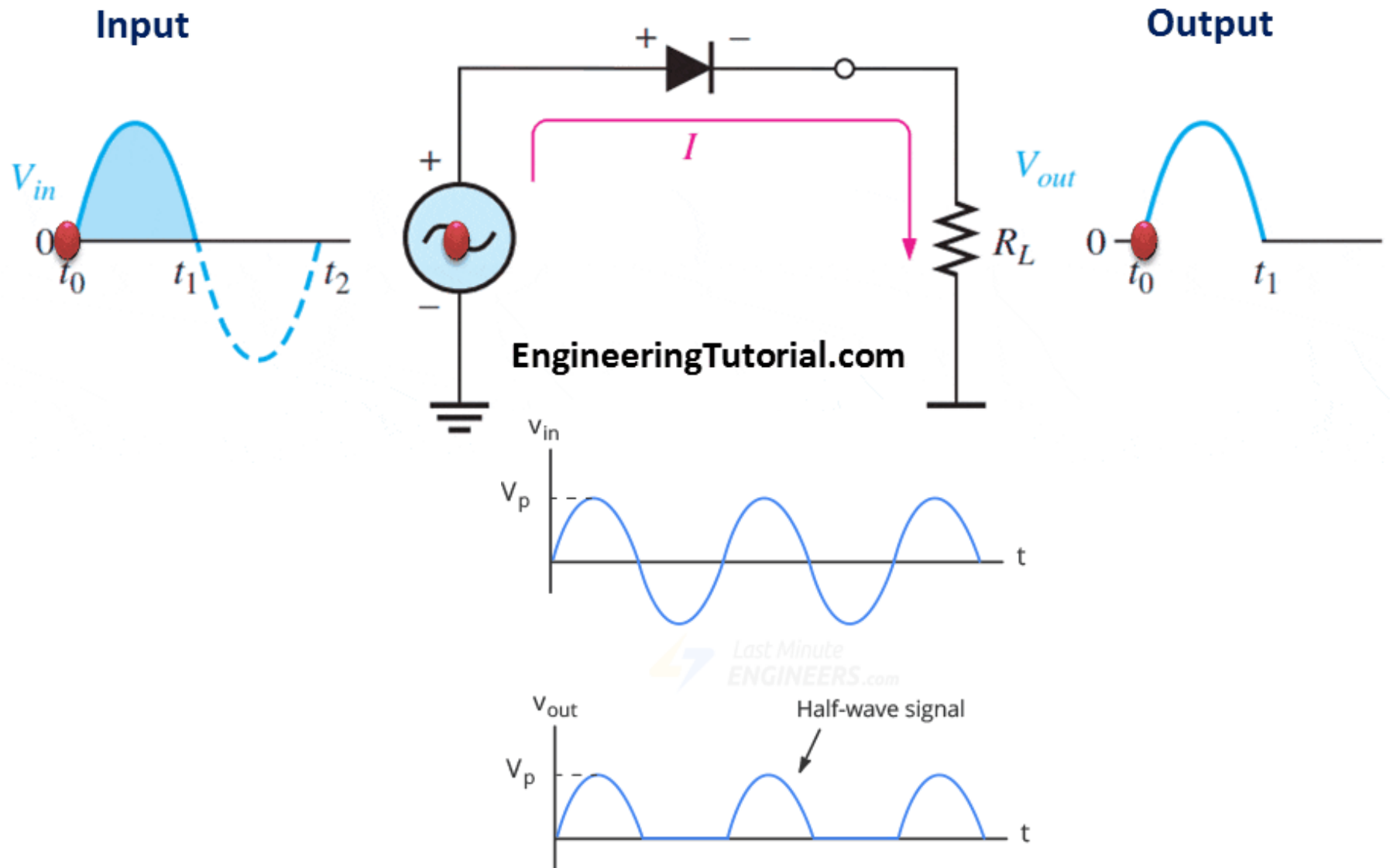

Center Tapped Full Wave Rectifier

During Negative Half Cycle

D_1 : Reverse Bias – Open Circuit

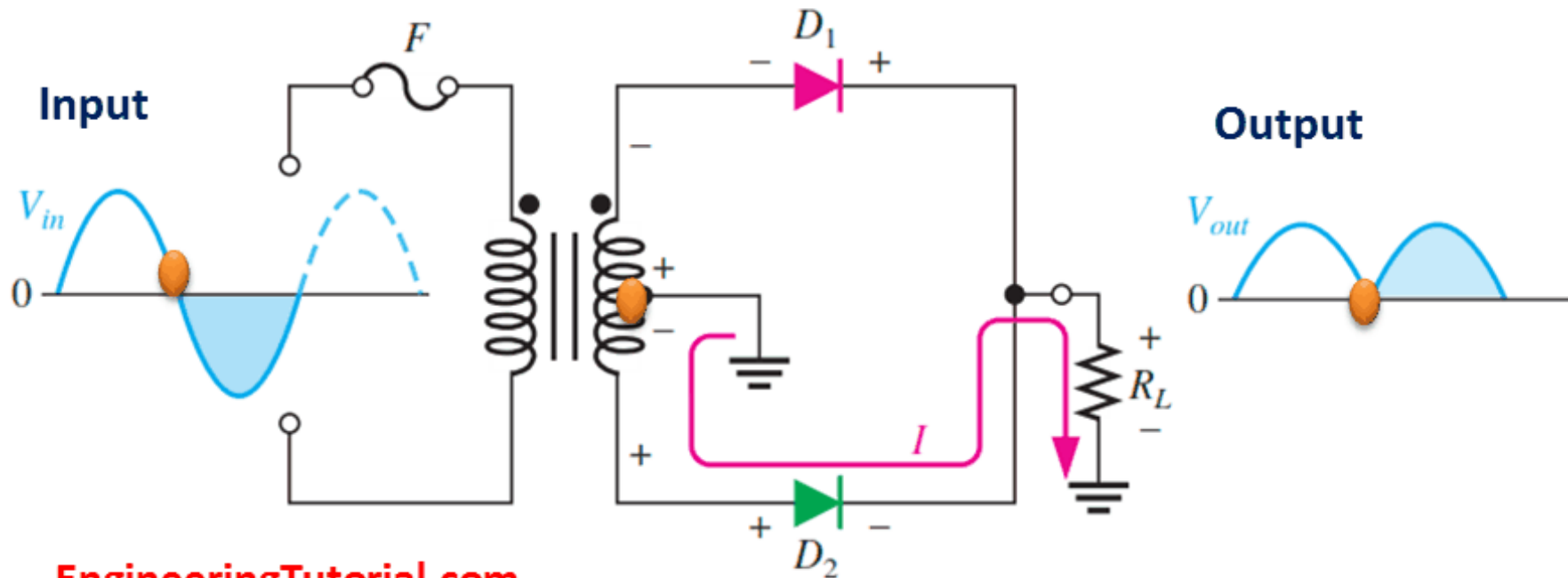


EngineeringTutorial.com

D_2 : Forward Bias – Closed Circuit


Center Tapped Full Wave Rectifier

During Positive Half Cycle


D1 : Forward Bias – Closed Circuit

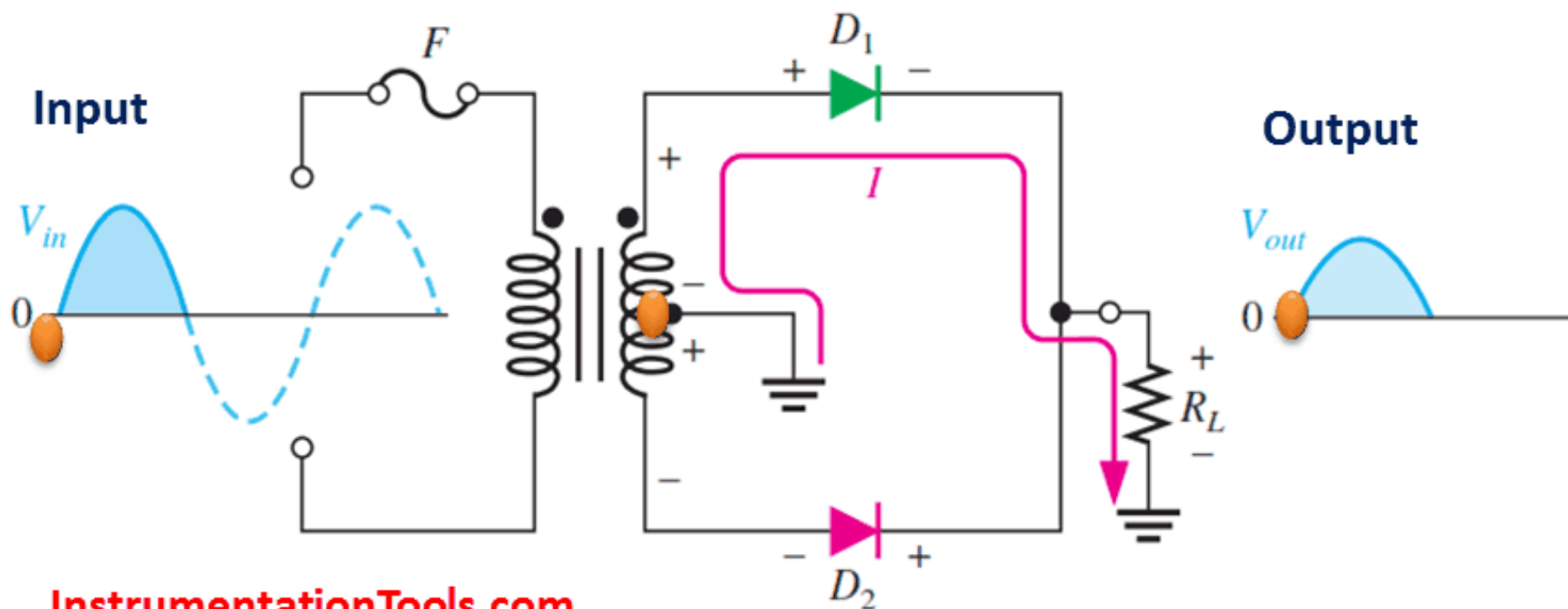

D2 : Reverse Bias – Open Circuit

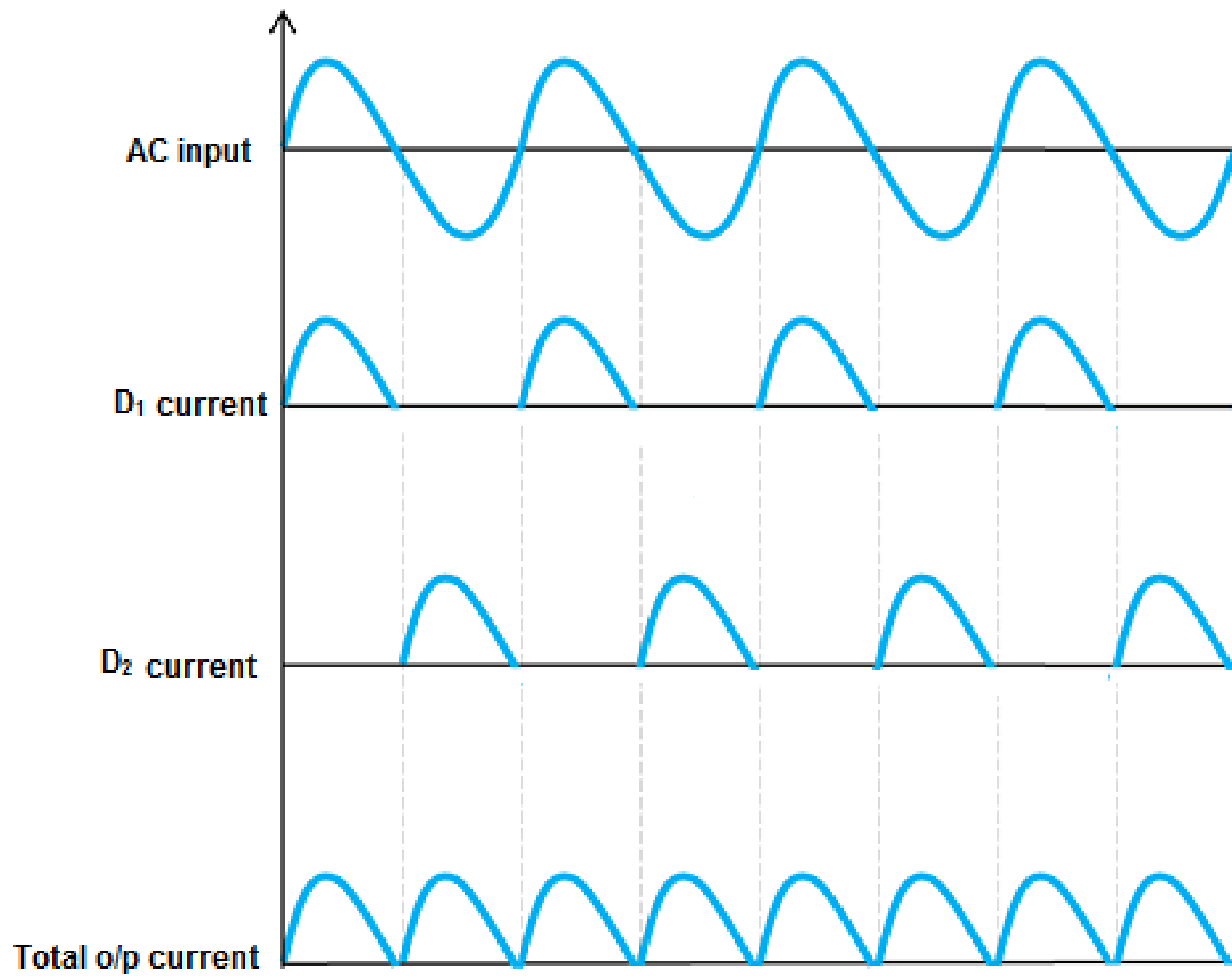

RMS and Average Value

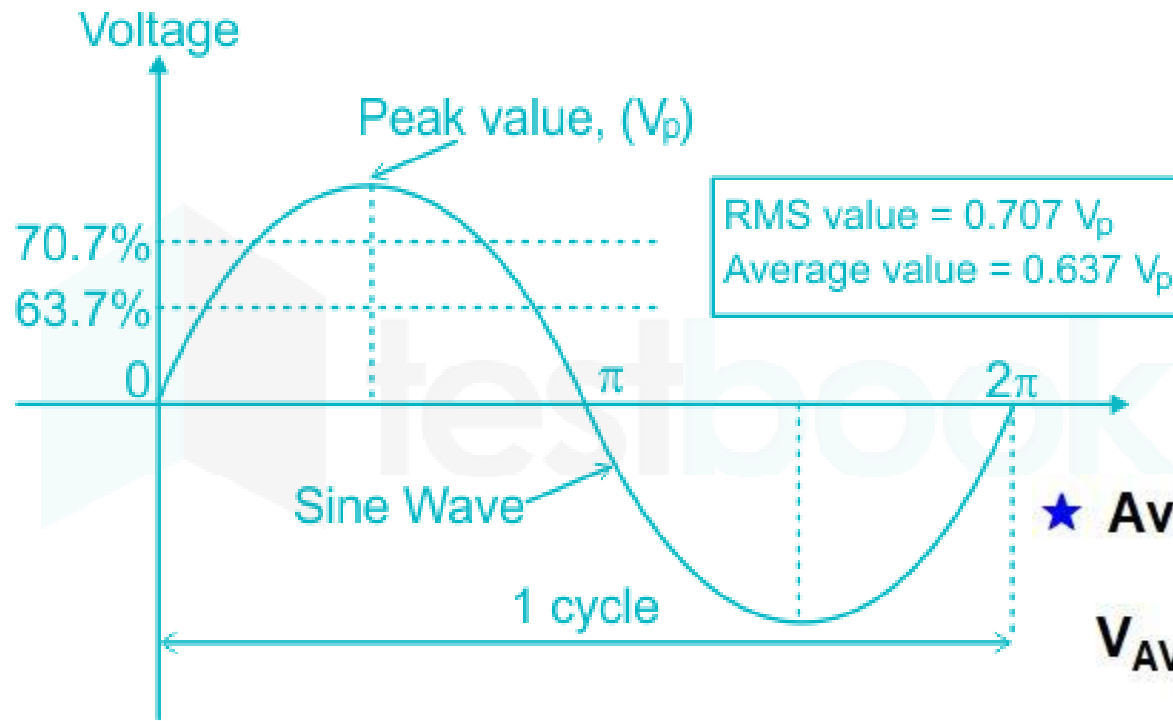


★ Average Voltage Value

$$V_{AV} = \frac{2V_P}{\pi} = 0.637 \times V_P$$

★ RMS Values of Current and Voltage related to **Peak Value** or **Max Value**.


$$V_{RMS} = \frac{V_{PK}}{\sqrt{2}} \quad , \quad I_{RMS} = \frac{I_{PK}}{\sqrt{2}}$$
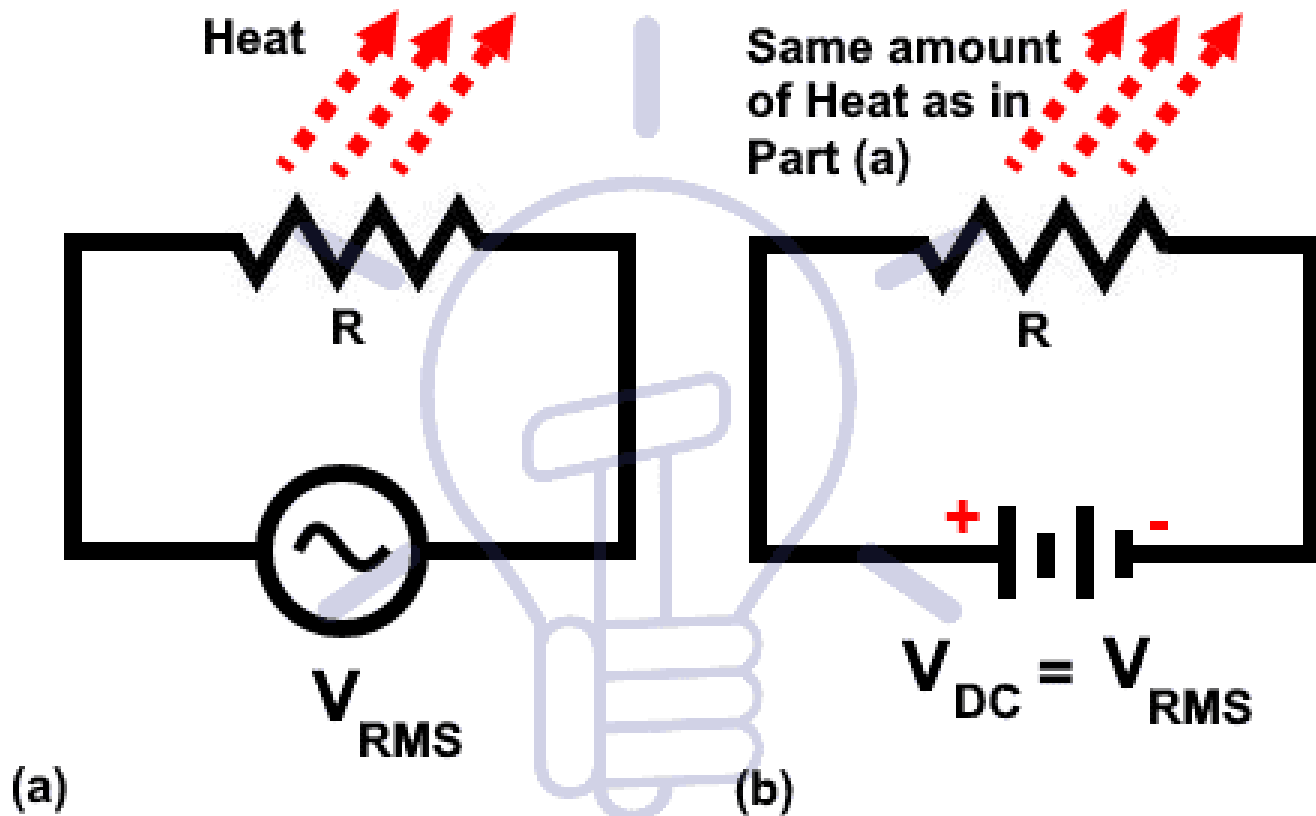
$$V_{RMS} = 0.707 \times V_{PK} \quad , \quad I_{RMS} = 0.707 \times I_{PK}$$




RMS Value of Current & Voltage in Sine wave

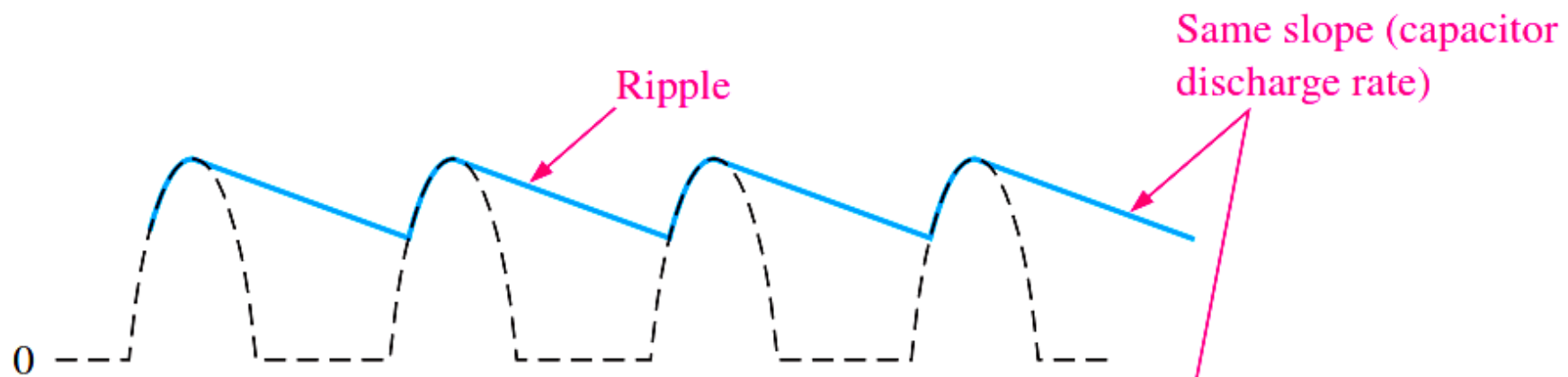The RMS (Root Mean Square) value AC is the value of DC when flowing through a resistor for the specific time period and produces same amount of heat which produced by the AC when flowing through the same circuit for a specific time.



(a) Half-wave

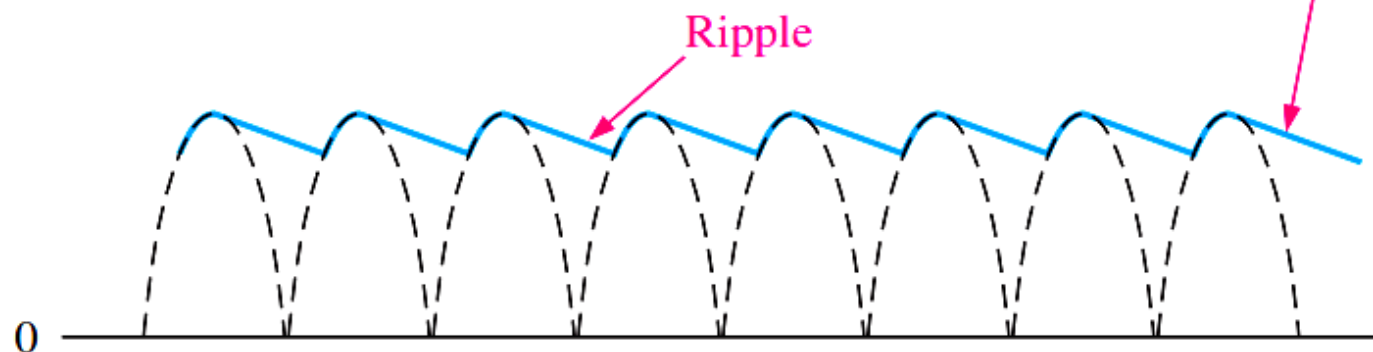

(b) Full-wave

RMS Value of Load Current of HWR

$$I_{RMS} = \frac{I_m}{2}$$

Average Value of Load Current of HWR

$$I_{avg} = \frac{I_m}{\pi}$$

Form Factor of HWR

$$\text{Form Factor} = \frac{\text{RMS Value}}{\text{Avg. Value}} = \frac{V_{rms}}{V_{avg}}$$

$$\text{Ripple Factor} = \sqrt{(\text{Form Factor})^2 - 1}$$

$$\eta = \frac{P_{dc}}{P_{ac}}$$

$$\eta = 40.6 \%$$

$$\text{RF} = 1.21$$

RMS Value of Load Current of FWR

$$I_{\text{RMS}} = \frac{I_m}{\sqrt{2}}$$

Average Value of Load Current of FWR

$$I_{\text{RMS}} = \frac{2I_m}{\pi}$$

Form Factor of FWR

$$\text{Form Factor} = \frac{\text{RMS Value}}{\text{Avg. Value}} = \frac{V_{\text{rms}}}{V_{\text{avg}}}$$

$$\text{Ripple Factor} = \sqrt{(\text{Form Factor})^2 - 1}$$



$$\eta = \frac{P_{\text{dc}}}{P_{\text{ac}}}$$

$$\eta = 81.2 \%$$

$$\text{RF} = 0.48$$

Half Wave Rectifier
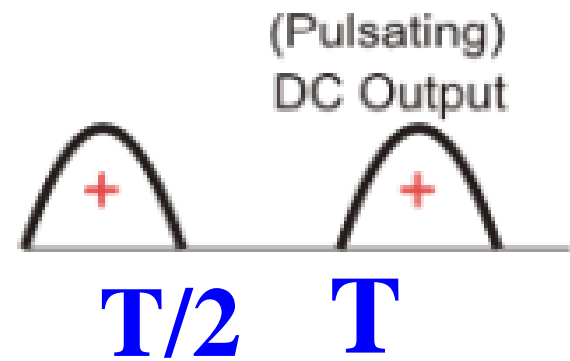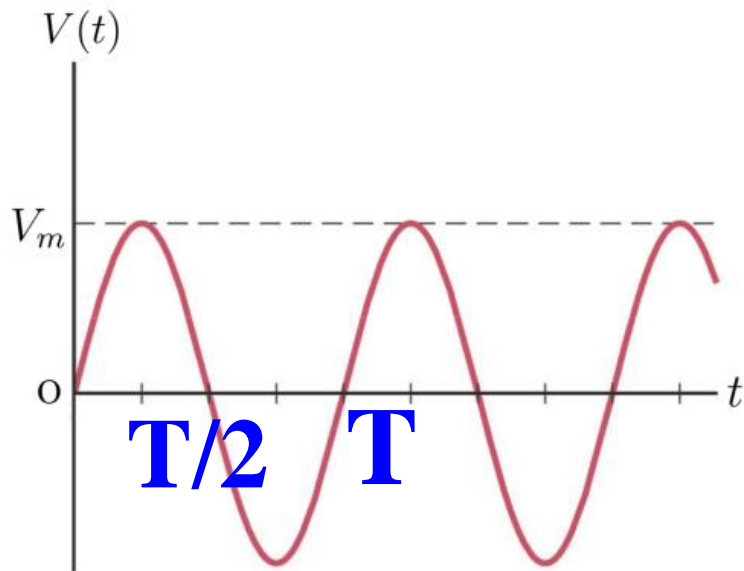
$$V_o(t) = \begin{cases} V_m \sin(\omega t), & 0 \leq t \leq T/2 \\ 0, & T/2 \leq t \leq T \end{cases}$$



Average voltage of half wave rectifier

$$\begin{aligned}V_{dc} &= \frac{1}{T} \int_0^T V_o(t) dt \\&= \frac{1}{T} \int_0^{T/2} V_m \sin(\omega t) dt + \frac{1}{T} \int_{T/2}^T 0 dt \\&= \frac{V_m}{T} \int_0^{T/2} \sin(\omega t) dt \\&= \frac{V_m}{T} \left[-\frac{\cos(\omega t)}{\omega} \right]_0^{T/2} \\&= \frac{V_m}{\omega T} \{ -\cos(\omega T/2) + \cos(0) \} \\V_{dc} &= \frac{V_m}{\pi} \{ -\cos(\pi) + \cos 0 \}\end{aligned}$$

$\omega = 2\pi/T$

RMS value of half wave rectifier

$$\begin{aligned}V_{\text{rms}}^2 &= \frac{1}{T} \int_0^T V_o^2(t) dt \\&= \frac{V_m^2}{T} \int_0^{T/2} \sin^2(\omega t) dt + \frac{V_m^2}{T} \int_{T/2}^T 0 dt \\&= \frac{V_m^2}{2T} \int_0^{T/2} 2 \sin^2(\omega t) dt \\&= \frac{V_m^2}{2T} \int_0^{T/2} \{1 - \cos(2\omega t)\} dt \\&= \frac{V_m^2}{2T} \int_0^{T/2} dt - \frac{V_m^2}{2T} \int_0^{T/2} \cos(2\omega t) dt \\&= \frac{V_m^2}{2T} \left[T \right]_0^{T/2} - \frac{V_m^2}{2T} \left[\frac{\sin(2\omega t)}{2\omega} \right]_0^{T/2} \\&= \frac{V_m^2}{4} - \frac{V_m^2}{4\omega T} \left\{ \sin(2\omega T) - \sin(0) \right\} \\&= \frac{V_m^2}{4}\end{aligned}$$

$$\omega = 2\pi/T$$

$$V_{\text{rms}} = \frac{V_m}{2}$$

Ripple factor of half wave rectifier

$$\gamma = \frac{\text{RMS value of the AC component}}{\text{value of DC component}} = \frac{V_{r(\text{rms})}}{V_{\text{dc}}}.$$

$$\gamma = \frac{V_{r(\text{rms})}}{V_{\text{dc}}} = \sqrt{\left(\frac{V_{\text{rms}}}{V_{\text{dc}}}\right)^2 - 1}$$

$$\gamma = \sqrt{\left(\frac{V_m}{2} \times \frac{\pi}{V_m}\right)^2 - 1} = \sqrt{\left(\frac{\pi}{2}\right)^2 - 1} \approx 1.21.$$

$$\text{Form factor} = \frac{V_{\text{rms}}}{V_{\text{dc}}} = \frac{V_m/2}{V_m/\pi} = \frac{\pi}{2} \approx 1.57.$$

Efficiency of half wave rectifier

$$\eta = \frac{\text{DC power output}}{\text{AC power input}} = \frac{P_{\text{dc}}}{P_{\text{ac}}}.$$

$$P_{\text{ac}} = I_{\text{rms}}^2 (R_L + r_f) = \frac{V_{\text{rms}}^2}{R_L + r_f}.$$

$$P_{\text{dc}} = I_{\text{dc}}^2 R_L = \frac{V_{\text{dc}}^2}{R_L}.$$

Efficiency of half wave rectifier

$$\begin{aligned}\eta &= \frac{P_{\text{dc}}}{P_{\text{ac}}} \\&= \frac{V_{\text{dc}}^2}{R_L} \times \frac{R_L + r_f}{V_{\text{rms}}^2} \\&= \frac{V_{\text{dc}}^2}{V_{\text{rms}}^2} \times \frac{R_L + r_f}{R_L} \\&= \left(\frac{V_{\text{dc}}}{V_{\text{rms}}} \right)^2 \times \left(1 + \frac{r_f}{R_L} \right) \\&= \left(\frac{V_m/\pi}{V_m/2} \right)^2 \times \left(1 + \frac{r_f}{R_L} \right) \\&\approx 0.4053 \left(1 + \frac{r_f}{R_L} \right)\end{aligned}$$

$$P_{\text{ac}} = I_{\text{rms}}^2 (R_L + r_f) = \frac{V_{\text{rms}}^2}{R_L + r_f}.$$

$$P_{\text{dc}} = I_{\text{dc}}^2 R_L = \frac{V_{\text{dc}}^2}{R_L}.$$

$\eta_{\text{max}} \approx 0.4053 = 40.53\%.$

Average voltage of Full wave Rectifier

$$\begin{aligned} V_{\text{avg}} &= \frac{1}{T/2} \int_0^{T/2} V(t) dt & V_o(t) &= \begin{cases} V_m \sin(\omega t), & 0 \leq t \leq T/2 \\ V_m \sin(\omega t - \pi), & T/2 \leq t \leq T \end{cases} \\ &= \frac{2V_m}{T} \int_0^{T/2} \sin(\omega t) dt \\ &= \frac{2V_m}{T} \left[-\frac{\cos(\omega t)}{\omega} \right]_0^{T/2} \\ &= \frac{2V_m}{\omega T} \{-\cos(\omega T/2) + \cos 0\} \\ &= \frac{2V_m}{2\pi} \{-\cos(\pi) + \cos 0\} \\ &= \frac{V_m}{\pi} (+1 + 1) \\ &= \frac{2}{\pi} V_m \\ &\approx 0.637 V_m. \end{aligned}$$

RMS value of Full wave rectifier

$$\begin{aligned} V_{\text{rms}}^2 &= \frac{V_m^2}{T} \int_0^T \sin^2(\omega t) dt \\ &= \frac{V_m^2}{2T} \int_0^T 2 \sin^2(\omega t) dt \\ &= \frac{V_m^2}{2T} \int_0^T \{1 - \cos(2\omega t)\} dt \\ &= \frac{V_m^2}{2T} \int_0^T dt - \frac{V_m^2}{T} \int_0^T \cos(2\omega t) dt \\ &= \frac{V_m^2}{2T} \left[T \right]_0^T - \frac{V_m^2}{2T} \left[\frac{\sin(2\omega t)}{2\omega} \right]_0^T \\ &= \frac{V_m^2}{2} - \frac{V_m^2}{4\omega T} \left\{ \sin(2\omega T) - \sin(0) \right\} \\ &= \frac{V_m^2}{2} - \frac{V_m^2}{4\omega T} \left\{ \sin(4\pi) - \sin(0) \right\} \\ &= \frac{V_m^2}{2} - \frac{V_m^2}{4\omega T} (0 - 0) \\ &= \frac{V_m^2}{2} \end{aligned}$$

$$V_{\text{rms}} = \frac{V_m}{\sqrt{2}} \approx 0.707 V_m.$$

Ripple factor of full wave rectifier

$$\begin{aligned}\gamma &= \sqrt{\left(\frac{V_{\text{rms}}}{V_{\text{dc}}}\right)^2 - 1} \\ &= \sqrt{\left(\frac{\pi}{2\sqrt{2}}\right)^2 - 1} \\ &\approx 0.48\end{aligned}$$

$$\text{Form factor} = \frac{V_{\text{rms}}}{V_{\text{dc}}} = \frac{\pi}{2\sqrt{2}} \approx 1.11.$$

Efficiency of Full wave rectifier

$$\eta = \frac{P_{dc}}{P_{dc}} \qquad V_{dc} \approx 0.637 V_m.$$

$$= \left(\frac{V_{dc}}{V_{rms}} \right)^2 \times \left(1 + \frac{r_f}{R_L} \right)$$

$$V_{rms} = \frac{V_m}{\sqrt{2}} \approx 0.707 V_m.$$


$$\approx 0.8106 \left(1 + \frac{r_f}{R_L} \right)$$

$$\eta_{\max} \approx 0.8106 = 81.06\%.$$

Comparison of Rectifiers

Parameters	Half wave rectifier	Full wave rectifier
Number of diodes	1	2 or 4
Maximum efficiency	40.53%	81.06 %
Peak inverse voltage	V_m	V_m or $2V_m$
Average voltage no load	V_m/π	$2V_m/\pi$
V_{rms} no load	$V_m/2$	$V_m/\sqrt{2}$
Ripple factor	1.21	0.48
Form factor	1.57	1.11
Output frequency	f	$2f$

RL Circuits

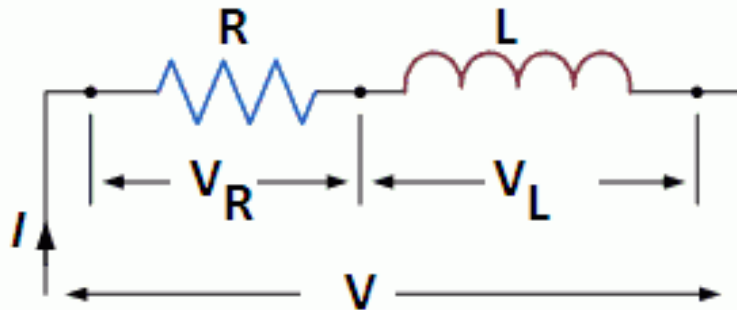


$$V = \sqrt{(IR)^2 + (IX_L)^2}$$

$$I = \frac{V}{\sqrt{(R)^2 + (X_L)^2}} = \frac{V}{Z}$$


$$\text{where } Z = \sqrt{(R)^2 + (X_L)^2}$$

is called impedance

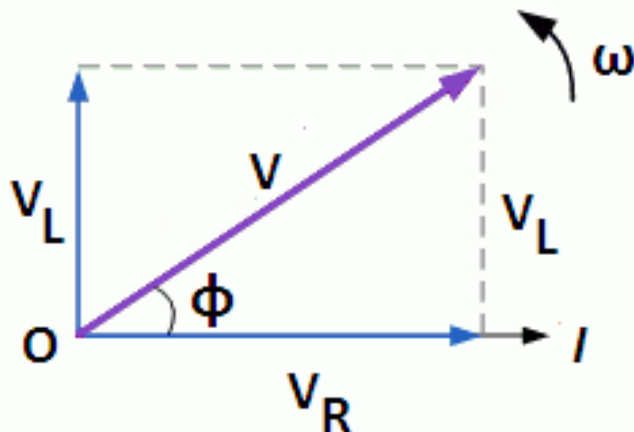
$$\phi = \tan^{-1} \frac{X_L}{R} \quad \text{Power, } P = VI \cos \phi$$



RL Circuits

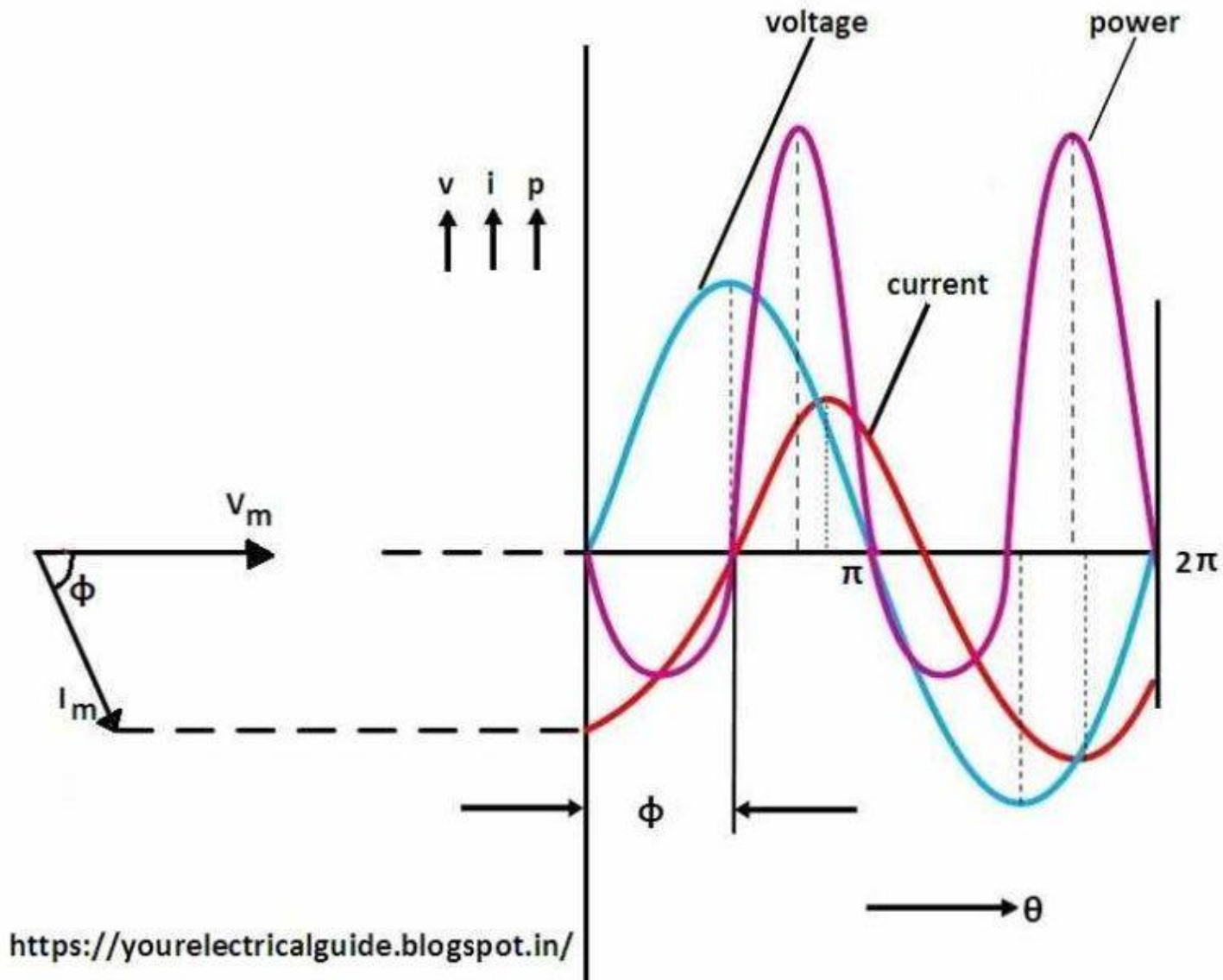

RC Series Circuit

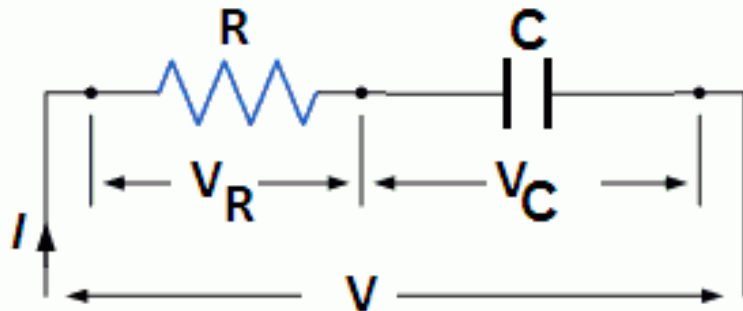


$$V = \sqrt{(IR)^2 + (IX_C)^2}$$

$$I = \frac{V}{\sqrt{(R)^2 + (X_C)^2}} = \frac{V}{Z}$$


$$\text{where } Z = \sqrt{(R)^2 + (X_C)^2}$$

is called impedance

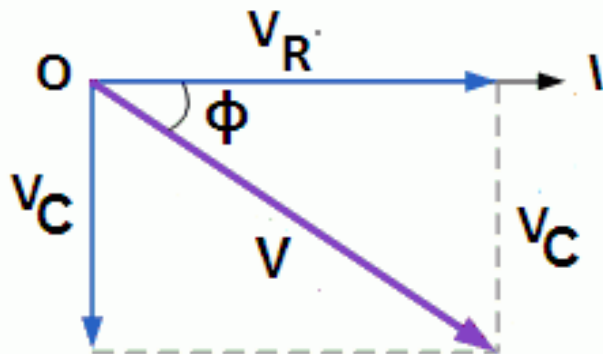
$$\phi = \tan^{-1} \frac{X_C}{R} \quad \text{Power, } P = VI \cos \phi$$




RC Series Circuit

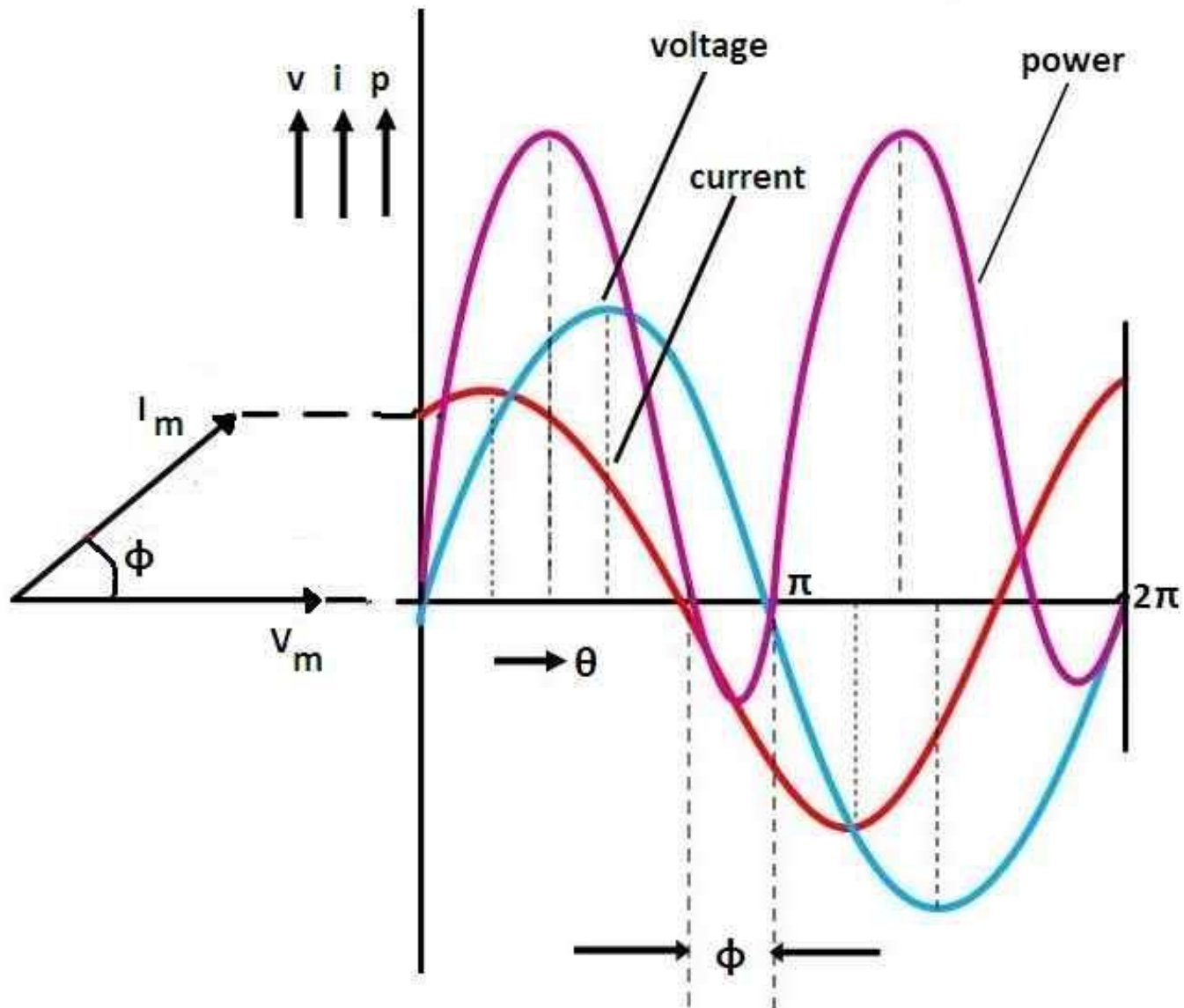

RLC Circuit

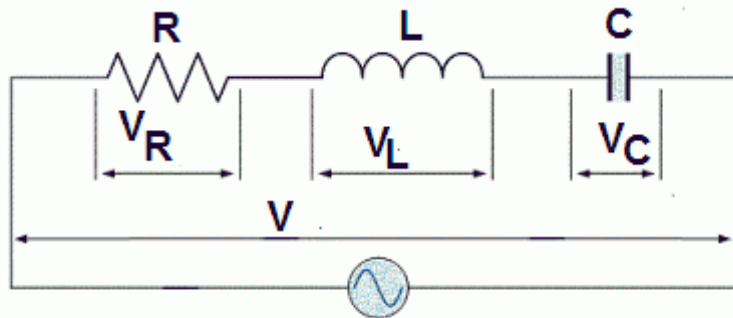

RLC Series Circuit

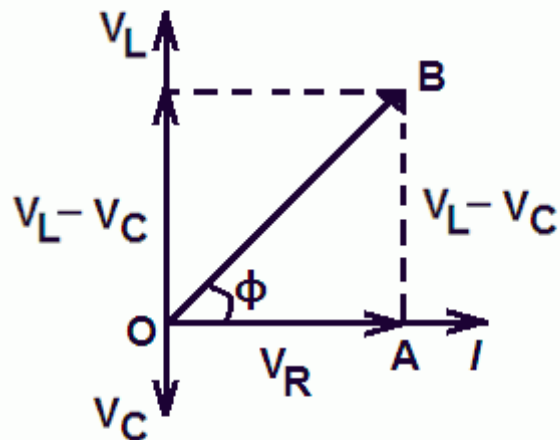

Phasor diagram $X_L > X_C$

$$V = \sqrt{(IR)^2 + I^2(X_L - X_C)^2}$$


$$I = \frac{V}{\sqrt{(R)^2 + (X_L - X_C)^2}} = \frac{V}{Z}$$

$$\text{where } Z = \sqrt{(R)^2 + (X_L - X_C)^2}$$


is called impedance

$$\phi = \tan^{-1} \frac{X}{R} \quad \text{Power, } P = VI \cos \phi$$

$$\text{where } X = X_L - X_C$$

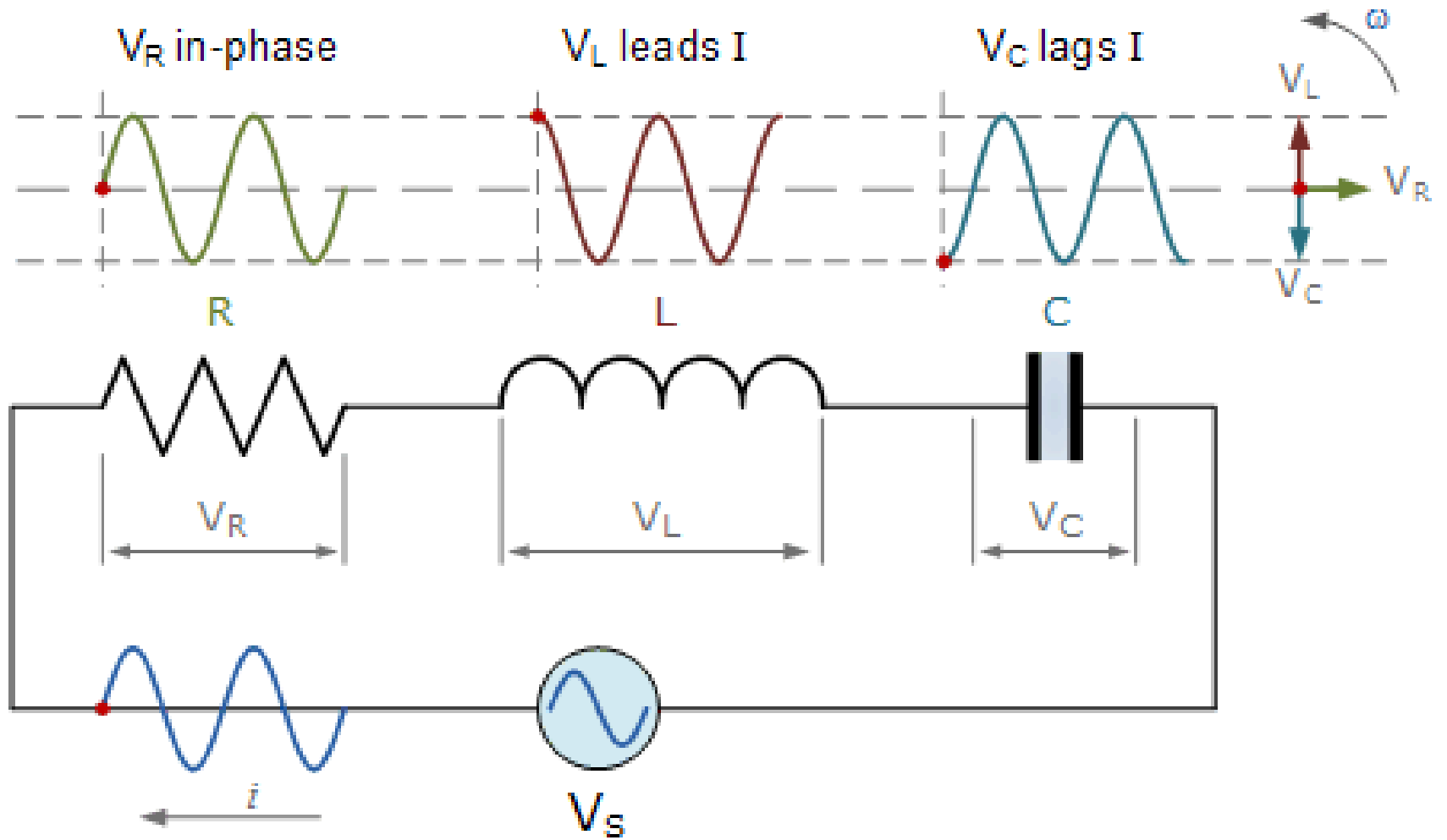

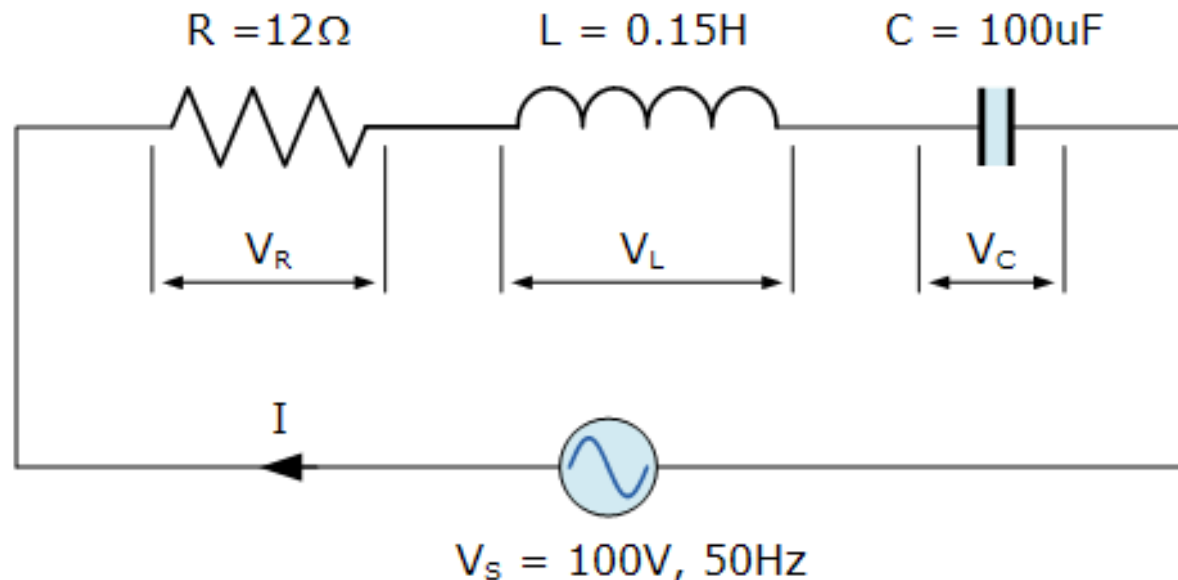A series RLC circuit containing a resistance of 12Ω , an inductance of 0.15H and a capacitor of $100\mu\text{F}$ are connected in series across a 100V , 50Hz supply. Calculate the total circuit impedance, the circuits current, power factor.



Inductive Reactance, X_L .

$$X_L = 2\pi fL = 2\pi \times 50 \times 0.15 = 47.13\Omega$$

Capacitive Reactance, X_C .

$$X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi \times 50 \times 100 \times 10^{-6}} = 31.83\Omega$$

Circuit Impedance, Z .

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$Z = \sqrt{12^2 + (47.13 - 31.83)^2}$$

$$Z = \sqrt{144 + 234} = 19.4\Omega$$

Circuits Current, I.

$$I = \frac{V_S}{Z} = \frac{100}{19.4} = 5.14 \text{ Amps}$$

Voltages across the Series RLC Circuit, V_R , V_L , V_C .

$$V_R = I \times R = 5.14 \times 12 = 61.7 \text{ volts}$$

$$V_L = I \times X_L = 5.14 \times 47.13 = 242.2 \text{ volts}$$


$$V_C = I \times X_C = 5.14 \times 31.8 = 163.5 \text{ volts}$$

Circuits Power factor and Phase Angle, θ .


$$\cos \phi = \frac{R}{Z} = \frac{12}{19.4} = 0.619$$

$$\therefore \cos^{-1} 0.619 = 51.8^{\circ} \text{ lagging}$$


3 Phase AC Circuit

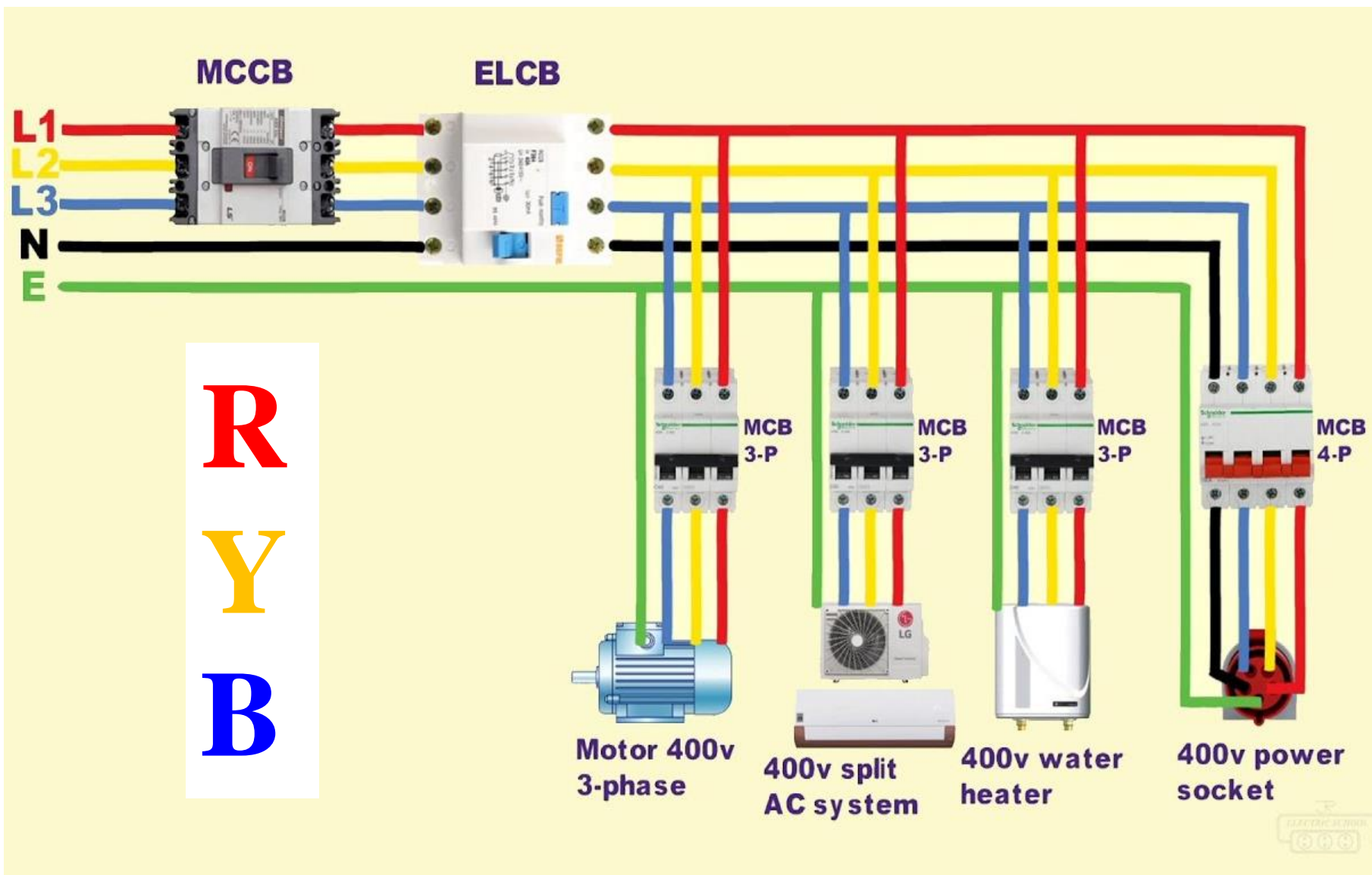


3-Phase Waveform

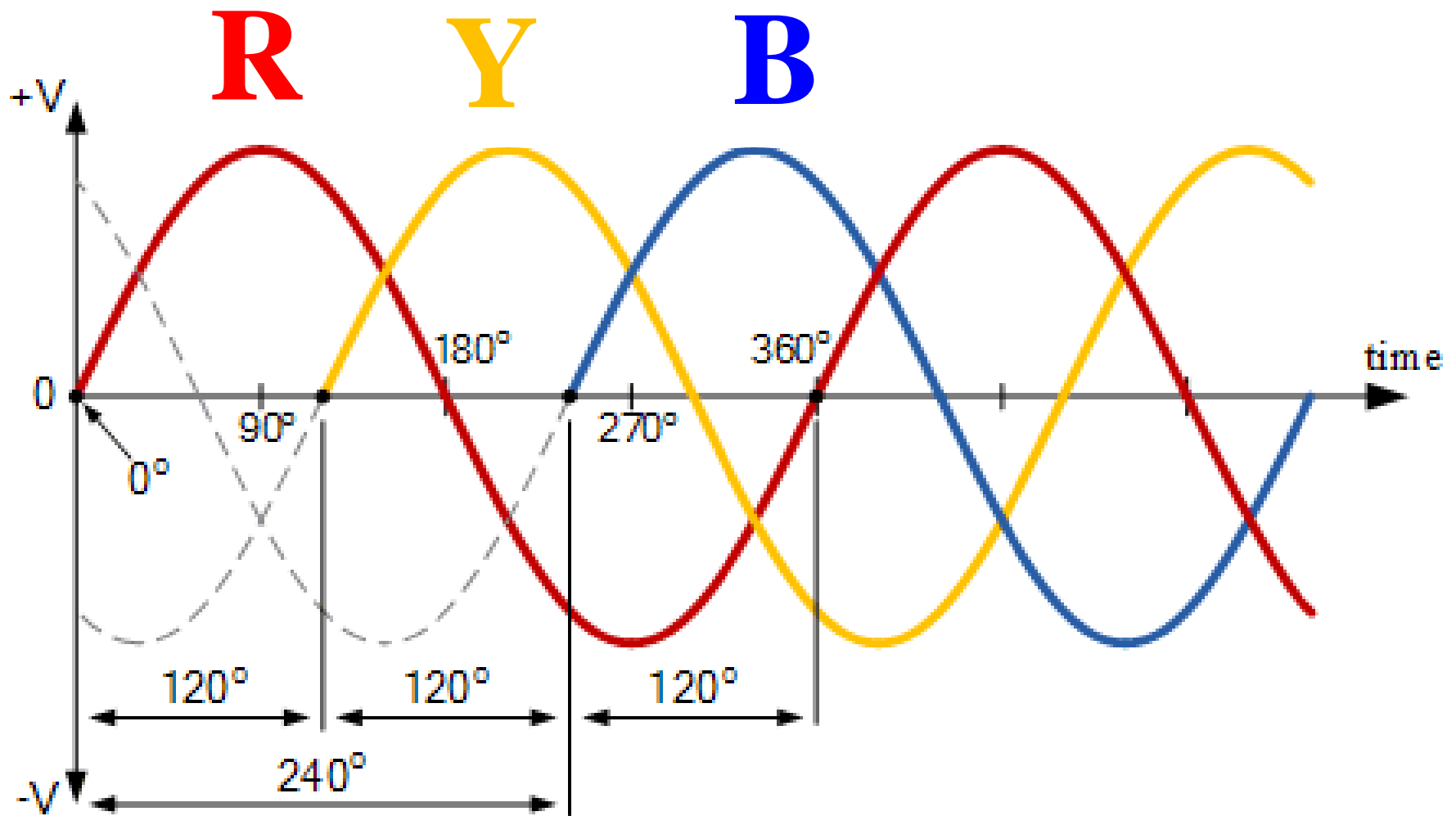


3-Phase Voltage

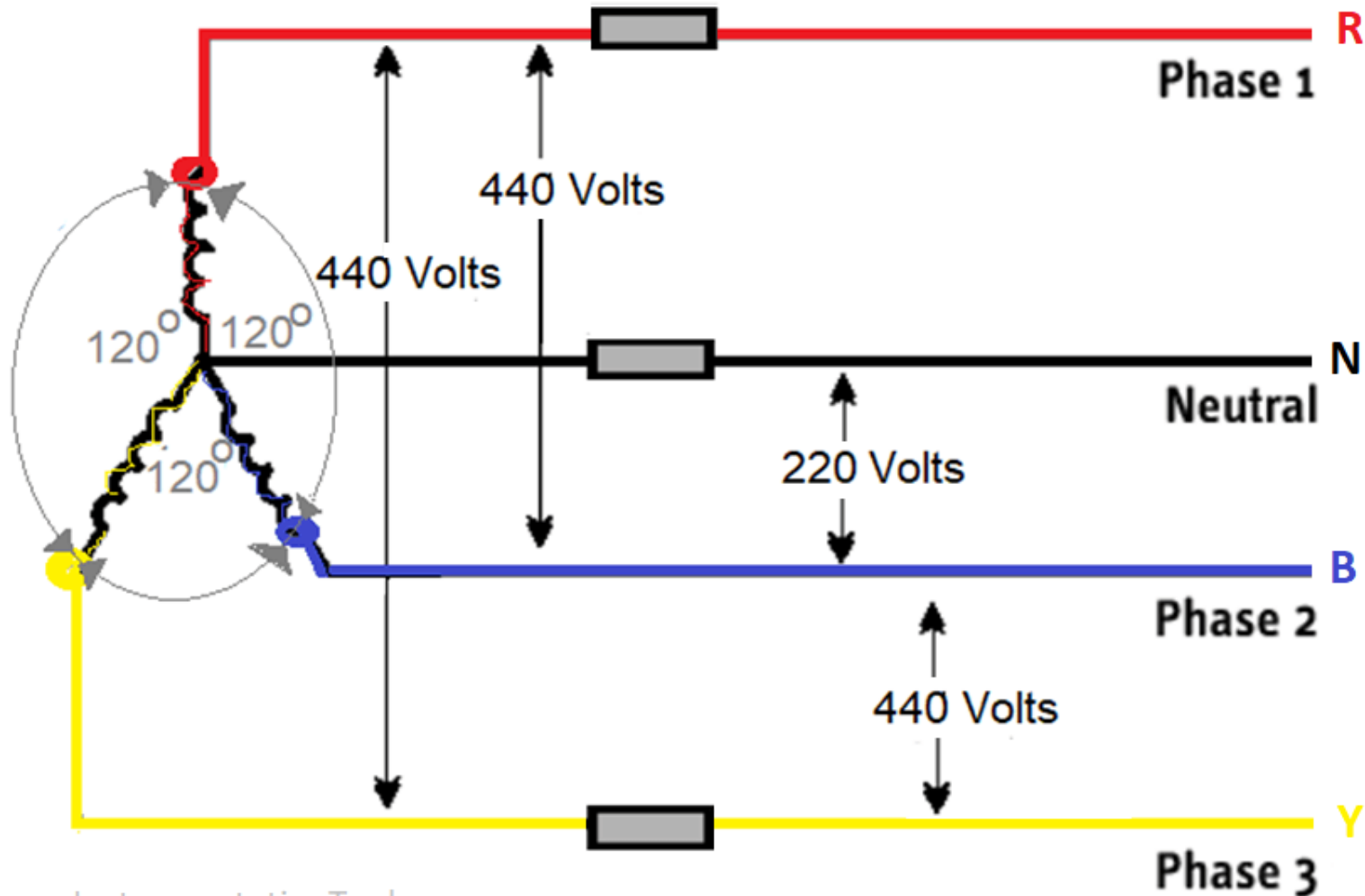


Balanced Load

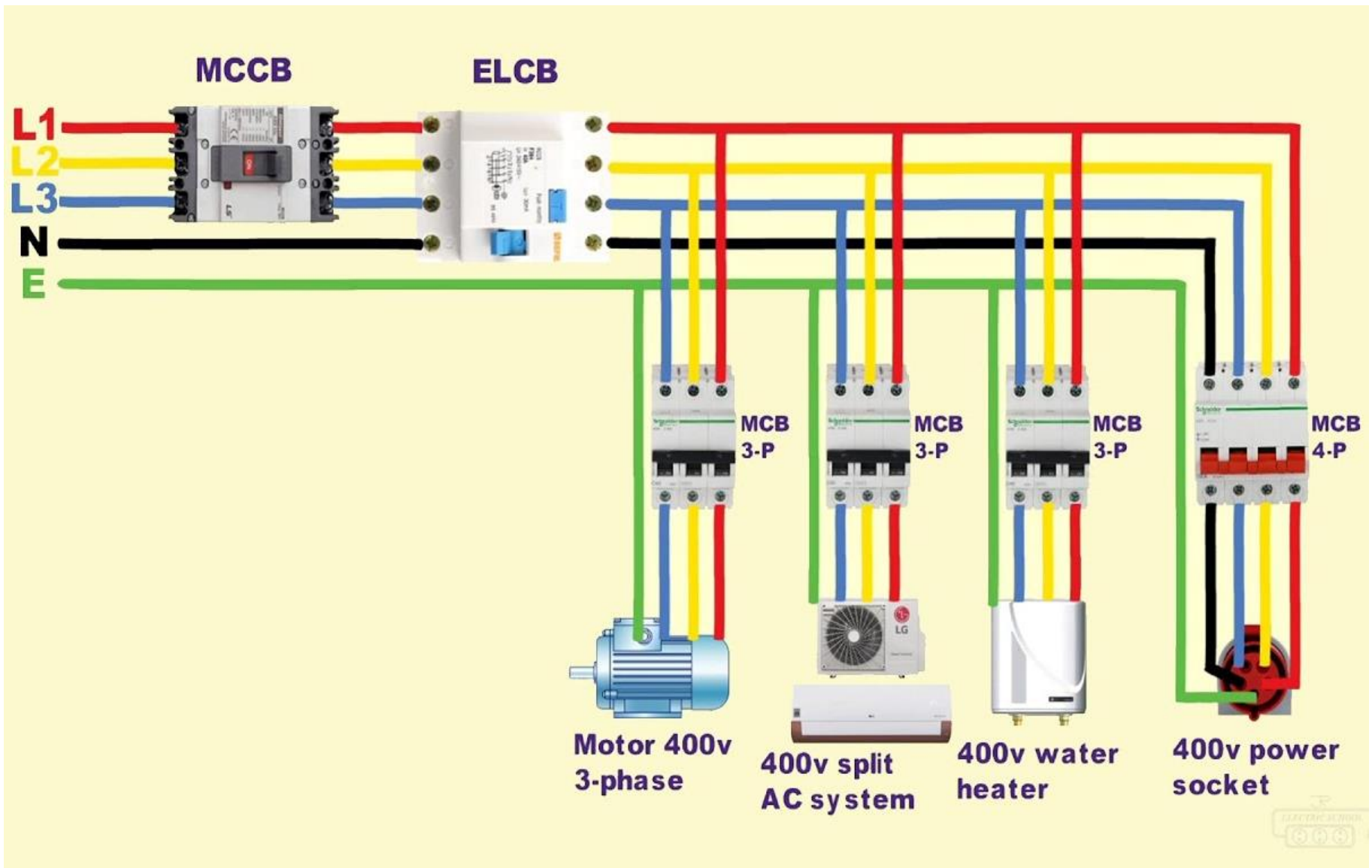


Unbalanced Load

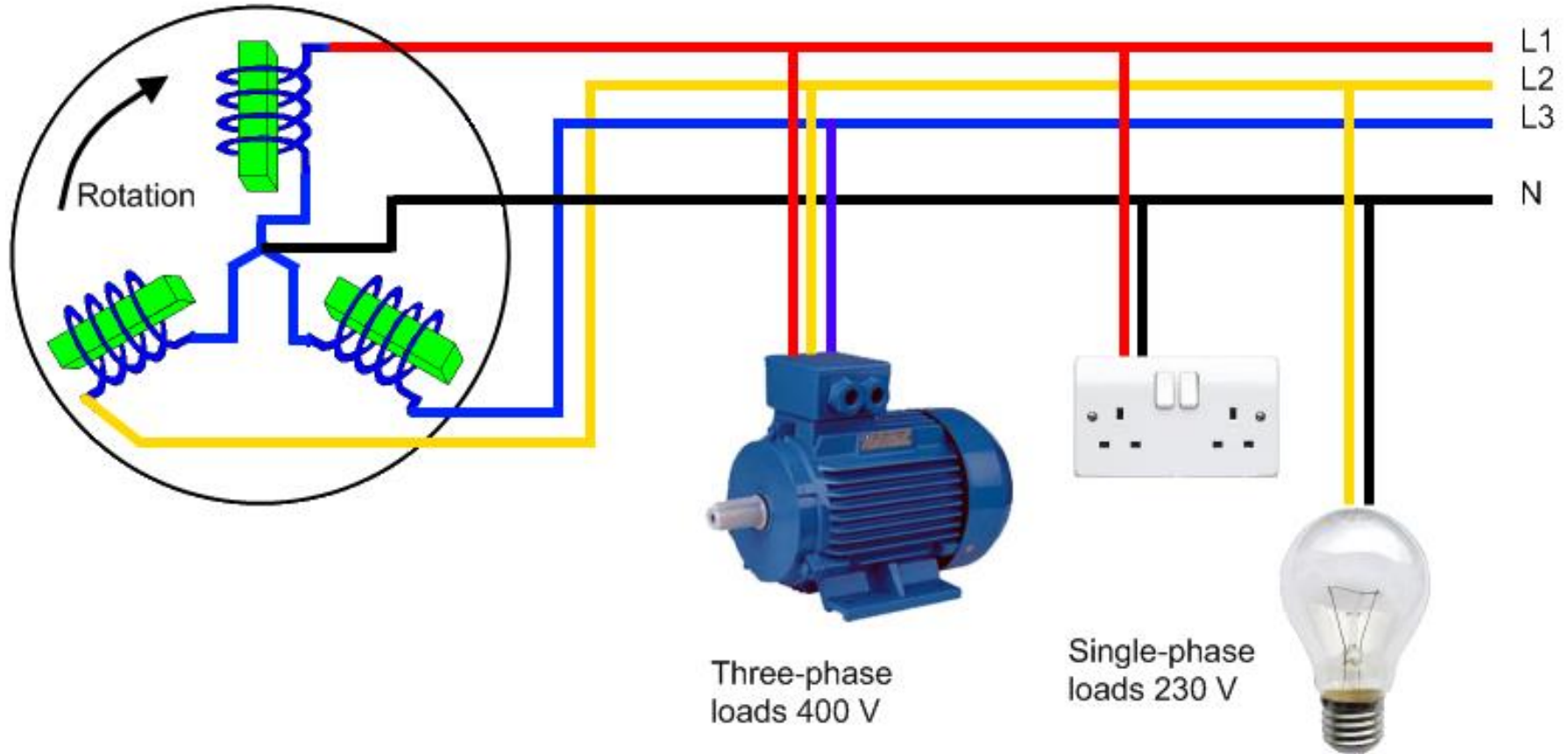

3 Phase Load

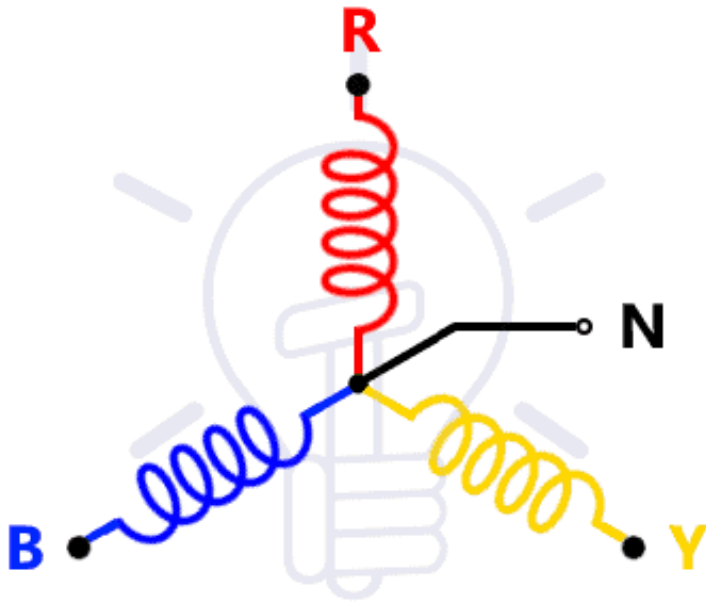


STAR (Y)

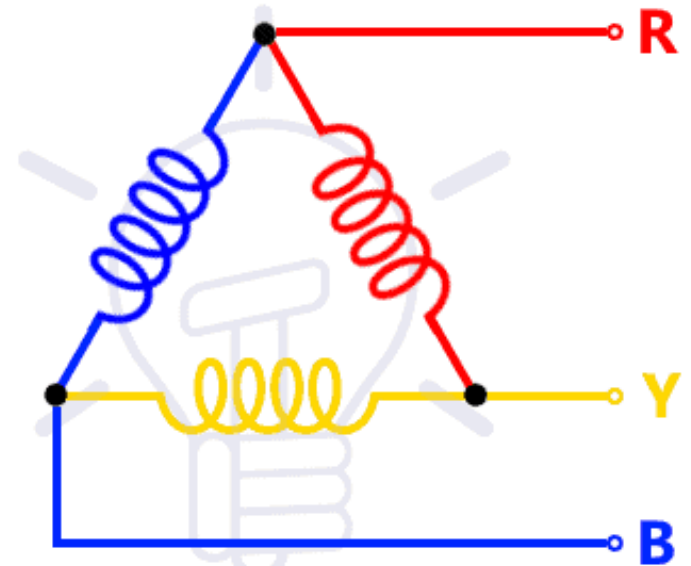


DELTA (Δ)

Star Load

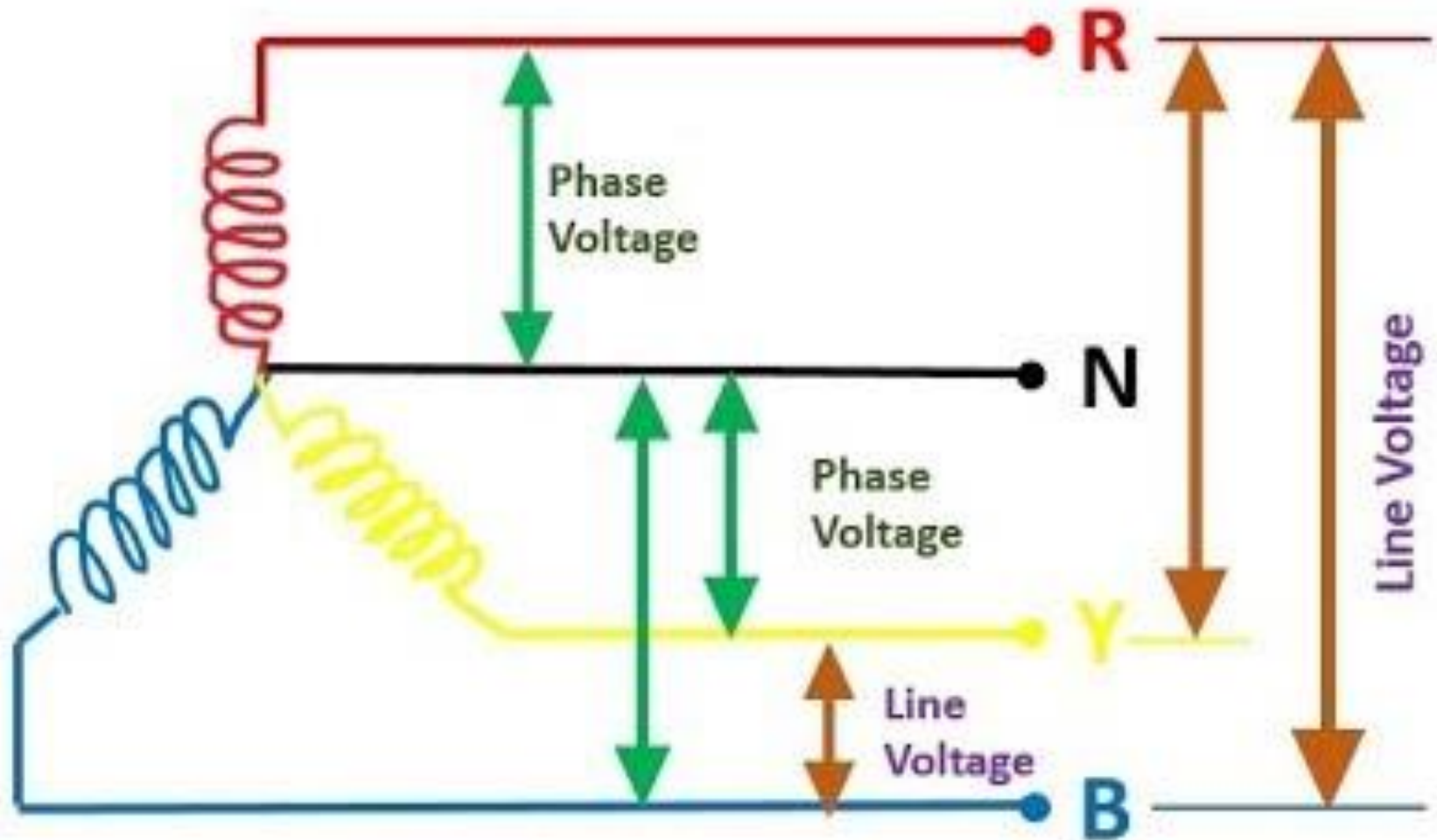

Delta Load

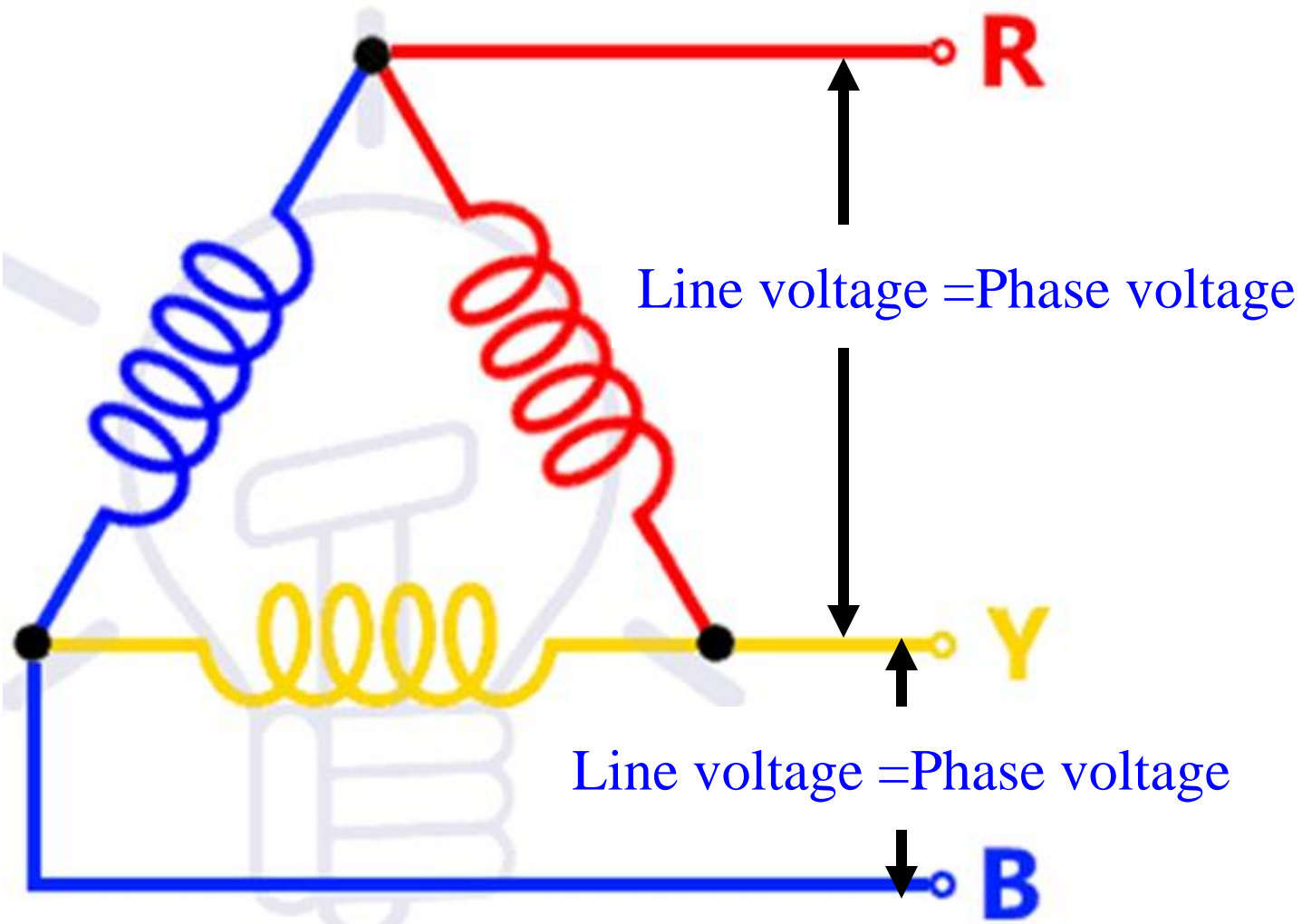

3-Phase Formulas

	Star	Delta
Voltage	$V_{Line} = \sqrt{3} \times V_{Phase}$	$V_{Line} = V_{Phase}$
Current	$I_{Line} = I_{Phase}$	$I_{Line} = \sqrt{3} \times I_{Phase}$

$$Power = \sqrt{3} V_{Line} I_{Line} \cos \phi$$

Total Phase Power = $V_P I_P \cos \phi$

Total line Power = $V_L I_L \cos \phi$

Three similar coils each of resistance $10\ \Omega$ and an inductance of 0.05H are connected in star and delta to three phase $400\text{V}, 50\text{Hz}$ symmetrical system. Find the phase current, line current, total phase power & total line power?

Given: $R=10\ \Omega$,

$L=0.05\text{H}$,

$V=400$

$f=50\ \text{Hz}$

STAR CONNECTION:-

$$V_L = \sqrt{3} V_p$$

$$X_L = 2\pi fL$$

$$\therefore V_p = \frac{400}{\sqrt{3}} = 231 \text{ V.}$$

$$\text{Impedance, } Z = \sqrt{R^2 + X_L^2} = \sqrt{10^2 + (15.7)^2}$$

$$Z = 18.61 \angle 57.6^\circ$$

$$\text{W.K.t } I_p = \frac{V_p}{18.61} = \underline{\underline{12.41 \text{ A}}}$$

$$\text{Total 3}\phi \text{ power} = V_p I_p \cos \phi$$

$$\text{w.k.t } I_p = \frac{V_p}{18.61} = \underline{12.41 \text{ A}}$$

$$\Rightarrow \text{Total 3}\phi \text{ power} = V_p \cdot \frac{V_p}{18.61} \cdot \cos 57.6^\circ \Rightarrow \underline{4608 \text{ W.}}$$

$$\text{Line Power} \Rightarrow V_L I_L \cos \phi.$$

$$= (\sqrt{3} \cdot V_p) I_p \cdot \cos \phi$$

$$= (\sqrt{3} \cdot 400) \left(\frac{231}{18.61} \right) \cos (57.6^\circ) = \underline{4608 \text{ W}}$$

(ii) DELTA CONNECTION:-

$$V_L = V_{ph} \quad ; \quad I_L = \sqrt{3} I_{ph} .$$

$$\text{Total } 3\phi \text{ power} = V_p I_p \cos \phi$$

$$= (400) \left(\frac{400}{18.61} \right) \cos 57.6^\circ .$$

$$= \underline{4608 \text{ W}} .$$

$$\text{Line Power} = V_L I_L \cos \phi$$

$$= (400) \cdot \sqrt{3} \cdot \left(\frac{400}{18.61} \right) \cdot \cos 57.6^\circ .$$

$$= \underline{7970 \text{ W}} .$$