
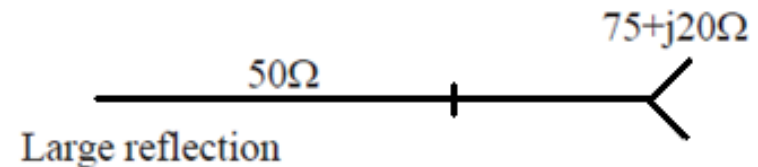


Transmission Lines

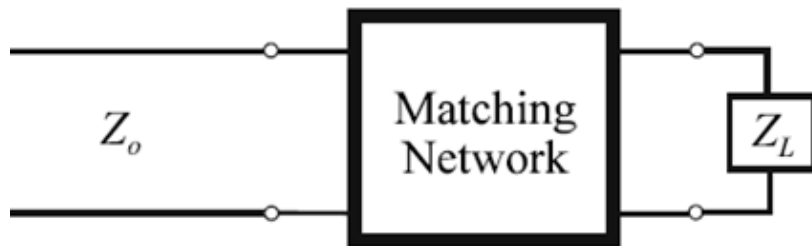11.6 Some Applications of Transmission Lines

Transmission lines are used for **Load Matching**.





- If a transmission line is connected to a load of different impedance to the T.L., **reflection** occurs.
- For maximum power transfer from source to load, a matching network is used.




Matching Networks

- Lumped element networks.
- Lumped T and PI networks.
- Distributed networks
 - $(\lambda/4)$ transformer.
 - Single Stub Tuner.
 - Double Stub Tuner.

Matching Networks

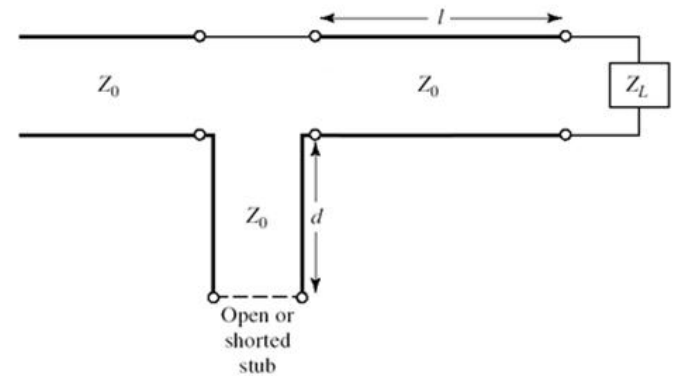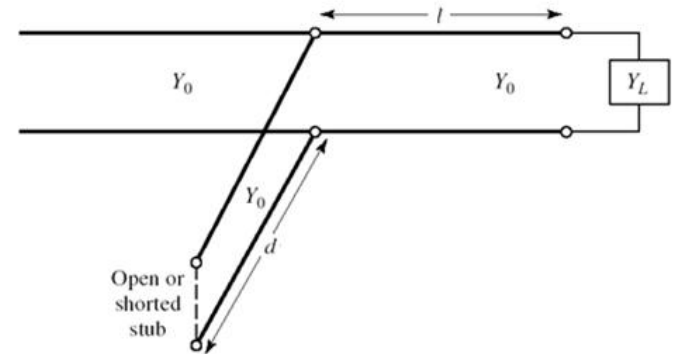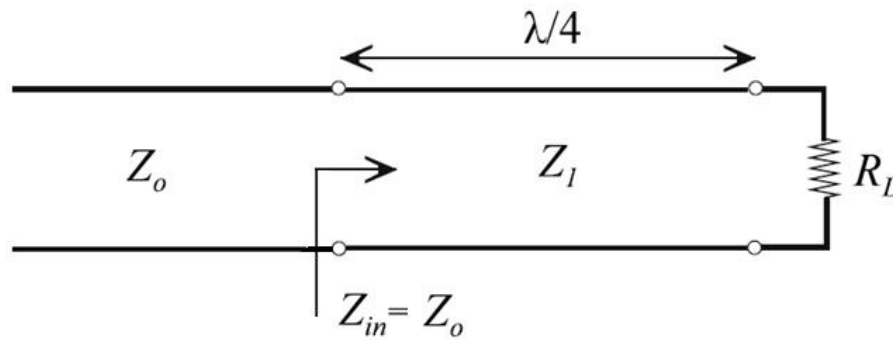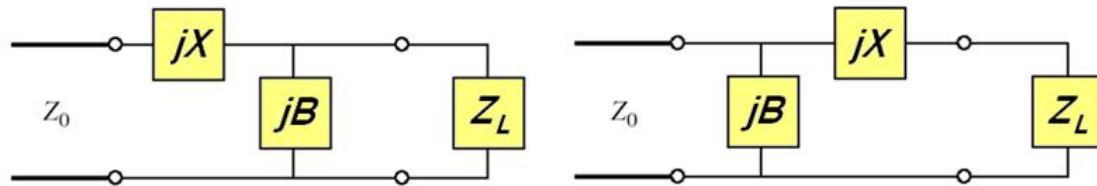


The stubs

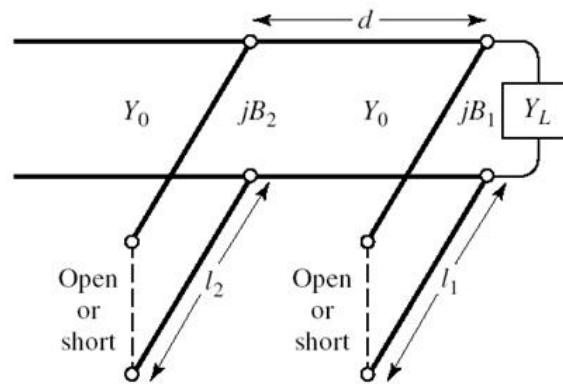


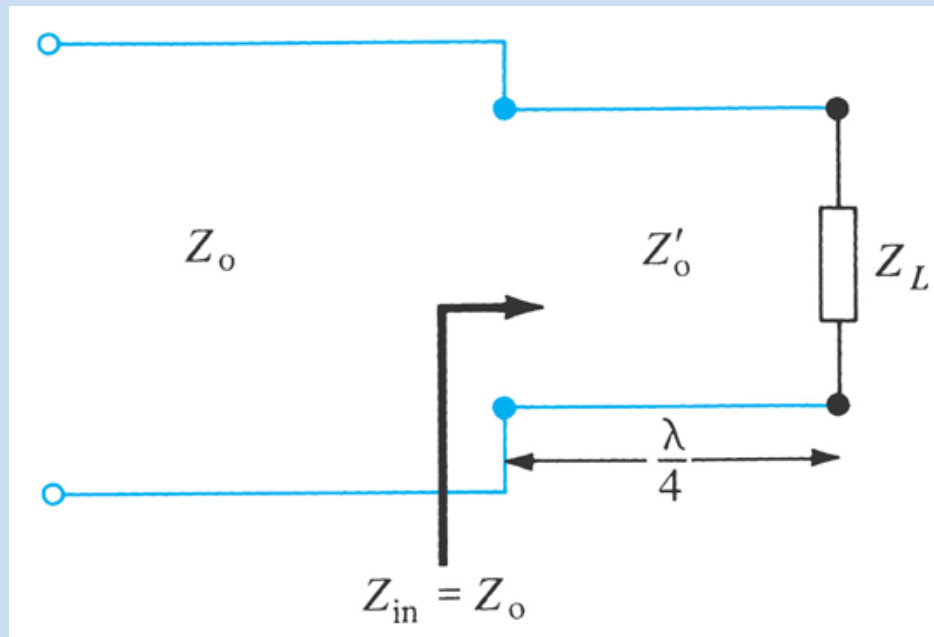A. Quarter-Wave Transformer (Matching)

- When $Z_L \neq Z_0$, the load is *mismatched* and a reflected wave exists on the line.
- The mismatched load Z_L can be properly matched to a line (with characteristic impedance Z_0) by inserting prior to the load a $\lambda/4$ transmission line (with characteristic impedance Z_0')



Quarter-Wave Transformer

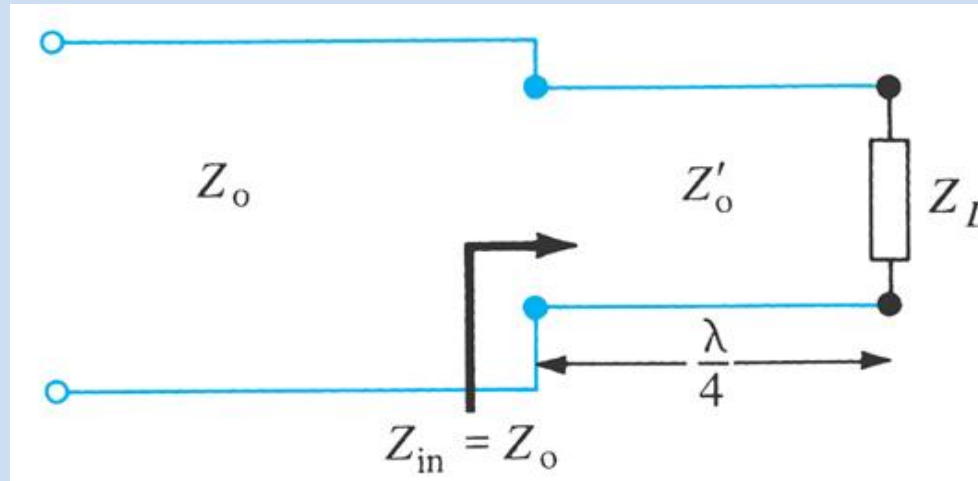

To find the value of Z'_0 required for matching:

$$Z_{in} = Z'_0 \left[\frac{Z_L + jZ'_0 \tan \beta l}{Z'_0 + jZ_L \tan \beta l} \right]$$


$$\text{But } \beta l = \left(\frac{2\pi}{\lambda} \right) \left(\frac{\lambda}{4} \right) = \frac{\pi}{2}, \quad \tan \beta l = \infty \quad \rightarrow \quad Z_{in} = \frac{(Z'_0)^2}{Z_L}$$

For a matched system, Z_{in} must equal Z_0 , Hence

$$Z_{in} = \frac{(Z'_0)^2}{Z_L} = Z_0 \quad \Rightarrow \quad \boxed{Z'_0 = \sqrt{Z_0 Z_L}}$$

Quarter-Wave Transformer

$$Z_0' = \sqrt{Z_0 R_L}$$

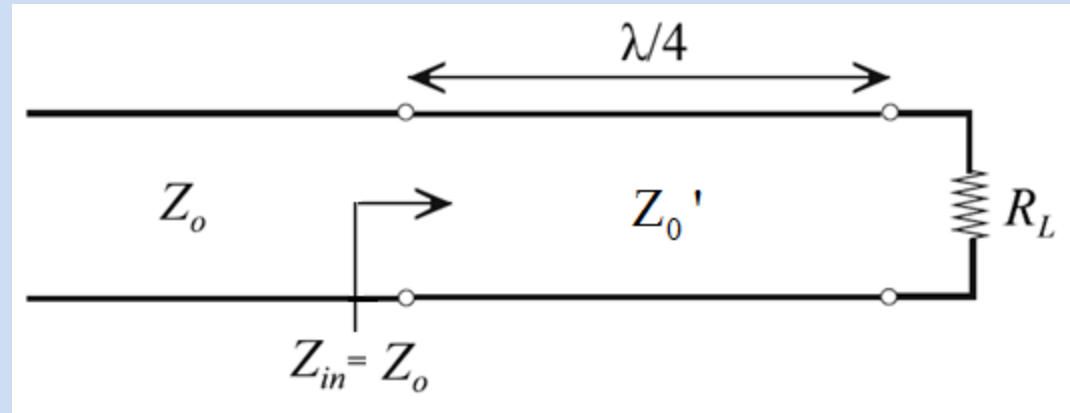


❑ This is not at every frequency, as the transmission line is only $\lambda/4$ at one frequency. (disadvantage: **narrow band**)

❑ Although the impedances can be complex in general, transmission lines have a real characteristic impedance. Hence this matching only applies to **real** load impedances.


❑ **Example:** To match a $120\ \Omega$ load to a $75\ \Omega$ line, the quarter-wave transformer must have a characteristic impedance of $\sqrt{(75)(120)} = 95\ \Omega$

B. Single Stub Tuner (Matching)

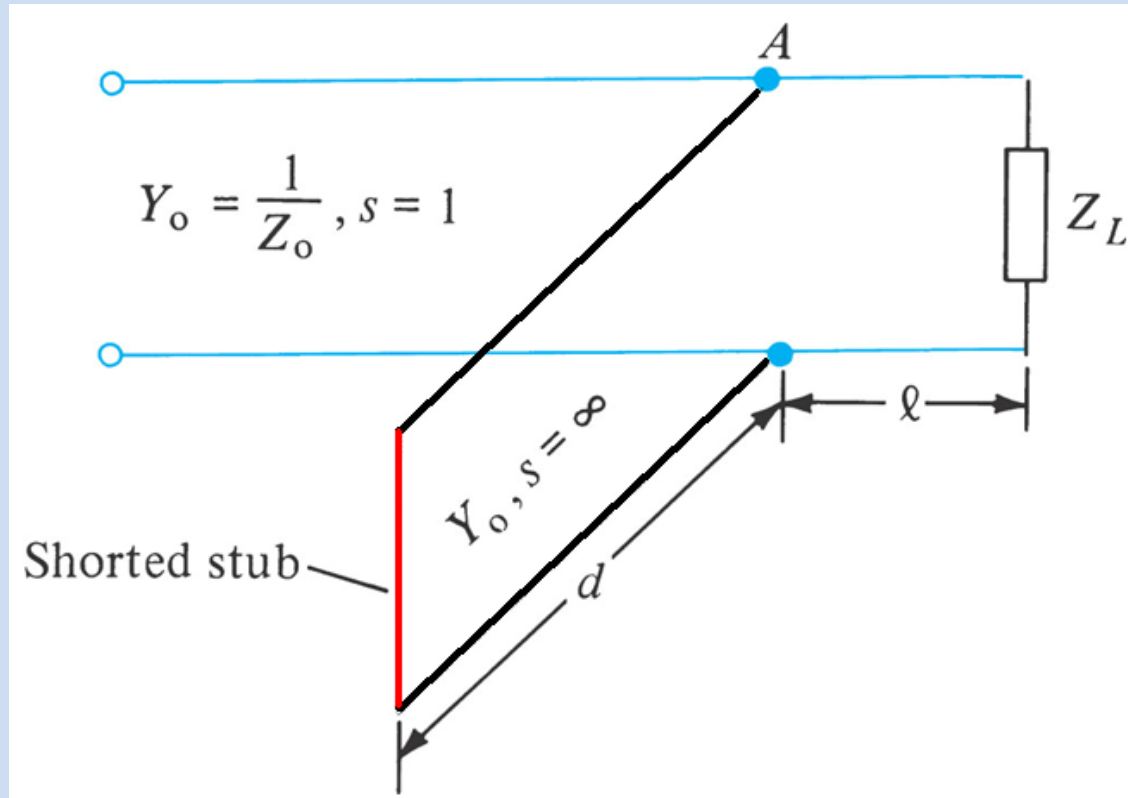

- When $Z_L \neq Z_0$, the load can be matched by using a single stub tuner.
- It consists of an open or shorted section of transmission line of length d connected in parallel with the main line at some distance ℓ from the load.

Single Stub Tuner (Matching)

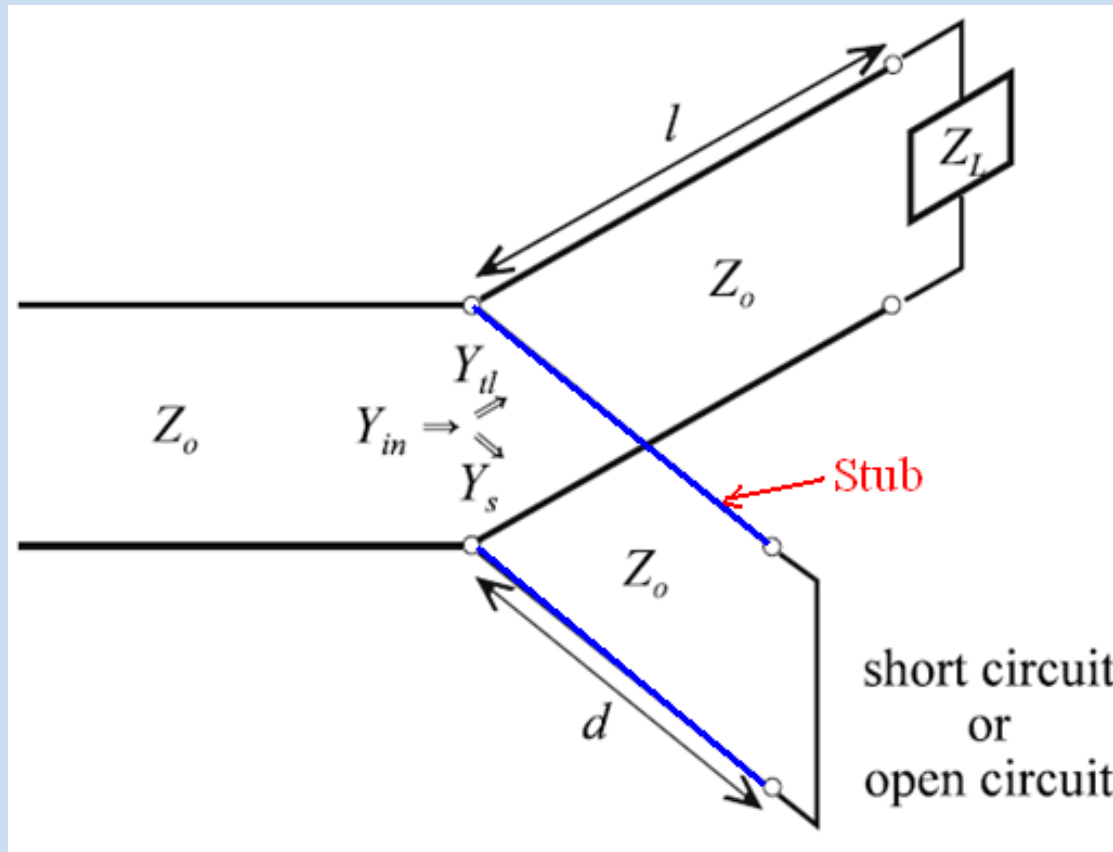

$$\begin{aligned} Y_{tl} &= Y_0 + jB && \text{[Input admittance of the terminated T-line section]} \\ Y_s &= -jB && \text{[Input admittance of the stub (short or open circuit)]} \\ Y_{in} &= Y_{tl} + Y_s = Y_0 && \text{[Overall input admittance] , } Y_0 = 1 / Z_0 \end{aligned}$$

Single Shunt Stub Tuner Design Procedure


- 1) Locate normalized load impedance and draw VSWR circle.
- 2) Convert to normalized load admittance y_L . (for the remaining steps consider the Smith Chart as **admittance** chart).
- 3) From y_L , rotate CW (toward generator) on the VSWR circle until it intersects the $1+jb$ circle in two points.
- 4) Thus the distance l , from the load to the stub, is given by either of these intersections.
- 5) Beginning at the stub end, rotate CW (toward generator) until the point at $0-jb$ is reached. This rotation distance is the stub length d .

Single Shunt Stub Tuner Design Procedure

Notes:

- ❑ Rightmost Smith chart point is the admittance of a short-circuit.
- ❑ Leftmost Smith chart point is the admittance of an open-circuit.
- ❑ There are usually two possible solutions, we normally choose the shorter stub or one at a position closer to the load.
- ❑ We may have two stubs arrangement, this is called *double-stub matching*, allows for adjustment of the load impedance.


Single Stub Tuner – Design using Smith Chart

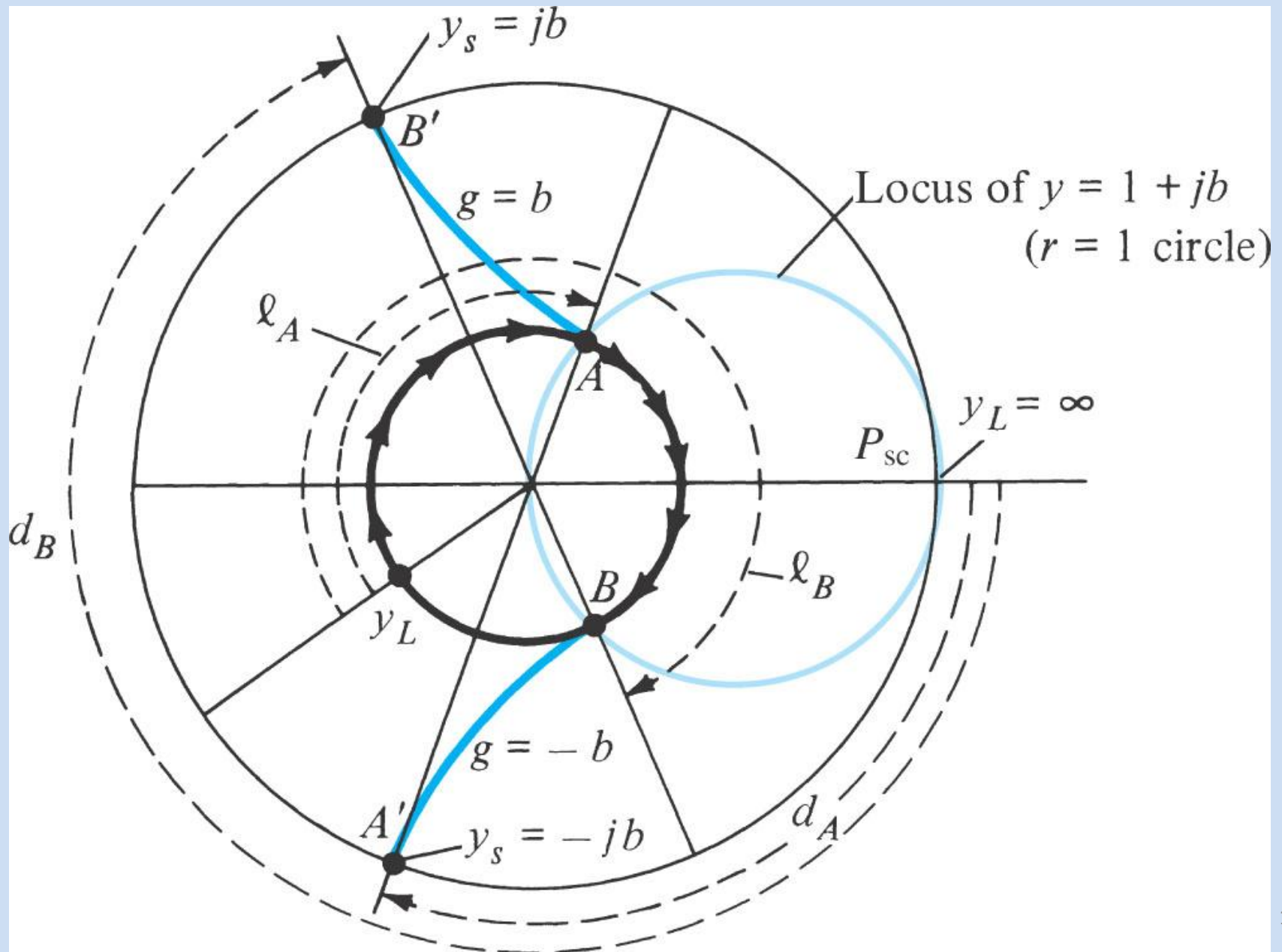


Example 11.7

An antenna with an impedance of $40 + j30 \, \Omega$ is to be matched to a $100 \, \Omega$ lossless line with a shorted stub. Determine

- (a) The required stub admittance
- (b) The distance between the stub and the antenna.
- (c) the stub length

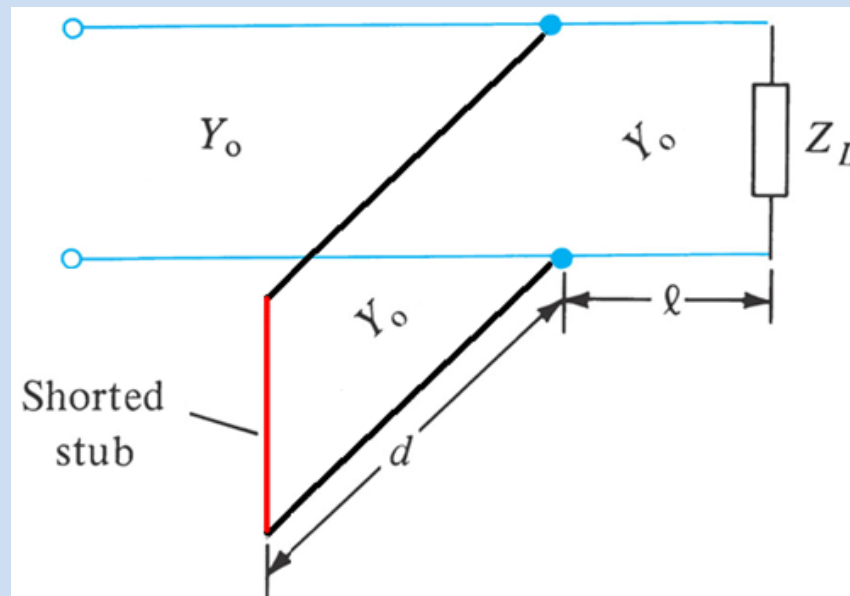

Example 11.7

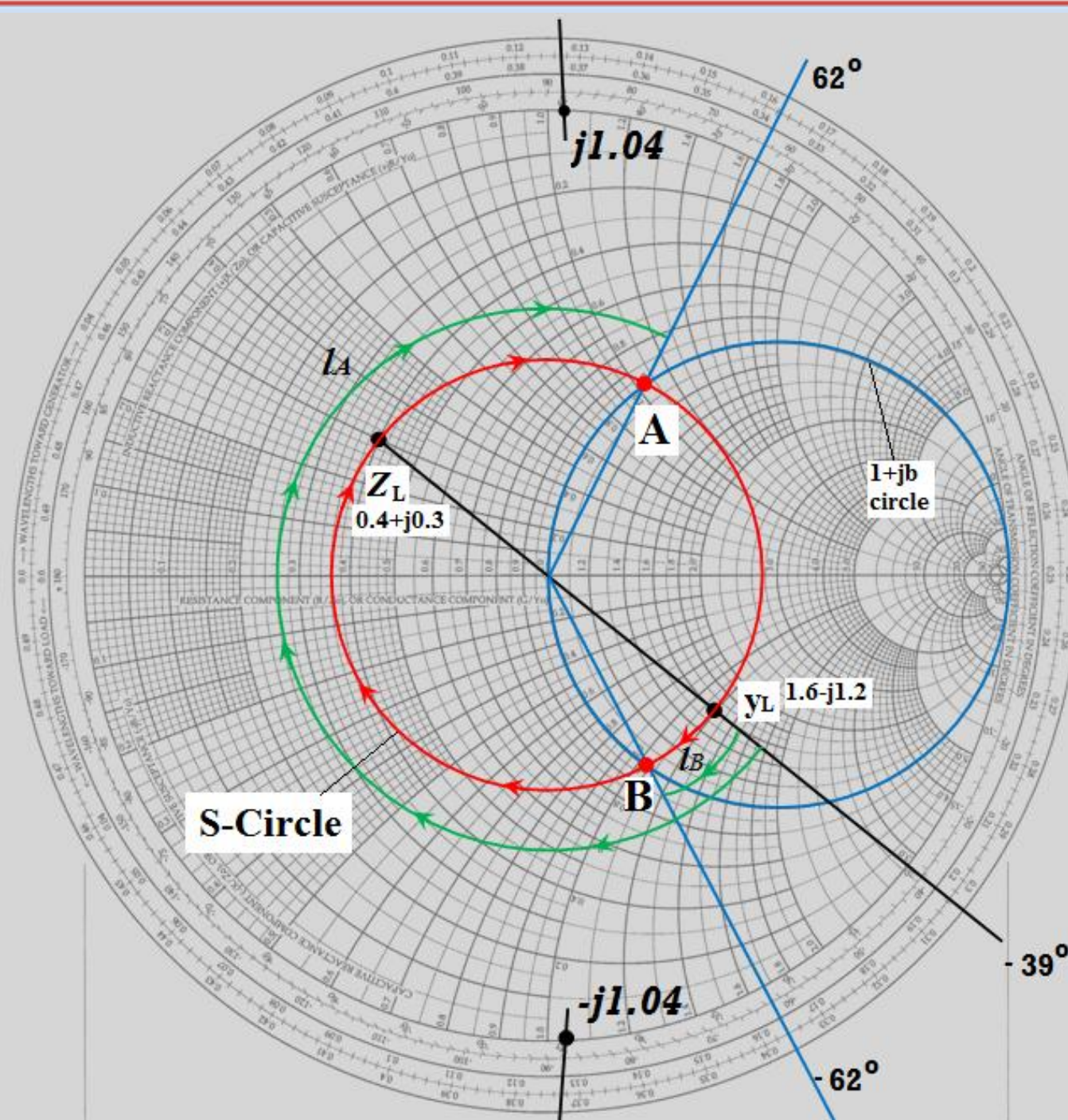

$$(a) z_L = \frac{Z_L}{Z_0}$$

$$= \frac{40 + j30}{100} = 0.4 + j0.3$$

→ Draw s-circle

→ Locate y_L

$$y_L = 1.6 - j1.2$$

→ Locate points A and B
(where s-circle intersects
the $1 + jb$ circle)

at A($1 + j1.04$), $y_s = -j1.04$

at B($1 - j1.04$), $y_s = +j1.04$

→ The required stub
admittance is:

$$Y_s = Y_0 y_s = \pm \frac{j1.04}{100}$$

$$Y_s = \pm 10.4 \text{ mS}$$

Example 11.7

(b) Distance between y_L and stub is:

$$l_A = \frac{\lambda}{2} - \frac{(62^\circ + 39^\circ)\lambda}{720^\circ}$$

$$l_A = 0.36\lambda$$


or $l_A =$

$$\frac{(180^\circ - 39^\circ) + (180^\circ - 62^\circ)}{(720^\circ)}\lambda$$

$$\rightarrow \boxed{l_A = 0.36\lambda}$$

$$l_B = \frac{(62^\circ - 39^\circ)\lambda}{720^\circ}$$

$$\boxed{l_B = 0.032\lambda}$$

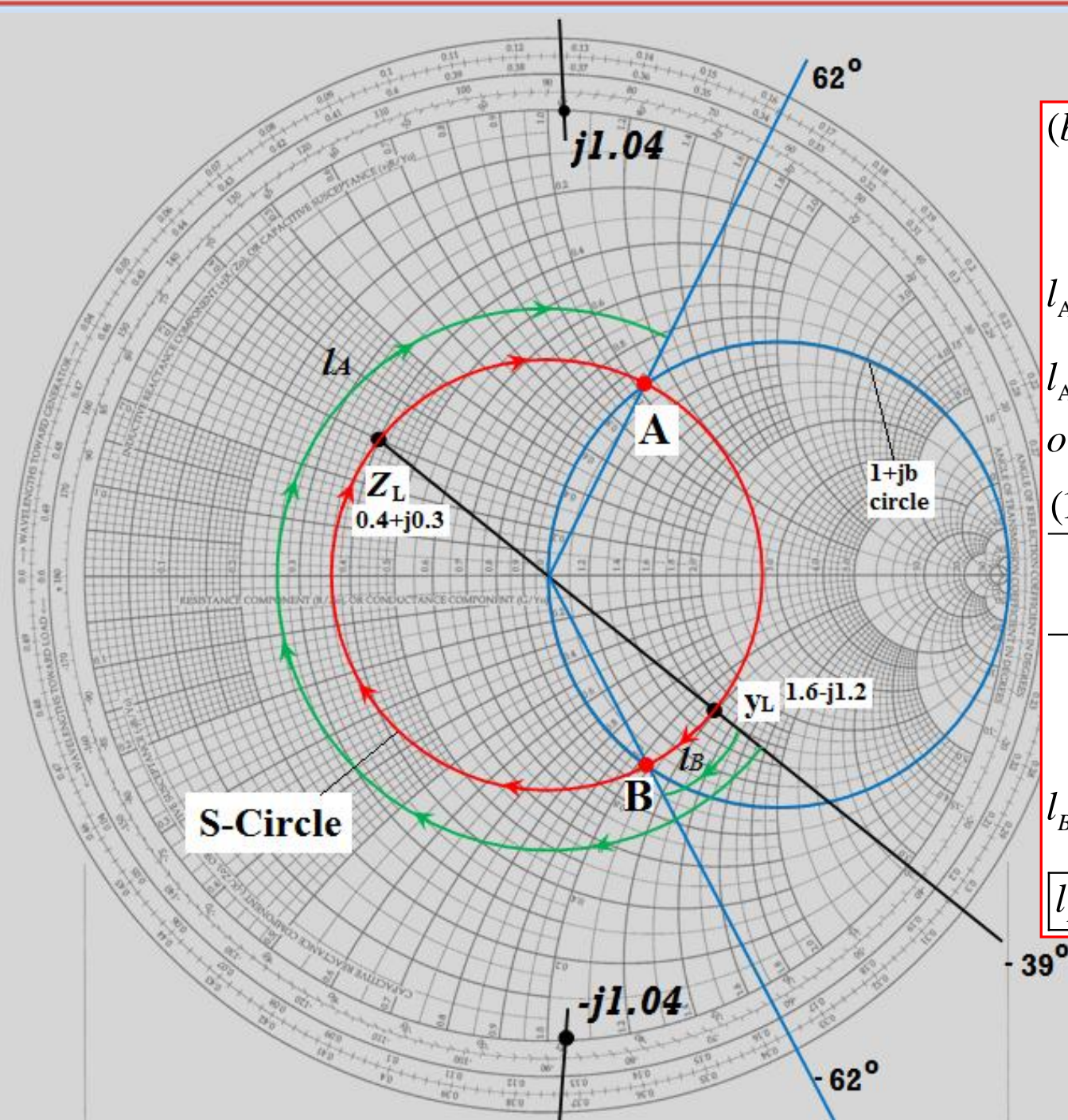

Example 11.7



(c) Stub Length

$$d_A = \frac{88^\circ}{720^\circ} \lambda$$

$$d_A = 0.1222 \lambda$$

$$d_B = \frac{(360^\circ - 88^\circ)}{720^\circ} \lambda$$

$$d_B = 0.3778 \lambda$$

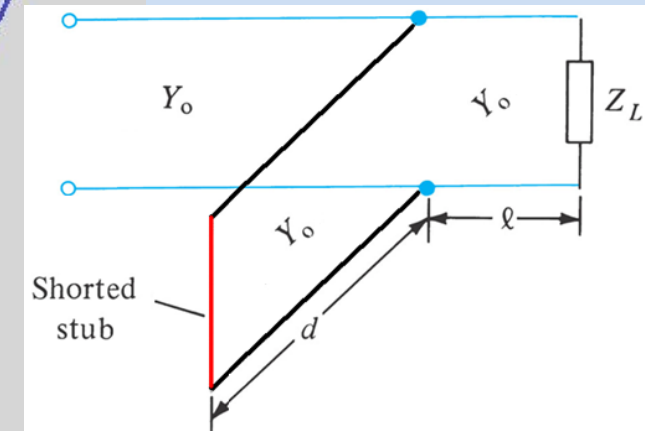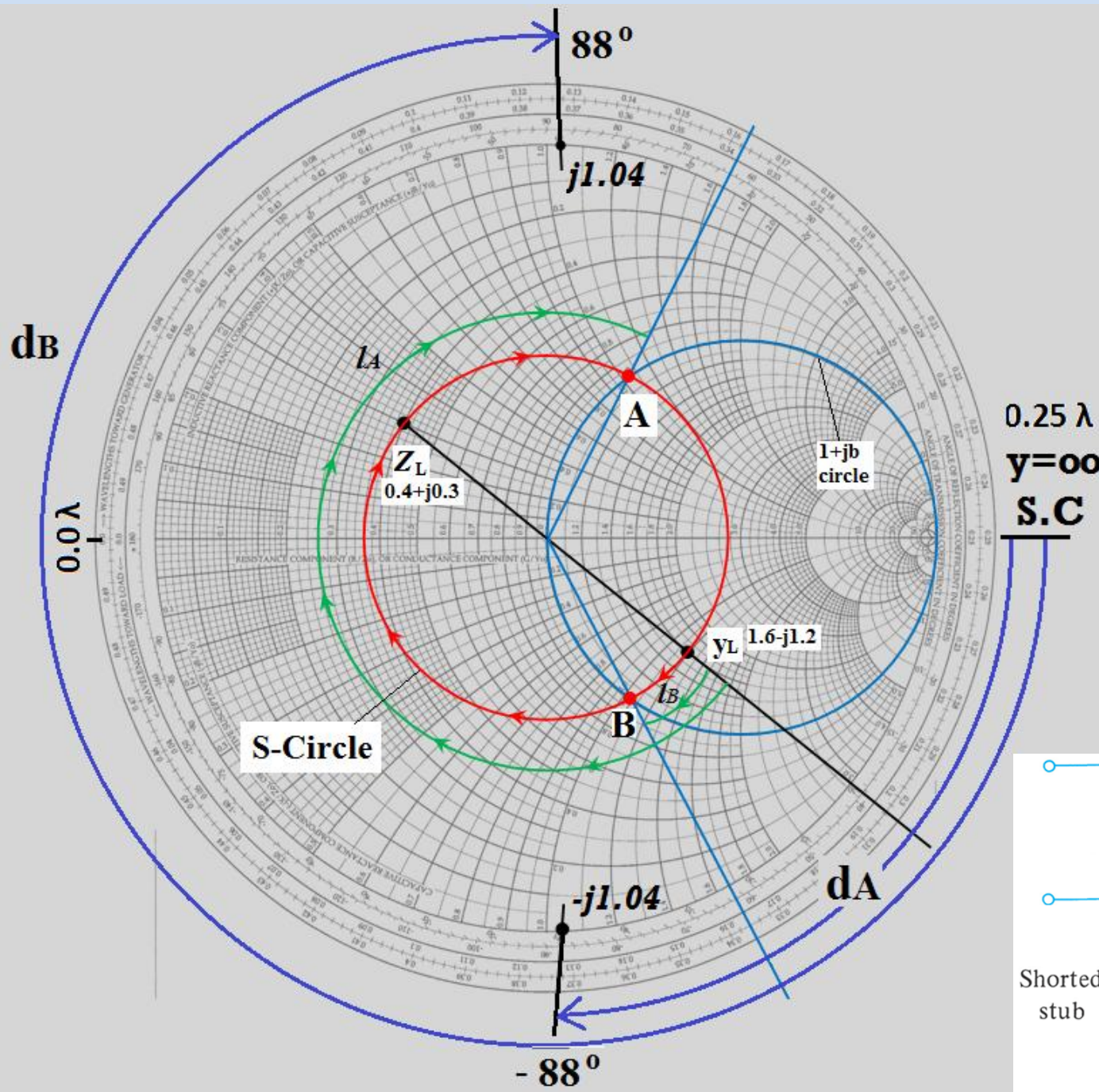

Transmission Line and Smith Chart - Tools

Software **TRLINE**


```
*** TRLINE ** VERSION 1H ***** Feb. 14, 2011 ***  
by Dr. C.W. Trueman, ECE Dept., Concordia University, Montreal.  
Click the mouse on any RED text string to an select action in this program.
```

Choose a transmission line circuit:

```
Transmission line with generator and load.  
Two transmission lines in series.  
Two transmission lines in series, with shunt load.  
Six transmission lines in series, with loads.  
Line branching to two loads.  
Quarter-wave transformer.  
Two-step quarter-wave transformer.  
Three-step quarter-wave transformer.  
Power splitter.  
Single-stub matching circuit.  
Double-stub matching circuit.  
Double-stub matching circuit with shifted load.  
Triple-stub matching circuit.  
Low-pass filter.  
Bandstop filter.  
Read a saved circuit from a .trl data file.
```


EXIT from the program.

Software **Smith V3.10**

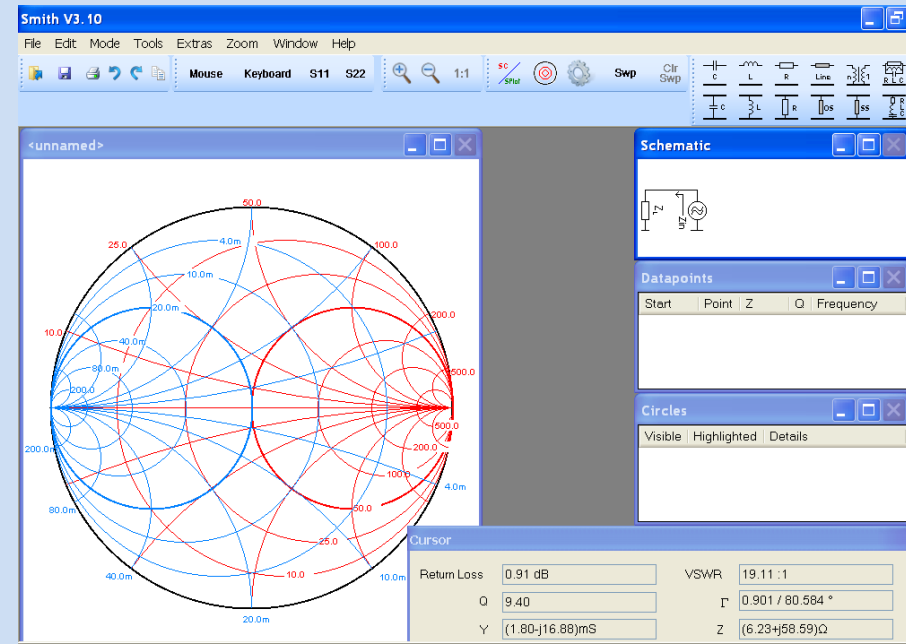


TRLINE - Example

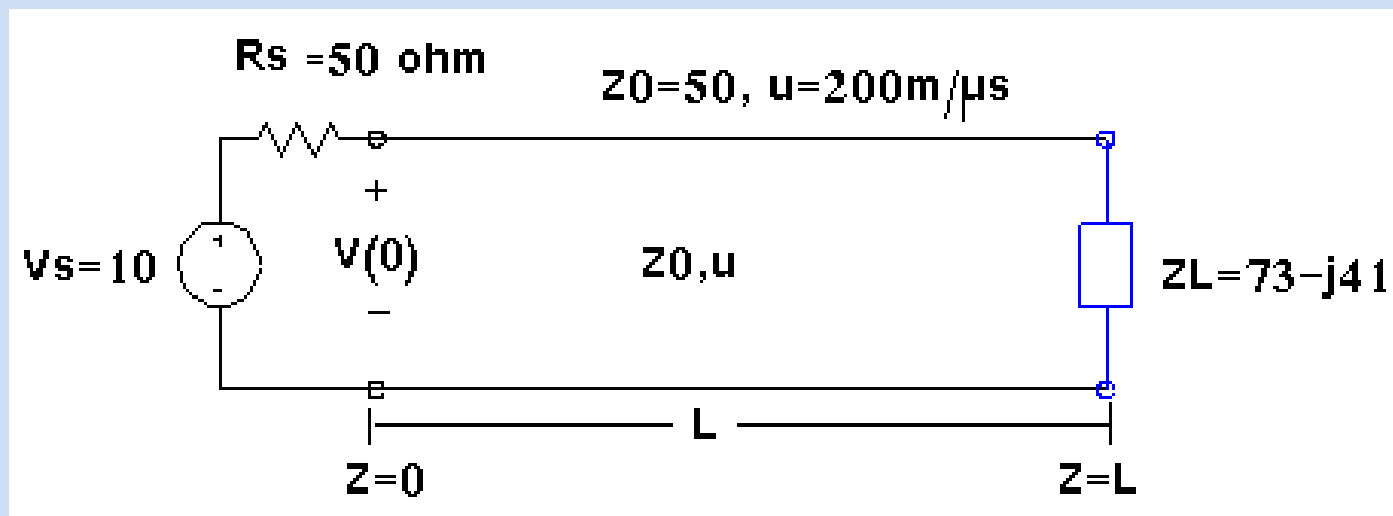Example: A radio-frequency generator at 100 MHz produces an open-circuit voltage of 10 volts amplitude and has an internal resistance of 50 ohms. It drives an antenna through a length of $L=7.7$ m of coaxial cable with characteristic resistance $R_0=50$ ohms and speed of travel $u=20$ cm/ns. The input impedance of the antenna is $Z_L=73-j41$ ohms.




TRLINE - Example

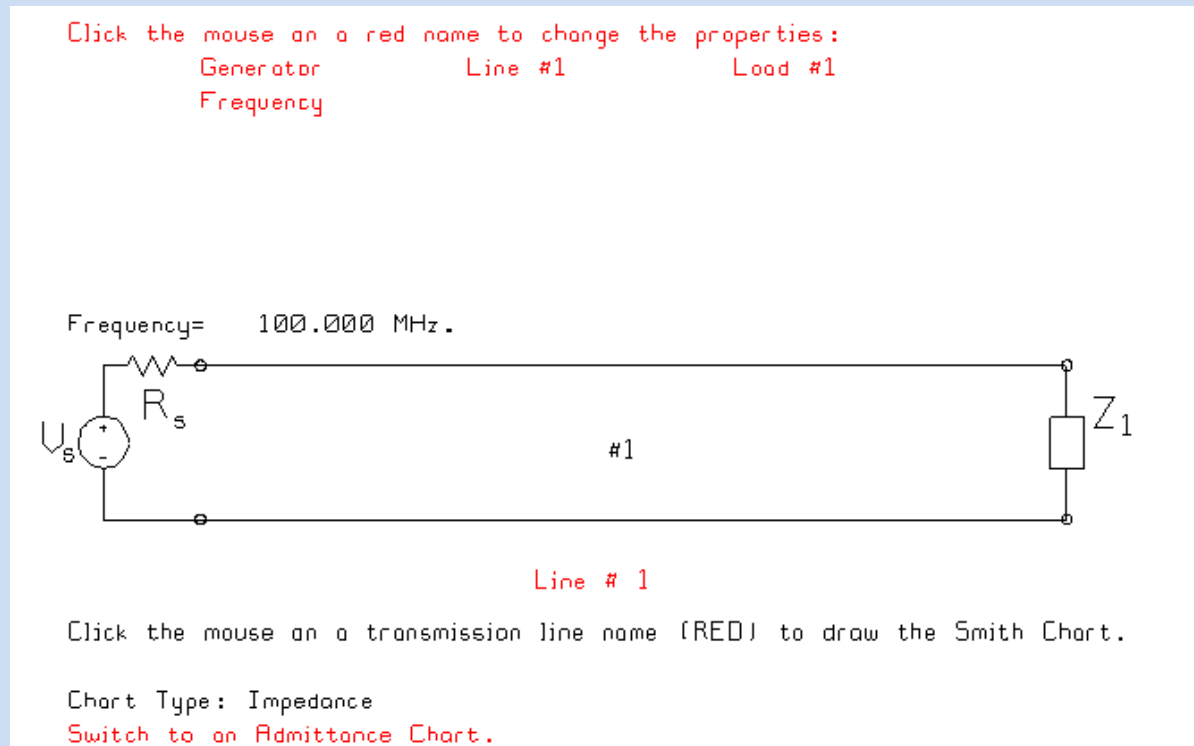- (1) Run “TRLINE.EXE”
- (2) Click the mouse on “Transmission line with generator and load”.
- (3) Enter Parameters of Generator, Line #1, Load #1.
- (4) Click the mouse on “Draw a Smith Chart”




TRLINE - Example

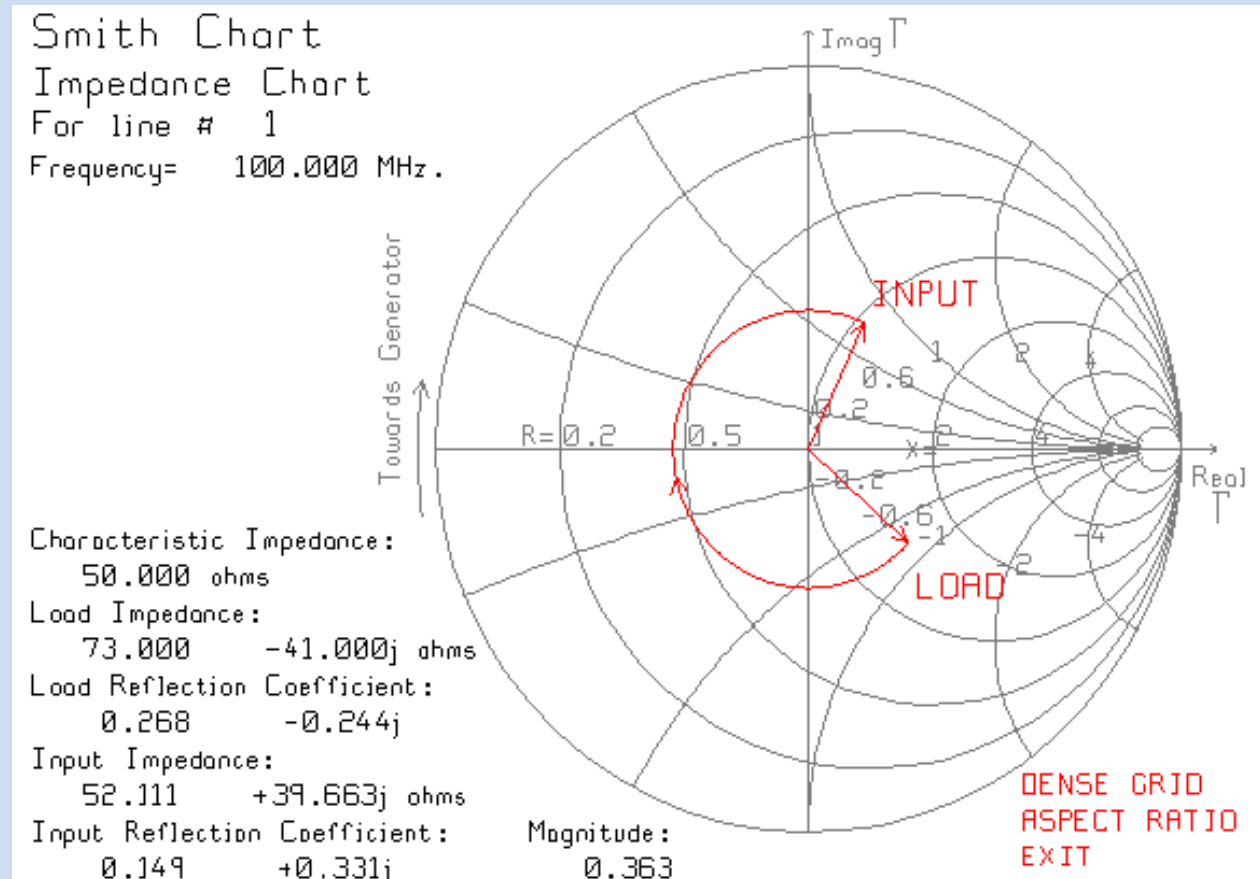- (5) Let the chart type "Impedance Chart", then to find the input impedance for the transmission line, click the mouse on "Line #1".



TRLINE - Example

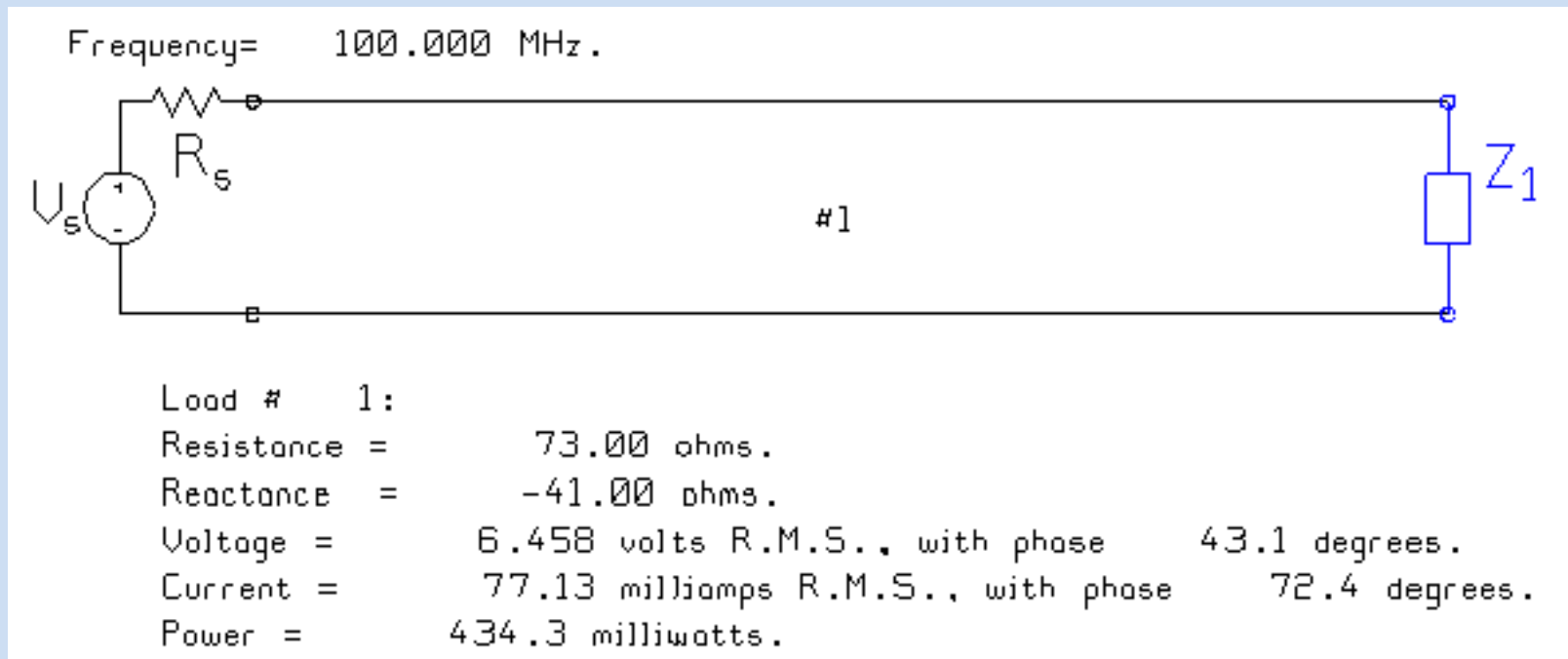(6) Exit Smith Chart, then click the mouse on “Find voltages, currents, and power”, then click “Load #1”




Smith Chart software - Example

Example: A 30m long lossless transmission line with $Z_0=50 \Omega$ operating at 2MHz is terminated with a load $Z_L=60+j40 \Omega$, $u=0.6c$ on the line. Use Smith software to find: The reflection coefficient, standing wave ratio and the input impedance.

- 1) run **Smith v2.00** software.
- 2) Choose DATAPOINT from Toolbox and then choose Keyboard, Fill in the Load Impedance $Z_L=60+j40$ and the frequency=2MHz then press OK to return to the main screen.
- 3) From the Toolbox choose series LINE, and fill the characteristic impedance of the line= 50Ω , and $\epsilon_r=2.777$ then press OK.
- 4) Note that $u = 0.6c = \frac{1}{\sqrt{\mu\epsilon}} = \frac{1}{\sqrt{\mu_0\epsilon_0\epsilon_r}} = \frac{1}{\sqrt{\epsilon_r}} c \Rightarrow \frac{1}{\sqrt{\epsilon_r}} = 0.6 \Rightarrow \epsilon_r = 2.7777$

Smith Chart software - Example

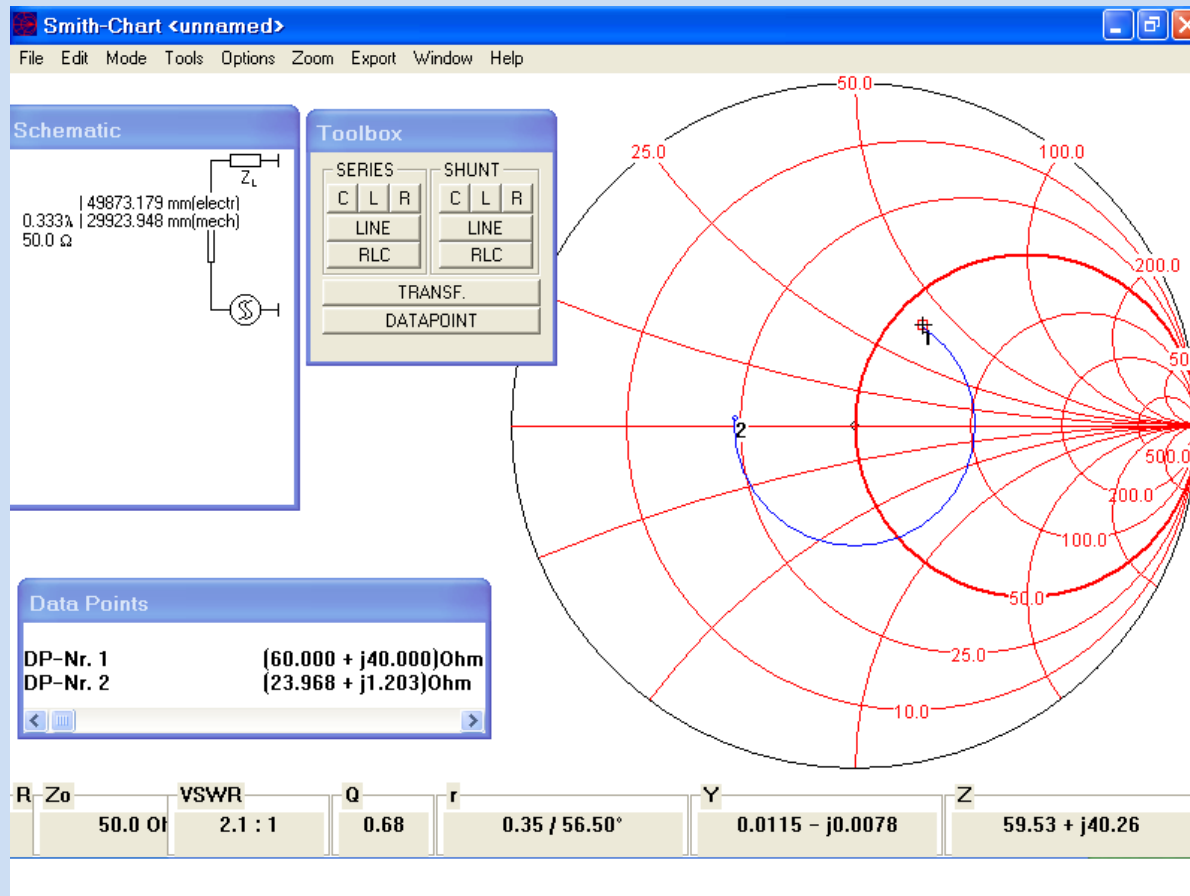- 5) move clockwise a distance toward generator equals 0.333λ .
 Note: $(\lambda = u/f = 0.6 \cdot 3 \cdot 10^8 / 2 \cdot 10^6 = 90\text{m})$, then the length of line $= 30\text{m} = 0.333 \lambda$.



Smith Chart software - Example

Now, Record the results:

- ❖ the input impedance is that at data point #2, $Z_{in} = 23.968 + j1.203$.
- ❖ to know the value of VSWR, put the mouse on any point in the circle, then $VSWR = 2.1$.
- ❖ To know the reflection coefficient, put the mouse pointer on data point #1, then record the reflection coefficient, or double click on data point # 1 then choose reflection coefficient, $\Gamma_L = 0.2 + j0.29 = 0.35/56^\circ$.