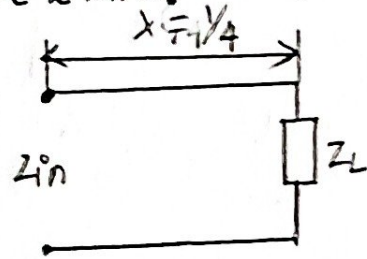


14. 5. Derive the expression for impedance matching using quarter wave transform. (Q-5 and Q-8).



$$Z_{in} = Z_0 \frac{Z_L + j Z_0 \tan \beta L}{Z_0 + j Z_L \tan \beta L}$$

$$l = \lambda/4 ; \beta l = \frac{2\pi}{\lambda} \times \frac{\lambda}{4}$$

$$\beta l = \frac{\pi}{2}$$

$$\tan \beta l = \tan \frac{\pi}{2} = \infty$$


$$Z_{in} = Z_0 \cdot \frac{Z_L + j Z_0 \tan(\pi/2)}{Z_0 + j Z_L \tan(\pi/2)} = Z_0 \frac{Z_0 \tan \beta l \left\{ \frac{Z_L}{\tan \beta l} + j Z_0 \right\}}{\tan \beta l \left\{ \frac{Z_0}{\tan \beta l} + j Z_L \right\}}$$

$$Z_{in} = Z_0 \left[\frac{\frac{Z_L}{\infty} + j Z_0}{\frac{Z_0}{\infty} + j Z_L} \right] = \left(\frac{j Z_0}{j Z_L} \right) \cdot Z_0$$

$\therefore Z_{in} = \frac{Z_0^2}{Z_L}$



Q6 Z_L is complex

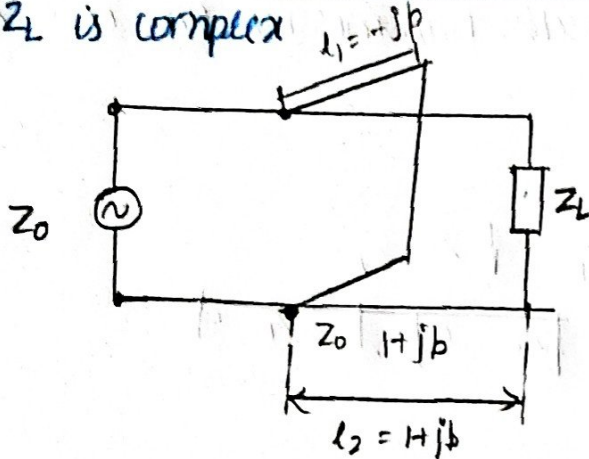

Q6 both the reflected waves are out of phase and equal in amplitude

→ Both reflected waves get cancelled

→ Reflection is zero

→ Impedance is Matched

$$Y = \frac{1}{Z_L} \Rightarrow g + jb$$

$$Y = 1 + jb$$

$$Y_{eq} = 1 + jb - j = 1$$

Q6 A lossless line has a characteristic impedance of 500Ω . Determine the reflection co-efficient of the receiving end impedance is $(800 + j10) \Omega$

$$Z_R = (800 + j10) \Omega; Z_0 = 500 \Omega; \Gamma_L = ?$$

$$\Gamma_L = \frac{Z_R - Z_0}{Z_R + Z_0} = \frac{800 + j10 - 500}{800 + j10 + 500} = \frac{300 + j10}{1300 + j10}$$

$$= \frac{300 \cdot 14 \angle 1.90}{1300 \cdot 0.3 \angle 0.44}$$

$$\boxed{\Gamma_L = 0.23 \angle 1.46}$$



11. Find the input impedance of lossless transmission line of length 0.2λ when the load is a short.

$$Z_{in} = ? ; Z_L \approx 0 (\because \text{short})$$

$$Z_{in} = \frac{(Z_0)^2}{Z_L}$$

$$Z_0 = \sqrt{Z_S \cdot Z_L}$$

$$Z_0 = 0 \quad \because Z_L = 0$$

For that load is short $Z_0 = 0$

$$\therefore Z_{in} = Z_0 \tan(\beta \cdot L)$$

$$= Z_0 \left[\frac{2\pi}{\lambda} \cdot L \right]$$

$$= Z_0 \left[\frac{2\pi}{\lambda} \cdot 0.2\lambda \right]$$

$$= Z_0 [2\pi \cdot 0.2]$$

$$= 0$$

$$\boxed{Z_{in} = 0}$$

7. A transmission line of length 0.3λ has a characteristic impedance of 50Ω and is terminated in a load impedance of $[100 + j150]\Omega$. Find the

- Voltage Reflection Co-efficient (Γ_L)
- Voltage Standing ~~of the line~~ Wave ratio
- Input impedance of the line

$$l = 0.3\lambda ; Z_L = [100 + j150]\Omega ; Z_0 = 50\Omega$$

$$a) \Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{100 + j150 - 50}{100 + j150 + 50} = \frac{50 + j150}{150 + j150} = \frac{158.11 \angle 71.5}{212.13 \angle 45}$$

$$\Gamma_L = \overset{\sqrt{|\Gamma|}}{0.74} \overset{\angle \theta}{\angle 26.5}$$

$$\Gamma_L = 0.66 + 0.33j$$

$$b) \frac{V_{max}}{V_{min}} = \frac{1 + |\Gamma|}{1 - |\Gamma|} = \frac{1 + 0.66}{1 - 0.66} = \frac{1 + 0.74}{1 - 0.7} = 6.69$$

$$VSWR = 6.7$$

$$c) Z_{in} = \frac{Z_0^2}{Z_L} = \frac{50^2}{100 + j150} = 7.69 - 11.5j$$

$$Z_{in} = 7.69 - 11.5j$$

$$14. Z_0 = 50 \Omega ; Z_L = (60 + j50) \Omega ; l = 0.4 \lambda$$

$$\bar{Z}_L = \frac{Z_L}{Z_0} = \frac{60 + j50}{50} = 1.2 + j1$$

$$\boxed{\bar{Z}_L = 1.2 + j1}$$

$$iv) \bar{Z}_{in} = 0.5 + j0.428$$

$$Z_{in} = \bar{Z}_{in} \cdot Z_0$$

$$= (0.5 + j0.428)(50)$$

$$= 25 + j21.4$$

$$i) VSWR = 2.4$$

$$ii) \Gamma_L = 0.42 \angle 54^\circ$$


$$iii) Y_L \neq \bar{Y}_L \cdot Z_0$$

$$\bar{Y}_L = 0.5 - j0.42$$

$$Y_L = \frac{1}{Z_L} = \frac{1}{(60 + j50) \Omega} = (1.8 - j8.19) \times 10^{-3}$$

$$= (1.8 - j8.2) \times 10^{-3} \Omega^{-1}$$

$$Y_L =$$
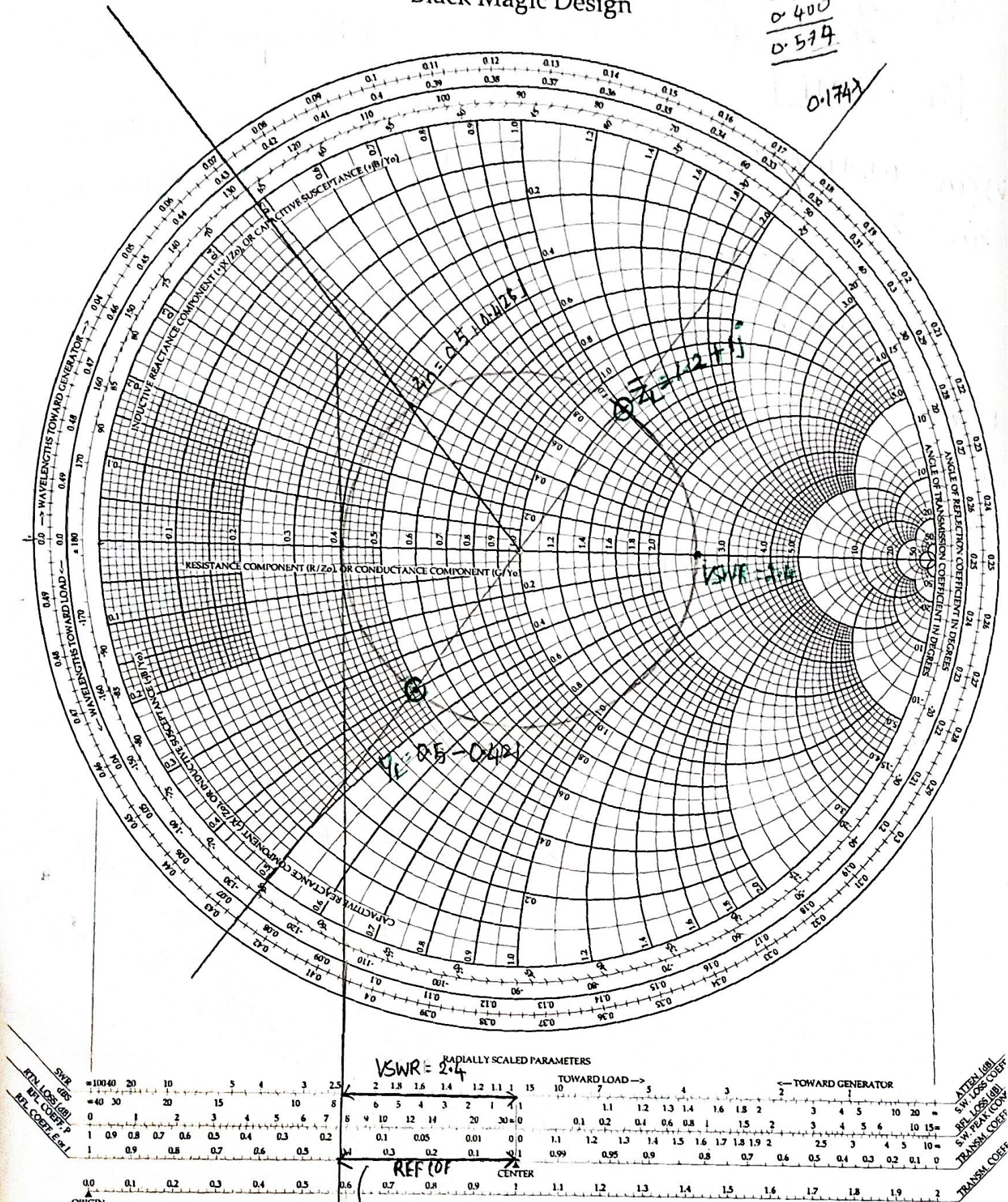
$$\begin{array}{r} 0.174 \\ 0.400 \\ \hline 0.574 \end{array}$$


$$(F_L) = 0.42 \underline{54'}$$