

SRM INSTITUTE OF SCIENCE AND TECHNOLOGY
Department of Electronics and Communication Engineering

21ECC311L-VLSI DESIGN LAB

Laboratory Manual



College of Engineering & Technology
SRM Institute of Science and Technology
Tiruchrappalli – 621 105,
Near Samamyapuram Toll Plaza,
Tamilnadu

**SRM Institute of Science and Technology Department of Electronics and
Communication Engineering**

Vision of the Department

1. To create and disseminate knowledge in the area of Electronics and Communication Engineering through national and international accredited educational process.
2. To facilitate a unique learning and research experience to the students and faculty.
3. To prepare the students as highly ethical and competent professionals.

Mission of the Department

1. Build an educational process that is well suited to local needs as well as satisfies the national and international accreditation requirements.
2. Attract the qualified professionals and retain them by building an environment that fosters work freedom and empowerment.
3. With the right talent pool, create knowledge and disseminate, get involved in collaborative research with reputed universities and produce competent grandaunts.

Program Educational Objectives (PEO)

Program Educational Objectives for the Electronics and Communication Engineering program describes accomplishments that graduates are expected to attain within a few years of graduation. Graduates will be able to:

PEO1: Establish themselves as successful and creative practicing professional engineers both nationally and globally in the related fields of Electronics and Communication Engineering.

PEO2: Apply the acquired knowledge and skills in solving real-world engineering problems; develop novel technology and design products, which are economically feasible and socially relevant.

PEO3: Develop an attitude of lifelong learning for sustained career advancement and adapt to the changing multidisciplinary profession.

PEO4: Demonstrate leadership qualities, effective communication skills, and to work in a team of enterprising people in a multidisciplinary and multicultural environment with strong adherence to professional ethics.

21ECC311L VLSI Design

| Sl. No. | Description of experiments | Session |
|---------------------------|---|---------|
| Software's: Xilinx vivado | | |
| 1 | Exp 1: Realization of Combinational and Sequential Circuits using gate level modeling | 1 |
| 2 | Exp 2: Realization of digital circuits using behavioral modeling | 2 |
| 3 | Exp 3: Design using FSM and ASM charts | 3 |
| 4 | Exp 4: Realization of VLSI Adders-I | 4 |
| 5 | Exp 5: Realization of VLSI Adders-II | 5 |
| 6 | Exp 6: Realization of VLSI Multiplier-I | 6 |
| 7 | Exp 7: Realization of VLSI Multiplier-II | 7 |
| 8 | Exp 8: Realization of RAM and ROM | 8 |
| 9 | Exp 9: Design and Analysis of CMOS inverter using HSPICE | 9 |
| 10 | Exp 10: Design and analysis of 4- input Dynamic NAND gate using HSPICE | 10 |

1.Evaluation Scheme

| Component | Assessment Tool | Weightage |
|------------------------------|---|-----------|
| Practical | Course Learning Assessment P1 | 5% |
| | Course Learning Assessment P2 | 7.5% |
| | Course Learning Assessment P3 | 7.5% |
| | Course Learning Assessment P4 (Model Practical Exam and Mini Project) | 5% |
| End-Semester Lab Examination | | 25% |

2.Assessment Method – Lab Report

| Component | Assessment Tool | Weightage |
|------------------------|--------------------------------------|-----------|
| Lab Report – Practical | Prelab and Post lab | 10 |
| | Design, HDL Code, In-Lab Performance | 15 |
| | Simulation and Results | 10 |
| | Lab Report | 05 |
| | Total | 40 |

□Soft copy of manual (student's Copy) will be posted in the Google classroom. □Lab report format should follow the following details

- Aim
- Software required
- Pre-Lab answers
- Circuit Diagram, Truth table, Boolean Expression for each problem statement
- Program code
- Test bench code
- Simulated output
- Post-Lab answers
- Results

Laboratory Report Cover Sheet

| |
|---|
| SRM INSTITUTE OF SCIENCE AND TECHNOLOGY College of Engineering and Technology Department of Electronics and Communication Engineering |
| 21ECC311L VLSI Design V Semester, 2024-2025 (Odd Semester) |

Name:

Register No.:

Title of Experiment:

Date of Conduction:

Date of Submission:

| Particulars | Max. Marks | Marks Obtained |
|--------------------------------------|------------|----------------|
| Pre-Lab and Post Lab | 10 | |
| Design, HDL Code, In-Lab Performance | 15 | |
| Output verification & viva | 10 | |
| Lab Report | 05 | |
| Total | 40 | |

REPORT VERIFICATION

Staff Name :

Signature:

Lab Experiment #1

Realization of Combinational and Sequential Circuits Using GateLevel and Dataflow Modeling

1.1 Objective: To learn the design of combinational and sequential circuits using Gate-Level and Dataflow modeling in Verilog then simulating and synthesizing using Xilinx vivado tools

1.2 Software tools Requirement

Software's: Xilinx vivado

1.3 Prelab Questions

(write pre lab Q & A in an A4 sheet)

1. List the types of design methodologies for digital design with an example?
2. Give the difference between module and module instance.
3. What are built in gate primitives?
4. Give the use of net, reg. and wire data types.
5. Declare the following variables in Verilog:


1.4 Problem : Write a Verilog code to implement Ripple Carry Adder.

The following points should be taken care of:


1. Use assign statement to design sub module half adder
2. Use gate primitives to design full adder using half adder
3. Construct the top module 4-bit ripple carry adder using 1-bit full adder

Logic Diagram – Problem 1


Half adder:

 

Full adder:

 

Ripple Carry Adder

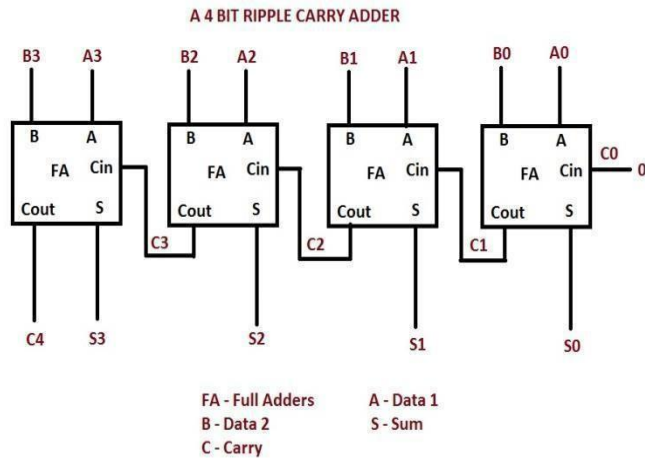

Verilog Code - Problem 1

1.(a) HALF ADDER USING DATA FLOW MODEL

```
module Half_adder(s, cout, x, y);
output s; output
cout; input x;
input y; assign
s=x^y; assign
cout=x&y;
endmodule
```

// TEST BENCH

```
module half_adder_tb_v;
// Inputs
reg x; // reg
y; //Outputs

wire s; wire cout;
// Instantiate the Unit Under Test (UUT)
Half_adder uut (.s(s), .cout(cout), .x(x), .y(y) );
initial begin // Initialize Inputs
x = 0;          y = 0;
Wait 100 ns for global reset to finish #100; x=0; y=1;

#100; x=1; y=0; #100; x=1; y=1; Add
stimulus here

end
endmodule
```

1.(b) FULL ADDER USING STRUCTURAL MODEL

```
module Full_adder(sum, carry, x, y, cin);
output sum; output carry; input x; input
y; input cin; wire w1,w2,w3;
Half_adder h1(w1,w2,x,y);
Half_adder h2(sum,w3,w1,cin);
or g1(carry,w2,w3);
endmodule
```

```

// TEST BENCH
module full_adder_tb_v;
// Inputs
reg x; reg y; reg cin;
// Outputs
wire sum; wire carry;
// Instantiate the Unit Under Test (UUT)
Full_adder uut (.sum(sum), .carry(carry), .x(x), .y(y), .cin(cin)); initial begin
//Initialize Inputs x = 0; y = 0; cin = 0; Wait 100 ns for global reset to finish #100; x=0;
y=0; cin=1;
// #100; x=0; y=1; cin=0; #100; x=0; y=1; cin=1; #100; x=1; y=0; cin=0; #100; x=1; y=0;
cin=1; #100; x=1; y=1; cin=0; #100; x=1; y=1; cin=1;
//Add stimulus here
end
endmodule

```

1.(c) RIPPLE CARRY ADDER USING 1-BIT FULL ADDER

```

module ripple_carry_adder(S, cout, A, B, cin);
output [3:0]S; output cout; input [3:0]A; input
[3:0]B;
input cin;

```

```

wire c1,c2,c3;
full_adder f1(S[0],c1,A[0],B[0],cin);
full_adder f2(S[1],c2,A[1],B[1],c1);
full_adder f3(S[2],c3,A[2],B[2],c2);
full_adder f4(S[3],cout,A[3],B[3],c3);
endmodule


```

```


// TEST BENCH
module ripple_carry_adder_tb_v;
// Inputs
reg [3:0] A; reg [3:0] B; reg cin;
// Outputs wire [3:0] S;
wire cout;
// Instantiate the Unit Under Test (UUT) ripple_carry_adder uut (.S(S),
.cout(cout), .A(A), .B(B), .cin(cin)); initial begin
//Initialize Inputs A = 0; B = 0; cin = 0;
//Wait 100 ns for global reset to finish #100; A=0; B=0; cin=1;
#100; A=0; B=1; cin=0; #100; A=0; B=1; cin=1; #100; A=1; B=0; cin=0; #100; A=1;
B=0; cin=1; #100; A=1; B=1; cin=0; #100; A=1; B=1; cin=1;
//Add stimulus here End
endmodule

```


Waveforms – Problem 1

 

Half Adder using Data Flow Model

 

Full Adder using Structural Model

 

Ripple Carry Adder using 1-Bit Full Addder

1.5 Result:

Thus, the design of combinational and Sequential logic circuits was simulated in Verilog and synthesized using Xilinx vivado tools.

Lab Experiment #2

Realization of Digital Circuits Using Behavioral Modeling

2.1 Objective: To realize the design of digital circuits in Verilog using behavioral and switch level modelling then simulating and synthesizing using Xilinx vivado tools.

2.2 Software tools Requirement

Software's: Xilinx vivado

2.3 Prelab Questions


(write pre lab Q & A in an A4 sheet)

1. Write the difference between initial and always block.
2. List the Reduction and Logical Operators.
3. Give the use of Blocking and Nonblocking statments.
4. Differentiate case, casex and casez statements.

2.4.1 Problem 1: Write a Verilog code to implement Flip flops. The following points should be taken care of:

1. Use If statement to design positive edge triggered D flip
2. Use case statement to design negative edge triggered T flip flop

Logic Diagram

 

1.(a) POSITIVE EDGE TRIGGERED D FLIPFLOP USING IF STATEMENT

```
module dff(q, qbar, d, clk, clear);
output q;
output qbar;
input d; input
clk; input
clear; reg q,
qbar;
always@(posedge clk or posedge clear)
begin
if(clear==
1) begin q
<= 0; qbar
<= 1; end
else begin
q <= d;
qbar = !d;
end
end
endmodule
```

// TEST BENCH

```
module
dff_tb_v; //
Inputs reg d; reg
clk; reg clear; //
Outputs wire q;
wire qbar;

// Instantiate the Unit Under Test (UUT)
dff uut ( .q(q),
.qbar(qbar),
.d(d),
.clk(clk),
.clear(clear)
);
initial begin // Initialize
Inputs d = 0; clk =
0; clear = 1;
// Wait 100 ns for global reset to finish
#100 d = 0; clear = 0;
#100 d = 1; clear = 0;
#100 d = 1; clear = 1;
// Add stimulus here
end
always #50 clk=~clk;
endmodule
```


1.2) NEGATIVE EDGE TRIGGERED T FLIPFLOP USING CASE STATEMENT

```
module tffcase(q, clk, clr, t);
output q; input clk; input
clr;
input t;
reg q;
initial
q=0;
always@(negedge clk)
begin
case({clr,t})
2'b10: q=0;
2'b00: q=q;
2'b01:
q=~q;
endcase end
endmodule
```


// TEST BENCH

```
module tffcase_tb_v;
// Inputs
reg clk; reg clr; reg t; //Outputs
wire q;
//Instantiate the Unit Under Test (UUT) tffcase uut (.q(q),.clk(clk),.clr(clr),.t(t)); initial begin
//Initialize Inputs clk = 0; clr = 1; t = 0;
//Wait 100 ns for global reset to finish #100; clr=0;
#100; clr=0; t=1;
//Add stimulus here
end
always #50
clk=~clk;
endmodule
```

Waveforms – Problem 1

 

D Flipflop using IF statement

 

T Flipflop using CASE statement

2.4.2 Problem 2: Write a Verilog code to implement Counters. The following points should be taken care of:

1. Use behavioral model to design Up-Down Counter. When mode = '1' do up counting and for mode = '0' do down counting.
2. Use behavioral model to design Mod-N counter.
3. Design SISO registers using behavioral model.


Logic Diagram – Problem 2 Up-Down Counter:

| Current State | | | | Next State Count UP | | | | Next State Count Down | | | |
|---------------|----|----|----|---------------------|-----|-----|-----|-----------------------|-----|-----|-----|
| C3 | C2 | C1 | C0 | C3+ | C2+ | C1+ | C0+ | C3+ | C2+ | C1+ | C0+ |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 1 |
| 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 0 | 0 | 1 | 1 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 1 | 0 | 1 | 0 | 0 | 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 | 0 | 1 | 0 | 1 | 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 | 0 | 1 | 1 | 0 | 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 0 | 0 | 1 | 1 | 1 | 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 | 1 | 0 | 1 | 0 | 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 1 | 0 | 1 | 1 | 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 1 | 1 | 0 | 0 | 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 | 1 | 1 | 0 | 1 | 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 | 1 | 1 | 1 | 0 | 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 0 |

Mod-N Counter:

| Count | Qd | Qc | Qb | Qa |
|----------------|----|----|----|----|
| (Start) 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 2 | 0 | 0 | 1 | 0 |
| 3 | 0 | 0 | 1 | 1 |
| 4 | 0 | 1 | 0 | 0 |
| 5 | 0 | 1 | 0 | 1 |
| 6 | 0 | 1 | 1 | 0 |
| 7 | 0 | 1 | 1 | 1 |
| 8 | 1 | 0 | 0 | 0 |
| 9 | 1 | 0 | 0 | 1 |
| (New Cycle) 10 | 0 | 0 | 0 | 0 |

SISO Register:

 

Verilog Code - Problem 2

2. UP DOWN COUNTER USING BEHAVIOURAL MODEL

```
module updownctr(q, clr, clk, mode);
output reg [3:0] q;
input clr; input clk;
input          mod;
always@(posedge clk)
begin case({clr,mod})
2'b11 : q=0;
2'b10 : q=0;
2'b01 : q=q+1;
2'b00 : q=q-1;
endcase end
endmodule
```

// TEST BENCH

```
module updownctr_tb_v;
// Inputs
reg clr; reg clk; reg mod; //Outputs
wire [3:0]q;

//Instantiate the Unit Under Test (UUT) updownctr uut (.q(q),.clr(clr),.clk(clk),.mod(mod));
initial begin // Initialize Inputs clr = 1; clk = 0; mod = 1;
//Wait 100 ns for global reset to finish #100; clr=0;
#1000; mod=0;
//Add stimulus here
end always #50
clk=~clk;
endmodule
```

2.(2) Mod N-COUNTER USING BEHAVIOURAL MODEL

```
module modN_ctr
# (parameter N = 10,
parameter WIDTH = 4)
( input  clk,
```

```

input      rstn,      output
reg[WIDTH-1:0]      out);
always @ (posedge clk) begin
if (rstn) begin
out <= 0; end
else begin if
(out == N-1)
out <= 0;
else out <=
out + 1; end
end
endmodule

```

// TEST BENCH

```

module modncounter_tb_v;

// Inputs
reg clk;
reg rstn;

// Outputs
wire [3:0] out;

// Instantiate the Unit Under Test (UUT)
modN_ctr uut (
.clk(clk),
.rstn(rstn),
.out(out)
); initial begin //
Initialize Inputs
clk = 1;rstn = 1;
// Wait 100 ns for global reset to finish
#100 rstn=0; // Add
stimulus here end
lways #50
clk=~clk;
endmodule

```

2.(3) SISO REGISTER USING BEHAVIOURAL MODEL

```

module siso_register(shift_out, shift_in, clk);
input shift_in; input clk; output shift_out;
reg shift_out; reg [2:0] data; always
@(negedge clk)
begin
data[0] <= shift_in ;
data[1] <= data[0];
data[2] <= data[1];
shift_out <= data[2];
end
endmodule

```




SISO register using behavioral modelling

2.2 Post Lab :

Write a Verilog HDL Code to implement a SIPO and PIPO shift registers.

2.3 Result:

Thus, the design of Digital circuits using behavioral and Switch level modelling is simulated in Verilog and synthesized using EDA tools.

Lab Experiment #3

Design of Finite State Machine (FSM) and Algorithmic State Machine

3.1 Objective:

To learn the design of Finite State Machine (FSM) and Algorithmic State Machine (ASM) for any application in Verilog, the simulating and synthesizing using Xilinx vivado tools.

3.2 Tools Required:

Software's: Xilinx vivado


3.3 Pre Lab Questions:

1. Draw the simple model of FSM.
2. What is the basic Algorithm of Sequence Detector?
3. List the difference between Mealy and Moore Model.
4. What is ASM Chart and what are its main components?

3.4.1 Problem:

1. Implement Sequence recognizer for detecting three successive 1's using Mealy Model (Behavioural Modelling).

Mealy model for 111 Detector (FSM):

 

Verilog code for Mealy Model FSM: (Behavioral Modelling)

```
module fsm_111_mealey(o,reset,a,clk); output reg o; input
reset,a,clk; reg[1:0]pre_s, nxt_s; initial begin
pre_s=2'b00; end
always@(posedge clk)
begin if(reset==1) begin
pre_s=2'b00; o=0;end else
begin case(pre_s)
2'b00:begin if (a==1)begin o=0; nxt_s=2'b01;pre_s=nxt_s; end
```

```

        else begin o=0; nxt_s=2'b00;pre_s=nxt_s; end end
2'b01:begin if (a==1)begin o=0; nxt_s=2'b10;pre_s=nxt_s; end
        else begin o=0; nxt_s=2'b00;pre_s=nxt_s; end end
2'b10:begin if (a==1)begin o=1; nxt_s=2'b00;pre_s=nxt_s; end
        else begin o=0; nxt_s=2'b00;pre_s=nxt_s; end end
        default:pre_s2'b00
    ; endcase end

end
endmodule

```


Test Bench:

```


module fsm_mealy_111_tb_v;
// Inputs
reg reset;
reg a; reg
clk; //
Outputs
wire o;
// Instantiate the Unit Under Test (UUT)
fsm_mealy_111 uut (
.o(o),
.reset(reset),
.a(a),
.clk(clk)
); initial begin //
Initialize Inputs
reset = 1; a = 1;
clk = 1;
    // Wait 100 ns for global reset to finish
    #100;
        reset = 0;
a = 1; #100;
reset = 0; a =
1;    #100;
reset = 0; a =
1;    #100;
reset = 0; a =
0;    #100;
reset = 0; a =
1; #100;
    // Add stimulus here end
    always #50 clk=~clk;
endmodule

```

Simulation Result:

 


 3.4.2 Consider the following state graph of a sequential network which has both Mealy and Moore outputs. The outputs Y1 and Y2 are the Mealy outputs and so should be conditional outputs. The Ya, Yb, and Yc are the Moore outputs so they should be part of state box. Input X can either be “0” or “1” and hence it should be part of the decision box.



Draw the ASM Chart for the above state graph and implement using Verilog.

ASM Chart:

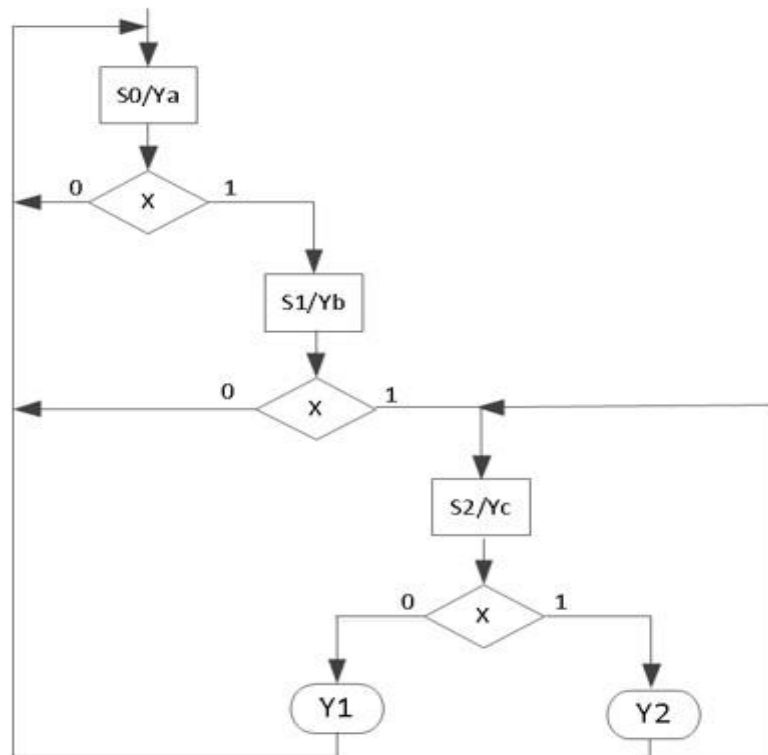

Verilog Program:

```
module asm (input clk, input x, output reg ya, output reg yb, output reg yc, output
reg y1, output reg y2);
reg [1:0] state, nextstate;
parameter [1:0] S0=0, S1=1, S2=2;
always @(posedge clk)// always block to update state state <= nextstate;

always @(state or x) // always block to compute both Mealy output & next
state begin    y1 = 1'b0; y2 = 1'b0; case (state) S0: if(x)    nextstate = S1;
else    nextstate = S0;
S1: if(x)
nextstate = S2;
else    nextstate
= S0; S2: if(x)
begin
y2 = 1'b1;
nextstate = S1; end
else begin
y1 = 1'b1;    nextstate = S0; end default:nextstate
= S0;    endcase end always @(state) // always block to
compute Moore output    begin ya = 1'b0; yb = 1'b0;
yc = 1'b0;    case(state) //begin
S0: ya = 1'b1;
S1: yb = 1'b1;
S2: yc =
1'b1; //end
default: begin
ya = 1'b0; yb
= 1'b0; yc =
1'b0; end
endcase
end

endmodule
```

Test Bench: module


```
asm_tb_v;
// Inputs
reg clk;
```

```

reg x; //
Outputs
wire ya;
wire yb;
wire yc;
wire y1;
wire y2;
// Instantiate the Unit Under Test (UUT)
asm uut ( .clk(clk),
.x(x),
.ya(ya),
.yb(yb),
.yc(yc),
.y1(y1), .y2(y2)
); initial begin //
Initialize Inputs x
= 1; clk = 1;
// Wait 100 ns for global reset to finish
#100;
    x = 1;
#100;
    x = 1;
#100;
    x = 1;
#100;
    x = 0;
#100;
// Add stimulus here
end always #50
clk=~clk;
    // Add stimulus
here endmodule

```

Output:

 

3.5 Post lab Questions:

1. Write Verilog code to implement an FSM using Moore Machine.

3.6 Result:

All the FSM Logic and ASM logic were executed and verified.

Lab Experiment # 4

Realization of Carry Look-Ahead Adder

4.1 Objective: To design and simulate the carry look-ahead adder (4-bit) in verilog and synthesize using Xilinx vivado tools.

4.2 Software tools Requirement

Software's: Xilinx vivado

4.3 Prelab Questions

(Write pre lab Q & A in an A4 sheet)

1. Write the expression for Propagate and generate term in a CLA.
2. List the efficient method for implementing 64- adder using CLA technique?

4.4 Problem: Write a Verilog code to implement the 4-bit Carry Look-ahead adder using structural model.

Logic Diagram:

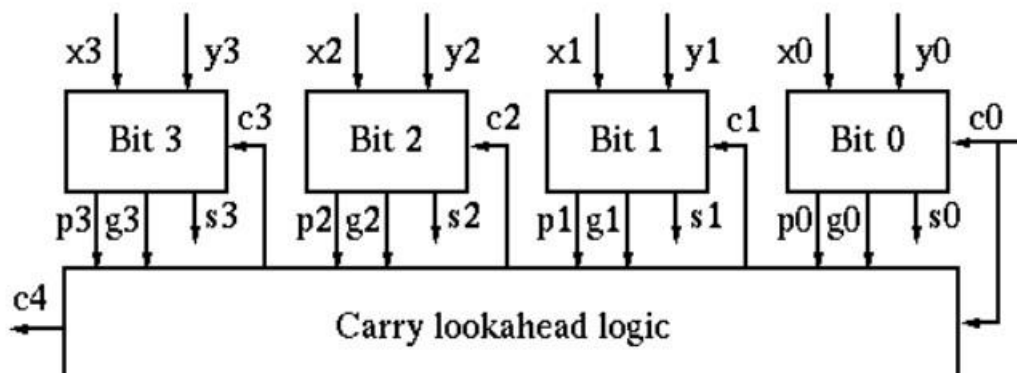


Fig. 4.1: 4-bit Carry Look-ahead Adder Source

code:

```
Module CLA_4bit(sum,c_4,a,b,c_0);
input [3:0]a,b;
input c_0; output
[3:0]sum; output
c_4;
wire
p0,p1,p2,p3,g0,g1,g2,g3;
wire c1,c2,c3,c4; assign
p0=a[0]^b[0], p1=a[1]^b[1],
p2=a[2]^b[2],
p3=a[3]^b[3], g0=a[0]&b[0],
g1=a[1]&b[1], g2=a[2]&b[2],
g3=a[3]&b[3]; assign
c1=g0|(p0&c_0),
c2=g1|(p1&g0)|(p1&p0&c_0)
,
```

```

c3=g2|(p2&g1)|(p2&p1&g0)|(p2&p1&p0&
c_0),
c4=g3|(p3&g2)|(p3&p2&p1&g1)|(p3&p2&
p1&g0)|(p3&p2&p1&p0&c_0);
assign
sum[0]=p0^c_0,
sum[1]=p1^c1,
sum[2]=p2^c2,
sum[3]=p3^c3,
c_4=c4;
endmodule

```

Test bench:


```

module carry_lookahead_adder_tb ();
parameter WIDTH = 3;
reg [WIDTH-1:0] r_ADD_1 = 0;
reg [WIDTH-1:0] r_ADD_2 = 0;
wire [WIDTH:0] w_RESULT;
CLA_4bit #(WIDTH(WIDTH)) carry_lookahead_inst
(.i_add1(r_ADD_1), .i_add2(r_ADD_2),
.o_result(w_RESULT) );

initial begin #10;
r_ADD_1 =
3'b000; r_ADD_2
= 3'b001;
#10; r_ADD_1 =
3'b010; r_ADD_2
= 3'b010;
#10; r_ADD_1 =
3'b101; r_ADD_2
= 3'b110;
#10; r_ADD_1 =
3'b111;
_ADD_2 = 3'b111;
#10;
end
endmodule // carry_lookahead_adder_t

```


Simulation Waveform:

 

Simulation waveforms of carry look ahead adder

4.5 Post Lab:

1. Compare the area, delay and power report of ripple carry & carry look-ahead adder in Xilinx ISE. Create a comparison chart and justify the results.
2. List the application of CLA in VLSI Design.
3. Prepare the synthesis Chart for a 4-bit CLA.
4. Can retiming mechanism improve the speed further in CLA architecture?

4.6 Result

Thus, the design of 4-bit carry look-ahead adder circuit was simulated in Verilog and synthesized using Xilinx vivado tools.

Lab Experiment # 5

Realization of Carry Skip Adder

5.1 Objective: To design and simulate the carry skip adder (4-bit) in Verilog and synthesize using Xilinx vivado tools.

5.2 Software tools Requirement Equipment's:
Software's: Xilinx vivado


5.3 Pre Lab Questions

(Write pre lab Q & A in an A4 sheet)

1. Why Carry-Skip adder has the same critical path as regular Carry-Ripple adder.
2. List the efficient method for implementing 16 Bit - adder using Carry-Skip technique?

5.4 Problem: Write a Verilog code to implement the 4-bit Carry Look-ahead adder using structural model.

Logic Diagram:

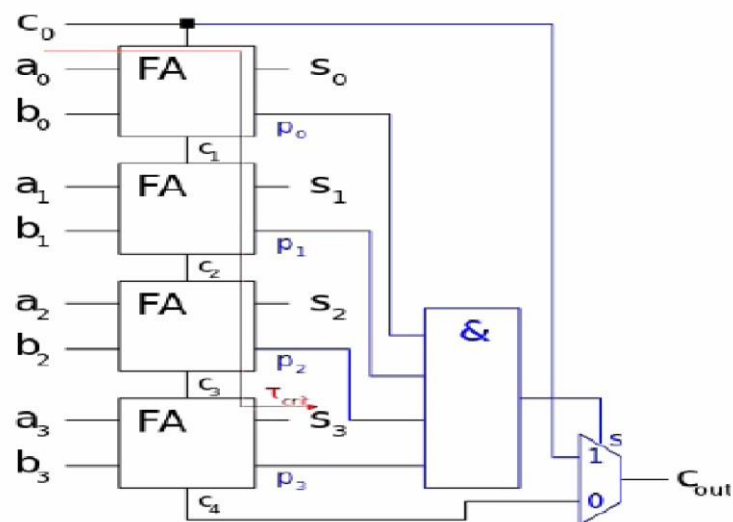

4-bit Carry Look-ahead Adder

Source code:

```

module carry_skip_4bit(a, b,
cin, sum, cout);
input [3:0] a,b; input cin; output [3:0] sum;
output cout; wire [3:0] p; wire c0; wire bp;
ripple_carry_4_bit rca1 (a[3:0],b[3:0],cin,
sum[3:0],c0); propagate_p p1(a, b, p, bp); mux2X1
m0(c0,cin,bp,cout); endmodule

```

```

module propagate_p(a,b,p,bp);
input [3:0] a,b; output [3:0] p; output
bp; assign p= a^b;//get all propagate
bits assign bp= &p;// and p0p1p2p3
bits

```


```
endmodule
```

```
module ripple_carry_4_bit(a, b, cin, sum, cout);  
input [3:0] a, b; input cin;  
wire c1, c2, c3; output [3:0]  
sum; output cout; full_adder  
fa0(a[0], b[0], cin,  
sum[0], c1); full_adder  
fa1(a[1], b[1], c1,  
sum[1], c2); full_adder  
fa2(a[2], b[2], c2,  
sum[2], c3); full_adder  
fa3(a[3], b[3], c3,  
sum[3], cout);  
endmodule
```

TEST BENCH:

```
module  
carry_skip_4bit_addertb; wire  
[7:0]Y; wire carryout; reg  
[7:0]A,B; reg carryin;  
carry_skip_4bit csa1 (Y,carryout,A,B,carryin);  
initial begin  
$display("RSLT\tA\tB\tCYIN\tCYOUT\tSU  
M");  
//A = 4'b0101; B = 4'b1101; carryin = 0; #50; // Set inputs and add delay  
A = 0; B = 0; carryin = 0; #50; // Set inputs and add delay  
A = 3; B = 2; carryin = 1; #50; // Set inputs and add delay  
A = 7; B = 10; carryin = 0; #50; // Set inputs and add delay  
A = 15; B = 15; carryin = 1; #50; // Set inputs and add delay  
A = 255; B = 55; carryin = 0; #50; // Set inputs and add delay  
A = 255; B = 255; carryin = 1; #50; // Set inputs and add delay  
/*  
//if ( (carryout == 1 ) && (Y === 4'b0010) )  
if ( (carryout == 1 ) && (Y === 2) )  
$display("PASS\t%p\t%p\t%d\t=\t%d\p%p",A,B,carryin,carryout,Y); else  
$display("FAIL\t%p\t%p\t%d\t=\t%d\p%p",A,B,carryin,carryout,Y);  
*/  
end  
//enabling the wave dump  
initial begin  
$dumpfile("dump.vcd"); $dumpvars;  
end  
endmodule
```

Simulation Waveform:

 

Simulation waveform of carry skip adder

5.5 Post Lab:

1. Write a Verilog code to design 4 Bit Carry Save Adder.

5.6 Result

Thus, the design of 4-bit carry look-ahead adder circuit was simulated in Verilog and synthesized using Xilinx vivado tools.

Lab Experiment #6

Realization of Multiplier-1

6.1 Objective: To design and simulate the Braun array multiplier in Verilog and synthesize using Xilinx vivado tools.

6.2 Software tools Requirement:

Software's: Xilinx vivado

6.3 Prelab Questions:


(write pre lab Q & A in an A4 sheet) 1.

What is called Booth recoding?

2. Give the booth's recoding transformation of the following number 01111001(0).

3. Give the difference between Booth's recoding and modified booth's recoding?

 6.4 Problem: Write a Verilog code to implement the 4-bit Braun Array multipliers using structural model. Logic Diagram



4-bit Braun Array multiplier

Verilog Code

```

module braun(a, b,
p);
input [3:0] a;
input [3:0] b;
output [7:0] p;

wire w0,w1,w2,w3,w4,w5,w6,w7,w8,w9,w10,w11,w12,w13,w14,w15,w16,w17, w18,
w19,w20,w21,w22,w23,w24,w25,w26,w27,w28,w29;

and g0 (w0, a[3], b[0]);
and g1 (w1, a[2], b[0]);

```

```

and g2 (w2, a[1], b[0]);
and g3 (p[0],a[0], b[0]);
and g4 (w6, a[3], b[1]);
and g5 (w3, a[2], b[1]);
and g6 (w4, a[1], b[1]);
and g7 (w5, a[0], b[1]);
and g8 (w12, a[3], b[2]);
and g9 (w13, a[2], b[2]);
and g10(w14, a[1], b[2]);
and g11(w15, a[0], b[2]);
and g12(w21, a[3], b[3]);
and g13(w22, a[2], b[3]);
and g14(w23, a[1], b[3]);
and g15(w24, a[0], b[3]);

```

```

fa_df f0 (w8 , w7 , w0 , w3 , 1'b0); fa_df
f1 (w10 , w9 , w1 , w4 , 1'b0); fa_df f2
(p[1], w11 , w2 , w5 , 1'b0); fa_df f3
(w17 , w16 , w6 , w13, w7); fa_df f4
(w19 , w18 , w8 , w14, w9); fa_df f5
(p[2], w20 , w10, w15, w11); fa_df f6
(w26 , w25 , w12, w22, w16); fa_df f7
(w28 , w27 , w17, w23, w18);
fa_df f8 (p[3], w29 , w19, w24, w20);
fa_df f9 (p[6], p[7], w21, w25, w31);
fa_df f10(p[5], w31 , w26, w27, w30);
fa_df f11(p[4], w30 , w28, w29, 1'b0);
endmodule

```


// TEST BENCH

```

module braun_test_v;
// Inputs
reg [3:0] a;
reg [3:0] b;
// Outputs
wire [7:0]p;
// Instantiate the Unit Under Test (UUT) braun uut (
    .a(a),
    .b(b),
    .p(p));
initial begin
// Initialize
    Inputs a =
    0; b = 0;
    #100;a=1101; b=1001; end
endmodule

```

Simulation waveforms:

 

Braun Array multiplier waveform

6.5 Post Lab:

1. Write the booth multiplier code in Verilog and implement using EDA tools.

6.6 Result

Thus, the design of 4-bit Braun array multiplier circuit was simulated in Verilog and synthesized using Xilinx vivado tools.

Lab Experiment #7

Realization of Multiplier-II

7.1 Objective: To design and simulate the Wallace tree multiplier in Verilog and synthesize using Xilinx vivado tools

7.2 Software tools Requirement

Software's: Xilinx vivado

7.3 Pre Lab Questions


(Write pre lab Q & A in an A4 sheet)

1. How carry save multiplier differs from array multiplier?
2. Why the partial sum adders are arranged in tree like fashion?

7.4 Problem:

Write a Verilog code to implement the 4-bit Wallace tree multipliers using structural model.

Logic Diagram:

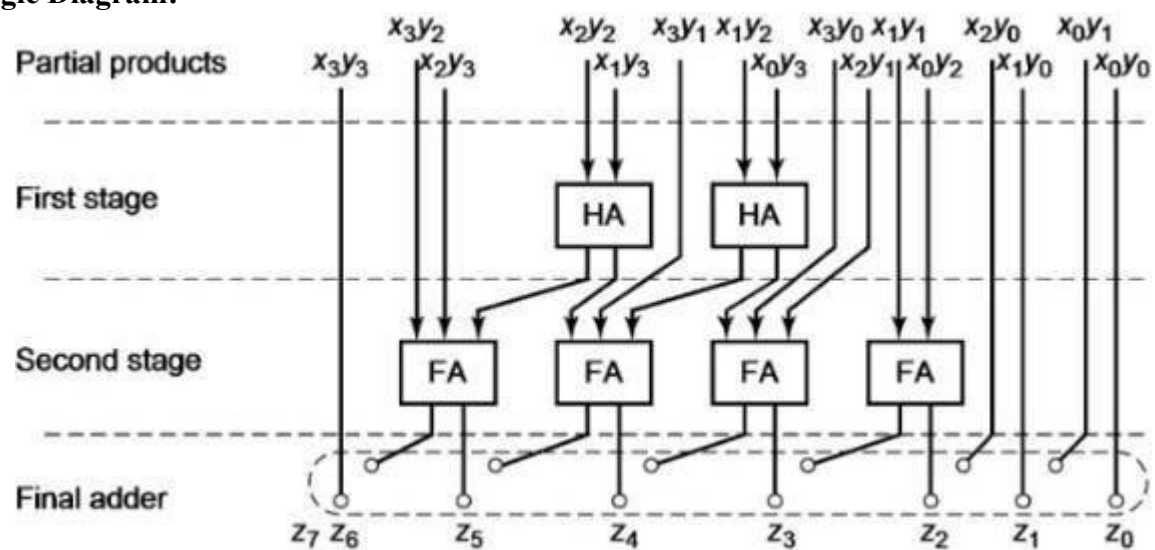

7.1 4-bit Wallace tree multiplier

Source code:

```
module wallace_tree_mul(a, b, z); input [3:0] a;
input [3:0] b; output [7:0] z; wire [32:0] w;
and g1 (z[0], a[0], b[0]);
and g2 (w[27], a[0], b[1]);
and g3 (w[0], a[1], b[0]); and
g4 (w[1], a[2], b[0]); and g5
(w[2], a[0], b[2]); and g6
(w[3], a[1], b[1]); and g7
(w[4], a[1], b[1]); and g8
(w[5], a[3], b[0]); and g9
```




```

(w[6] , a[0], b[3]); and
g10(w[7] , a[1], b[2]); and
g11(w[8] , a[3], b[1]); and
g12(w[9] , a[1], b[3]); and
g13(w[10], a[2], b[2]); and
g14(w[11], a[2], b[3]); and
g15(w[12], a[3], b[2]); and
g16(w[13], a[3], b[3]);
ha_gate h0(w[16], w[17], w[10], w[9]);
ha_gate h1(w[14], w[15], w[7], w[6]); ha_gate
h2(z[1] , w[28], w[27], w[0]);
fa_df f0(w[19] , w[20] , w[2] , w[3] , 1'b0);
fa_df f1(w[21] , w[22] , w[4] , w[5] , w[14]);
fa_df f2(w[23] , w[24] , w[15] , w[8] , w[15]);
fa_df f3(w[25] , w[26] , w[17] , w[11] , w[12]);
fa_df f4(z[2] , w[29] , w[0] , w[1] , w[28]);
fa_df f5(z[3] , w[30] , w[20] , w[21] , w[29]);
fa_df f6(z[4] , w[31] , w[22] , w[23] , w[30]);
fa_df f7(z[5] , w[32] , w[24] , w[25] , w[31]);
fa_df f8(z[6] , z[7] , w[26] , w[13] , w[32]);
endmodule Test
bench: module
wallace_test_v; //
Inputs reg [3:0] a; reg
[3:0] b; // Outputs
wire [7:0] z;
// Instantiate the Unit Under Test (UUT) wallace_tree_mul uut (
.a(a),
.b(b), .z(z)); initial
begin // Initialize
Inputs a = 0; b = 0;
//wait 100 ns for global reset to finish
#100a=1101; b=1001;
end
endmodule

```

Simulation

Waveform:

 

Simulation waveform of Wallace tree multiplier

7.5 Post Lab:

1. Write the Verilog code for 4-bit Baugh Woolley multiplier in structural modelling and implement using EDA tools.

7.6 Result

Thus, the design of 4-bit Wallace tree multiplier circuit was simulated in Verilog and synthesized using Xilinx vivado tools

Lab Experiment #8

Realization of Memory

8.1 Objective:

Design memory using Verilog and Simulate using Xilinx Tool.

8.2 Software tools Requirement:

Software's: Xilinx vivado


8.3 Prelab:

- 1.What are the different types of memory? Compare its performance.
- 2.Write the difference between static and dynamic memory.
- 3.Define port for 32*64k RAM memory.

8.4.1 Problem Statement 1:

- 1.Design a 16X4 RAM Memory.

Logic Diagram:

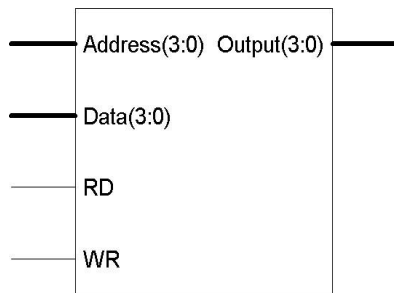

Program:

```
module Memory_Design( Data, RD, WR, Address, Output);
input[3:0] Data;
input RD, WR;
input[3:0] Address;
output reg[3:0] Output;
reg[3:0] RAM[15:0];
reg[3:0] Temp;
always@(Address)
begin if(WR) begin
RAM[Address]=Data; Temp=RAM[Address];
end if(RD)
begin
Output=RAM[Address];
end
end
endmodule
```

TEST BENCH:

```
module RAM_Test_v;
// Inputs
reg [3:0] Data;
reg RD;
reg WR;
reg [3:0] Address;
//
```

```

Outputs wire
[3:0] Output;
// Instantiate the Unit Under Test (UUT)
memory_Design uut
(.Data(Data),.RD(RD),.WR(WR),.Address(Address),.Output(Output));
initial begin
    Data = 4'b0000;      RD = 0;      WR = 1;      Address = 4'b0000; #30;
    Data = 4'b0001;      RD = 0;      WR = 1;      Address = 4'b0001; #30;
    Data = 4'b0010;      RD = 0;      WR = 1;      Address = 4'b0010; #30;
    Data = 4'b0011;      RD = 0;      WR = 1;      Address = 4'b0011; #30;
    Data = 4'b0100;      RD = 0;      WR = 1;      Address = 4'b0100; #30;
    Data = 4'b0101;      RD = 0;      WR = 1;      Address = 4'b0101; #30;
    Data = 4'b0110;      RD = 0;      WR = 1;      Address = 4'b0110; #30;
    Data = 4'b0111;      RD = 0;      WR = 1;      Address = 4'b0111; #30;
    Data = 4'b1000;      RD = 0;      WR = 1;      Address = 4'b1000; #30;
    Data = 4'b1001;      RD = 0;      WR = 1;      Address = 4'b1001; #30;
    Data = 4'b1010;      RD = 0;      WR = 1;      Address = 4'b1010; #30;
    Data = 4'b1011;      RD = 0;      WR = 1;      Address = 4'b1011; #30;
    Data = 4'b1100;      RD = 0;      WR = 1;      Address = 4'b1100; #30;

    Data = 4'b1101;      RD = 0;      WR = 1;      Address = 4'b1101; #30;
    Data = 4'b1110;      RD = 0;      WR = 1;      Address = 4'b1110; #30;
    Data = 4'b1111;      RD = 0;      WR = 1;      Address = 4'b1111; #30;

    RD = 1;      WR = 0;      Address = 4'b0000; #30;
    RD = 1;      WR = 0;      Address = 4'b0001; #30;
    RD = 1;      WR = 0;      Address = 4'b0010; #30;

    RD = 1;      WR = 0;      Address = 4'b0011; #30;
    RD = 1;      WR = 0;      Address = 4'b0100; #30;
    RD = 1;      WR = 0;      Address = 4'b0101; #30;
    RD = 1;      WR = 0;      Address = 4'b0110; #30;
    RD = 1;      WR = 0;      Address = 4'b0111; #30;
    RD = 1;      WR = 0;      Address = 4'b1000; #30;
    RD = 1;      WR = 0;      Address = 4'b1001; #30;
    RD = 1;      WR = 0;      Address = 4'b1010; #30;
    RD = 1;      WR = 0;      Address = 4'b1011; #30;
    RD = 1;      WR = 0;      Address = 4'b1100; #30;

```

```

RD = 1;          WR = 0;          Address = 4'b1101; #30;

RD = 1;          WR = 0;          Address = 4'b1110; #30;
RD = 1;          WR = 0;          Address = 4'b1111; #30;


#100;

```

```
End
```

```
endmodule
```

Simulation Output:

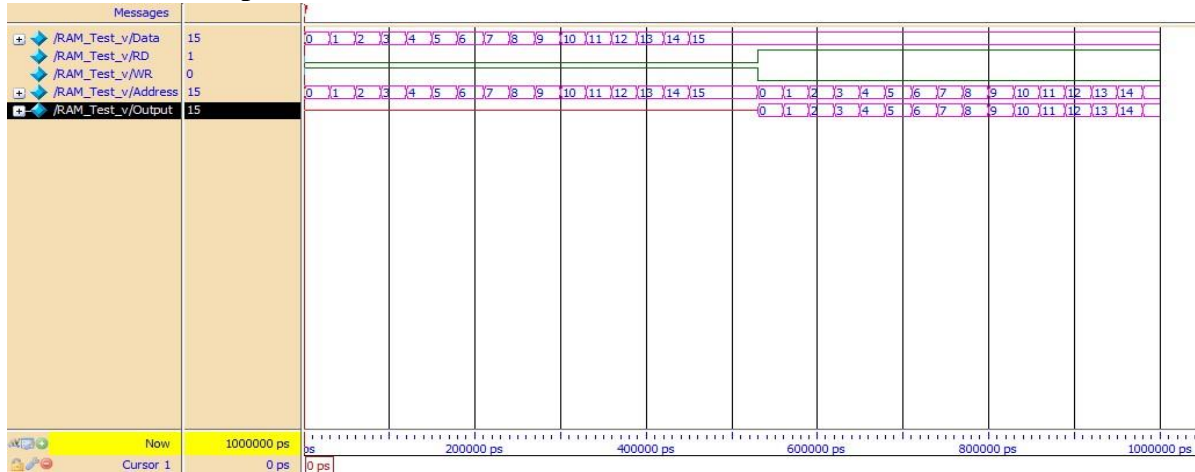


Statement 2:

8.4.2 Problem Design 16X4 ROM Memory.

To Design a 16x4 ROM in Verilog and Simulate using Xilinx Tool.

Block Diagram:

 

Program:

```
Module ROM_16x4(Address, RD, Output); input[3:0] Address; input
RD;
output reg[3:0] Output; reg[3:0]
ROM[15:0]; initial begin
ROM[4'b0000]=4'b1111; ROM[4'b0001]=4'b1110;

ROM[4'b0010]=4'b1101;          ROM[4'b0011]=4'b1100;          ROM[4'b0100]=4'b1011;
ROM[4'b0101]=4'b1010;          ROM[4'b0110]=4'b1001;          ROM[4'b0111]=4'b1000;
ROM[4'b1000]=4'b0111;          ROM[4'b1001]=4'b0110;          ROM[4'b1010]=4'b0101;
ROM[4'b1011]=4'b0100;          ROM[4'b1100]=4'b0011;          ROM[4'b1101]=4'b0010;
ROM[4'b1110]=4'b0001; ROM[4'b1111]=4'b0000; end
always@(RD , Address) begin
if(RD)
begin
Output=ROM[Address];
end
end
endmodule
```

Test Bench:

```
module ROM_Test_v;
// Inputs
reg [3:0] Address; reg RD;
// Outputs wire
[3:0] Output;
// Instantiate the Unit Under Test (UUT)
ROM_16x4 uut (.Address(Address),.RD(RD),.Output(Output)); initial begin
// Initialize Inputs
Address = 4'b0000;          RD = 1;          #50;
```

```

Address = 4'b0001;          RD = 1;      #50;

Address = 4'b0010;          RD = 1;      #50;

Address = 4'b0011;          RD = 1;      #50;

Address = 4'b0100;          RD = 1;      #50;

Address = 4'b0101;          RD = 1;      #50;

Address = 4'b0110;          RD = 1;      #50;

Address = 4'b0111;          RD = 1;      #50;

Address = 4'b1000;          RD = 1;      #50;

Address = 4'b1001;          #50;

Address = 4'b1010;          #50;

Address = 4'b1011;          #50;

Address = 4'b1100;          #50;

Address = 4'b1101;          #50;

Address = 4'b1110;          #50;


Address = 4'b1111;          #50;

end

```

```
endmodule
```

Simulation:

 

8.5 Post Lab:

Draw the block diagram and explain about FIFO memory.

8.6 Result:

Design of a 16x4 ROM in Verilog is Performed and Verified using Xilinx Tool.

Lab Experiment #9

Design and Analysis of CMOS inverter

9.1 Objective: To learn the design of CMOS inverter in circuit level and get the spice netlist using LTSPICE tool.

9.2 Software tools Requirement

LTSPICE tool.


9.3 Prelab Questions

(Write pre lab Q & A in an A4 sheet)


1. What are the advantages of SPICE software?
2. What are the differences between enhancement and depletion mode transistors?
3. What is the difference between strong 1 and weak 1?
4. What is meant by transistor sizing?

9.4 Problem 1: Design and analyse the CMOS inverter in circuit level, verify the transfer characteristics and infer the SPICE netlist using LTSPICE.


9.4.1 Logic Diagram

 

 9.4.2 Circuit design of CMOS Inverter in LTSPICE:



9.4.3 Output of CMOS INVERTER:

 

9.4.4 SPICE NETLIST:

```
* C:\Users\PRITHIVI\Documents\LTspiceXVII\INVERTER.asc
V1 IN 0 PULSE(0 5 0 0 0 5m 10m 100)
V2 VDD 0 5
M1 OUT IN 0 0 NMOS
M2 VDD IN OUT VDD PMOS
.model NMOS NMOS
.model PMOS PMOS
.lib C:\Users\PRITHIVI\Documents\LTspiceXVII\lib\cmp\standard.mos .tran
50m
.backanno .end
```

9.5 Post lab

1. Perform DC Analysis for CMOS Inverter in LTSPICE.

9.6 Result:

Thus, the design and analysis of CMOS Inverter has been performed, transfer characteristics have been verified using LTSPICE tool.

LAB EXPERIMENT # 10

Dynamic NAND gate

10.1 Objective: To study and design the two inputs n-type dynamic NAND gate using HSPICE and verify the simulation result.

10.2 Software required: Hspice

10.3 Pre-lab Questions

1. Differentiate static and dynamic CMOS logic.
2. Explain NORA CMOS logic.

10.4 Design two input dynamic NAND Gate

Circuit Diagram:

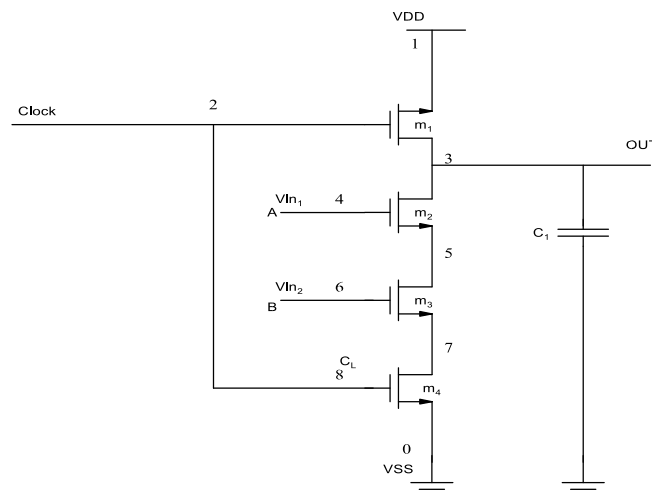


Figure 1. Two input dynamic NAND gate

10.4 Spice Netlist:


```
.option post
.include c:\synopsys\tsmc018.lib
vdd 1 0 dc 1.8v
vin1 4 0 pulse(-5 5 2ns 2ns 2ns 80us 160us) //(input A)
vin2 6 0 pulse(-5 5 2ns 2ns 2ns 50us 100us) //(input B)
vin3 2 0 pulse(-5 5 2ns 2ns 2ns 50us 100us) //(CLOCK)
vin4 8 0 pulse(-5 5 2ns 2ns 2ns 50us 100us) //(CLOCK)
```

```

m1 3 2 1 1 cmosp w=4u l=180nm
m2 3 4 5 5 cmosn w=2u l=180nm
m3 5 6 7 7 cmosn w=2u l=180nm
m4 7 8 0 0 cmosn w=2u l=180nm
c1 3 0 100p // (CAPACITOR→
Vary the capacitor value to see the
dynamic performance) .tran 100u
800u
.plot v(3) v(4) V(6)
.end

```

OUTPUT : N TYPE DYNAMIC- NAND GATE

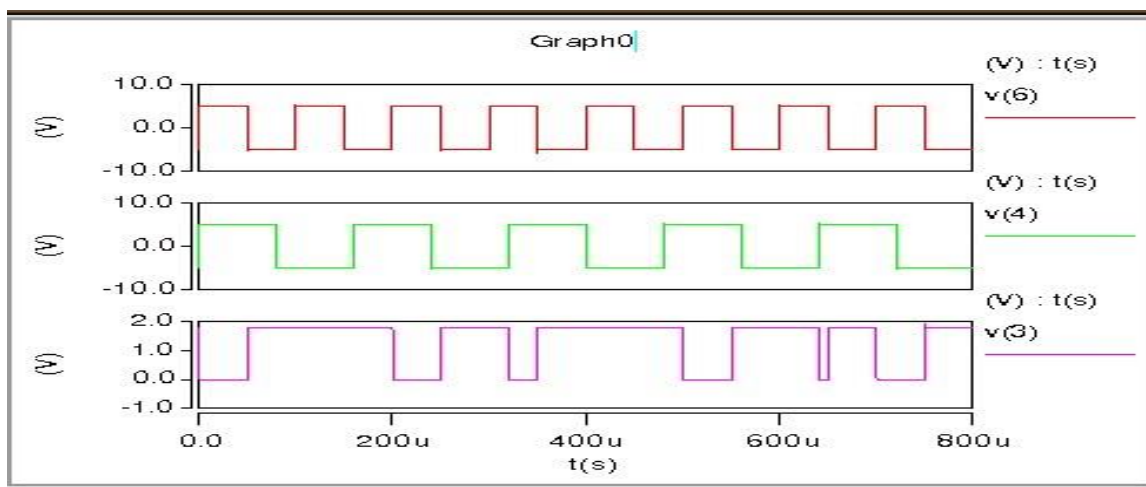

10.7 Netlist :

```

.option post
.include c:\synopsys\tsmc018.lib
* t58f spice bsim3 version 3.1 parameters
*
* spice 3f5 level 8, star-hspice level 49, utmost level 8 *
* temperature_parameters=default
*
vdd 1 0 dc 1.8v
vin1 4 0 pulse(-5 5 2ns 2ns 2ns 80us 160us)
vin2 6 0 pulse(-5 5 2ns 2ns 2ns 50us 100us)
vin3 2 0 pulse(-5 5 2ns 2ns 2ns 50us 100us)
vin4 8 0 pulse(-5 5 2ns 2ns 2ns 50us 100us)
m1 3 2 1 1 cmosp w=4u l=180nm
m2 3 4 5 5 cmosn w=2u l=180nm
m3 5 6 7 7 cmosn w=2u l=180nm
m4 7 8 0 0 cmosn w=2u
l=180nm c1 3 0 100p .tran
100u 800u
.plot v(3) v(4) v(6)

```

.end

dynamic nand

***** mos model parameters tnom= 25.000 temp= 25.000

model parameters model name: 0:cmosn model type:nmos ***

*** general parameters ***

deriv= 0.

*** level 49 model parameters ***

hspver= 2006.03 level= 49
version= 3.1 paramchk= 0 apwarn=
1 lite= 0 vgslim= 0
binUnit= 1 capMod= 2 xpart=
0.5 mobMod= 1 nqsMod= 0
stiMod= 0 elm= 5 sfvtflag=
0 tox= 4.1e-009 meter xj= 1e-007
meter binflag= 0 lmin= 0 meter
lmax= 0 meter wmin= 0 meter
wmax= 0 meter lref= 0 meter wref=
0 meter lint=1.69004e-008 meter wint=
0 meter
lmult= 1 wmult= 1
ll= 0 llm= 1
lw= 0 lwn= 1
lwl= 0 wl= 0
wln= 1 ww= 0
wwn= 1 ww1= 0
dwg=-4.72872e-009 m/V dwb=-2.45241e-009
m/V^{1/2} a0= 2 ags= 0.444996 V⁻¹
b0=1.90108e-007 meter b1=4.99995e-006 meter keta=
-0.0164863 V⁻¹ voff= -0.0948017 V ngate= 0
cm⁻³ vbx= 0 V vbm= -3 V xt=
1.55e-007 meter vth0= 0.366247 V
nch=2.3549e+017 cm⁻³ nsub= 6e+016 cm⁻³
nlx=1.63068e-007 meter gamma1= 0 V^{-1/2}
gamma2= 0 V^{-1/2} k1= 0.5865 V^{1/2} k2=
0.00112727 k3= 0.001 k3b= 0.0294061
V⁻¹ w0= 1e-007 meter dvt0= 1.20646
dvt1= 0.421549 dvt2= 0.0197749 V⁻¹ dvt0w=
0 meter⁻¹ dvt1w= 0 meter⁻¹ dvt2w= 0 V⁻¹
dsub= 0.0145467 eta0= 0.00223093
etab=6.02898e-005 V⁻¹ u0= 273.809 cm²/V/sec
ua=-1.40499e-009 m/V ub=2.40832e-018 (m/V)²

```

uc=6.50483e-011 V^-1      vsat= 135501 m/sec
a1=0.000386877 v^-1      a2= 0.464027      delta=
0.01 V      rdsw= 123.338 ohm-um      prwg= 0.5 V^-1
prwb= -0.197728 V^-1/2    wr= 1      pclm=
1.38221      pdiblc1= 0.176279
      pdiblc2= 0.00166653      pdiblc3= -0.1 V^-1
pscbe1=8.91287e+009 V/m    pscbe2=7.34961e-009 V/m
      drout= 0.769469      pvag= 0.00168592
nfactor= 2.18601      cdsc= 0.00024 f/m^2
cdscb= 0 f/V/m^2      cdsd= 0 f/V/m^2
cit= 0 f/m^2      alpha0= 0 m/V      beta0=
30 V      dlc=1.69004e-008 meter      dwc=
0 meter      clc= 1e-007 meter      cle= 0.6
cgso= 8.23e-010 f/m      cgdo= 8.23e-010 f/m
cgbo= 1e-012 f/m
      cgsl= 0 f/m      cgdl= 0 f/m
ckappa= 0.6      cf= 0 f/m
tnom= 300.15 K      kt1= -0.11 V
kt1l= 0      kt2= 0.022
ute= -1.5      ua1= 4.31e-009 m/V
      ub1= -7.61e-018 (m/V)^2      uc1= -5.6e-011 m/V^2
      at= 33000 m/s      prt= 0
using Berkeley noise model      noiMod= 2
noia=1.31826e+019      noib= 144544
noic=-1.24516e-012      em= 4.1e+007
ef= 0.92      af= 1      kf=
0      gdsnoi=-1.23457e-029      using
Hspice diodes      using ACM      acm= 0
hdif= 0 meter      ldif= 0 meter
js= 0 amp/m^2      jsw= 0 amp/m
xti= 0      n= 1
cj=0.000946643 f/m^2      mj= 0.382027
pb= 0.8 V      cjsw=2.60815e-010 f/m
mjsw= 0.102322      php= 0.8 V
pbsw (not used)      cjgate=2.60815e-010 f/m
cjswg (not used)      mjswg (not used)
pbswg (not used)      lketa= 0.00716508
wketa=-0.00288098      pketa=-0.00675928
pvth0=-0.00219937      pk2= 0.00159325
peta0=0.000100316      pu0= 6.77752
pua=5.50542e-012      pub=8.84133e-025
pvsat= 2006.29      prdsw= -0.936896

```

```

*****
***      model parameters model name: 0:cmosp model type:pmos ***
*****

```

```

*** general parameters ***
deriv= 0.

```

*** level 49 model parameters ***

hspver= 2006.03 level= 49
version= 3.1 paramchk= 0
apwarn= 1 lite= 0
vgslim= 0 binUnit= 1
capMod= 2 xpart= 0.5
mobMod= 1 nqsMod= 0
stiMod= 0 elm= 5
sfvtflag= 0 tox= 4.1e-009 meter
xj= 1e-007 meter binflag= 0
lmin= 0 meter lmax= 0 meter
wmin= 0 meter wmax= 0 meter
lref= 0 meter wref= 0 meter
lint=2.94454e-008 meter wint= 0
meter lmult= 1 wmult=
1 ll= 0 lln= 1
lw= 0 lwn= 1 lwl=
0 wl= 0 wln= 1
ww= 0 wwn= 1
wwl= 0
dwg=-2.79872e-008 m/V dwb=-4.83797e-010
m/V^{1/2} a0= 1.99766 ags= 0.418694 V⁻¹
b0=1.94918e-007 meter b1=6.42291e-007 meter keta=
0.0166345 V⁻¹ voff= -0.095236 V ngate= 0
cm⁻³ vbx= 0 V vbm= -3 V xt=
1.55e-007 meter vth0= -0.390601 V
nch=4.1589e+017 cm⁻³ nsub= 6e+016 cm⁻³
nlx=1.19407e-007 meter gamma1= 0 V^{-1/2}
gamma2= 0 V^{-1/2} k1= 0.534131 V^{1/2} k2=
0.0395326 k3= 0 k3b= 7.49162 V⁻¹
w0= 1e-006 meter dvt0= 0.506055 dvt1=
0.242384 dvt2= 0.1 V⁻¹ dvt0w= 0
meter⁻¹ dvt1w= 0 meter⁻¹ dvt2w= 0 V⁻¹
dsub= 0.00181655 eta0= 0.0010355 etab=-
0.00043584 V⁻¹ u0= 115.689 cm²/V/sec
ua=1.57375e-009 m/V ub=1.87431e-021 (m/V)²
uc= -1e-010 V⁻¹ vsat= 113098 m/sec a1=
0.474915 v⁻¹ a2= 0.300003 delta= 0.01 V
rdsw= 198.321 ohm-um prwg= 0.5 V⁻¹ prwb= -
0.498665 V^{-1/2} wr= 1 pclm= 1.32999
pdiblc1= 0.00176656 pdiblc2=7.72839e-007
pdiblc3= -0.001 V⁻¹ pscbe1=4.87218e+010 V/m
pscbe2= 5e-010 V/m drout= 0.00101189 pvag=
0.0209921 nfactor= 2 cdsc= 0.00024
f/m² cdsbc= 0 f/V/m² cdsdc= 0 f/V/m²
cit= 0 f/m² alpha0= 0 m/V beta0= 30
V dlc=2.94454e-008 meter dwc= 0 meter
clc= 1e-007 meter cle= 0.6 cgso= 6.35e-010

```

f/m      cgdo= 6.35e-010 f/m      cgbo= 1e-012 f/m
cgsl=    0 f/m      cgdl=    0 f/m
      ckappa=    0.6      cf=    0 f/m
tnom=    300.15 K      kt1=    -0.11 V
kt1l=    0      kt2=    0.022
ute=    -1.5      ua1= 4.31e-009 m/V
      ub1= -7.61e-018 (m/V)^2      uc1= -5.6e-011 m/V^2
      at=    33000 m/s      prt=    0
using Berkeley noise model      noiMod=    2
noia=3.57457e+018      noib=    2500
noic=2.6126e-011      em= 4.1e+007
ef=    1.1388      af=    1      kf=
0      gdsnoi=-1.23457e-029      using
Hspice diodes      using ACM      acm=    0
hdif=    0 meter      ldif=    0 meter
js=    0 amp/m^2      jsw=    0 amp/m
xti=    0      n=    1
cj=0.00114452 f/m^2      mj= 0.409952
pb= 0.846869 V      cjsw=2.49075e-010 f/m
mjsw= 0.347856      php= 0.846869 V
pbsw (not used)      cjgate=2.49075e-010 f/m
cjswg (not used)      mjswg (not used)
pbswg (not used)      lketa=-0.00149587
wketa= 0.0222457      pketa=-0.00253656
pvth0= 0.00230202      pk2= 0.00182191
peta0=2.82779e-005      pu0= -1.55806
pua=-6.36889e-011      pub= 1e-021
pvsat= 49.842      prdsw= 9.05753

```

Model: 0:cmosn
W = 1.99e-006, L = 1.8e-007

dynamic nand

```

***** operating point information      tnom= 25.000 temp= 25.000
*****

```

```

***** operating point status is voltage simulation time is 0.
node =voltage node =voltage node =voltage

```

```

+0:1    = 1.8000 0:2    = -5.0000 0:3    = 1.8000
+0:4    = -5.0000 0:5    = 1.2000 0:6    = -5.0000
+0:7    = 600.0000m 0:8    = -5.0000

```

dynamic nand

```

***** transient analysis      tnom= 25.000 temp= 25.000
*****

```

a

legend:

Thus the design of two input dynamic NAND gate, MOS transistor level using HSPICE was studied and simulated.