

Static CMOS logic Styles

Tristate circuits :- (restoring logic)


Tristate Buffer :-

When $ENABLE = 1$ output $Y = \text{input } A$



$ENABLE = 0$ output $Y = Z$

Truth table

EN/\overline{EN}	A	Y
0/1	0	Z
0/1	1	Z
1/0	0	0
1/0	1	1

 


Tristate Inverter :-

  

Truth table

Transistor Inverter Circuit

EN/ \overline{EN}	A	Y
0/1	0	Z
0/1	1	Z
1/0	0	1
1/0	1	0

 


Multiplexers :-

2:1 MUX


S/ \overline{S}	D1	D0	Y
0/1	X	0	0
0/1	X	1	1
1/0	0	X	0
1/0	1	X	1

$$Y = \overline{S}D_0 + SD_1$$

 


2:1 MUX using Tri-state

Multiplexer using Tri-state logic



 


CMOS logic

 


Tri-state 2:1 mux


Clocked CMOS logic :-

   

CMOS positive level sensitive Latch

 

Ratified circuits:-

 

Pseudo nMOS:-

* Static load build from f_i PMOS transistor rather than from f_i neither a high value nor depletion mode or f_i (strong)

* in pseudo nmos circuits

static PMOS load is always f_i so the transistor is always ON.


* Draw back is static power consumption but requires less no. of transistors to implement a logic.

* The main drawback of complementary logic circuit design is that it occupies larger area on the chip because for a given n inputs, the required number of transistors is $2n$ in the design.

* Also CMOS logic is slower because the applied input must drive both pull-up network (pMOS) and pull-down network (nMOS).

* pMOS has lower mobility than electrons of nMOS and must be sized larger to achieve comparable current.

 * One approach to reduce the no. of transistors and area is to use single pMOS transistor with gate connected to ground so that pMOS is always ON and act as load. This is pseudo-nMOS logic.



Adv of pseudo nmos logic over CMOS logic:-

- * less no. of transistors is used.

For a given n inputs, the number of transistors required is $(n+1)$ compared to $2n$ in CMOS logic

- * less area on the chip

- * compatible with CMOS

- * hardwired logic compatible

Dis Adv:


- * reduced voltage swing at the o/p

- * has non zero static power dissipation if output is zero.


- * Ratioed logic

Examples:-


INV

 


2-i/p NAND

 

2-i/p NOR

 


 CVSL (Cascoded Voltage switch to 'c')
 or DCVSL (Differential cascode voltage
 switch logic)



$f \rightarrow$ True form
 $\bar{f} \rightarrow$ complement
 down
 gate


Eg :- 2 i/p AND gate

 

DCVSL is an improved circuit design to eliminate the static current problem in pseudo-nmos logic style.

* DCVSL uses both true and complementary input signals and computes both true and complementary output signals.

 
* It uses a pair of nmos pull down networks



* Two functions of pull down n/w pair are complement of each other

$$Y = \overline{A \cdot B}$$
 
$$\bar{Y} = \overline{\bar{A} + \bar{B}} = A \cdot B$$



$$Y = \overline{A+B}$$

$$\overline{Y} = \overline{A} \cdot \overline{B}$$

