

Reg. No:

SRM Institute of Science and Technology

Tiruchirappalli Campus, Trichy – 621 105

Faculty of Engineering and Technology

Continuous Learning Assessment - I, First Semester, October -2022.

Department of Electronics and Communication Engineering

21EES101T: Electrical and Electronics Engineering



(Regulations 2021)


Date: 28.10.2022


Time: 90 Minutes






Max. Marks: 50

	Answer ALL Questions.		
	PART A – (10 x 1 = 10 marks)		
1.	<p>A circuit containing resistor and a capacitor in series connection has an impedance of $25\ \Omega$ and the resistance of $10\ \Omega$. Obtain the power factor.</p> <p>A. 0.4 leading B. 0.4 lagging C. 0.866 leading D. 0.866 lagging</p>	CO 1	K 1
2.	<p>By applying KVL, determine the voltages V_a and V_b in the given circuit</p> <p>A. 2 V, 4 V B. 6 V, 5 V C. 10V, 6 V D. 9 V, 12 V</p>	CO 1	K 1
3.	<p>A wire is carrying a direct current of 20A and a sinusoidal alternating current of peak value 20</p> <p>A. 24A B. 25A</p>	CO 1	K 1

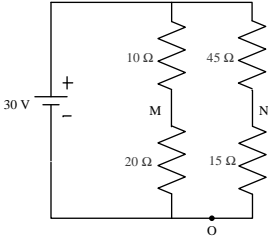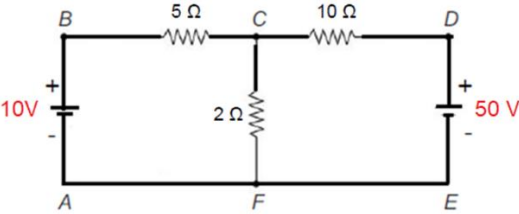
	<p>C. 26A D. 24.5A</p>		
4.	<p>A circuit consists of three identical resistors connected in series. When one resistor is removed the circuit current will</p> <p>A. Decrease B. Increase by one third C. Decrease by one third D. Remains the same</p>	CO 1	K 1
5.	<p>Find out the voltage V_{MN}</p>  <p>A. 10.5 V B. 8.5V C. 16.5 V D. 12.5 V</p>	CO 1	K 1
6.	<p>Consider the following circuit. Find the current across 5Ω .resistor</p>  <p>A. 0.1 A B. 0.3 A C. 0.5 A D. 0.25 A</p>	CO1	K 1
7.	<p>Determine the average value of voltage $v(t) = 300 \sin \omega t$</p> <p>A. 85.5 V B. 191.08 V C. 90 V D. 125.08 V</p>	CO1	K 1
8.	<p>If the value of the resistors are doubled in a circuit which consists of an ideal voltage source and linear resistors, the voltage appeared across each resistor is</p>	CO1	K 1

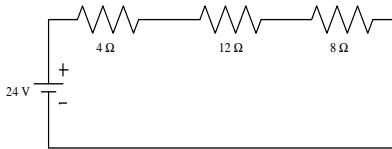	A. Not changed B. Doubled C. Halved D. Increased by three times		
9.	Voltage of a coil when it has $di/dt = 20 \text{ mA/s}$ and $L = 8 \text{ H}$ is A. 16 mV B. 1.6 mV C. 160 mV D. 0.16 MV	CO1	K 1
10.	Find the voltage present in the 12Ω of the circuit shown  A. 10.5V B. 8.6V C. 16.2V D. 12.0V	CO1	K 1

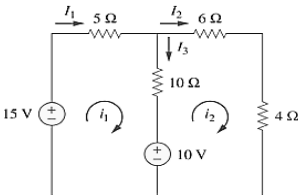
	Answer Any Five Questions.		
	PART B – (5 x 5 = 25 Marks)		
11.	<p>For the shown circuit, find the branch currents by using mesh analysis</p>  $-15 + 5i_1 + 10(i_1 - i_2) + 10 = 0$ $3i_1 - 2i_2 = 1 \quad (1)$ <p>For mesh 2</p> $6i_2 + 4i_2 + 10(i_2 - i_1) - 10 = 0$ $i_1 - 2i_2 = -1 \quad (2)$ <p>Solve equations 1 and 2 to get i_1 and i_2</p> $\begin{array}{rcl} 3i_1 - 2i_2 & = & 1 \quad (1) \\ i_1 - 2i_2 & = & -1 \quad (2) \\ \hline 2i_1 & = & 2 \end{array}$ $i_1 = 1\text{A}$ <div style="display: flex; justify-content: space-around; align-items: center;"> <div style="border: 1px solid black; padding: 5px; margin: 5px;"> $i_2 = 1\text{A}$ </div> <div style="border: 1px solid black; padding: 5px; margin: 5px;"> $I_1 = i_1 = 1\text{A}$ </div> <div style="border: 1px solid black; padding: 5px; margin: 5px;"> $I_2 = i_2 = 1\text{A}$ </div> </div> <div style="border: 1px solid black; padding: 5px; margin: 5px; width: fit-content; margin-left: auto;"> $I_1 = i_1 - i_2 = 1 - 1 = 0\text{A}$ </div>	CO 1	K 2

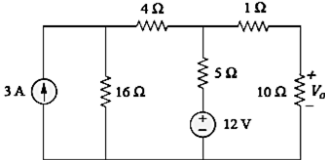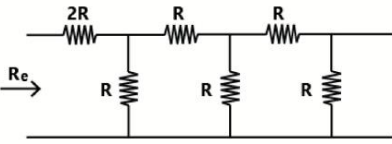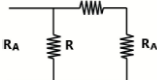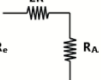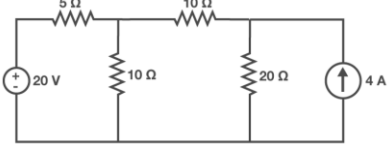12.	<p>Find the value of current across 10Ω resistor, using Thevenin's theorem in the circuit shown.</p>  <p>$R_{th}=5\Omega$ and $V_{th}=10V$</p>	CO 1	K 2
13.	<p>The ladder network shown in the figure, find the equivalent resistance of R_e.</p>  <p>To find R_e, we need to find equivalent resistance of remaining network</p> $R_A = \frac{R \times (R + R_A)}{2R + R_A}$ $2RR_A + R_A^2 = R^2 + RR_A$ $R_A^2 + RR_A - R^2 = 0$ $R_A = \frac{-R \pm \sqrt{R^2 + 4R^2}}{2} = \frac{-R + \sqrt{5}R}{2}$ $R_A = 0.62 R$ $R_e = 2 + 0.62 R$ $\frac{R_e}{R} = 2.62$  	CO 1	K 2
14.	<p>For a given circuit, find the current across 20Ω resistor by using super position theorem.</p>  <p>$I = I_1 + I_2$</p> <p>Substituting the values of I_1 and I_2 in the above equation, we get</p> <p>$I = 0.4 + 1.6 = 2 A$</p> <p>Therefore, the current flowing through the resistor is 2 A.</p>	CO 1	K 2

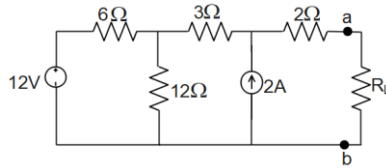Find the value of R_L by the principle of maximum power transfer theorem for the circuit shown.


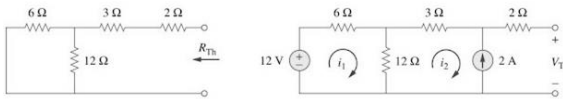
$$R_{Th} = 2 + 3 + 6 \parallel 12 = 5 + \frac{6 \times 12}{18} = 9 \Omega$$



$$-12 + 18i_1 - 12i_2 = 0, \quad i_2 = -2 \text{ A}$$

Solving for i_1 , we get $i_1 = -2/3$. Applying KVL around the outer loop to get V_{Th} across terminals $a-b$, we obtain

$$-12 + 6i_1 + 3i_2 + 2(0) + V_{Th} = 0 \quad \Rightarrow \quad V_{Th} = 22 \text{ V}$$

For maximum power transfer,

$$R_L = R_{Th} = 9 \Omega$$

and the maximum power is

$$p_{\max} = \frac{V_{Th}^2}{4R_L} = \frac{22^2}{4 \times 9} = 13.44 \text{ W}$$

CO 1

K 2


Derive the expression of average and RMS value of full wave rectifier.


$$\begin{aligned} V_{\text{avg}} &= \frac{1}{T/2} \int_0^{T/2} V(t) dt \\ &= \frac{2V_m}{T} \int_0^{T/2} \sin(\omega t) dt \\ &= \frac{2V_m}{T} \left[-\frac{\cos(\omega t)}{\omega} \right]_0^{T/2} \\ &= \frac{2V_m}{\omega T} \{-\cos(\omega T/2) + \cos 0\} \\ &= \frac{2V_m}{2\pi} \{-\cos(\pi) + \cos 0\} \\ &= \frac{V_m}{\pi} (+1 + 1) \\ &= \frac{2}{\pi} V_m \\ &\approx 0.637 V_m. \end{aligned}$$

$$\begin{aligned} V_{\text{rms}}^2 &= \frac{V_m^2}{T} \int_0^T \sin^2(\omega t) dt \\ &= \frac{V_m^2}{2T} \int_0^T 2 \sin^2(\omega t) dt \\ &= \frac{V_m^2}{2T} \int_0^T \{1 - \cos(2\omega t)\} dt \\ &= \frac{V_m^2}{2T} \int_0^T dt - \frac{V_m^2}{T} \int_0^T \cos(2\omega t) dt \\ &= \frac{V_m^2}{2T} \left[T \right]_0^T - \frac{V_m^2}{2T} \left[\frac{\sin(2\omega t)}{2\omega} \right]_0^T \\ &= \frac{V_m^2}{2} - \frac{V_m^2}{4\omega T} \{\sin(2\omega T) - \sin(0)\} \\ &= \frac{V_m^2}{2} - \frac{V_m^2}{4\omega T} \{\sin(4\pi) - \sin(0)\} \\ &= \frac{V_m^2}{2} - \frac{V_m^2}{4\omega T} (0 - 0) \\ &= \frac{V_m^2}{2} \end{aligned}$$

CO 1

K 2

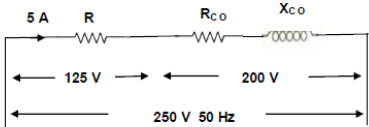17.	<p>A resistance is connected in series with a coil. With a supply of 250 V, 50 Hz, the circuit takes a current of 5 A. If the voltages across the resistance and the coil are 125 V and 200 V respectively, calculate (i) impedance, resistance and reactance of the coil (ii) power absorbed by the coil and the total power.</p> <p>diagram.</p>  <p>Resistance $R = \frac{125}{5} = 25 \Omega$</p> <p>$Z_{co} = \frac{200}{5} = 40 \Omega$; $Z_T = \frac{250}{5} = 50 \Omega$</p> <p>Since $Z_{co} = 40 \Omega$, $R_{co} + jX_{co} = 40$; $R_{co}^2 + X_{co}^2 = 1600$</p> <p>Since $Z_T = 50 \Omega$; $(25 + R_{co}) + jX_{co} = 50$</p> <p>$625 + 50 R_{co} + R_{co}^2 + X_{co}^2 = 2500$ i.e. $50 R_{co} = 2500 - 625 - 1600 = 275$</p> <p><u>Resistance of the coil</u> $R_{co} = 5.5 \Omega$ Also $X_{co}^2 = 1600 - 5.5^2 = 1569.75$</p> <p><u>Reactance of the coil</u> $X_c = 39.62 \Omega$</p> <p><u>Impedance of the coil</u> $Z_{co} = (5.5 + j 39.62) = 40 \angle 82.1^\circ \Omega$</p> <p><u>Power absorbed by the coil</u> $P_{co} = 5^2 \times 5.5 = 137.5 \text{ W}$</p> <p><u>Total power</u> $P_T = (5^2 \times 25) + 137.5 = 762.5 \text{ W}$</p> <p><u>Total impedance</u> $Z_T = (30.5 + j 39.62) = 50 \angle 52.41^\circ \Omega$</p> <p>$I R_{co} = 5 \times 5.5 = 27.5 \text{ V}$; $I X_{co} = 5 \times 39.62 = 198.1 \text{ V}$</p>	CO 1	K 2
18.	<p>A series RLC circuit with $R = 10\Omega$, $L = 10\text{mH}$ and $C = 1\mu\text{F}$ is connected to 200 V variable frequency supply. Find the resonance frequency, current, voltages Quality factor and Bandwidth.</p> <p>$\omega_0^2 = \frac{1}{LC} = \frac{10^6}{0.01 \times 1} = 10^8$; Therefore $\omega_0 = 10^4 \text{ rad. / sec.}$</p> <p><u>Resonant frequency</u> $f_0 = \frac{\omega_0}{2\pi} = 1591.55 \text{ Hz.}$; At resonance $X_L = X_C = \omega_0 L = 100 \Omega$</p> <p><u>Circuit current at resonance</u> $I_0 = \frac{200}{10} = 20 \text{ A}$</p> <p><u>Voltage across resistor</u> $V_R = 10 \times 20 = 200 \text{ V}$</p> <p><u>Voltage across L and C:</u> $V_L = V_C = X_L I_0 = 100 \times 20 = 2000 \text{ V}$</p> <p><u>Quality factor</u> $Q = \frac{X_L}{R} = \frac{100}{10} = 10$</p> <p><u>Bandwidth</u> $\omega_{BW} = \frac{R}{L} = \frac{10}{0.01} = 1000 \text{ rad. / sec.} = 159.155 \text{ Hz}$</p>	CO 1	K 2

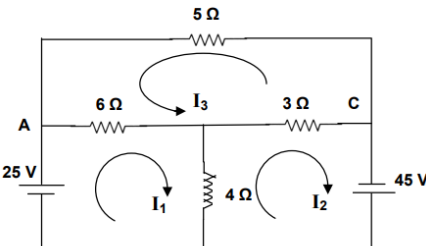Answer ALL Questions.		
PART C – (01 x 15 = 15 marks)		
20.	<p>For a given circuit, find the current and voltage drop across each resistor.</p>  <p>Three loops equations are:</p> $- 25 + 6 (I_1 + I_3) + 4 (I_1 - I_2) = 0$ $- 45 + 4 (I_2 - I_1) + 3 (I_2 + I_3) = 0$ $5 I_3 + 6 (I_3 + I_1) + 3 (I_2 + I_3) = 0$ $\begin{bmatrix} 10 & -4 & 6 \\ -4 & 7 & 3 \\ 6 & 3 & 14 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 25 \\ 45 \\ 0 \end{bmatrix} : \text{On solving}$ <p>$I_3 = -14 \text{ A}$ Current in 5Ω resistor = 14 A from A to C</p>	CO 1 K 2
OR		
21.	<p>Three similar coils each of resistance 10Ω and an inductance of 0.05H are connected in star and delta to three phase $400\text{V}, 50\text{Hz}$ symmetrical system. Find the phase current, line current, total phase power & total line power?</p> <p>(i) <u>STAR CONNECTION:-</u></p> $V_L = \sqrt{3} V_p$ $\therefore V_p = \frac{400}{\sqrt{3}} = 231 \text{ V.}$ $\text{Impedance, } Z = \sqrt{R^2 + X_L^2} = \sqrt{10^2 + (15.7)^2}$ $Z = 18.61 / 57.6^\circ$ $\text{Total } 3\phi \text{ power} = V_p I_p \cos \phi$ $\text{W.K.t } I_p = \frac{V_p}{18.61} = 12.41 \text{ A}$ $\Rightarrow \text{Total } 3\phi \text{ power} = V_p \cdot \frac{V_p}{18.61} \cdot \cos 57.6^\circ \Rightarrow 4608 \text{ W.}$	CO 1 K 2

$$\begin{aligned}
 \text{Line Power} &\Rightarrow V_L I_L \cos \phi \\
 &= (\sqrt{3} \cdot V_p) I_p \cdot \cos \phi \\
 &= (\sqrt{3} \cdot 400) \left(\frac{231}{18.61} \right) \cos(57.6^\circ) = \underline{4608 \text{ W}}
 \end{aligned}$$

(ii) DELTA CONNECTION:-

$$V_L = V_{ph} \quad ; \quad I_L = \sqrt{3} I_{ph}$$

$$\begin{aligned}
 \text{Total } 3\phi \text{ power} &= V_p I_p \cos \phi \\
 &= (400) \left(\frac{400}{18.61} \right) \cos 57.6^\circ \\
 &= \underline{4608 \text{ W}}
 \end{aligned}$$

$$\begin{aligned}
 \text{Line Power} &= V_L I_L \cos \phi \\
 &= (400) \cdot \sqrt{3} \cdot \left(\frac{400}{18.61} \right) \cdot \cos 57.6^\circ \\
 &= \underline{7970 \text{ W}}
 \end{aligned}$$