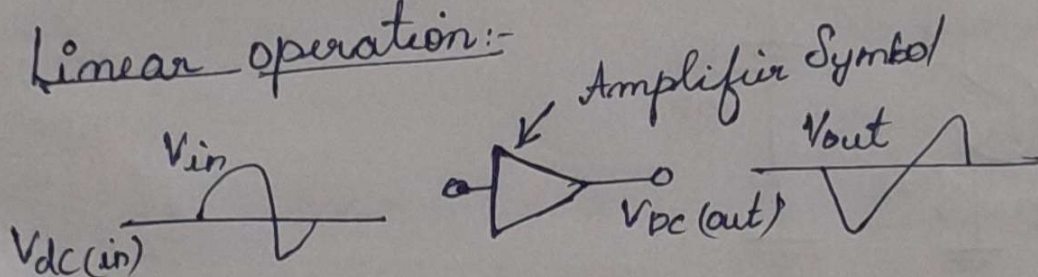


03/10/2023
Tuesday



Transistor

- Used to amplify the weak signals.

Linear operation:-



Non-Linear:

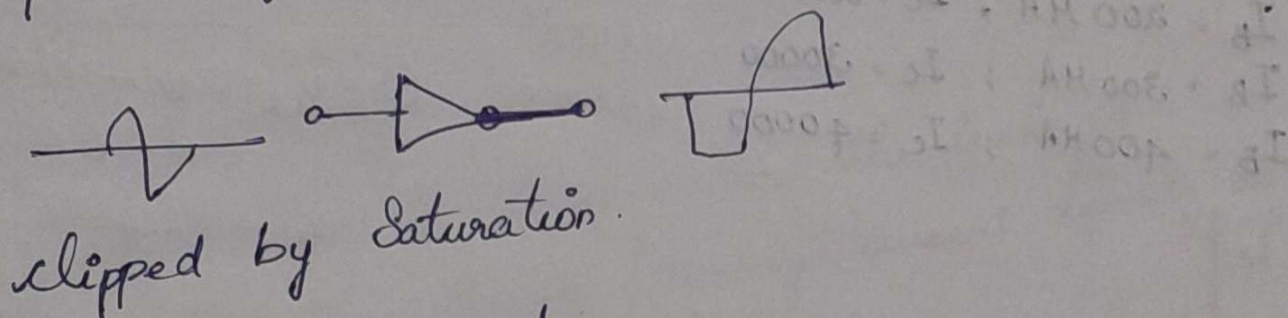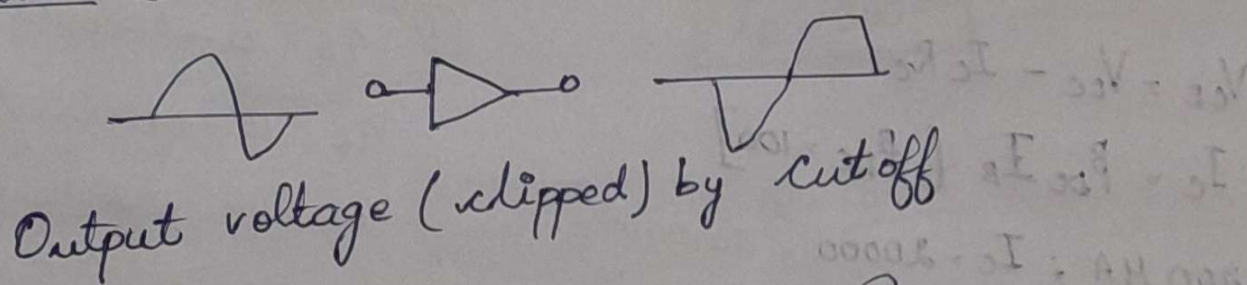

Analysis of a Transistor

→ Knowledge of both DC and AC.


→ DC level of Operation.

- Setting a desired DC voltage and current
- Set up a point where the transistor operates.
- A network must be constructed that will establish the desired operating point.

→ External dc Supply → [Biasing Circuits]

Operating point → Q-point

Q → [Quiescent point]

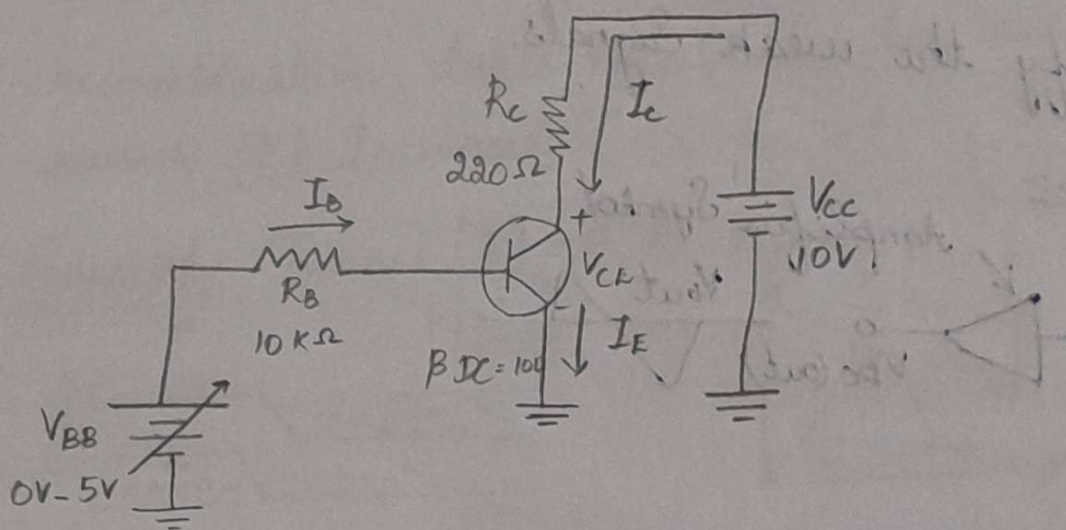

220
 20000
 220
 00000
 40000
 40000
 4400000

$$V_{CE} = V_{CC} - I_C R_C$$

$$I_C = \beta_{DC} I_B \quad [\beta_{DC} = 100]$$

$$I_B = 200 \mu A ; I_C = 20000 = 20 \times 10^{-3}$$

$$I_B = 300 \mu A ; I_C = 30000 = 30 \times 10^{-3}$$

$$I_B = 400 \mu A ; I_C = 40000 = 40 \times 10^{-3}$$

$$① V_{CE} = 10 - 20000(220)$$

$$V_{CE} = 10 - 4400000$$

$$V_{CE} = 10 - 4.4 = 5.6$$

$$② V_{CE} = 10 - 30(220)$$


$$= 10 - 6.6$$

$$V_{CE} = 3.4$$

$$③ V_{CE} = 10 - 40(220)$$

$$= 10 - 8.8$$

$$V_{CE} = 1.2$$

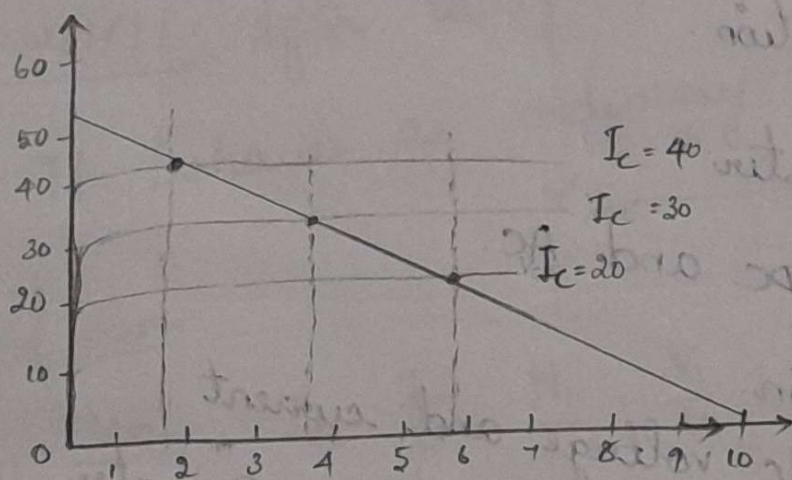

Simpler way: (DC load line)


$$V_{CE} = V_{CC} - I_C R_C$$


$$0 = V_{CC} - I_C R_C$$

$$I_C = \frac{V_{CC}}{R_C}$$

$$V_{CE} = V_{CC} - I_C R_C$$

$$V_{CE} = V_{CC}$$

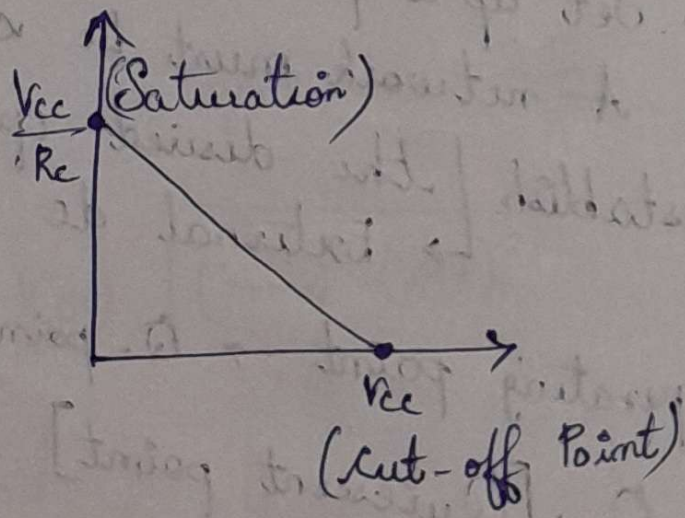

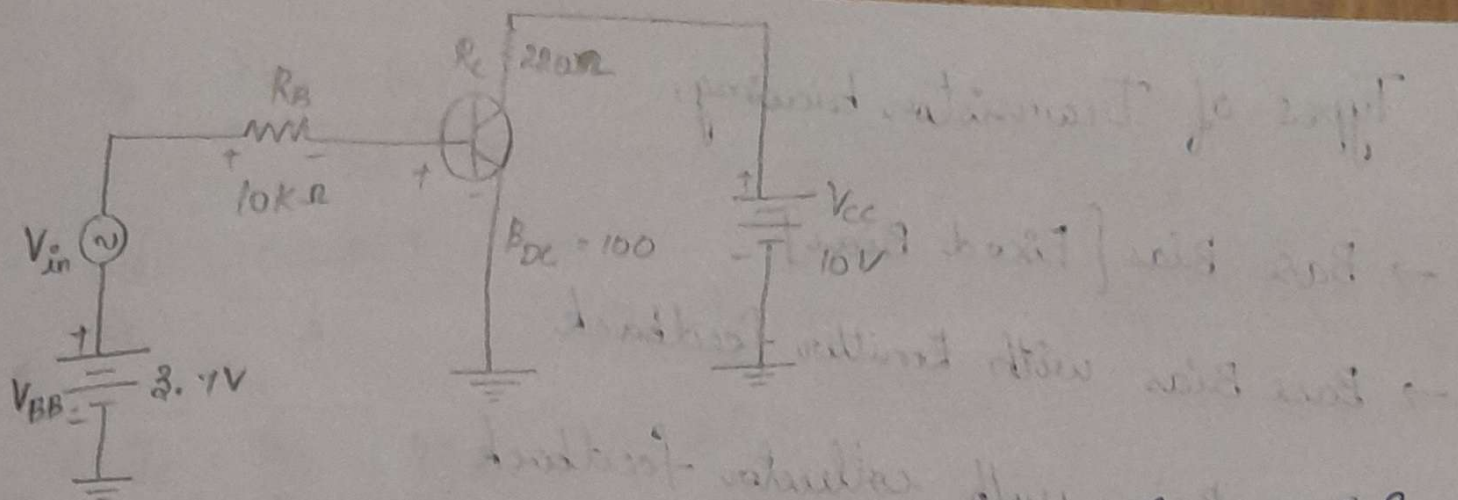

$$I_B = \frac{V_{BB} - 0.7}{R_B}$$

$$I_B = \frac{3.7 - 0.7}{10}$$

$$I_B = \frac{3}{10} = 0.3 \text{ K} = 300 \Omega$$

$$I_B = 3000 \Omega$$

$$I_B = \frac{3.7 - 0.7}{10} = \frac{3}{10} = 0.3 \text{ K} = 300 \Omega$$

$$I_B = 300 \Omega$$

04/10/2023
Wednesday

Variations in Q-Point

Thermal Runaway:

- For every 10° rise in temperature the leakage current (I_{CBO} & I_{CEO}) double. [Leakage current depends on temperature]
- Power = Voltage \times Current
- Dissipation released in the form of heat.

$$T \uparrow \rightarrow I_{CBO} \uparrow \rightarrow I_C \uparrow \rightarrow P_D$$

$$I_C = \beta I_B + I_{CEO} = \beta I_B + (1 + \beta) I_{CO}$$


Stability factor:

$$S = \frac{dI_C}{dI_{CO}}$$

Types of Transistor biasing,

- Base Bias [Fixed Bias]
- Base Bias with emitter feedback.
- Base Bias with collector feedback.
- Voltage divider Bias (Self bias)
- Emitter Bias

①. Base Bias:

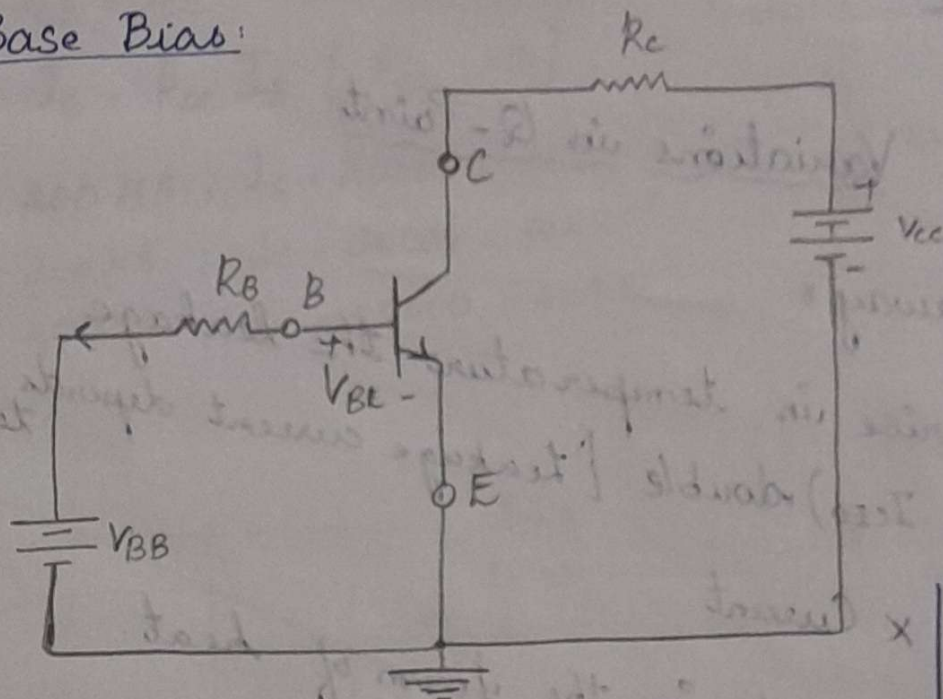

$$\begin{aligned} V_{BB} &= 10V \\ R_B &= 47K\Omega \\ R_C &= 330\Omega \\ V_{CC} &= 20V \\ P_{DC} &= 200 \end{aligned}$$

$$I_C = \beta_{DC} I_B$$

$$= 200 \left(\frac{190}{197} \right)$$

$$I_C = \frac{V_{CC}}{R_C} = \frac{20}{330}$$

$$I_C = 0.06$$

$$I_C = 39000$$



$$\downarrow$$

$$28 \times 10^{-3}$$

PROBLEMS:

- ①. Determine the Q point of the circuit and draw the DC load line. Find the maximum peak value of Base Current (I_B) for linear operation.

Assume $P_{DC} = 200$

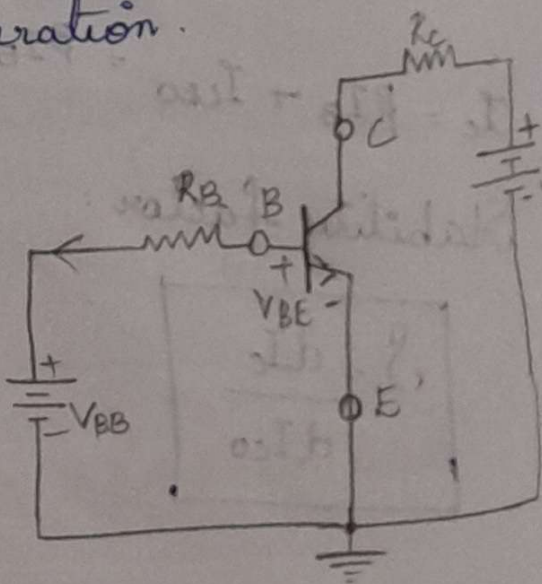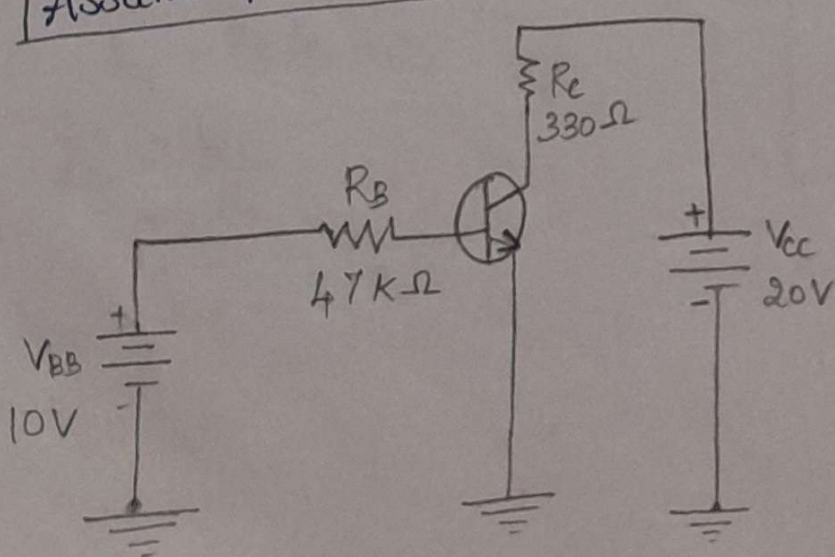

$$I_B = \frac{V_{BB} - 0.7}{R_B}$$

$$I_B = \frac{10 - 0.7}{47} = \frac{9.30}{47 \times 10^{-3}} = 0.197 \text{ mA} \approx 190 \mu\text{A}$$

DC Line $\leftarrow I_C = \frac{V_{CC}}{R_C} = \frac{20}{330} = 0.06 \text{ mA (or) } 60.6 \mu\text{A}$

$$V_{CE} = V_{CC} - I_C R_C$$

$$= 20 - (0.06)(330)$$

$$= 20 - 19.8$$

9/10/23 $V_{CE} = 0.2$

Q-Point:

Input Loop:

$$I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{10 - 0.7}{47}$$

$$I_B = 198 \mu\text{A}$$

$$I_C = \beta_{DC} I_B = (200)(198)$$

$$I_C = 39.6$$

Output Loop:

$$V_{CE} = V_{CC} - I_C R_C$$

$$= 20\text{V} - 13.07\text{V} = 6.93\text{V}$$


$$V_{CE} = 6.93\text{V}$$

$$I_C(\text{sat}) - I_{CQ} = 60.6 \mu\text{A} - 39.6 \mu\text{A}$$

$$= 21.0 \mu\text{A}$$

$$I_B = \frac{I_C}{\beta_{DC}} = \frac{21.0 \mu\text{A}}{200} = 105 \mu\text{A}$$

$$I_B(\text{peak}) = 105 \mu\text{A}$$

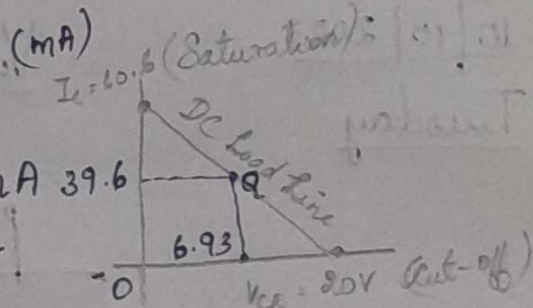

$$V_{CE} = V_{CC}$$

$$V_{CE} = 20\text{V}$$

9/10/23

Stability factor:


$$S = \frac{dI_C}{dI_{CQ}} ; I_C = \beta \cdot I_B + (1 + \beta) I_{CQ}$$

$$= \beta \times \frac{dI_B}{dI_C} + (1 + \beta) \frac{dI_{CQ}}{dI_C}$$

$$= \beta \times \frac{dI_B}{dI_C} + (1 + \beta) \frac{1}{S}$$

$$S = \frac{1 + \beta}{1 - \beta \left(\frac{dI_B}{dI_C} \right)}$$

Base Bias with Collector feedback

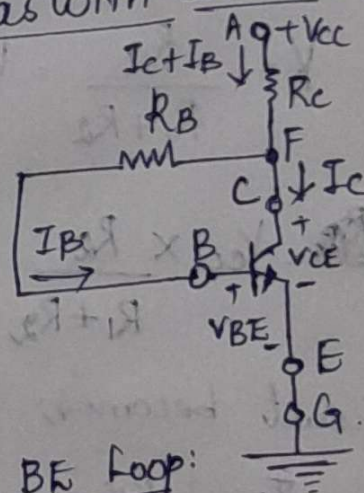

(i) KVL to BE Loop:

$$V_{BE} - V_{CC} + (I_B + I_C) R_C + I_B R_B = 0$$

$$\therefore I_C = \beta I_B$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1) R_C} = \frac{V_{CC} - V_{BE}}{R_B + \beta R_C}$$




$$I_C = \beta \cdot I_B = \frac{V_{CC} - V_{BE}}{R_C + R_B/\beta} = \frac{V_{CC}}{R_C + R_B/\beta}$$

$$(\because V_{CC} \gg V_{BE})$$

10/10/2023

Tuesday

Voltage divider Bias

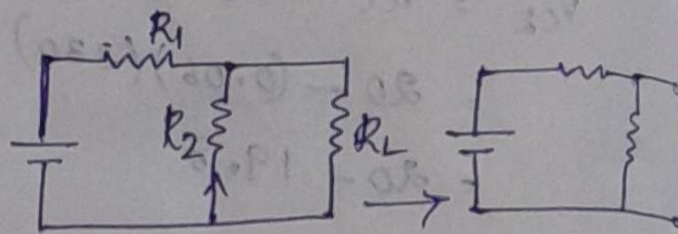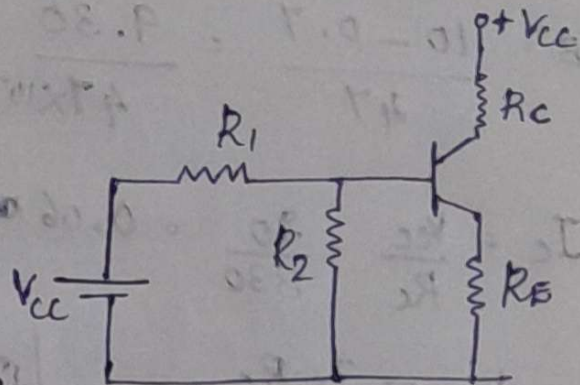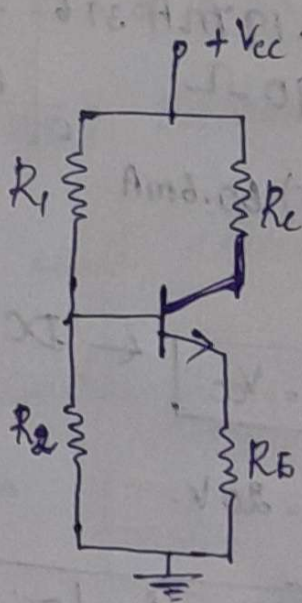

Thevenin's Theorem

Remove the load Resistance (R_L) and find the open circuit voltage.


Voltage divider rules

$$\text{Total Supply voltage} \times \frac{\text{Resistance}}{\text{Total resistance}} = \text{Voltage}$$

$$V_1 = \frac{R_2}{R_1 + R_2} = V_2$$

$$V_{th} = V_{cc} \times \frac{R_2}{R_1 + R_2} ; R_{th} = \frac{R_1 R_2}{R_1 + R_2}$$

The circuit becomes;

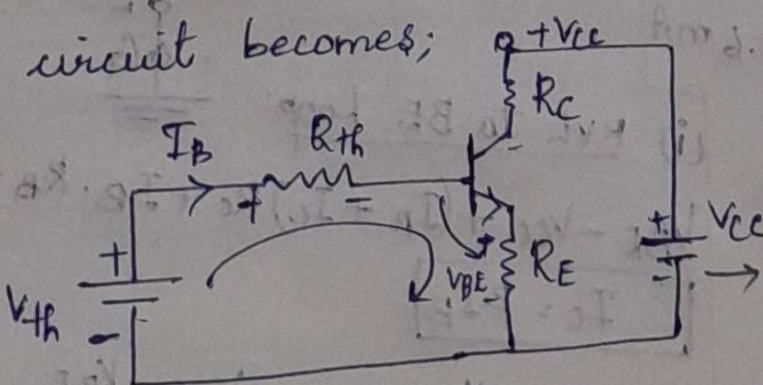

$$V_{th} = I_B R_{th} + V_{BE} + I_E R_E$$

$$I_B = \frac{V_{th} - V_{BE} - I_E R_E}{R_{th} + R_E}$$

$$\text{output loop} \Rightarrow V_{cc} = I_C R_C + V_{CE} + I_E R_E$$


$$\therefore I_E = I_C + I_B$$

$$V_{th} = I_B R_{th} + V_{BE} + I_E R_E$$

$$V_{th} = I_B R_{th} + V_{BE} + (I_C + I_B) R_E$$

$$I_B = \frac{V_{th} - V_{BE} - I_C R_E}{R_{th} + R_E}$$

$$\therefore I_C = \beta I_B$$

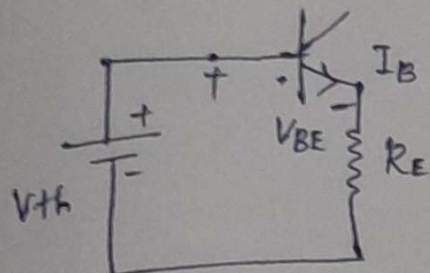

$$V_{th} = V_{BE} + I_E R_E$$

$$I_E = \frac{V_{BE} - V_{th}}{R_E}$$

Output loop:

$$V_{cc} = I_C R_C + V_{CE} + I_E R_E$$

$$V_{CE} = V_{cc} - I_C R_C - I_E R_E$$

$$= V_{cc} - I_C R_C - I_C R_E$$

$$V_{CE} = V_{cc} - I_C (R_C + R_E)$$

$$S = \frac{1 + \beta}{1 - \beta \left(\frac{dI_B}{dI_C} \right)}$$

$$I_B = \frac{V_{th} - V_{BE} - I_C R_E}{R_{th} + R_E}$$

$$\frac{dI_B}{dI_C} = \frac{1}{R_{th} + R_E} \cdot \frac{d}{dI_C} (V_{th} - V_{BE} - I_C R_E)$$

$$\frac{dI_B}{dI_C} = \frac{-R_E}{R_{th} + R_E}$$

$$\Rightarrow S = \frac{1 + \beta}{1 + \beta \left(\frac{R_E}{R_{th} + R_E} \right)}$$

$$[R_{th} \ll R_E]$$

$$S = \frac{1 + \beta}{1 + \beta \left(\frac{R_{th}}{R_E} + 1 \right)}$$

$$= \frac{1 + \beta}{1 \left(1 + \frac{R_{th}}{R_E} \right) + \beta} = \frac{(1 + \beta) \left(1 + \frac{R_{th}}{R_E} \right)}{1 + \beta + \frac{R_{th}}{R_E}}$$

$$[R_{th} \ll R_E]$$

$S = 1 \rightarrow$ circuit more stable
 $[R_{th} \ll R_E]$

$$S = \frac{1 + \beta}{1 + \beta} = 1 \quad \boxed{S = 1}$$

9/10/23

Base bias with collector

feedback Contd.:-

(P) KVL to CE Loop:

$$V_{CE} - V_{cc} + (I_C + I_B) R_C = 0$$

$$V_{CE} = V_{cc} - I_C R_C \quad [I_C = 1 \text{ mA}, I_B = 1 \text{ mA}]$$

Stability factor:

$$V_{BE} - V_{cc} + (I_B + I_C) R_C + I_B R_B = 0$$

$$I_B = \frac{V_{cc} - V_{BE} - I_C R_C}{R_C + R_B}$$

$$S = \frac{1 + \beta}{1 - \beta \left(\frac{dI_B}{dI_C} \right)}$$

$$= \frac{1 + \beta}{1 - \beta \left[\frac{-R_C}{R_C + R_B} \right]} = \frac{1 + \beta}{1 + \beta \left[\frac{R_C}{R_C + R_B} \right]}$$