

Design a 8x1 Mux using Verilog.

Design code:

```
module mux8x1(  
    input [7:0] in,  
    input [2:0] sel,  
    output reg out  
);
```

```
always @(*) begin
```

```
    case(sel)
```

```
        3'b000: out = in[0];
```

```
        3'b001: out = in[1];
```

```
        3'b010: out = in[2];
```

```
        3'b011: out = in[3];
```

```
        3'b100: out = in[4];
```

```
        3'b101: out = in[5];
```

```
        3'b110: out = in[6];
```


```
        3'b111: out = in[7];
```

```
        default: out = 1'b0;
```

```
    endcase
```

```
end
```

```
endmodule
```

 

Test Bench:

```
`module tb_mux8x1;
```

```
    reg [7:0] in;
```

```
    reg [2:0] sel;
```

```
    wire out;
```

```
    mux8x1 uut (
```

```
        .in(in),
```

```
        .sel(sel),
```

```
        .out(out)
```

```
    );
```

```
    initial begin
```

```
        in = 8'b00000000; sel = 3'b000;
```

```
        #10 in = 8'b10101010; sel = 3'b000;
```

```
        #10 in = 8'b10101010; sel = 3'b001;
```

```
        #10 in = 8'b10101010; sel = 3'b010;
```

```
        #10 in = 8'b10101010; sel = 3'b011;
```

```
        #10 in = 8'b10101010; sel = 3'b100;
```

```
        #10 in = 8'b10101010; sel = 3'b101;
```

```
        #10 in = 8'b10101010; sel = 3'b110;
```

```
        #10 in = 8'b10101010; sel = 3'b111;
```

```
    After change:
```

```
        #10 in = 8'b11110000; sel = 3'b000;
```

```
        #10 in = 8'b11110000; sel = 3'b001;
```

```
        #10 in = 8'b11110000; sel = 3'b010;
```

```
        #10 in = 8'b11110000; sel = 3'b011;
```

```
        #10 in = 8'b11110000; sel = 3'b100
```

```
#10 in = 8'b11110000; sel = 3'b101;  
#10 in = 8'b11110000; sel = 3'b110;  
#10 in = 8'b11110000; sel = 3'b111;
```

```
#10 $finish;
```


```
end
```

```
initial begin
```

```
$monitor("Time=%0d, in=%b, sel=%b, out=%b", $time, in, sel, out);
```

```
end
```


```
endmodule
```

 

Design a 4x1 mux using Verilog hdl

Design code:
 
```
module mux4x1(  
    input [3:0] in,  
    input [1:0] sel,  
    output reg out  
);  
  
always @(*) begin  
    case (sel)  
        2'b00: out = in[0];  
        2'b01: out = in[1];  
        2'b10: out = in[2];  
        2'b11: out = in[3];  
        default: out = 1'b0;  
    endcase  
end  
  
endmodule
```



Test Bench:

```
module tb_mux4x1;

    reg [3:0] in;
    reg [1:0] sel;
    wire out;
    mux4x1 uut (
        .in(in),
        .sel(sel),
        .out(out)
    );

    initial begin
        in = 4'b0000; sel = 2'b00;

        #10 in = 4'b1010; sel = 2'b00;
        #10 in = 4'b1010; sel = 2'b01;
        #10 in = 4'b1010; sel = 2'b10;
        #10 in = 4'b1010; sel = 2'b11;

        After change:
        #10 in = 4'b1100; sel = 2'b00;
        #10 in = 4'b1100; sel = 2'b01;
        #10 in = 4'b1100; sel = 2'b10;
        #10 in = 4'b1100; sel = 2'b11;

        #10 $finish;
    end

    initial begin
        $monitor("Time=%0d, in=%b, sel=%b, out=%b", $time, in, sel, out);
    end

endmodule
```

Name	Value								
in[3:0]	0			2,029,035,149,996 ps		2,029,035,149,998 ps			2,029,035,150,000 ps
in[3]	0				1				
in[2]	0								
in[1]	0								
in[0]	0								
sel[1:0]	1				1				
sel[1]	0								
sel[0]	1								
out	1								

Design SISO reg using Verilog hdl

Design code:

```
module siso(  
    input wire clk,  
    input wire reset,  
    input wire serial_in,  
    output wire serial_out  
);  
  
    reg [3:0] shift_reg;  
  
    always @(posedge clk or posedge reset) begin  
        if (reset) begin  
            shift_reg <= 4'b0000;  
        end else begin  
            shift_reg <= {shift_reg[2:0], serial_in};  
        end  
    end  
  
    assign serial_out = shift_reg[3];  
  
endmodule
```

Test Bench:

```
module tb_siso_shift_register;

// Testbench signals

reg clk;          // Clock signal
reg rst;          // Reset signal
reg serial_in;    // Serial input
wire serial_out;  // Serial output

// Instantiate the SISO Shift Register
siso_shift_register uut (
    .clk(clk),
    .rst(rst),
    .serial_in(serial_in),
    .serial_out(serial_out)
);

// Clock generation
initial begin
    clk = 0;
    forever #5 clk = ~clk; // 10 time units clock period
end
endmodule
```


end

// Test

sequence

initial

begin

 // Initialize signals

 rst = 1; //

 Activate reset serial_in

 = 0;

 #10; // Wait for some time

 rst = 0; // Deactivate reset

 // Apply serial input bits

 serial_in = 1; #10; //

 Shift in 1

 serial_in = 0; #10; // Shift in 0

 serial_in = 1; #10; // Shift in 1

 serial_in = 0; #10; // Shift in 0

 serial_in = 1; #10; // Shift in 1

 serial_in = 1; #10; // Shift in 1

 serial_in = 0; #10; // Shift in 0


 serial_in = 1; #10; // Shift in 1

 #10;

 \$stop;

end

endmodule

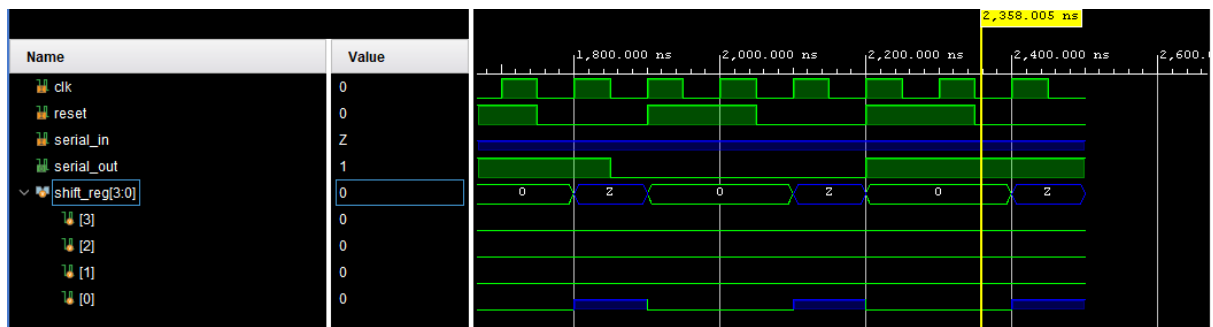

Design a Carry Look Ahead Adder using Verilog hdl

Design code:

```
module claa(
```

```
    input [3:0] a,
    input [3:0] b,
    input cin,
    output [3:0] sum,
    output cout
```

```
);
```

```
    wire [3:0] p, g;
    wire [3:0] carry;
```

```
    assign p = a ^ b;
```

```
    assign g = a & b;
```

```
    assign carry[0] = cin;
```

```
    assign carry[1] = g[0] | (p[0] & cin);
```


```
    assign carry[2] = g[1] | (p[1] & g[0]) | (p[1] & p[0] & cin);
```

```
    assign carry[3] = g[2] | (p[2] & g[1]) | (p[2] & p[1] & g[0]) | (p[2] & p[1] & p[0] & cin);
```

```
    assign cout = g[3] | (p[3] & carry[3]);
```

```
    assign sum = p ^ {carry[2:0], cin};
```

```
endmodule
```

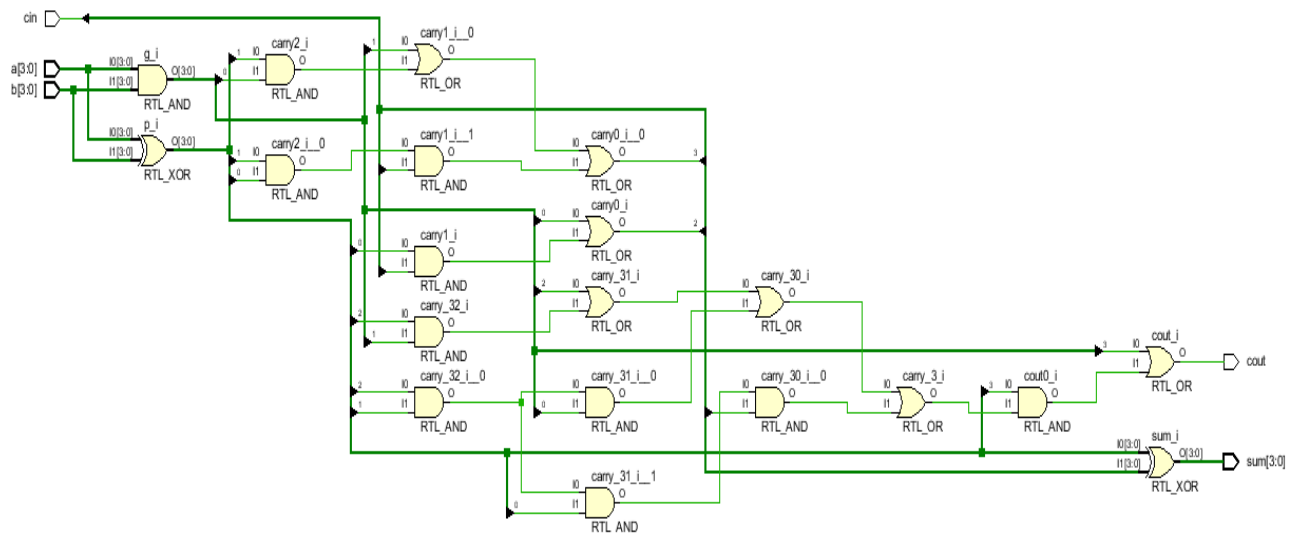

Test Bench:

```
module tb_carry_lookahead_adder_4bit;
```

```
    reg [3:0] a;  
    reg [3:0] b;  
    reg cin;
```

```
    wire [3:0] sum;  
    wire cout;
```

```
    carry_lookahead_adder_4bit uut (  
        .a(a),  
        .b(b),  
        .cin(cin),  
        .sum(sum),  
        .cout(cout)  
    );
```

```
    initial begin
```

```
        a = 4'b0000;  
        b = 4'b0000;  
        cin = 1'b0;
```

```
        #10;
```

```
        Test Case 1: Add 0 + 0 + 0
```

```
        a = 4'b0000;  
        b = 4'b0000;  
        cin = 1'b0;
```

```
        #10;
```

```
        $display("TC1: a=%b, b=%b, cin=%b, sum=%b, cout=%b", a, b, cin, sum, cout);
```

```
        Test Case 2: Add 5 + 3 + 0
```

```
        a = 4'b0101;  
        b = 4'b0011;  
        cin = 1'b0;
```

```
        #10;
```

```
        $display("TC2: a=%b, b=%b, cin=%b, sum=%b, cout=%b", a, b, cin, sum, cout);
```

```
        Test Case 3: Add 9 + 6 + 0
```

```
        a = 4'b1001;  
        b = 4'b0110;  
        cin = 1'b0;
```

```
        #10;
```

```
        $display("TC3: a=%b, b=%b, cin=%b, sum=%b, cout=%b", a, b, cin, sum, cout);
```

```
        Test Case 4: Add 15 + 15 + 1
```

```
        a = 4'b1111;
```

```









b = 4'b1111;
cin = 1'b1;
#10;
$display("TC4: a=%b, b=%b, cin=%b, sum=%b, cout=%b", a, b, cin, sum, cout);

Test Case 5: Add 8 + 7 + 1
a = 4'b1000;
b = 4'b0111;
cin = 1'b1;
#10;
$display("TC5: a=%b, b=%b, cin=%b, sum=%b, cout=%b", a, b, cin, sum, cout);

$finish;
end

endmodule

```

Name		Value	271,319,700,000 ps			
>  a[3:0]		1	271,319,699,996 ps			
>  b[3:0]		0	271,319,699,998 ps			
 cin		0	271,319,700,000 ps			
>  sum[3:0]		0				
 cout		1				
>  p[3:0]		0				
>  g[3:0]		1				
>  carry[3:0]		1				

Design a Carry Skip Adder using Verilog hdl

Design Code:

```

module csa(
    input [3:0] a,
    input [3:0] b,
    input cin,
    output [3:0] sum,
    output cout
);
    wire [3:0] p;
    wire [3:0] g;
    wire carry_in;
    wire carry_skip;

    assign p = a ^ b;

    assign g = a & b;

    assign sum = p ^ {carry_in, carry_in, carry_in, cin};


    assign carry_in = (g[0] | (p[0] & cin));

    assign carry_skip = p[3] & p[2] & p[1] & p[0];

    assign cout = (carry_skip) cin : (g[3] | (p[3] & carry_in));

endmodule

```

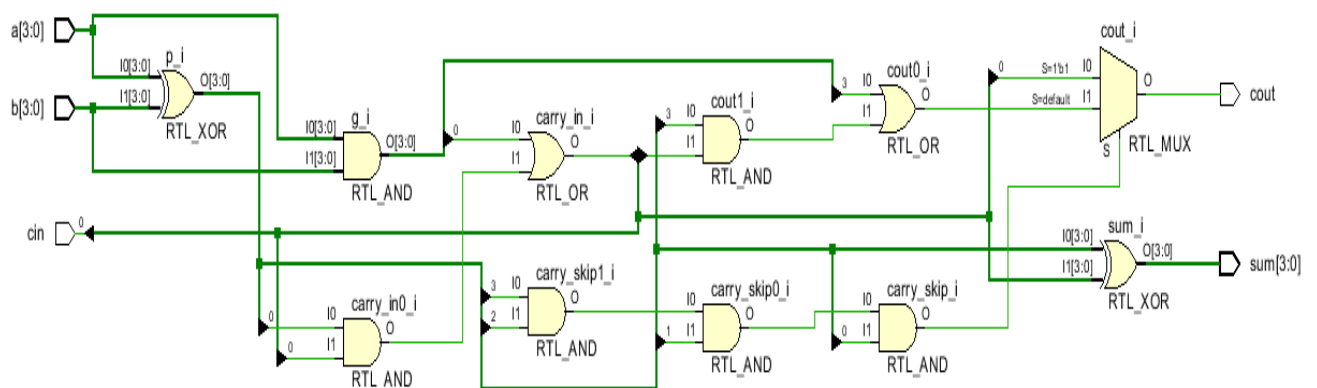

Test Bench:

```
module tb_carry_skip_adder_4bit;

    reg [3:0] a;
    reg [3:0] b;
    reg cin;
    wire [3:0] sum;
    wire cout;

    carry_skip_adder_4bit uut (
        .a(a),
        .b(b),
        .cin(cin),
        .sum(sum),
        .cout(cout)
    );

    initial begin
        a = 4'b0000;
        b = 4'b0000;
        cin = 1'b0;

        #10;

        Test Case 1: Add 0 + 0 + 0

        a = 4'b0000;
        b = 4'b0000;
        cin = 1'b0;

        #10;

        $display("TC1: a=%b, b=%b, cin=%b, sum=%b, cout=%b", a, b, cin, sum, cout);

        Test Case 2: Add 5 + 3 + 0

        a = 4'b0101;
        b = 4'b0011;
```

```
cin = 1'b0;  
#10;  
$display("TC2: a=%b, b=%b, cin=%b, sum=%b, cout=%b", a, b, cin, sum, cout);
```

Test Case 3: Add 9 + 6 + 1

```
a = 4'b1001;  
b = 4'b0110;  
cin = 1'b1;  
#10;  
$display("TC3: a=%b, b=%b, cin=%b, sum=%b, cout=%b", a, b, cin, sum, cout);
```

Test Case 4: Add 15 + 15 + 1

```
a = 4'b1111;  
b = 4'b1111;  
cin = 1'b1;  
#10;  
$display("TC4: a=%b, b=%b, cin=%b, sum=%b, cout=%b", a, b, cin, sum, cout);
```

Test Case 5: Add 8 + 7 + 0

```
a = 4'b1000;  
b = 4'b0111;  
cin = 1'b0;  
#10;  
$display("TC5: a=%b, b=%b, cin=%b, sum=%b, cout=%b", a, b, cin, sum, cout);
```

```
$finish;
```

```
end
```

```
endmodule
```