

DEPARTMENT OF ECE


SRM Nagar, Kattankulathur – 603203, Chengalpattu District, Tamilnadu

Academic Year: 2023-2024 (EVEN)
Test: CLAT- 1
Date: 17.02.2024
Course Code & Title: 21ECC202T & Analog and Linear Electronic Circuits
Duration: 4 PM-4:50 PM
Year & Sem: II & IV
Max. Marks: 25
Course Articulation Matrix:


Course Articulation Matrix		Program Outcomes (POs)														
		Graduate Attributes												PSOs		
COs	At the end of this course, learners will be able to:	1	2	3	4	5	6	7	8	9	10	11	12	1	2	3
CO-1:	Apply the small-signal equivalent circuit in the analysis of single and multistage transistor amplifier circuits	2	2	3		-	-	-	-	-	-	-	-	-	-	3
CO-2:	Infer the DC and AC characteristics of the operational amplifier	2	2	3		-	-	-	-	-	-	-	-	-	-	3
CO-3:	Classify and identify the suitable feedback topologies and oscillators	2	2	3		-	-	-	-	-	-	-	-	-	-	3
CO-4:	Elucidate and design linear and non-linear applications of op-amp	2	2	3		-	-	-	-	-	-	-	-	-	-	3
CO-5:	Illustrate the function of application-specific ICs	2	2	3		-	-	-	-	-	-	-	-	-	-	3

Part – A (5x1 = 5 Marks)					
Answer all the questions					
Q. No	Question	Marks	BL	CO	PO
1.	c) Linear	1	1	1	1
2.	d) increase in overall gain and reduction in overall bandwidth	1	1	1	1
3.	c) MOSFET	1	1	1	1
4.	b) All Capacitor	1	1	1	1
5.	a) Darlington pair	1	1	1	1
Part – B (2 x 4 = 8 Marks)					
Instructions: Answer any 2 Questions					

6.

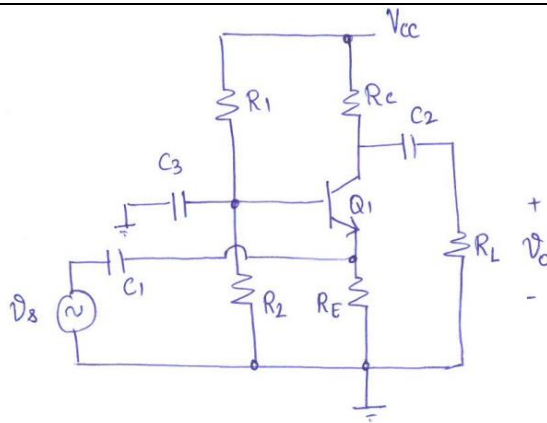

(1 Mark)

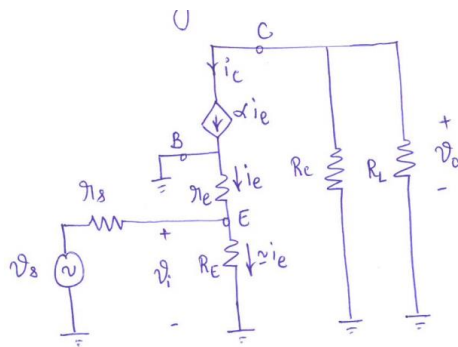

(1 Mark)

Voltage Gain

$$\begin{aligned} \text{Open-Circuit Voltage gain, } A_{vo} &= \frac{v_o}{v_i} \bigg|_{R_L = \infty} = \frac{-i_o R_o}{-i_e (r_e \parallel R_E)} \\ &= \frac{\alpha i_e R_c}{i_e (r_e \parallel R_E)} \approx \frac{R_c}{r_e \parallel R_E} \text{ as } \alpha \approx 1 \\ &\approx \frac{R_c}{r_e} \text{ if } r_e \ll R_E \\ &= g_m R_c \end{aligned}$$

By taking into account the effect of R_L , the voltage gain of the amp. can be expressed as

$$A_v = A_{vo} \times \frac{R_L}{R_o + R_L} = g_m R_c \times \frac{R_L}{R_c + R_L} = g_m (R_c \parallel R_L)$$

By taking into account the effect of r_s , the voltage gain of the CB amp. can be expressed as

$$\begin{aligned} A_{vs} &= A_v \times \frac{r_{in}}{r_s + r_{in}} \approx g_m (R_c \parallel R_L) \times \frac{r_e}{r_s + r_e} \\ &\approx \frac{R_c \parallel R_L}{r_s + r_e} \text{ since } g_m \approx \frac{1}{r_e} \end{aligned}$$





(2 Marks)

4

2

1

2
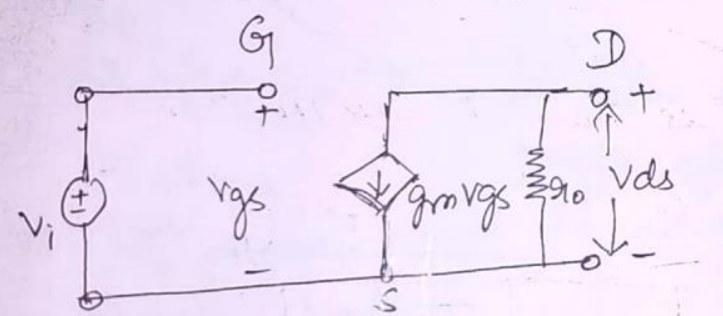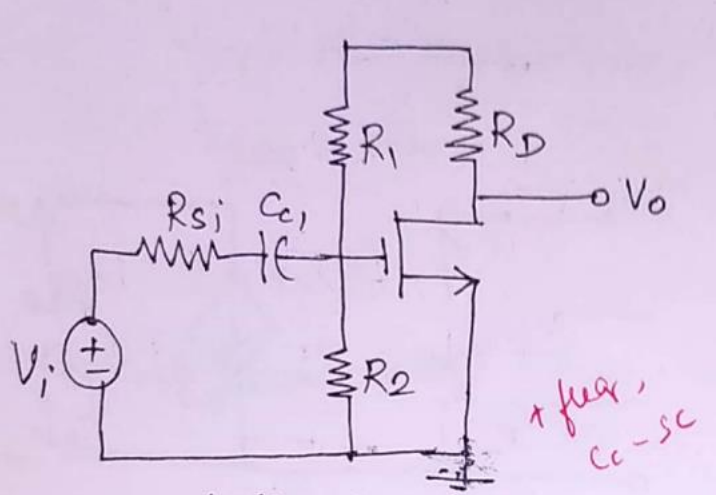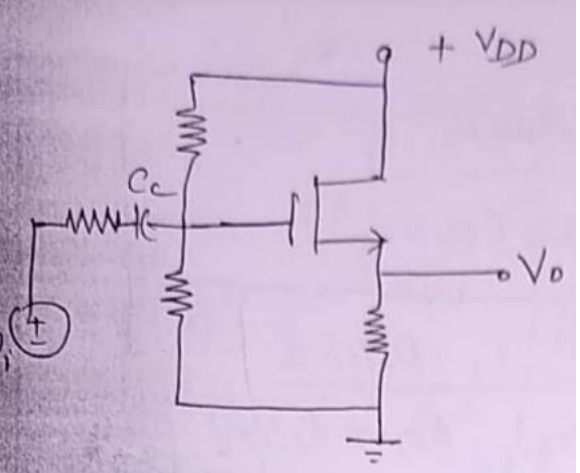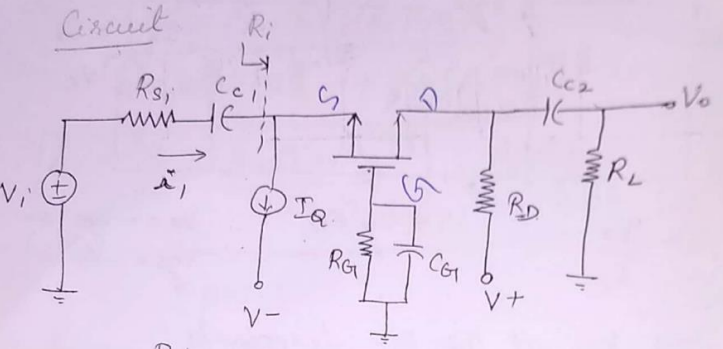
<p>7.</p>	 <p>(1 Marks)</p>  <p>(1 Marks)</p>  <p>(1 Marks)</p>  <p>(1 Marks)</p>	<p>4</p>	<p>2</p>	<p>1</p>	<p>2</p>
<p>8.</p>	<p>The Miller effect and Miller capacitance are factors in the high-frequency characteristics of MOSFET circuits</p> $C_M = C_{gd} (1 + g_m R_L)$	<p>4</p>	<p>2</p>	<p>1</p>	<p>2</p>

* Using Millers Theorem, equivalent capacitance is
 $C_{eq} = (1 + A_v) C = (1 + A_v) C_{gd}$


(2 marks)

When the MOSFET is biased in the saturation region, as in an amplifier circuit, the major contribution to the total gate-to-drain capacitance C_{gd} is the overlap capacitance. This overlap capacitance is multiplied because of the Miller effect and may become a significant factor in the bandwidth of an amplifier.

(2 Marks)

Part – C (1 x 12 = 12 Marks)


9.

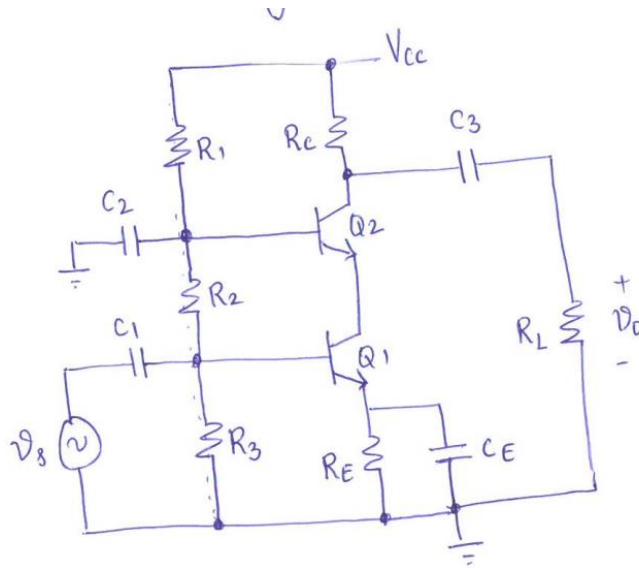

(2 Marks)

Ac analysis

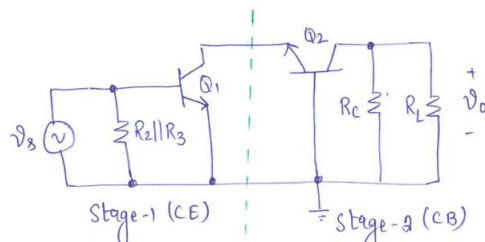The Ac equivalent ckt of the cascode amp. can be drawn as



(2 Marks)

Input Resistance, Rin

$$R_{in1} = R_2 \parallel R_3 \parallel R_{ib1} \quad \text{where } R_{ib1} = r_{i\pi}$$

$$R_{in2} \approx r_{ie}$$

(1 Marks)

output Resistance, R_{out}

$$R_{out1} = R_{in2}$$

$$R_{out2} = R_c \parallel R_L$$

(1 Marks)

Voltage gain, A_v

$$A_{v1} = -g_m \times \text{eff. resis. @ collector of stage-1}$$
$$= -g_m r_e \approx 1$$

$$A_{v2} = g_m \times \text{eff. resis. @ collector of stage-2}$$
$$= g_m (R_c \parallel R_L)$$

\therefore The overall voltage gain of the amps. is given by

$$A_v = A_{v1} \times A_{v2}$$
$$= g_m (R_c \parallel R_L)$$

(2 Marks)

Current Gain, A_i

$$A_i = A_v \times \frac{R_{in}}{R_{out}} = \frac{g_m (R_c \parallel R_L) \times (R_2 \parallel R_3 \parallel R_{ib1})}{(R_c \parallel R_L)}$$


$$= g_m (R_2 \parallel R_3 \parallel R_{ib1})$$

(2 Marks)

$$A_v = g_m (R_c \parallel R_L) = 20 \text{ mA/V} * (1.5 \text{ k}\Omega \parallel 10 \text{ k}\Omega) = 26 \text{ (2 Marks)}$$

Or

10.

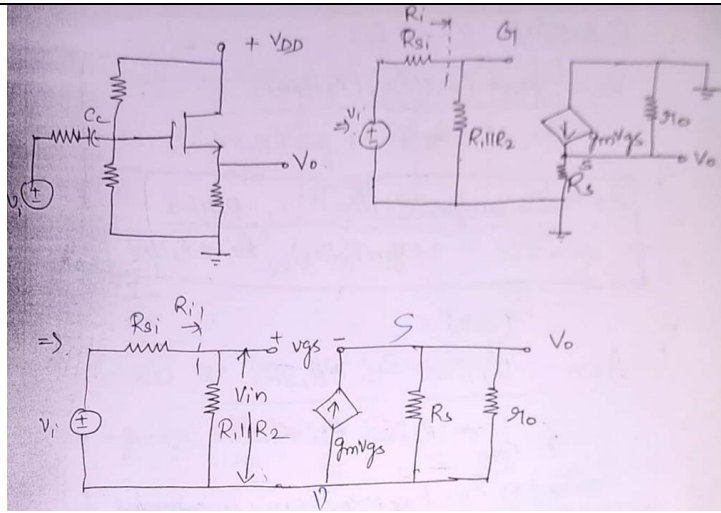

(6 Marks)

$$A_v = \frac{V_o}{V_i}$$

$$V_o = g_m v_{gs} (R_s \parallel R_o)$$

$$V_{in} = \frac{V_i \times R_1 \parallel R_2}{R_{si} + R_1 \parallel R_2} \rightarrow (1)$$

But

$$V_{in} = v_{gs} + (g_m v_{gs}) (R_s \parallel R_o)$$

$$V_{in} = v_{gs} [1 + g_m (R_s \parallel R_o)]$$

$$v_{gs} = \frac{V_{in}}{1 + g_m (R_s \parallel R_o)}$$

Sub in V_o

$$V_o = \frac{g_m V_{in} (R_s \parallel R_o)}{1 + g_m (R_s \parallel R_o)} \rightarrow (2)$$

12

3

1

3

Substitute ① in ②

$$V_o = \frac{g_m V_i (R_1 \parallel R_2) (R_s \parallel R_o)}{(R_{s_i} + R_1 \parallel R_2) (-1 + g_m (R_s \parallel R_o))}$$

$$A_v = \frac{V_o}{V_i} = \frac{g_m (R_s \parallel R_o)}{1 + g_m (R_s \parallel R_o)} \cdot \frac{R_1 \parallel R_2}{R_{s_i} + R_1 \parallel R_2}$$

(Q4)

$$A_v = \frac{\frac{R_s \parallel R_o}{\frac{1}{g_m} + (R_s \parallel R_o)}}{R_{s_i} + R_1 \parallel R_2}$$

(2 Marks)

Input Impedance

$$R_i = R_1 \parallel R_2$$

Output Impedance

A small o/p resistance is desirable when the circuit is to act as ideal voltage source & drive load circuit without suffering loading effects.

To find the o/p resistance let $V_i = 0$ & test voltage is applied to the o/p.

$R_o = \frac{V_x}{I_x}$

$V_x + V_{gs} = 0 \quad \therefore V_x = -V_{gs} \text{ or } V_{gs} = -V_x$

Apply KCL at the o/p terminal.

$$I_x + g_m V_{gs} = \frac{V_x}{R_L} + \frac{V_x}{R_s}$$

Sub $V_{gs} = -V_x$ in the above equation

$$I_x = \frac{V_x}{R_L} + \frac{V_x}{R_s} + g_m V_x$$

$$I_x = V_x \left[\frac{1}{R_L} + \frac{1}{R_s} + g_m \right]$$

$$V_x = I_x \left(R_L \parallel R_s \parallel \frac{1}{g_m} \right)$$

$$R_o = \frac{V_x}{I_x} = (R_L \parallel R_s \parallel \frac{1}{g_m})$$

(2 Marks)

Voltage gain A_v

$$A_v = \frac{g_m (R_s \parallel R_L)}{1 + g_m (R_s \parallel R_L)} \cdot \frac{R_i}{R_i + R_{s_i}}$$

$$= \frac{(11.3)(0.75 \parallel 12.5)}{1 + (11.3)(0.75 \parallel 12.5)} \cdot \frac{120}{120 + 4} = 0.860$$

$\underline{R_i} = R_1 \parallel R_2 = 120 \text{ k}\Omega$

(2 Marks)

Signature of Course Teacher

Approved by the Course Coordinator

Approved by the Academic Advisor