

**Test: CLA-T1**
**Date: xx-Feb-2024**
**Course Code & Title: 21ECC202T – Analog and Integrated Electronic Circuits**
**Time: 12:30 to 01:20 P.M**
**Year & Sem: 2<sup>nd</sup> Year / 4<sup>th</sup> Sem / B.Tech / ECE**
**Max. Marks: 25**

Course Articulation Matrix		Program Outcomes (POs)														
		Graduate Attributes												PSOs		
COs	At the end of this course, learners will be able to:	1	2	3	4	5	6	7	8	9	10	11	12	1	2	3
<b>CO-1:</b>	Apply the small-signal equivalent circuit in the analysis of single and multistage transistor amplifier circuits	2	2	3		-	-	-	-	-	-	-	-	-	-	3
<b>CO-2:</b>	Infer the DC and AC characteristics of the operational amplifier	2	2	3		-	-	-	-	-	-	-	-	-	-	3
<b>CO-3:</b>	Classify and identify the suitable feedback topologies and oscillators	2	2	3		-	-	-	-	-	-	-	-	-	-	3
<b>CO-4:</b>	Elucidate and design linear and non-linear applications of op-amp	2	2	3		-	-	-	-	-	-	-	-	-	-	3
<b>CO-5:</b>	Illustrate the function of application-specific ICs	2	2	3		-	-	-	-	-	-	-	-	-	-	3

**Part – A (5 x 1 = 5 Marks)**
**Answer ALL the following questions**

	Marks	BL	CO	PO
1. A small-signal amplifier	1	2	1	1
(a) always has an output signal in the mV range.				
(b) uses only a small portion of its load line.				
(c) goes into saturation once in each input cycle.				
(d) refers to a multi-stage amplifier.				
2. Each stage of a four-stage amplifier has a voltage gain of 15. The overall voltage gain is	1	3	1	2
(a) 94.1 dB				
(b) 19.4 dB				
(c) 35.6 dB				
(d) 69.1 dB				
3. A certain common-source amplifier has a voltage gain of 50. If the source bypass capacitor is removed,	1	3	1	2
(a) the transconductance will increase				
(b) the transconductance will decrease				
(c) the voltage gain will increase				
(d) the voltage gain will decrease				
4. The common-gate (CG) amplifier differs from both the CS and CD configurations in that it has a	1	4	1	2
(a) much higher voltage gain				
(b) much lower voltage gain				
(c) much higher input resistance				
(d) much lower input resistance				
5. A certain FET has a $g_m=4 \text{ mS}$ , internal $r_{ds}=10 \text{ K}\Omega$ and external $R_D=1.5 \text{ K}\Omega$ . What is the voltage gain of the FET including the effect of $r_{ds}$ ?	1	3	1	2
(a) 6				
(b) 40				
(c) 5.2				
(d) 46				

**Part – B (2 x 4 = 8 Marks)**
**Answer ANY 2 of the following questions**



	Marks	BL	CO	PO
6. Sketch the circuit of a two-stage direct-coupled BJT amplifier using a common-emitter input stage and an emitter-follower output stage. Discuss the circuit operation.	4	3	1	2

	Marks	BL	CO	PO
7. Discuss the effect of coupling capacitors, bypass capacitors and internal transistor capacitances on the frequency response of an amplifier.	4	2	1	1
8. Sketch the low- and mid-frequency equivalent circuit for a MOSFET. Identify all the components and briefly explain how the equivalent circuit represents the device.	4	3	1	2

**Part – C (1 x 12 = 12 Marks)**  
**Answer ANY 1 of the following question**

9.a. The emitter-follower circuit has $R_B=74\text{ K}\Omega$ , $R_E=750\Omega$ , $R_L=5\text{ K}\Omega$ , $r_s=200\Omega$ , $V_{CC}=18\text{V}$ and $V_{BE}=0.7\text{V}$ . Assume $\beta_F=100$ and $V_A=\infty$	12	5	1	3
(i) Derive expressions for the input resistance $R_{in}$ , output resistance $R_{out}$ , voltage gain $A_v$ and current gain $A_i$ . (ii) Find the Q-point defined by $I_B$ , $I_C$ and $V_{CE}$ , and the small-signal parameters $g_m$ and $r_\pi$ . (iii) Calculate $R_{in}$ , $R_{out}$ , $A_v$ and $A_i$ values.				
[or]				
9.b. The source-follower circuit has $R_1=700\text{ K}\Omega$ , $R_2=300\text{ K}\Omega$ , $R_S=10\text{K}\Omega$ , $R_L=20\text{ K}\Omega$ , $r_s=50\Omega$ , $V_{DD}=15\text{V}$ , $C_1=C_2=\infty$ , $V_A=\infty$ , $k_n=1\text{mA/V}^2$ . and $V_t=1.7\text{V}$ . Assume $\beta_F=100$ and $V_A=\infty$ .	12	5	1	3
(i) Derive expressions for the input resistance $R_{in}$ , output resistance $R_{out}$ and voltage gain $A_v$ . (ii) Determine $I_D$ , $V_{GS}$ , $V_{DS}$ and $g_m$ . (iii) Calculate the values for $R_{in}$ , $R_{out}$ and $A_v$ .				

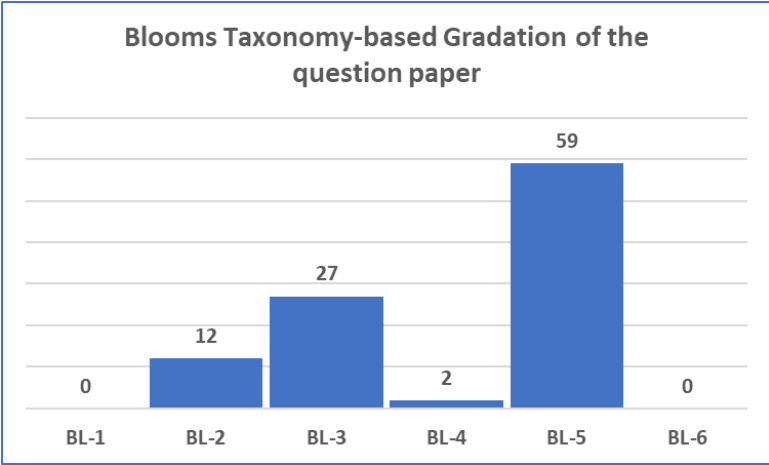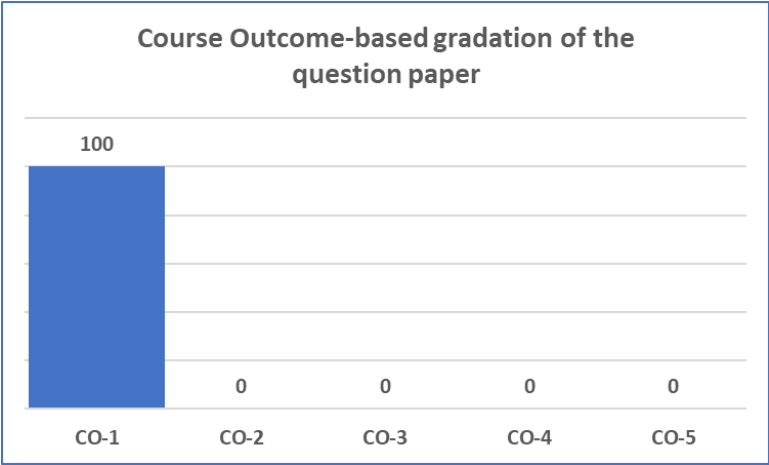**Course Outcome (CO) and Bloom’s Level (BL) Coverage in Questions**



**Evaluation Sheet**

Name of the Student:

Register No.:

Part-A (5 x 1 = 5 marks)					
Q. No.	CO	PO	Max. Marks	Marks Scored	Total Marks
1.	CO-1	PO-1	1		
2.	CO-1	PO-2	1		
3.	CO-1	PO-2	1		
4.	CO-1	PO-2	1		
5.	CO-1	PO-2	1		
Part-B (2 x 4 = 8 marks)					
6.	CO-1	PO-2	4		
7.	CO-1	PO-1	4		
8.	CO-1	PO-2	4		
Part-C (1 x 12 = 12 marks)					
9.a.	CO-1	PO-3	12		
9.b.	CO-1	PO-3	12		
Grand Total					

CO	Max. Marks	Marks Scored
CO-1	25	
CO-2	-	-
CO-3	-	-
CO-4	-	-
CO-5	-	-
CO-6	-	-
Total	25	

PO	Max. Marks	Marks Scored
PO-1	1	
PO-2	12	
PO-3	12	
PSO-3	-	-
Total	25	

## Answer Key

Test : CLA-T1

Date : 17/2/2024

Year & Sem : II year / IV Sem / B-Tech / ECE

Max. Marks : 25


Course : 21ECC202T - Analog and Integrated Electronic Circuits

### Part-A

1. (b) Uses only a small portion of its load line
2. (a) 94.1 dB
3. (d) the Voltage gain will decrease
4. (d) much lower input resistance
5. (c) 5.2

### Part-B

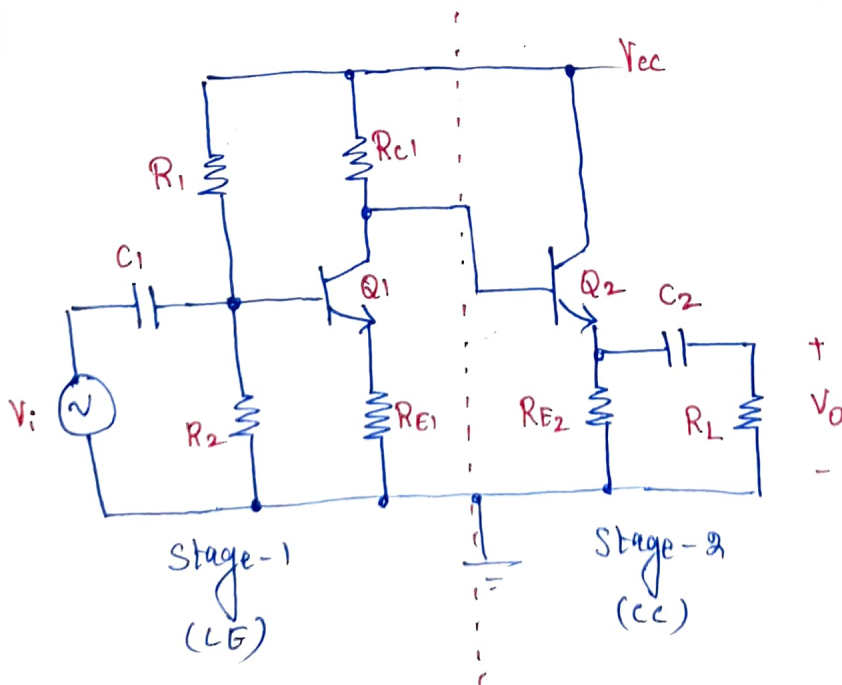6. Two-Stage Direct-Coupled BJT amplifier with i/p stage as a CE amp. and op stage as an o/p stage.



- in direct-coupled amplifiers, the o/p of one stage is directly connected to the o/p of the next stage.
- the dc biasing point of the 1<sup>st</sup> stage affects the dc conditions of the 2<sup>nd</sup> stage.
- the 1<sup>st</sup> stage is a CE amplifier that is designed to offer the maximum voltage gain.
- the 2<sup>nd</sup> stage is a CE amplifier that is designed to offer a low o/p resistance.
- if  $A_{v1}$  and  $A_{v2}$  are the voltage gains of the 1<sup>st</sup> & 2<sup>nd</sup> stage, respectively, then the overall voltage gain is


$$A_v = A_{v1} \times A_{v2}$$

- there will be a loading effect due to the interaction between stages, and the effective voltage gain will be reduced.
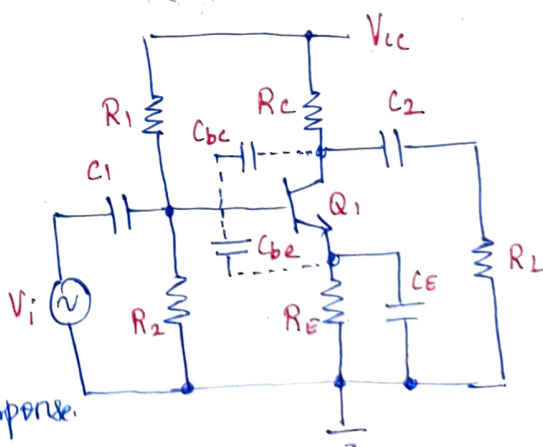
## 7 Effects of the capacitive elements on an amplifier's operation.

consider a CE BJT amps.

- $C_1$  &  $C_2$  are the coupling capa.
- $C_E$  is the bypass capa.
- $C_{be}$  &  $C_{bc}$  are the transistor's internal capacitances.
- The coupling & bypass capa. affect the amp's low-freq. response.
- The internal capa. affect the amp's high-freq. response.





When an amplifier is operating at mid-range frequencies

- the coupling and bypass capa. are considered to be ideal shorts and the internal transistor capa. are considered to be ideal opens.
- So, the effect of these capa. on the amplifier's operation are negligible.

Recall that  $X_c = \frac{1}{2\pi fC}$ . This formula shows that the capacitive reactance varies inversely with frequency.

At lower frequencies,


- the reactances of the coupling and bypass capacitors ~~de~~ increases with decreasing frequency, and hence, these capacitors can no longer be considered as shorts because their reactances are large enough to cause a significant signal drop across these capacitors, thus reducing the voltage gain.

At higher frequencies,


- the coupling and bypass capa. become effective ac shorts and do not affect the amp's response.
- however, the transistor internal capa. can no longer ~~to~~ be considered as opens because their reactances become small enough reducing the amplifier's gain.

# 8. Small-Signal models of MOSFET.


## CS MOSFET amplifier

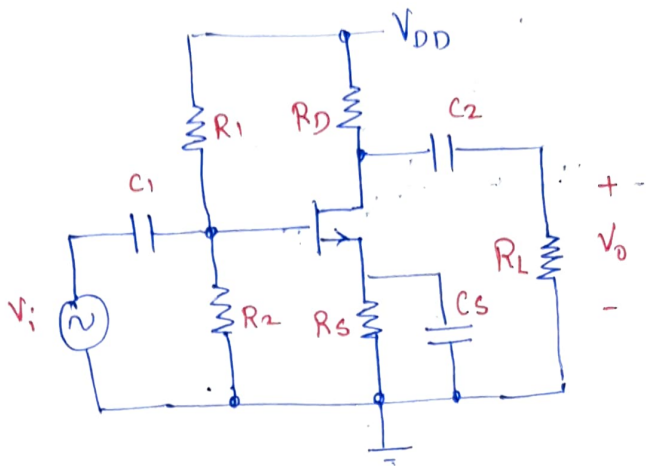

## Low-Frequency Equivalent circuit

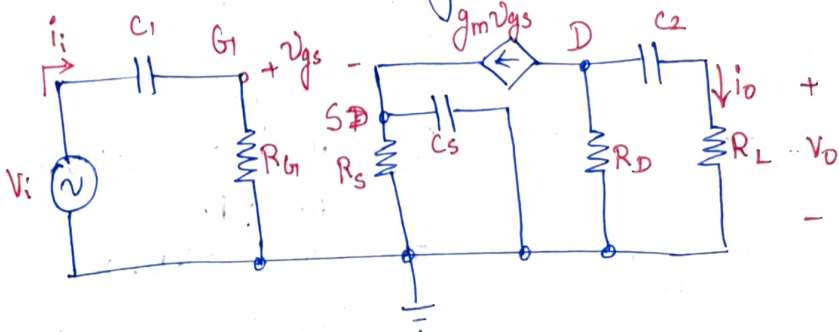


## Mid-Frequency equivalent circuit

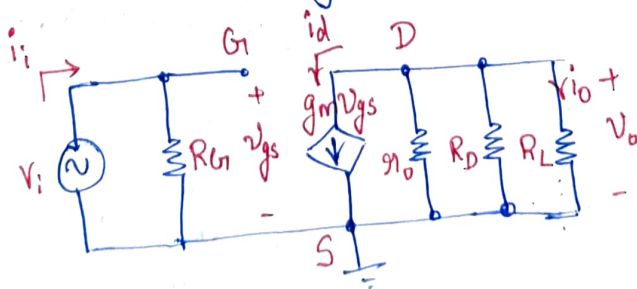


## Part - c

9.a. Emitter follower

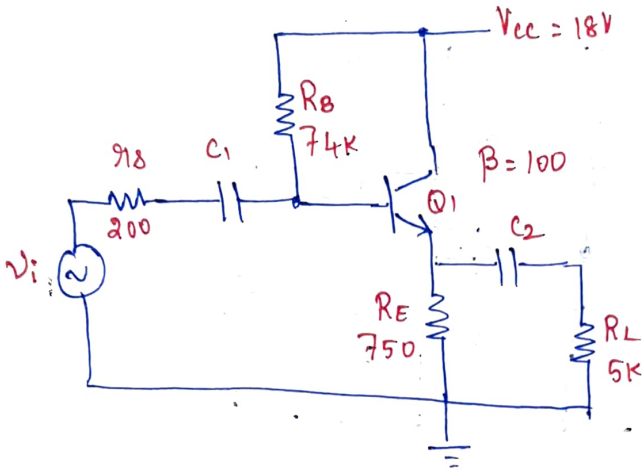

Dc operation

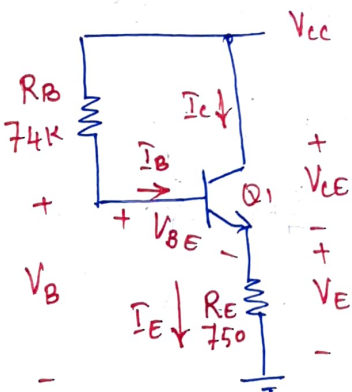

$$V_B = V_{BE} + I_E R_E$$


$$\Rightarrow I_E = \frac{V_B - V_{BE}}{R_E}$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + \beta R_E} = 116 \mu A$$

$$I_C = \beta I_B = 11.6 \text{ mA}$$

$$I_E = (\beta + 1) I_B = 11.72 \text{ mA}$$

Small-signal operation.

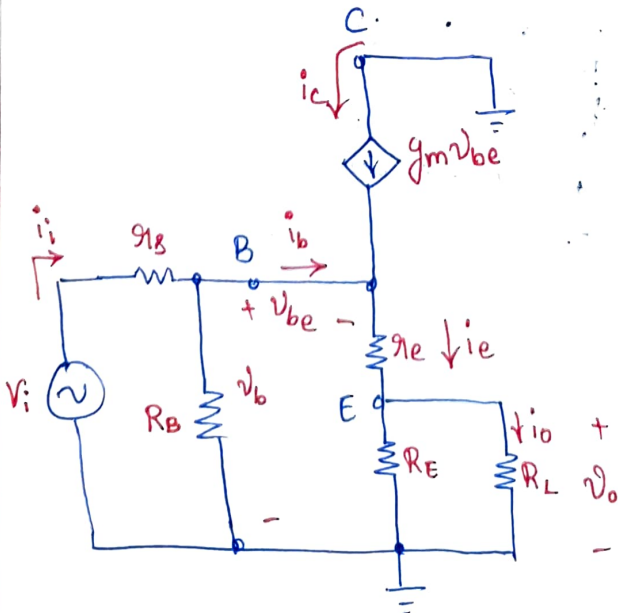

$$g_m = \frac{I_C}{V_T} = 0.446 \frac{A}{V}$$

$$r_{\pi} = \frac{\beta}{g_m} = 224 \Omega$$

$$r_e = \frac{\alpha}{g_m} \approx \frac{1}{g_m} = 2.24 \Omega$$

Input impedance looking into the base is

$$Z_b = \beta (r_e + R_E) = 75.22 \text{ K}$$

Input impedance of the amplifier is

$$R_{in} = R_B \parallel Z_b = 37.3 \text{ K}$$

Output impedance of the amplifier is

$$R_o = r_e \parallel R_E = 2.23 \text{ } \Omega$$

open-circuit voltage gain (ie, excluding  $R_L$ ) of the amp. is

$$A_{vo} = \frac{R_E}{r_e + R_E} = 0.997$$

Voltage Gain of the amp. including the effect of  $R_L$  is

$$A_v = \frac{A_{vo} \times R_L}{R_o + R_L} = 0.9966$$


Total Voltage gain of the amplifier including the effect of the internal resistance of the signal source is

$$A_{vs} = A_v \times \frac{R_i}{r_{is} + R_i} = 0.991$$

Current gain of the amplifier is


$$A_i = -(\beta + 1) = -101$$

#### 9.b. Source Follower

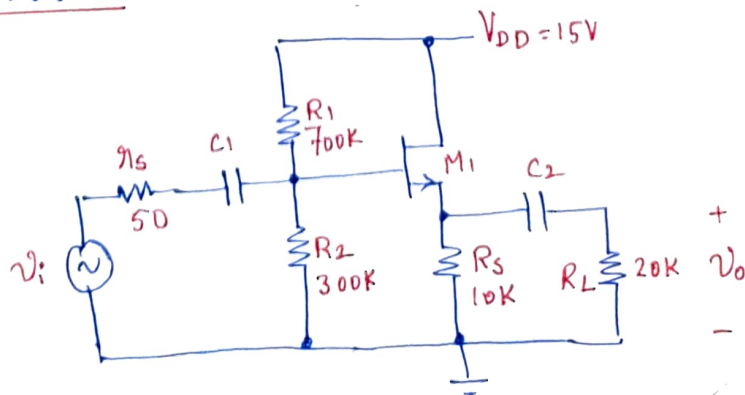



## Small-Signal operation

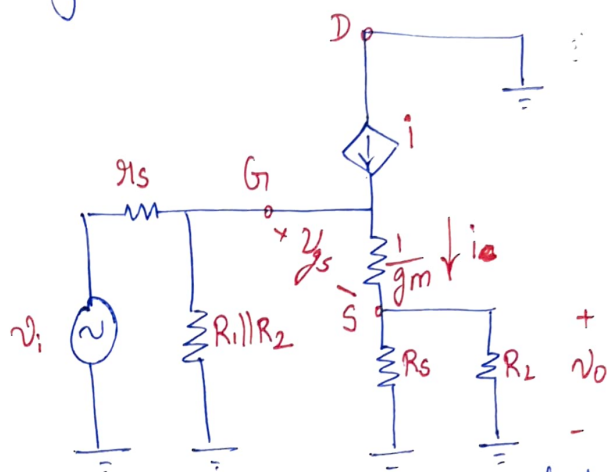

Since  $g_m$  value is not provided, the student has the freedom to choose its value. Assume a nominal value of  $g_m$  as  $\frac{1\text{mA}}{\text{V}}$ .

Input impedance,  $R_{in} = R_1 \parallel R_2 = 210\text{ k}\Omega$

output impedance,  $R_o = \frac{1}{g_m} \parallel R_s \parallel R_L = 869\Omega$

open-circuit voltage gain (excluding  $R_L$ )  $\left. \vphantom{\begin{matrix} \text{open-circuit voltage gain} \\ \text{(excluding } R_L \end{matrix}} \right\} A_{vo} = \frac{R_s}{\frac{1}{g_m} + R_s} = 0.91$

Voltage gain (including  $R_L$ ),  $A_v = \frac{R_s \parallel R_L}{\frac{1}{g_m} + (R_s \parallel R_L)} = 0.87$

Voltage gain (including  $r_s$ ),  $A_{vs} = A_v \times \frac{R_{in}}{r_s + R_{in}} = 0.8698$