

Multiplier

- Multiplicand: $Y = (y_{M-1}, y_{M-2}, \dots, y_1, y_0)$


- Multiplier: $X = (x_{N-1}, x_{N-2}, \dots, x_1, x_0)$

- Product:
$$P = \left(\sum_{j=0}^{M-1} y_j 2^j \right) \left(\sum_{i=0}^{N-1} x_i 2^i \right) = \sum_{i=0}^{N-1} \sum_{j=0}^{M-1} x_i y_j 2^{i+j}$$


						y_5	y_4	y_3	y_2	y_1	y_0	multiplicand
						x_5	x_4	x_3	x_2	x_1	x_0	multiplier
						$x_0 y_5$	$x_0 y_4$	$x_0 y_3$	$x_0 y_2$	$x_0 y_1$	$x_0 y_0$	
					$x_1 y_5$	$x_1 y_4$	$x_1 y_3$	$x_1 y_2$	$x_1 y_1$	$x_1 y_0$		
				$x_2 y_5$	$x_2 y_4$	$x_2 y_3$	$x_2 y_2$	$x_2 y_1$	$x_2 y_0$			
			$x_3 y_5$	$x_3 y_4$	$x_3 y_3$	$x_3 y_2$	$x_3 y_1$	$x_3 y_0$				
		$x_4 y_5$	$x_4 y_4$	$x_4 y_3$	$x_4 y_2$	$x_4 y_1$	$x_4 y_0$					
	$x_5 y_5$	$x_5 y_4$	$x_5 y_3$	$x_5 y_2$	$x_5 y_1$	$x_5 y_0$						
p_{11}	p_{10}	p_9	p_8	p_7	p_6	p_5	p_4	p_3	p_2	p_1	p_0	product

				1	0	1	0	1	0		Multiplicand
x				1	0	1	1				Multiplier
<hr/>											
				1	0	1	0	1	0		} Partial products
			1	0	1	0	1	0			
		0	0	0	0	0	0				
+	1	0	1	0	1	0					
<hr/>											
	1	1	1	0	0	1	1	1	0		Result

Array Multiplier

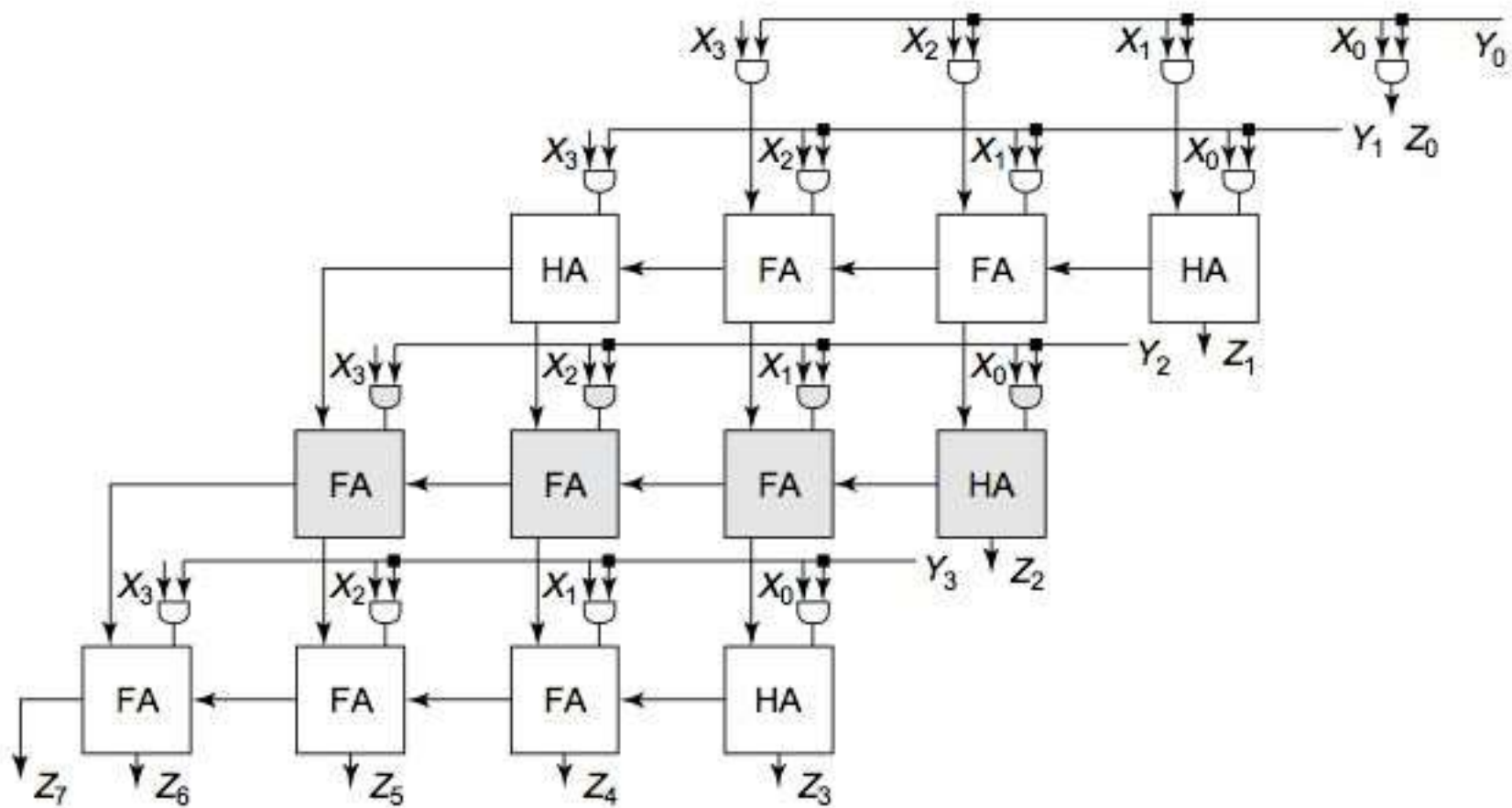

Critical path

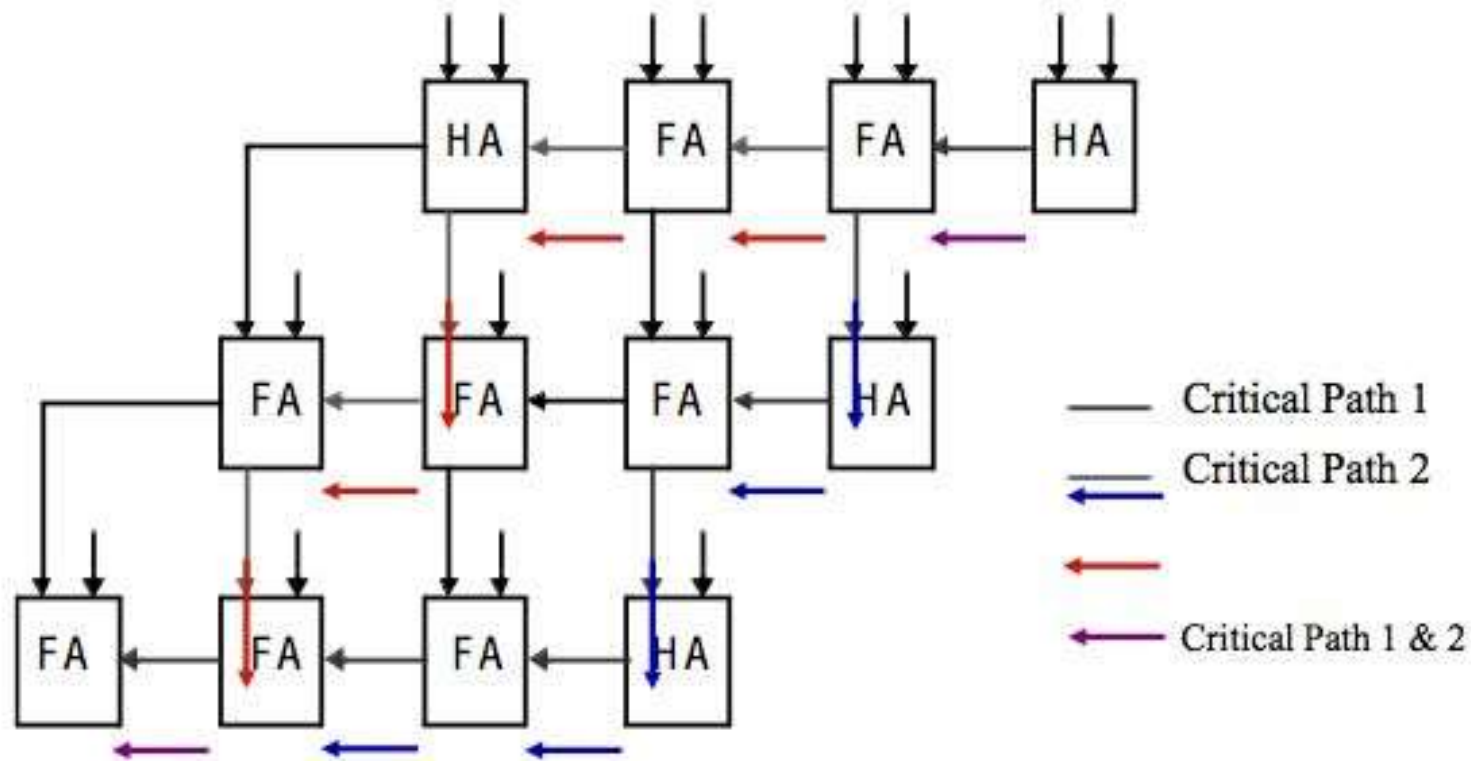


$$t_{mult} \approx [(M-1) + (N-2)]t_{carry} + (N-1)t_{sum} + (N-1)t_{and}$$


Multiplication Algorithm

- Generation of partial products
- Adding up partial products
 - Sequentially (sequential shift and add)
 - Serially (combinational shift and add)
 - In parallel
- Speed-up techniques
 - Reduce the number of partial products
 - Accelerate addition of partial products

BRAUN Multiplier

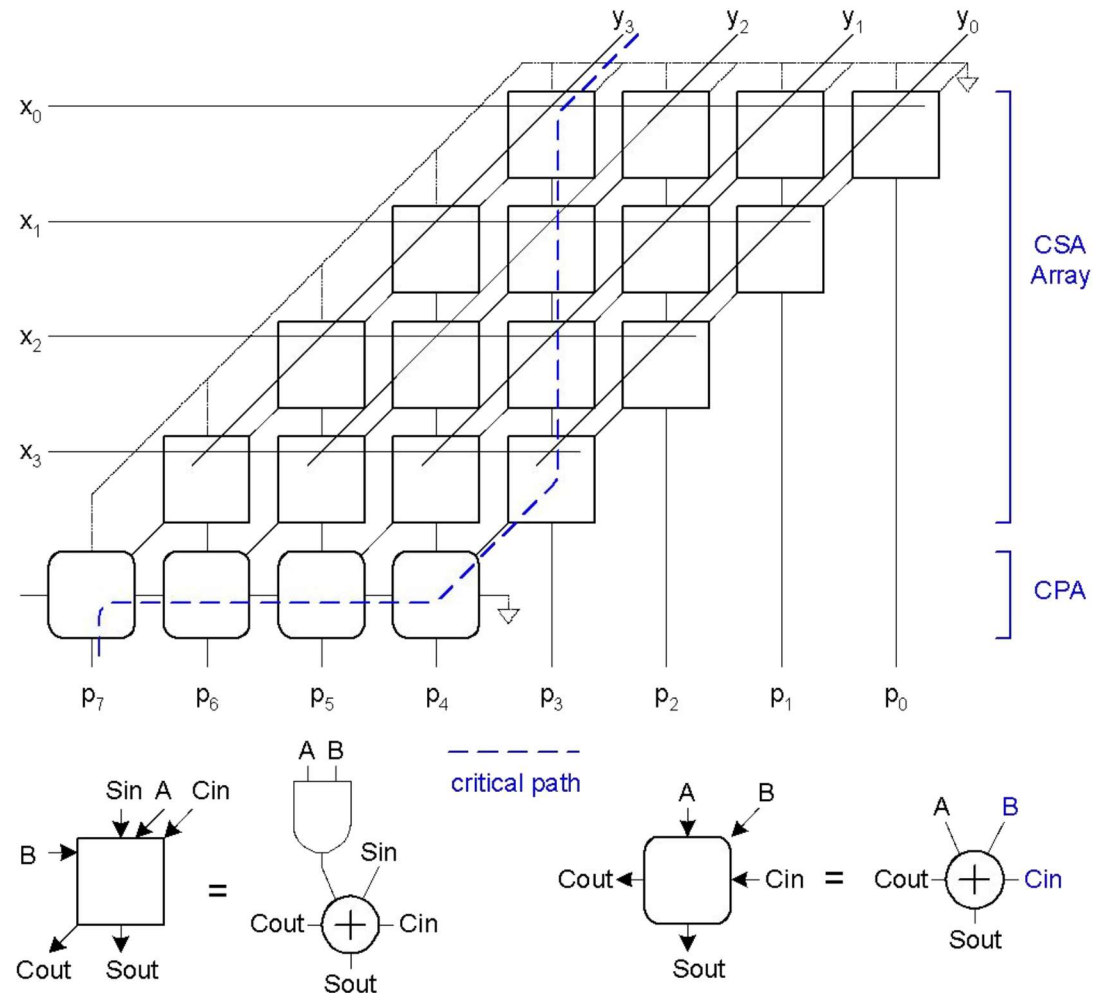- Consists of an array of AND gates and CSA arranged in an iterative structure and a final CPA
- Does not require any logic registers
- Restricted to multiplication of two unsigned numbers



 

- Performs well for unsigned operands that are less than 16 bits in terms of speed, power and area
- Simple and regular structure as compared to the other multipliers
- No. of components required increases quadratically with the no. of bits
- The delay of the multiplier is given by

$$t_{mult} = (N-1)t_{carry} + (N-1)t_{and} + t_{merge}$$

Booth's Multiplier

- Multiplies two signed binary numbers in two's complement notation.
- Uses shifting than adding to increase their speed.
- Recall grade school trick
When multiplying by 9:
 - Multiply by 10 (easy, just shift digits left)
 - Subtract once
- Booth's algorithm applies same principle

When using Booth's Algorithm:

- You will need twice as many bits in your **product** as you have in your original two **operands**.
- The **leftmost bit** of your operands (both your multiplicand and multiplier) is a SIGN bit, and cannot be used as part of the value.
- Decide which operand will be the **multiplier** and which will be the **multiplicand**
- Convert both operands to **two's complement** representation using X no. of bits

- X must be at least one more bit than is required for the binary representation of the numerically larger operand
- Begin with a product that consists of the multiplier with an additional 'X no. of leading zero bits'.
- For our example, let's multiply **$(-5) \times 2$**
The numerically larger operand (5) would require 3 bits to represent in binary (101). So we must use AT LEAST 4 bits to represent the operands, to allow for the sign bit.
- Let's use 5-bit 2's complement
-5 is 11011 (multiplier)
2 is 00010 (multiplicand)

- The multiplier is:
11011 (-5 in 2's complement)
- Add 5 leading zeros to the **multiplier** to get the **beginning product**:

00000 11011

STEP 1

- Use the **LSB** and the **previous LSB** to determine the arithmetic action.
If it is the **FIRST** pass, use 0 as the previous LSB.
- Possible arithmetic actions:
 - 00 ☐ no arithmetic operation
 - 01 ☐ add multiplicand to left half of product
 - 10 ☐ subtract multiplicand from left half of product
 - 11 ☐ no arithmetic operation

STEP 2

- Perform an **arithmetic right shift (ASR)** on the entire product.
- **NOTE:** For X-bit operands, Booth's algorithm requires X passes.
- Initial Product and **previous LSB**
00000 11011 0
- (Note: Since this is the first pass, we use 0 for the previous LSB)
- **Pass 1, Step 1:** Examine the last 2 bits
00000 1101**1** 0
- The last two bits are **10**, so we need to subtract the **multiplicand** from left half of product

Pass 1, Step 1: Arithmetic action

(1) 00000 (left half of product)
 -00010 (multiplicand)

 11110 (uses a phantom borrow)

Place result into **left half** of product

11110 11011

Step 2: ASR (arithmetic shift right)

Before ASR

11110 11011

After ASR

11111 01101

(left-most bit was 1, so a 1 was shifted in on the left)

Pass 1 is complete.

- Current Product and previous LSB

11111 01101 1

- Pass 2, Step 1: Examine the last 2 bits

11111 01101 1

- The last two bits are 11, so we do NOT need to perform an arithmetic action just proceed to step 2.
- Step 2: ASR (arithmetic shift right)

Before ASR

11111 01101 1

After ASR

11111 10110 1

(left-most bit was 1, so a 1 was shifted in on the left)

- Pass 2 is complete.

- Current Product and **previous LSB**
11111 10110 1
- **Pass 3**, Step 1: Examine the last 2 bits
11111 10110 1
The last two bits are **01**, so we need to add the **multiplicand** to the left half of the product

Arithmetic action

$$\begin{array}{r}
 (1) \quad 11111 \quad (\text{left half of product}) \\
 \quad +00010 \quad (\text{multiplicand}) \\
 \hline
 \quad 00001 \quad (\text{drop the leftmost carry})
 \end{array}$$

Place result into **left half** of product

00001 10110 1

- Step 2: ASR (arithmetic shift right)

Before ASR

00001 10110 1

After ASR

00000 11011 0

(left-most bit was 0, so a 0 was shifted in on the left)

- Pass 3 is complete.

PASS 4

- Current Product and previous LSB

00000 11011 0

- Step 1: Examine the last 2 bits

00000 11011 0

- The last two bits are 10, so we need to subtract the **multiplicand** from the left half of the product

- Step 1: Arithmetic action

$$\begin{array}{r}
 (1) \quad 00000 \quad (\text{left half of product}) \\
 \underline{-00010} \quad (\text{multiplicand}) \\
 11110 \quad (\text{uses a phantom borrow})
 \end{array}$$

- Place result into **left half** of product

11110 11011 0

- Step 2: ASR (arithmetic shift right)

Before ASR

11110 11011 0

After ASR

11111 01101 1

(left-most bit was 1, so a 1 was shifted in on the left)

- Pass 4 is complete.

- Current Product and **previous LSB**
11111 01101 1
- **Pass 5**, Step 1: Examine the last 2 bits
11111 0110**1 1**
- The last two bits are **11**, so we do NOT need to perform an arithmetic action just proceed to step 2.
- Step 2: ASR (arithmetic shift right)
Before ASR
11111 01101 1
After ASR
11111 10110 1
(left-most bit was 1, so a 1 was shifted in on the left)
- Pass 5 is complete.


- Dropping the **previous LSB**, the resulting **final product** is:

11111 10110

- To confirm we have the correct answer, convert the 2's complement **final product** back to decimal.
- Final product: **11111 10110**
- Decimal value: **-10**

which is the **CORRECT** product of:

$$\mathbf{(-5) \times 2}$$

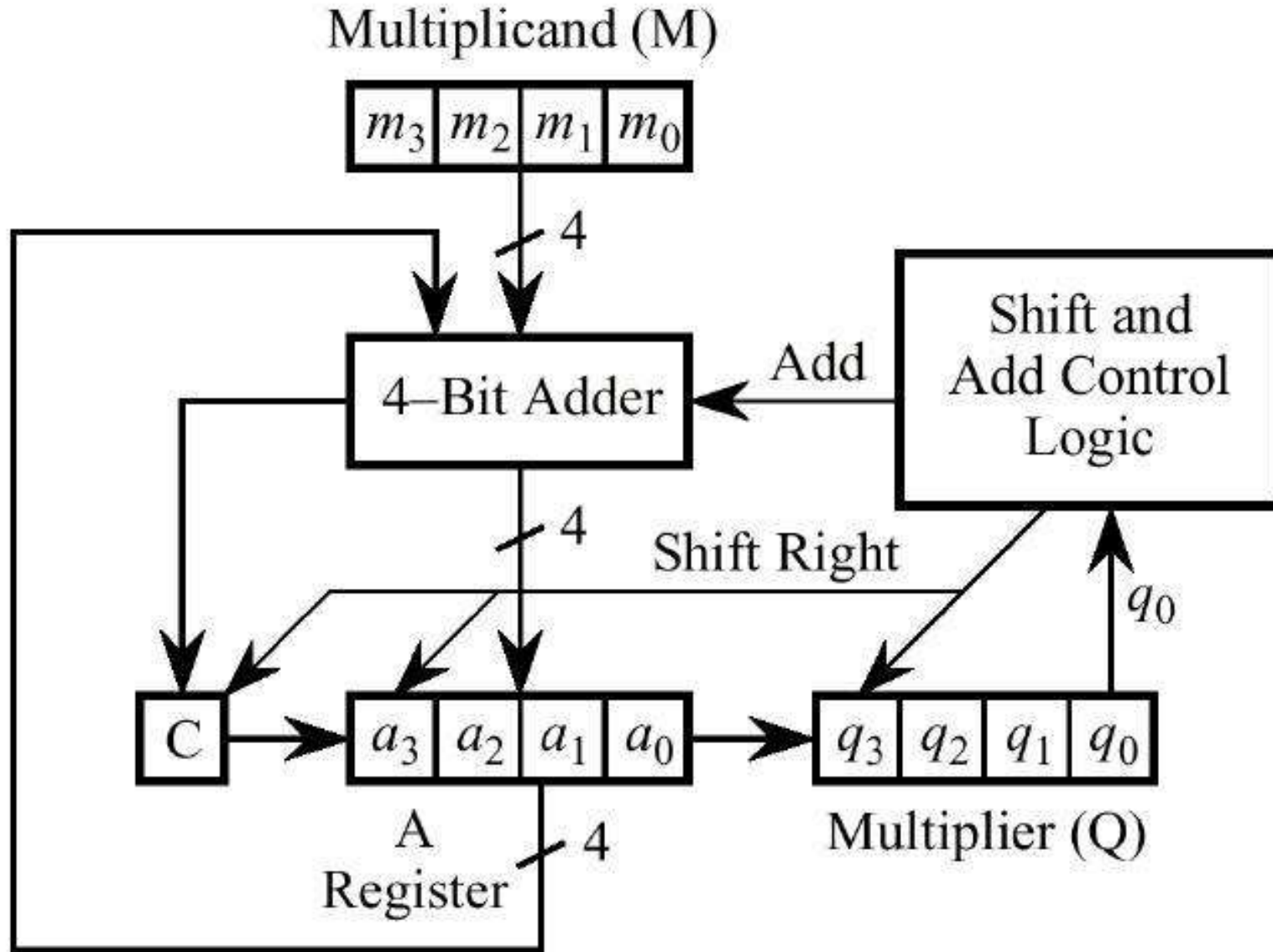

Modified Booth Multiplier (Booth Encoding)

- Can encode the digits by looking at three bits at a time




- Booth recoding table:

$i+1$	i	$i-1$	add
0	0	0	$0*M$
0	0	1	$1*M$
0	1	0	$1*M$
0	1	1	$2*M$
1	0	0	$-2*M$
1	0	1	$-1*M$
1	1	0	$-1*M$
1	1	1	$0*M$

- Must be able to add *multiplicand* times -2 , -1 , 0 , 1 and 2

Algorithm

   
1. Pad the LSB with one zero.
2. Pad the MSB with 2 zeros if n is even and 1 zero if n is odd.
3. Divide the multiplier into overlapping groups of 3-bits.
4. Determine partial product scale factor from modified booth 2 encoding table.
5. Compute the *Multiplicand Multiples*
6. Sum Partial Products



1. Pad LSB with 1 zero

2. n is even then pad the MSB with two zeros

Example

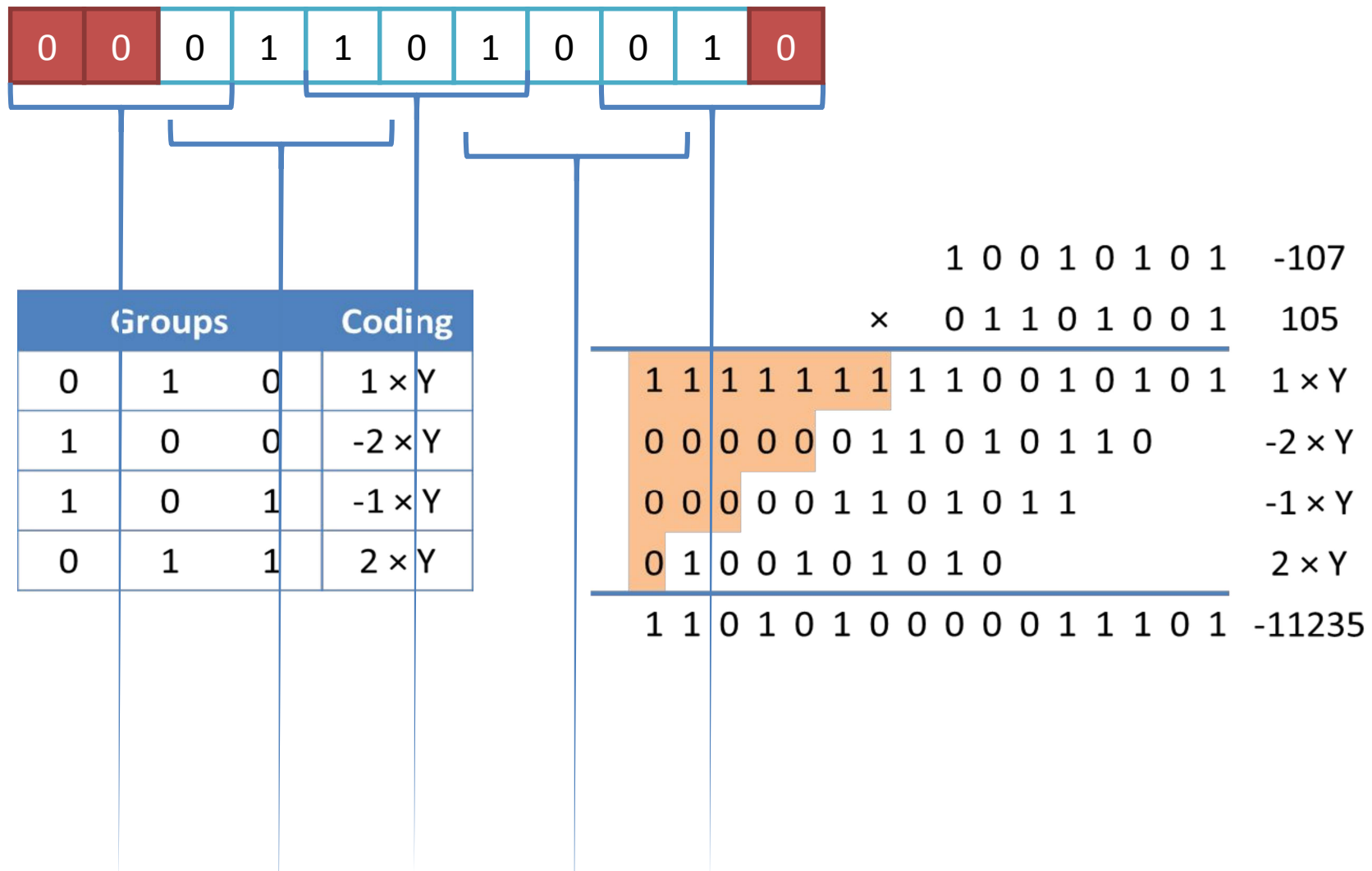


Barrel Shifter

- A barrel shifter is a digital circuit that can shift a data word by a specified number of bits in one clock cycle.
- It can be implemented with multiplexers (MUX)

Function Table for 4-Bit Barrel Shifter

Select		Output				Operation
S_1	S_0	Y_3	Y_2	Y_1	Y_0	
0	0	D_3	D_2	D_1	D_0	No rotation
0	1	D_2	D_1	D_0	D_3	Rotate one position
1	0	D_1	D_0	D_3	D_2	Rotate two positions
1	1	D_0	D_3	D_2	D_1	Rotate three positions

 

i positions of left rotation is the same as $2^n - i$ bits of right rotation


implementing a barrel shifter would be to use N (where N is the number of input bits) parallel N -to-1 multiplexers, one multiplexer that multiplexes all inputs into one of the outputs.

This would create an equivalent $N \times N$ to N multiplexer, which would use significant hardware resources (**multiplexer input grows in $O(N^2)$**).

A more efficient implementation is possible by creating a hierarchy of multiplexers.

- 32-bit barrel shifter: can use 32 32-to-1 multiplexers
- However, large fan-in undesirable. So, use layers of multiplexers

 Example:
Use 2 layers of 4
2-to-1 multiplexers
for 4-bit barrel
shifter



For an 8 bit rotate component the multiplexers would be constructed as follows:

- the top level multiplexers rotate the data by 4 bits
- the second level rotates the data by 2 bits
- the third level rotates the data by 1 bit.

The number of multiplexers required is $n * \log_2(n)$, for an n bit word.

Four common word sizes and the number of multiplexers needed are:

$$64\text{-bit} - 64 * \log_2(64) = 64 * 6 = 384$$

$$32\text{-bit} - 32 * \log_2(32) = 32 * 5 = 160$$

$$16\text{-bit} - 16 * \log_2(16) = 16 * 4 = 64$$

$$8\text{-bit} - 8 * \log_2(8) = 8 * 3 = 24$$

```
module barrel_shifter(d,out,q,c); / Main module of 8-Bit Barrel shifter
    input [7:0]d;
    output [7:0]out,q;
    input[2:0]c;
    mux m1(q[0],d,c);
    mux m2(q[1],{d[0],d[7:1]},c);
    mux m3(q[2],{d[1:0],d[7:2]},c);
    mux m4(q[3],{d[2:0],d[7:3]},c);
    mux m5(q[4],{d[3:0],d[7:4]},c);
    mux m6(q[5],{d[4:0],d[7:5]},c);
    mux m7(q[6],{d[5:0],d[7:6]},c);
    mux m8(q[7],{d[6:0],d[7:7]},c);
    assign out=q;
endmodule
```

Baugh-Wooley Multiplier

- Efficient way to handle sign bits
- Regular Multipliers, suited for 2's-complement numbers
- Signed number representation

$$X = -x_{n-1}2^{n-1} + \sum_{i=0}^{n-2} x_i 2^i$$

eg: $(1110)_2$

= (-2)

$$A = -a_{n-1}2^{n-1} + \sum_{i=0}^{n-2} a_i 2^i$$

$$B = -b_{n-1}2^{n-1} + \sum_{i=0}^{n-2} b_i 2^i$$

$$P = A \times B$$

$$= \left(-a_{n-1}2^{n-1} + \sum_{i=0}^{n-2} a_i 2^i \right) \times \left(-b_{n-1}2^{n-1} + \sum_{j=0}^{n-2} b_j 2^j \right)$$

$$= a_{n-1}b_{n-1}2^{2n-2} + \sum_{i=0}^{n-2} \sum_{j=0}^{n-2} a_i b_j 2^{i+j}$$

$$-2^{n-1} \sum_{i=0}^{n-2} a_i b_{n-1} 2^i - 2^{n-1} \sum_{j=0}^{n-2} a_{n-1} b_j 2^j$$

The Baugh-Wooley Method and Its Modified Form

$$\begin{aligned} -a_4x_0 &= a_4(1 - x_0) - a_4 \\ &= a_4x_0' - a_4 \end{aligned}$$

$$\begin{array}{cc} -a_4 & a_4x_0' \\ \uparrow & \\ a_4 & \end{array}$$

In next column



					X	$\overline{a_4}$ x_4	$\overline{a_3}$ x_3	$\overline{a_2}$ x_2	$\overline{a_1}$ x_1	$\overline{a_0}$ x_0
						$\overline{a_4 x_0}$	$\overline{a_3 x_0}$	$\overline{a_2 x_0}$	$\overline{a_1 x_0}$	$\overline{a_0 x_0}$
						$\overline{a_4 x_1}$	$\overline{a_3 x_1}$	$\overline{a_2 x_1}$	$\overline{a_1 x_1}$	$\overline{a_0 x_1}$
						$\overline{a_4 x_2}$	$\overline{a_3 x_2}$	$\overline{a_2 x_2}$	$\overline{a_1 x_2}$	$\overline{a_0 x_2}$
						$\overline{a_4 x_3}$	$\overline{a_3 x_3}$	$\overline{a_2 x_3}$	$\overline{a_1 x_3}$	$\overline{a_0 x_3}$
						$\overline{a_4 x_4}$	$\overline{a_3 x_4}$	$\overline{a_2 x_4}$	$\overline{a_1 x_4}$	$\overline{a_0 x_4}$
						$\overline{a_4}$	$\overline{a_3}$	$\overline{a_2}$	$\overline{a_1}$	$\overline{a_0}$
1	$\frac{\overline{a_4} x_4}{\overline{a_4}}$	$\frac{\overline{a_4} x_3}{\overline{a_3} x_4}$	$\frac{\overline{a_4} x_2}{\overline{a_3} x_3}$	$\frac{\overline{a_4} x_1}{\overline{a_3} x_2}$	$\frac{\overline{a_4} x_0}{\overline{a_3} x_1}$	$\overline{a_4}$				
						x_4				
p_9	p_8	p_7	p_6	p_5	p_4	p_3	p_2	p_1	p_0	

$$\begin{aligned} -a_4x_0 &= (1 - a_4x_0) - 1 \\ &= (a_4x_0)' - 1 \end{aligned}$$

$$\begin{array}{cc} -1 & (a_4x_0)' \\ \uparrow & \\ 1 & \end{array}$$


In next column

					X	$\overline{a_4}$ x_4	$\overline{a_3}$ x_3	$\overline{a_2}$ x_2	$\overline{a_1}$ x_1	$\overline{a_0}$ x_0
						$\overline{a_4 x_0}$	$\overline{a_3 x_0}$	$\overline{a_2 x_0}$	$\overline{a_1 x_0}$	$\overline{a_0 x_0}$
						$\overline{a_4 x_1}$	$\overline{a_3 x_1}$	$\overline{a_2 x_1}$	$\overline{a_1 x_1}$	$\overline{a_0 x_1}$
						$\overline{a_4 x_2}$	$\overline{a_3 x_2}$	$\overline{a_2 x_2}$	$\overline{a_1 x_2}$	$\overline{a_0 x_2}$
						$\overline{a_4 x_3}$	$\overline{a_3 x_3}$	$\overline{a_2 x_3}$	$\overline{a_1 x_3}$	$\overline{a_0 x_3}$
						$\overline{a_4 x_4}$	$\overline{a_3 x_4}$	$\overline{a_2 x_4}$	$\overline{a_1 x_4}$	$\overline{a_0 x_4}$
						$\overline{a_4}$	$\overline{a_3}$	$\overline{a_2}$	$\overline{a_1}$	$\overline{a_0}$
1						1				
\bar{p}_9	p_8	p_7	p_6	p_5	p_4	p_3	p_2	p_1	p_0	

 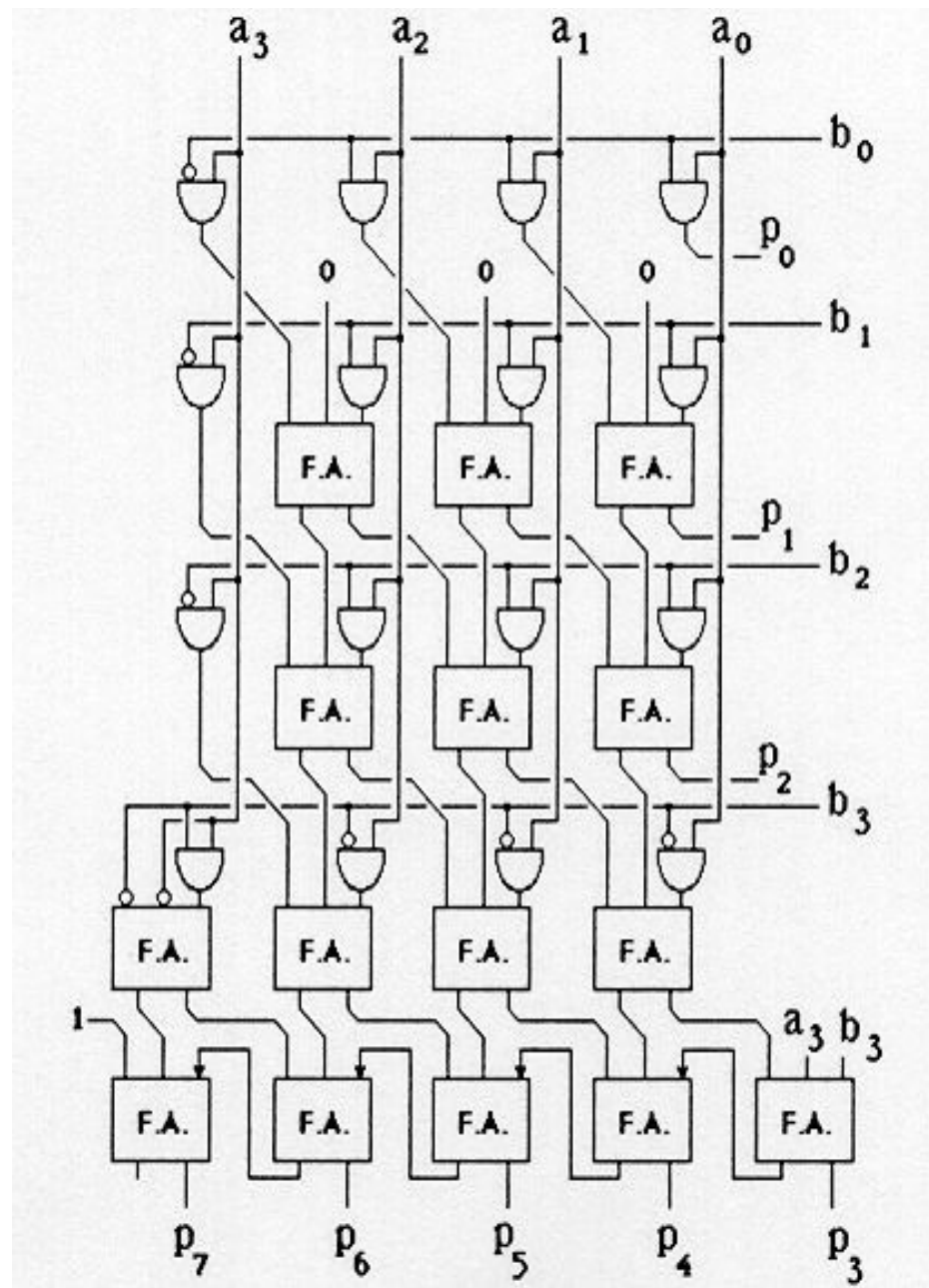


Wallace-Tree Multiplier

Partial products

 


(a)

First stage

 


(b)

Second stage

 


(c)

Final adder

 


(d)

 


Full adder = (3,2) compressor

(4,2) Counter

 


 - Built out of two (3,2) counters (just FA's!)
 - all of the inputs (4 external plus one internal) have the **same weight** (i.e., are in the **same** bit position)
 - the **internal** carry output is fed to the next higher weight position (indicated by the)




Note: Two carry outs - one "**internal**" and one "**external**"

Tiling (4,2) Counters

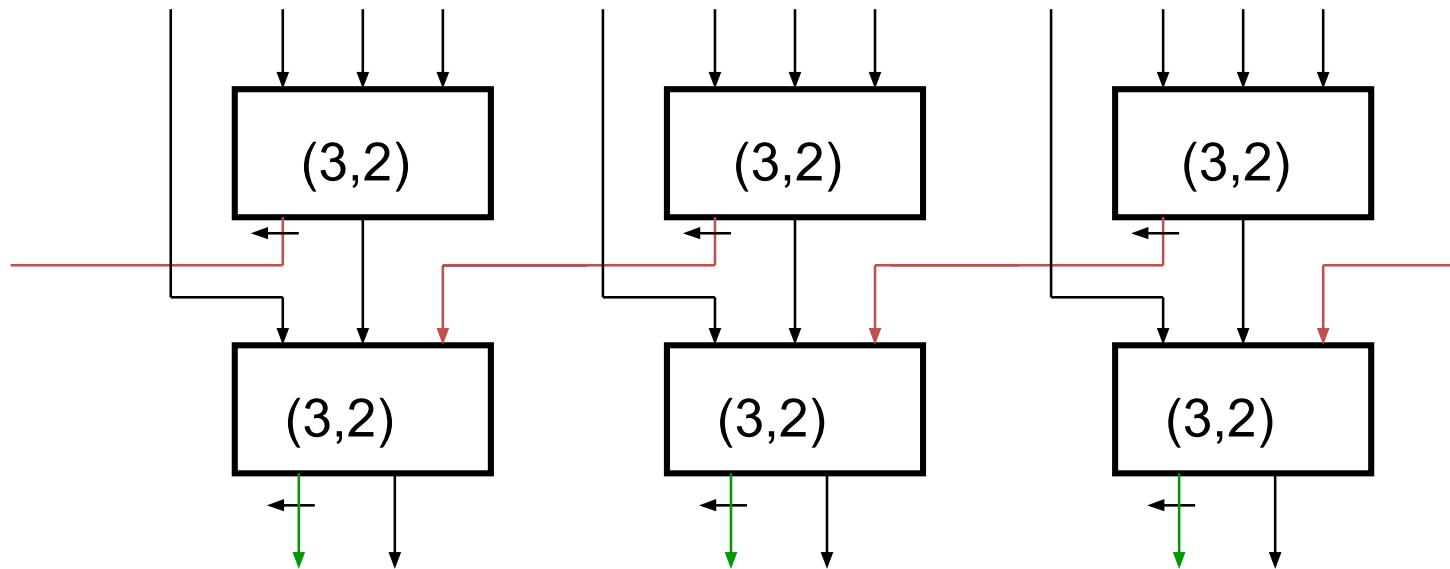


- ❑ Reduces columns **four** high to columns only **two** high
 - Tiles with neighboring (4,2) counters
 - **Internal** carry in at same “level” (i.e., bit position weight) as the **internal** carry out

Tiling (4,2) Counters


 


4x4 Partial Product Array Reduction

 - Fast 4x4 multiplication using (4,2) counters



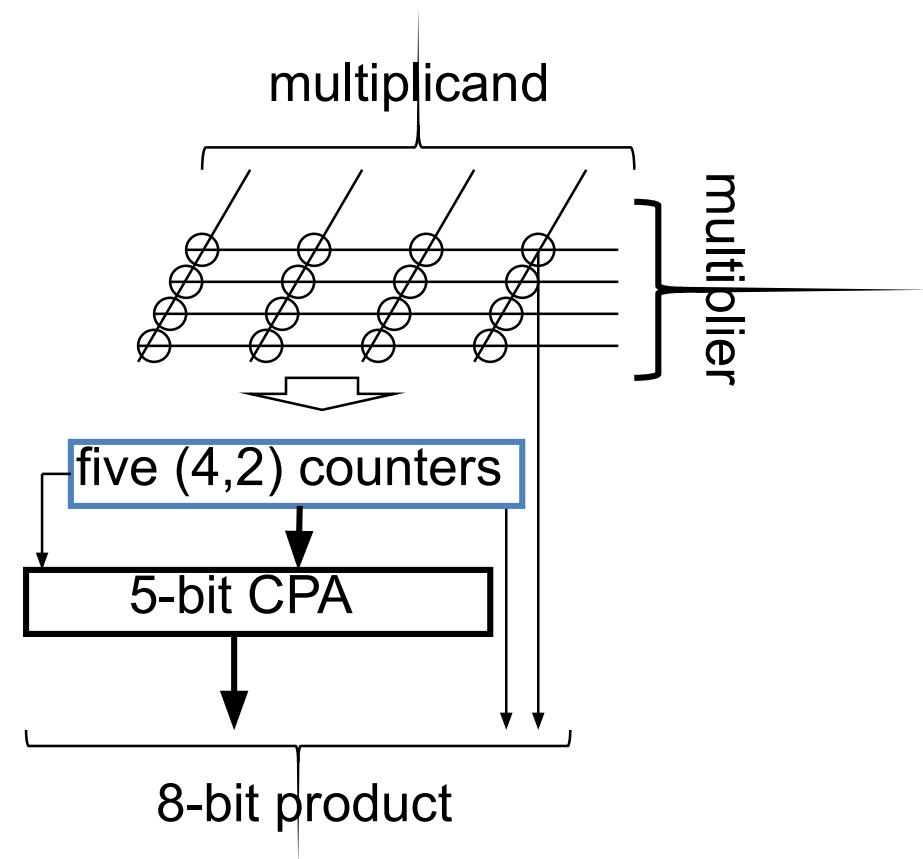 Fast 4x4 multiplication using (4,2) counters



8x8 Partial Product Array Reduction

- Wallace tree multiplier

