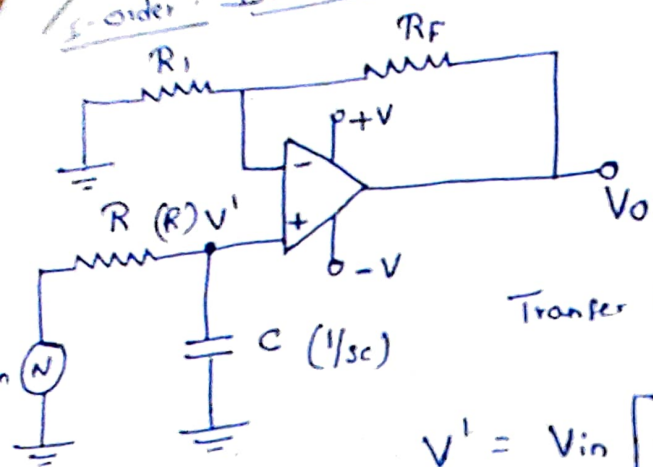


1st-order Butterworth Low-Pass Filter



First order has one pole

Negative Feedback, i/p to Non-inv. terminal.

Transfer Function $H(s) = \frac{V_o(s)}{V_i(s)}$

$$V' = V_{in} \left[\frac{1/sC}{R + 1/sC} \right] = V_{in} \left[\frac{1}{1 + RCs} \right]$$

$$V_{out} = V' \left[1 + \frac{R_f}{R_1} \right]$$

$$V_{out} = \underbrace{\left[1 + \frac{R_f}{R_1} \right]}_A \left[\frac{1}{1 + RCs} \right] \cdot V_{in}$$

$$\frac{V_{out}}{V_{in}} = H(s) = \frac{A}{1 + RCs}$$

This system has one pole

Root of this system $1 + RCs = 0$


$$s = -1/RC$$

$$s = j\omega; \quad \omega_H = \frac{1}{RC}$$

$$H(j\omega) = \frac{A}{1 + j \left(\frac{\omega}{\omega_H} \right)} = \frac{A}{1 + j \left(f/f_H \right)}$$

Magnitude. $|H(j\omega)| = \frac{A}{\sqrt{1 + (f/f_H)^2}}$

$$A = 1 + R_f/R_1$$

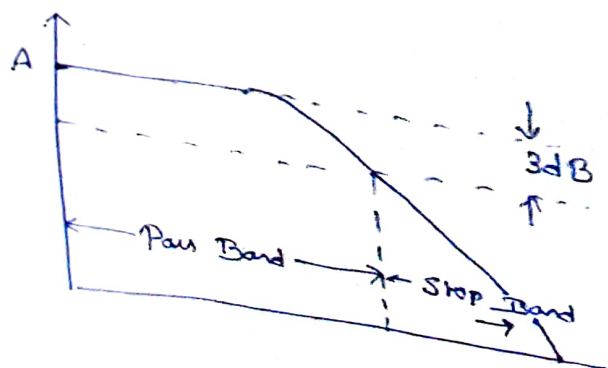

$$f < f_H, \quad |H(j\omega)| \approx A$$



$$f = f_H, \quad |H(j\omega)| = A/\sqrt{2}$$

$$= 0.707 A$$

Second order Low-Pass Filter

- * Constant gain A_f from 0Hz to high cut-off freq f_h
- * Frequency response of Filter must be very close to an ideal
- * Non-inverting Opamp Configuration, Two RC-Networks

Circuit Diagram:

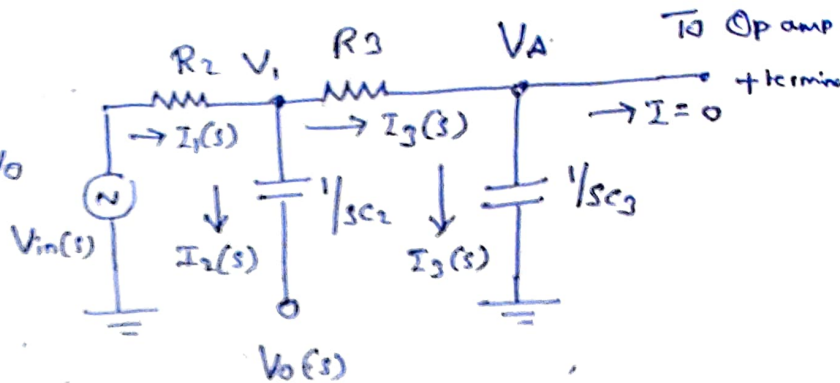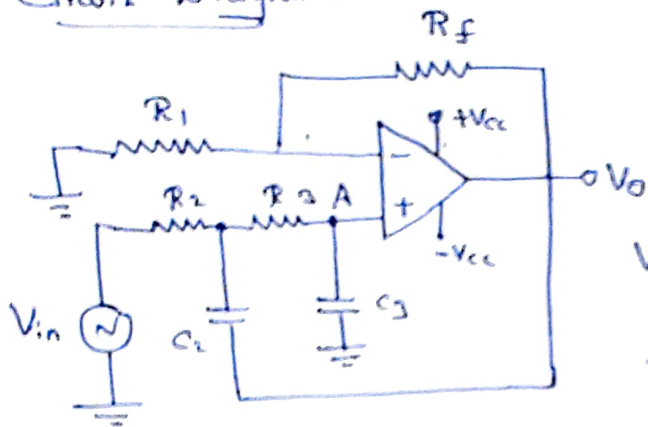

RC N/w in Laplace Domain

$$I_1 = I_2 + I_3$$

$$\frac{V_{in} - V_1}{R_2} = \frac{V_1 - V_0}{(1/sC_2)} + \frac{V_1 - V_A}{R_3}$$

$\rightarrow (1)$

Sub (2) in (1)

$$\frac{V_{in} - V_A [1 + sR_3C_3]}{R_2} = \frac{V_A [1 + sR_3C_3] - V_0}{(1/sC_2)} + \frac{V_A [1 + sR_3C_3] - V_A}{R_3}$$

$$\frac{V_{in}}{R_2} + V_0(sC_2) = V_A \left[\frac{(1 + sR_3C_3)}{R_2} + \frac{sC_2 [1 + sR_3C_3] + R_2 [1 + sR_3C_3] - R_2}{R_2 R_3} \right]$$

$$\therefore (R_3 V_{in} + V_0 s R_2 R_3 C_2) = V_A [(1 + sR_3C_3) (R_3 + R_2 R_3 s C_3 + R_2) - R_2]$$

$$V_A = \frac{R_3 V_{in} + V_0 s R_2 R_3 C_2}{[(1 + sR_3C_3) (R_3 + R_2 R_3 s C_3 + R_2) - R_2]} \rightarrow (3)$$

From non-inverting mode

$$V_o = A_F V_A$$

$$A_F = 1 + \frac{R_f}{R_1} \quad ; \quad V_A - \text{the voltage at the non-inverting terminal.}$$

$$V_o = V_A A_F \left[\frac{R_3 V_{in} + V_o s R_2 R_3 C_2}{(1 + s R_3 C_3) (R_3 + R_2 R_3 C_2 s + R_2) - R_2} \right]$$

$$\frac{A_F R_3 V_{in}}{(1 + s R_3 C_3) (R_3 + R_2 R_3 C_2 s + R_2) - R_2} = V_o \left[1 - \frac{s R_2 R_3 C_2}{(1 + s R_3 C_3) (R_3 + R_2 R_3 C_2 s + R_2) - R_2} \right]$$

$$\therefore A_F R_3 V_{in} = V_o \left[(1 + s R_3 C_3) (R_3 + R_2 R_3 C_2 s + R_2) - R_2 - s R_2 R_3 C_2 \right]$$

$$\frac{V_o}{V_{in}} = \frac{A_F}{s^2 + \frac{(R_3 C_3 + R_2 C_3 + R_2 C_2 - A_F R_2 C_2)}{R_2 R_3 C_2 C_3} s + \frac{1}{R_2 R_3 C_2 C_3}}$$

→ (4)


$$\frac{V_o(s)}{V_{in}(s)} = \frac{A}{s^2 + 2\xi\omega_n s + \omega_n^2}$$

A - overall gain, ξ - damping of system; ω_n = natural freq. of oscillation

$$\omega_n^2 = \frac{1}{R_2 R_3 C_2 C_3} \quad ; \quad \omega_n^2 =$$

$$(2\pi f_H)^2 = \frac{1}{R_2 R_3 C_2 C_3}$$
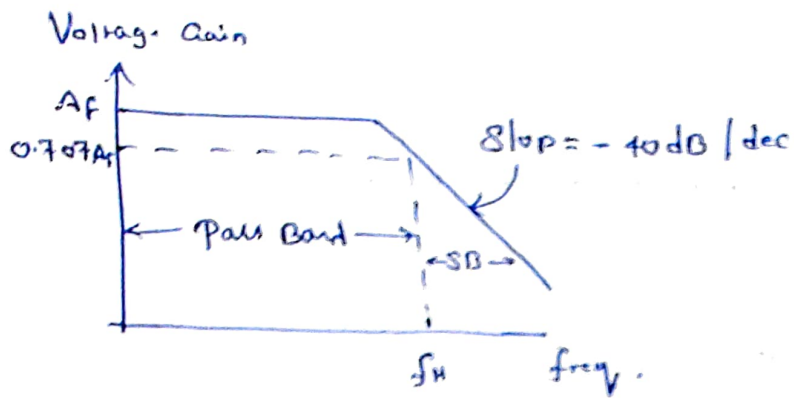
$$f_H = \frac{1}{2\pi \sqrt{R_2 R_3 C_2 C_3}}$$



$$\frac{V_o}{V_{in}} = \left| \frac{V_o}{V_{in}} \right| \angle \phi$$

$$\left| \frac{V_o}{V_{in}} \right| = \frac{A_f}{\sqrt{1 + (f/f_H)^2}}$$

A_f = Gain of filter in pass Band

f = Input freq. in Hz

f_H = High cut-off freq. in Hz.

For $0 < f < f_H$, the gain is almost constant.

At $f = f_H$, gain reduces to $0.707 A_f$, 3dB down from A_f

At $f > f_H$, the gain decreases at a rate of 40 dB/dec .