

Exp. No: 06

30.10.2023

CHARACTERISTICS OF FLIP FLOP

Aim:

To Study informations about Flip Flop and its types.

Theory:

A flip flop is a memory element that is capable of storing one bit informations.

A flip flop can maintain a binary state for an unlimited period of time as long as,


- Power is supplied to circuit
- Or until it is directly by an Input Signal to Switch States.

Types:

- | | |
|-------------------|-------------------|
| (i) SR Flip Flop | (iii) D Flip Flop |
| (ii) JK Flip Flop | (iv) T Flip Flop |

SR-FLIP FLOP

CIRCUIT DIAGRAM

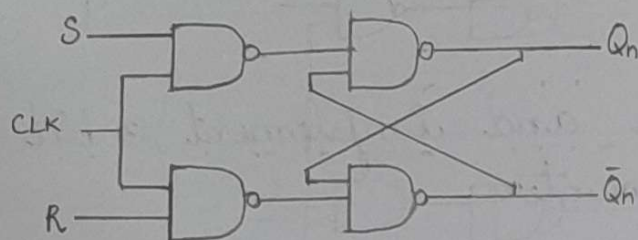

CHARACTERISTIC TABLE

C	S	R	Q_n	Q_{n+1}
1	0	0	0	1
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	
1	1	1	1	

CHARACTERISTIC FLIP FLOP:


Q_n	$\bar{S}\bar{R}$	$\bar{S}R$	$S\bar{R}$	$S\bar{R}$
Q_n			x	1
Q_n	1		x	1

$$Q_{n+1} = S + Q_n R$$

EXCITATION TABLE:


Q_n	Q_{n+1}	S	R
0	0	0	x
0	1	1	0
1	0	0	1
1	1	x	0

STATE DIAGRAM:

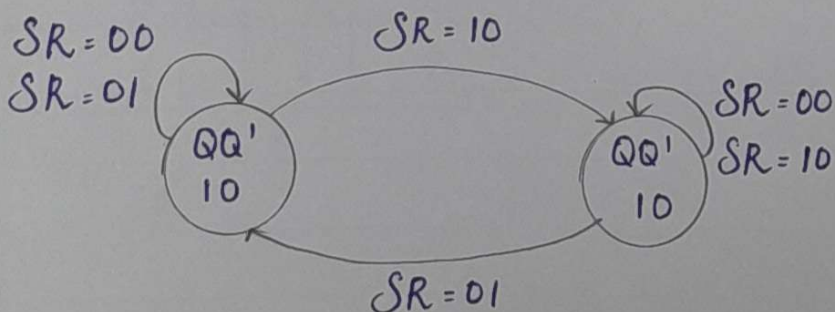

JK FLIP FLOP:

CIRCUIT DIAGRAM:

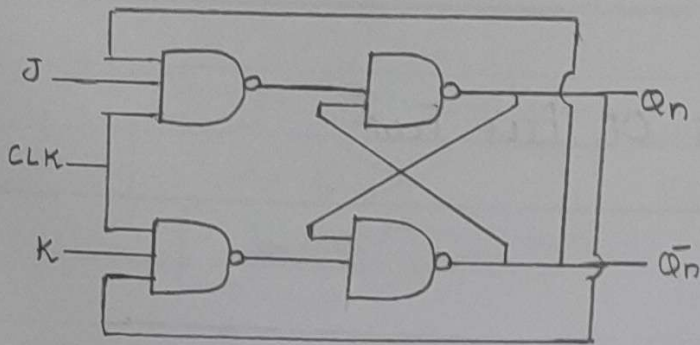

CHARACTERISTIC TABLE:

C	J	K	Q_n	Q_{n+1}
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

CHARACTERISTIC EQUATION:


	$J\bar{K}$	$\bar{J}K$	JK	$\bar{J}\bar{K}$
Q_n				
\bar{Q}_n			1	1
Q_n	1			1

$$Q_{n+1} = Q_n'J + Q_nK'$$

EXCITATION TABLE:


Q_n	Q_{n+1}	J	K
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0

STATE DIAGRAM:

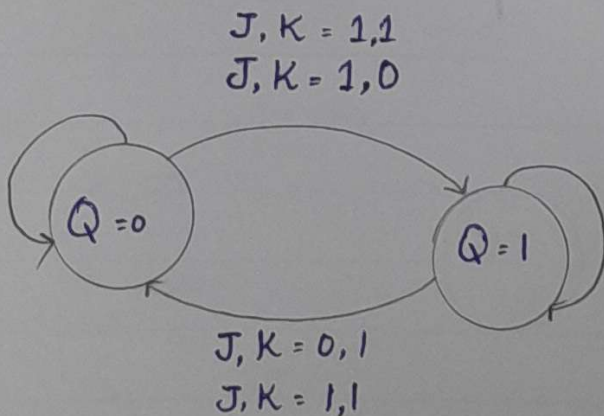

D-FLIP FLOP:

CIRCUIT DIAGRAM:

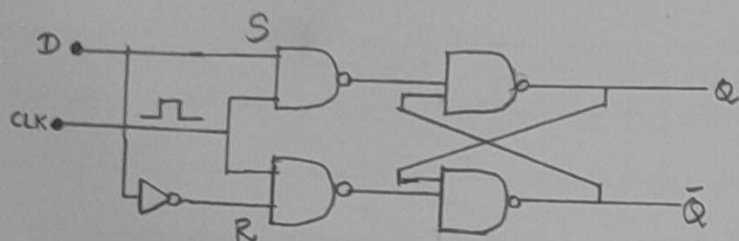

CHARACTERISTIC TABLE:

C	D	Q_n	Q_{n+1}
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

EXCITATION TABLE:


Q_n	Q_{n+1}	D
0	0	0
0	1	1
1	0	0
1	1	1

CHARACTERISTIC EQUATION:

	Q_n'	Q_n
D'	0	0
D	1	1


$$Q_{n+1} = D$$

STATE DIAGRAM:

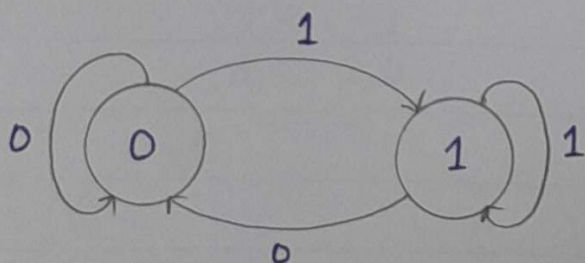

T-FLIP FLOP:

CIRCUIT DIAGRAM:

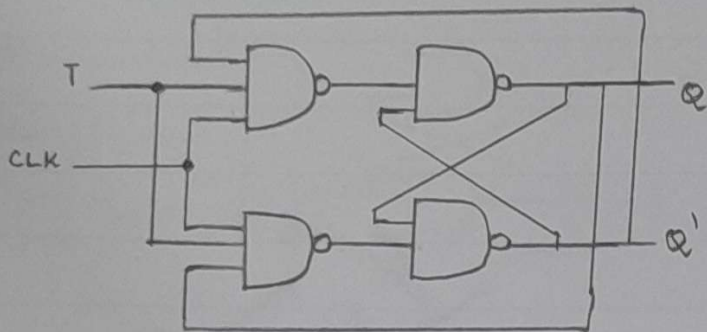

CHARACTERISTIC TABLE:

T	PREVIOUS		NEXT	
	Q_{PREV}	Q'_{PREV}	Q_{NEXT}	Q'_{NEXT}
0	0	1	0	1
0	1	0	1	0
1	0	1	1	0
1	1	0	0	1

CHARACTERISTIC EQUATION:

$Q_p \backslash T$	0	1
0		(1)
1	(1)	


$$Q = TQ_p' + T'Q_p$$

$$Q = T \text{ XOR } Q_p$$

EXCITATION TABLE:

Q	Q^+	T
0	0	0
0	1	1
1	0	1
1	1	0

STATE DIAGRAM:

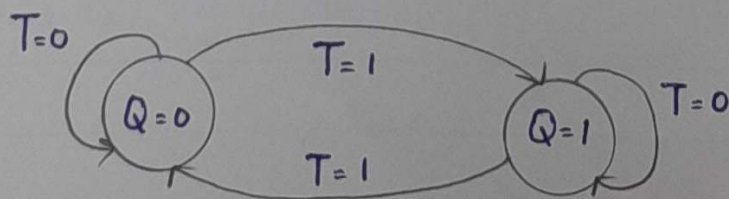

RESULT:

Thus, with the help of circuit diagram, characteristic table and equation with help of state diagram able to understand characteristics of Flip Flop.