
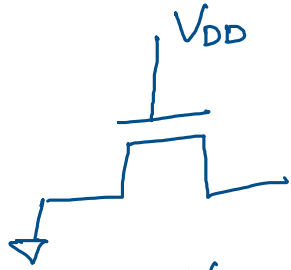


# Pass Transistor DC characteristics:-

nMOS passes '0' well  
'1' poorly

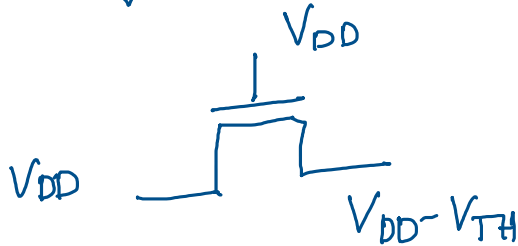


$$\Rightarrow V_S = 0V$$




$$\Rightarrow V_S = V_{DD} - V_{TH}$$

pMOS passes '1' well  
'0' poorly

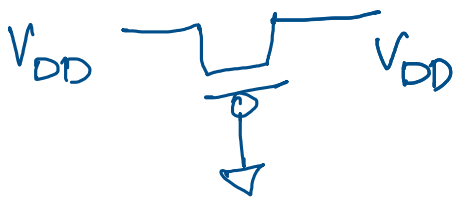



$$\Rightarrow V_S = V_{DD}$$

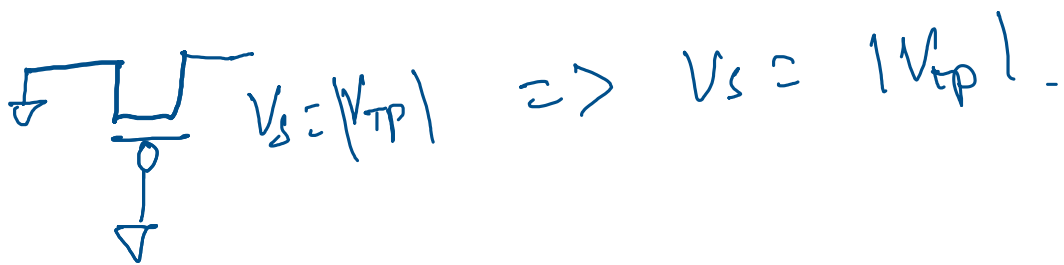

$$\Rightarrow V_S = |V_{TP}|$$

Examples:

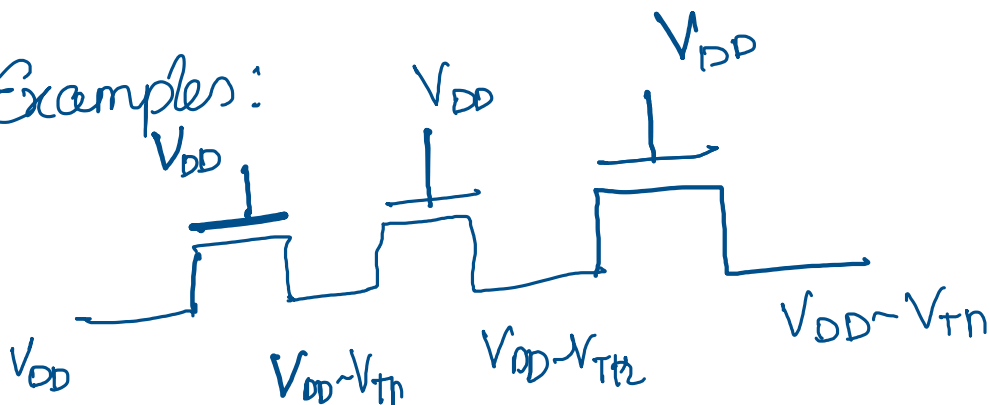

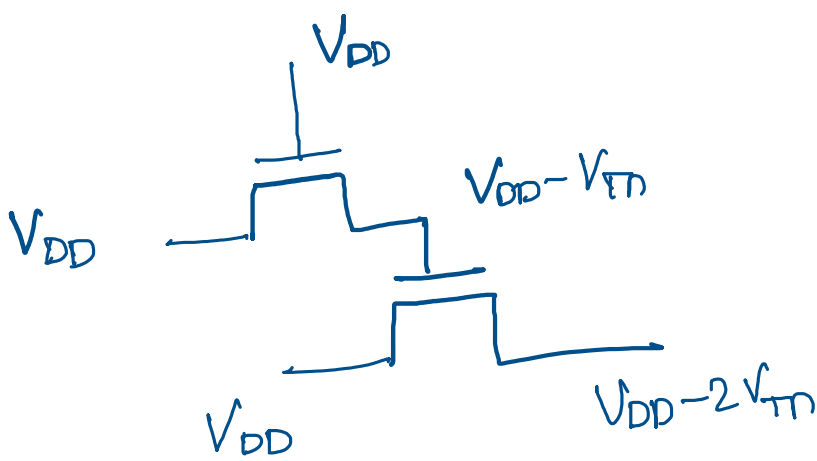

Pass transistors:

nmos perfect switch in passing '0'

Strong '0'

nmos is imperfect at passing '1' less than

$V_{DD}$  by a threshold  
degraded or weak '1'

pmos has opposite behaviour

pmos perfect switch in passing '1'

Strong '1'

pmos is imperfect at passing '0' it  
should have one  $V_{tp}$  at source

degraded or weak '0'.

When nmos or pmos is used alone  
as an imperfect switch, we call it  
pass transistor.

Transmission gate :- (TG) or pass gate (PG)  
 combining an NMOS and PMOS in parallel  
 we obtain a switch that turns on  
 when a 1 is applied to  $g$  in which  
 0s and 1s are both passed in acceptable  
 fashion. This is called double rail  
 logic

