

$$= (11)(10 \text{ mV}) + 10 \times 10^3 \times 50 \times 10^{-9}$$

$$= 110 \text{ mV} + 500 \times 10^{-6}$$

$$= 110 \text{ mV} + 0.5 \times 10^{-3}$$

$$= 110.5 \text{ mV}$$

Thermal drift

→ Bias current, offset current, and offset voltage change with temperature.

→ A circuit carefully nulled at 25°C may not remain so when the temperature rises to 35°C . This is called drift.

→ Often offset current drift is expressed in $\text{nA}/^\circ\text{C}$ and offset voltage drift in $\text{mV}/^\circ\text{C}$. These indicate the change in offset for each degree Celsius change in temperature.

Techniques used to minimize the drift

→ Carefully printed circuit board (PCB) must be used keep op-amps away from source of heat.

→ Forced air cooling may be used to stabilize the ambient temperature.

11Q: A non-inverting amplifier with a gain 100 is nulled at 25°C . What will happen to output voltage if the temperature rise to 50°C for an offset voltage drift of $0.15 \text{ mV}/^\circ\text{C}$.

Ans: Input offset voltage due to temperature rise

$$= 0.15 \text{ mV}/^\circ\text{C} (50^\circ\text{C} - 25^\circ\text{C}) = 3.75 \text{ mV}.$$

→ The output voltage will change by $V_o = V_{os} \cdot A_{CL}$

$$= 3.75 (100) = 375 \text{ mV}.$$

Q2: In an inverting amplifier $R_1 = 1\text{ k}\Omega$, $R_f = 100\text{ k}\Omega$

The op-amp has the following specifications: ...

$$\frac{\Delta V_{ios}}{\Delta T} = 30 \mu\text{V}/^\circ\text{C} \text{ max.}$$

$$\frac{\Delta I_{os}}{\Delta T} = 0.3 \text{ nA}/^\circ\text{C} \text{ max.}$$

Assume that the amplifier is nulled at 25°C . Calculate the value of the error voltage and the output voltage V_o at 35°C , if (i) $V_i = 1 \text{ mV dc}$ (ii) $V_i = 5 \text{ mV dc}$.

Ans: Input offset voltage due to temperature rise $= 30 \mu\text{V}/^\circ\text{C} (35$

$$= 300 \mu\text{V}$$

$$= 0.3 \text{ mV}$$

Input offset current due to temperature rise $=$

$$0.3 \text{ nA}/^\circ\text{C} (35 - 25)$$

$$= 3 \text{ nA}$$

$$V_{OT} = \left(1 + \frac{R_f}{R_1}\right) V_{ios} + R_f I_{os}$$

$$= \left(1 + \frac{100\text{ k}\Omega}{1\text{ k}\Omega}\right) \times 0.3 \text{ mV} + 100\text{ k}\Omega \times 3 \text{ nA}$$

$$= (101) \times 0.3 \text{ mV} + 300 \mu\text{V}$$

$$= 30.3 \text{ mV} + 0.3 \text{ mV}$$

$$= 30.6 \text{ mV} = \text{maximum output offset voltage.}$$

(i) For $V_i = 1 \text{ mV dc}$, the output voltage

$$= V_o = \left(-\frac{R_f}{R_1}\right) V_i \pm V_{OT}$$

$$= \left(\frac{-100k\Omega}{1k\Omega} \right) 1mV \pm 30.6mV$$

$$= -100mV \pm 30.6mV$$

$$= -130.6mV \quad \text{or} \quad -69.4mV$$

ii) $V_i = 5mV$ dc, the output voltage $= V_o$

$$= \left(\frac{-R_f}{R_i} \right) V_i \pm V_{oT}$$

$$= \left(\frac{-100k\Omega}{1k\Omega} \right) (5mV) \pm 30.6mV$$

$$= -500mV \pm 30.6mV$$

$$= -530.6mV \quad \text{or} \quad -469.4mV$$

13Q: Repeat the problem (12) for non-inverting amplifier.

$$\text{Ans: } V_{oT} = 30.6mV$$

(i) For $V_{in} = 1mV$ dc, the output voltage =

$$V_o = \left(1 + \frac{R_f}{R_i} \right) V_i \pm V_{oT}$$

$$= \left(1 + \frac{100k\Omega}{1k\Omega} \right) 1mV \pm 30.6mV$$

$$= 101mV \pm 30.6mV = +131.6mV \quad \text{or} \quad +70.4mV$$

(ii) For $V_i = 5mV$ dc, the output voltage $= V_o$

$$= \left(1 + \frac{R_f}{R_i} \right) V_i \pm V_{oT}$$

$$= 101 (5mV) \pm 30.6mV = 505mV \pm 30.6mV$$

$$= +535.6mV \quad \text{or} \quad +474.4mV$$

Infinite Slew-rate: The Slew rate is defined as the maximum rate of change of output voltage caused by a step input voltage. An ideal Slew rate is Infinite, which means that Op-Amp's output voltage should be change instantaneously in response to input step voltage. It is expressed as

$$S = \frac{dv}{dt}_{\max} \quad \text{and measured in Voltage/second,}$$

usually $V/\mu s$

For Example: A $1V/\mu s$ Slew rate means that the output rises or falls by $1V$ in one micro second.

There is usually a capacitor within (or) outside an op-amp to prevent oscillation. It is this capacitor which prevents the output voltage from responding immediately to a fast changing input. The rate at which the voltage across the capacitor increases is given by,

$$\frac{dV_c}{dt} = \frac{I}{C}, \quad \text{here } I \text{ is the maximum current furnished by Op-amp to the capacitor } C$$

This means that to obtaining faster slew rate, Op-amp should have either a higher current or a small compensating capacitor.

For IC 741, $I = 15 \mu A$

$$\begin{aligned} \text{So, Slew rate} &= \left. \frac{dV_c}{dt} \right|_{\max} = \frac{I_{\max}}{C} = \frac{15 \mu A}{30 pF} \\ &= 0.5 V/\mu s. \end{aligned}$$